

451

Basic Electrical Circuits

EEE1241
13.08.17
2A-SKG

- Syllabus:
- DC Circuit
 - AC Circuit
 - Electronics
 - Machine (DC)
 - Electrical wiring

জুয়েল ফটোশাট
নর্দান ইউনিভার্সিটির সামনে
মোবাস ০১৯২২-০৭০৭০৫


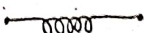
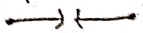
Circuit:

An electric circuit is an interconnection of electrical elements. There are two types of elements:

i. Active elements: Active elements produce energy or electricity.

Example: Battery, Generator, OP-Amp
 ↓ ↓ ↓
 Independent source Dependent source

ii. Passive elements: Passive elements consumed or dissipation or store energy.

Example: Resistance, Inductors, capacitors.
   

Every elements has two terminals.


Sub: _____

Charge and current:

Charge is an electrical property of the atomic particles of which matter consists, measured in coulombs (C).


* Properties of electric charge:

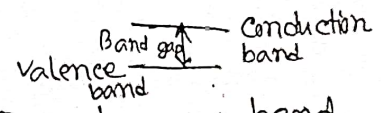1. The coulomb is a large unit for charges. In 1C of charge, there are $(1/1.602 \times 10^{-19}) = 6.24 \times 10^{18}$ electrons.
2. According to experimental observations, the only charge occur in nature are integral multiples of the electronic charge ($e = -1.602 \times 10^{-19} C$).
3. The law of conservation of charge states that charge can neither be created nor destroyed, only transferred. Thus the algebraic sum of the electric charges in a system does not change.



Conductor: Charge can move freely. There has no band gap between conduction band and valence band.

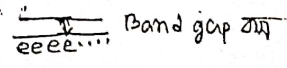Semiconductor: It is intermediated between \updownarrow



Insulator: Huge band gap and charge can not move freely.

Sub:

SAT SUN MON TUE WED THU FRI


Time: Date: / /

Electric current is the time rate of change of charge, measured in amperes (A).


Mathematically relation: $I = \frac{dq}{dt}$ 1 ampere = $\frac{1 \text{ coulomb}}{1 \text{ second}}$

There are two types of current.

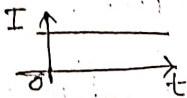i. DC: A direct current is a current that remains constant with time. The current does not change with time.



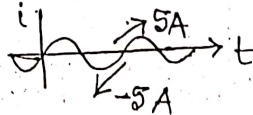ii. AC: An alternating current is a current that varies with respect to time.



Voltage:

Voltage (or potential difference) is the energy required to move a unit charge through an element, measured in volts (V).


The V_{ab} can be interpreted in two ways:

1. Point a is at a potential of V_{ab} volts higher than point b.

2. The potential at point a with respect to point

b is V_{ab} . It follows logically that in general: $V_{ab} = -V_{ba}$

$$V_{ab} = \frac{dW}{dQ}$$

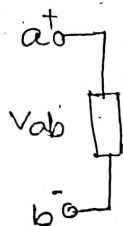

4

Sub:

A

SAT

SUN

MON

TUE

WED

THU

FRI


Time:



Date: 16/05/2017



Page:

Sub:

Series Resistor

DC voltage source (V, \pm)Current source AC voltage source (V_e, \sim)Current \uparrow

Ideal: There are no internal resistance in ideal current  source and ideal voltage  source. The given current and voltage can get back fully in ideal current and voltage source.

Practical: There is some internal resistance in practical current  source and in practical voltage  source.

I.C.S: Internal resistance is (∞) infinity.

P.C.S: Internal resistance is parallel to the source.

Power:

Power is the time rate of expending or absorbing energy, measured in watts (W).

$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = v \cdot i$$

$$dw = P dt$$

$$\Rightarrow \int_0^w dw = \int P dt$$

$$P = v(t) \overset{\leftarrow \text{current time varying}}{i(t)}$$


$$\Rightarrow P(t) = \overset{\rightarrow \text{voltage time varying}}{\text{instantaneous power}}$$

$$P = VI$$

Sub: _____

29.08.17
 4A-EEE

Series resistance of voltage division?

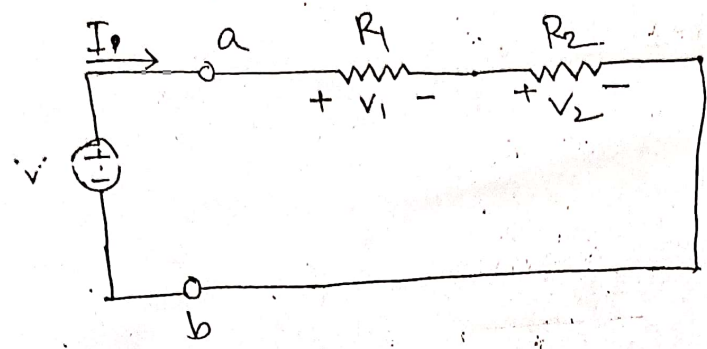


If one point be common between two element, then they are connected by series.

Ohm's law:

$V_1 = IR_1$ — (i)
 $V_2 = IR_2$ — (ii)

Clock wise direction

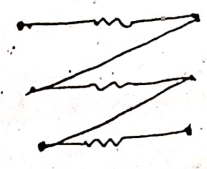KVL:
 $-V + V_1 + V_2 = 0$
 $\Rightarrow V = V_1 + V_2$



$= I(R_1 + R_2)$
 $= I R_{eq}$

$R_{eq} = R_1 + R_2$

$\Rightarrow I = \frac{V}{R_{eq}}$ — (iii)

If $R_1, R_2, R_3, \dots, R_n$ be stay in series connection, then

$R_{eq} = R_1 + R_2 + R_3 + R_4 + \dots + R_n$

$V_1 = \frac{R_1}{R_1 + R_2} \times V$
 $V_2 = \frac{R_2}{R_1 + R_2} \times V$ } voltage division rule.

$\therefore V_n = \frac{R_n}{R_1 + R_2 + \dots + R_n} \times V$

1A


Sub: _____

 SAT SUN MON TUE WED THU FRI
 Time: _____ Date: / /

Calculate conductance,

$$G_1 = \frac{1}{R_1}, \quad G_2 = \frac{1}{R_2}$$

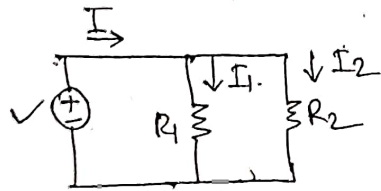* Parallel resistance of current division:



By applying KCL:

$$I = I_1 + I_2$$

$$= \frac{V}{R_1} + \frac{V}{R_2}$$

$$= V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= V/R_{eq}$$

$$\therefore V = \frac{I}{R_{eq}} \cdot I R_{eq}$$

$$I_1 = \frac{V}{R_1} = \frac{I R_{eq}}{R_1}$$

$$= I \times \frac{R_1 R_2}{R_1 + R_2} \times \frac{1}{R_1}$$

$$= \frac{R_2}{R_1 + R_2} \times I$$

$$V = I_1 R_1 \quad V = I_2 R_2$$

$$\Rightarrow I_1 = \frac{V}{R_1} \quad \Rightarrow I_2 = \frac{V}{R_2}$$

$$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$I_2 = \frac{V}{R_2} = \frac{I R_{eq}}{R_2}$$

$$= I \times \frac{R_1 R_2}{R_1 + R_2} \times \frac{1}{R_2}$$

$$= \frac{R_1}{R_1 + R_2} \times I$$

$$\frac{1}{R_{eq}} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$


 Sub: _____
 $R_{eq} = \frac{1}{G}$
 Conductance

Sub: _____

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

Conductance: $G_{eq} = G_1 + G_2 + G_3 + \dots + G_n$

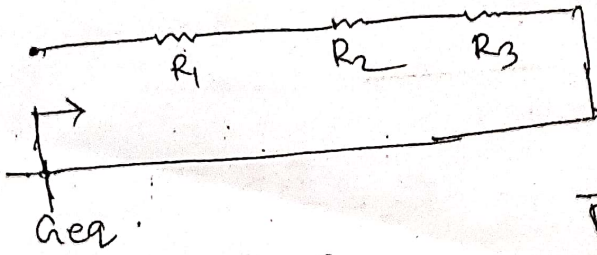** Calculate the conductance in series **



$$R_{eq} = R_1 + R_2 + R_3$$

$$\Rightarrow \frac{1}{G_{eq}} = \frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3}$$



$$\Rightarrow G_{eq} = \frac{G_1 G_2 G_3}{G_1 G_2 + G_2 G_3 + G_3 G_1}$$

$$\frac{1}{R_1} = G_1$$



$$\frac{1}{R_2} = G_2$$

$$\frac{1}{R_3} = G_3$$

Y connection

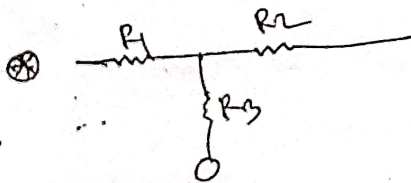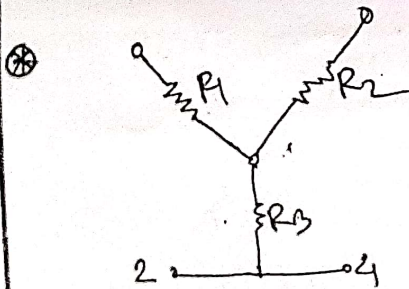


Δ-connection

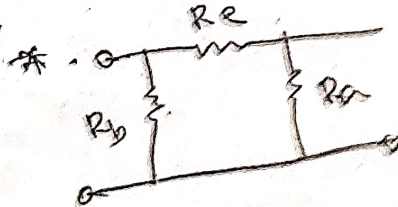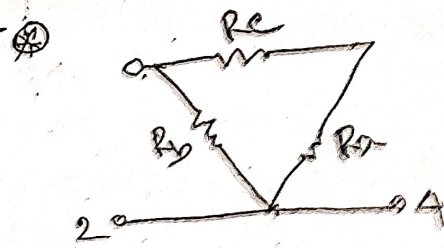

Y connection

Transfer:

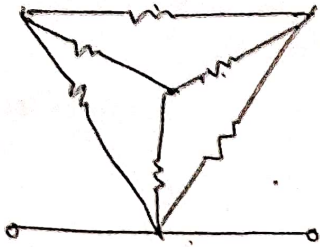


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Δ Connection

Transfer:


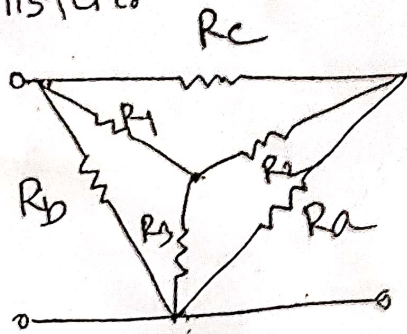


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

* Problems

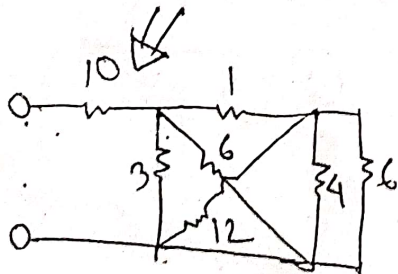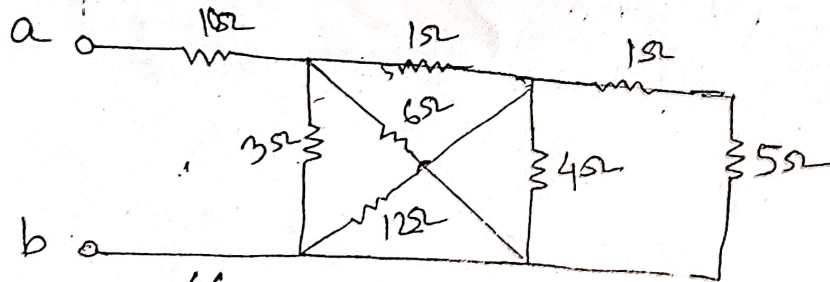


⇒

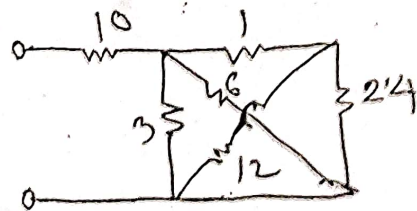


⇒




Solve:

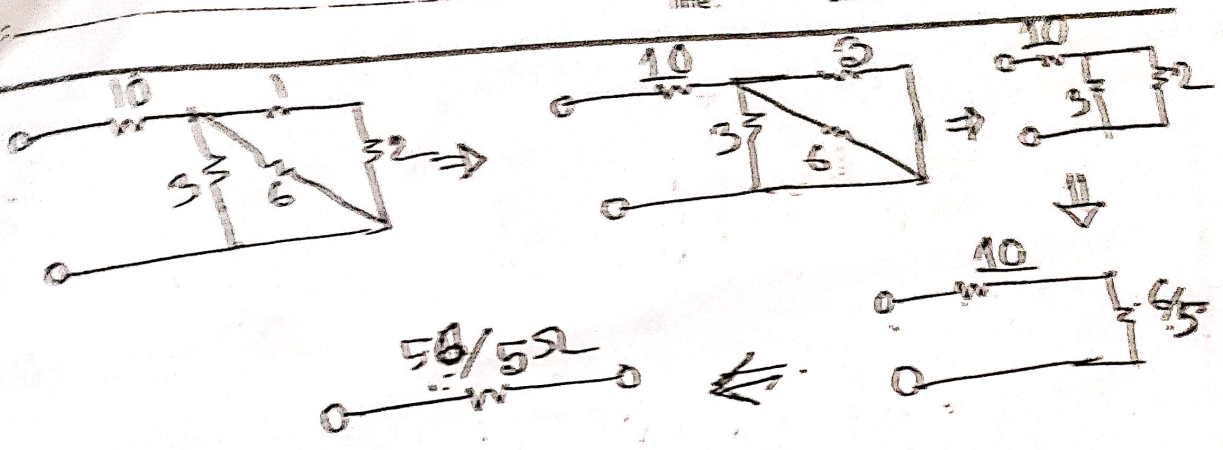

Problem:

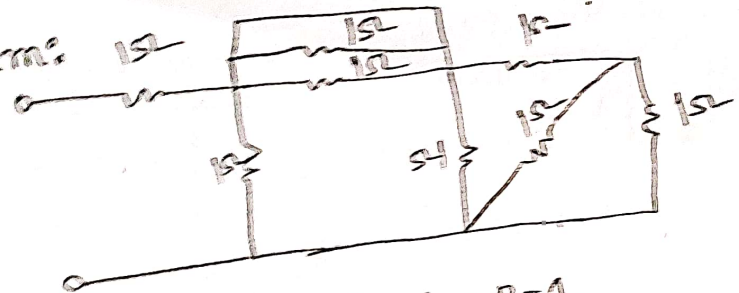

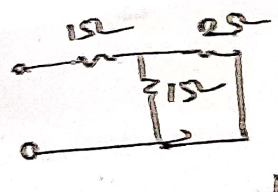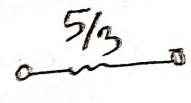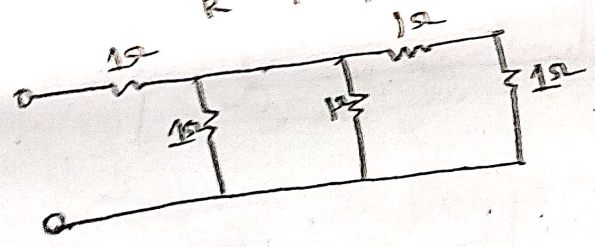
$$\frac{1}{R} = \frac{1}{1} + \frac{1}{1} \Rightarrow R = 1$$





$$\frac{1}{R} = \frac{1}{2} + \frac{1}{1}$$

$$\frac{1}{R} = \frac{1+2}{2}$$

$$R = \frac{2}{3}$$


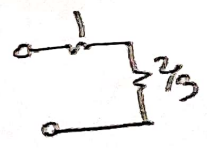


****Equivalent circuit:**

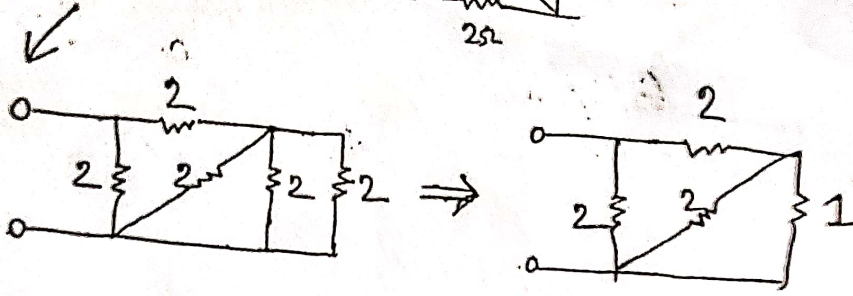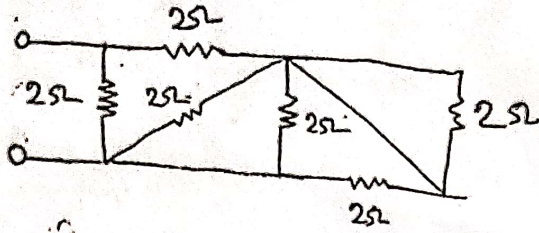




$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{2} = 1$$

$$\therefore R_{eq} = 1$$

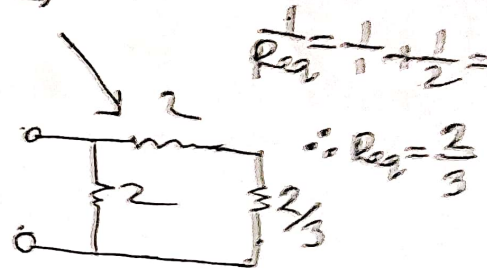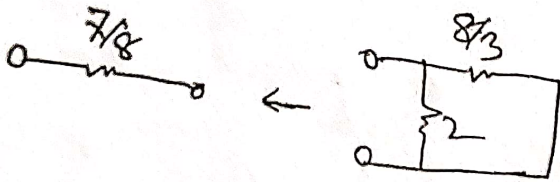

$$\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{2} = \frac{3}{2}$$

$$\therefore R_{eq} = \frac{2}{3}$$

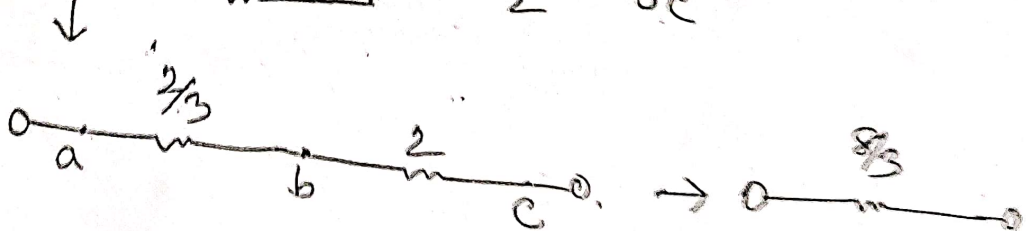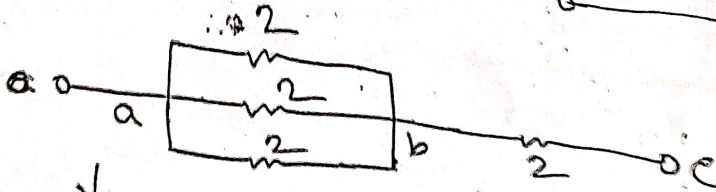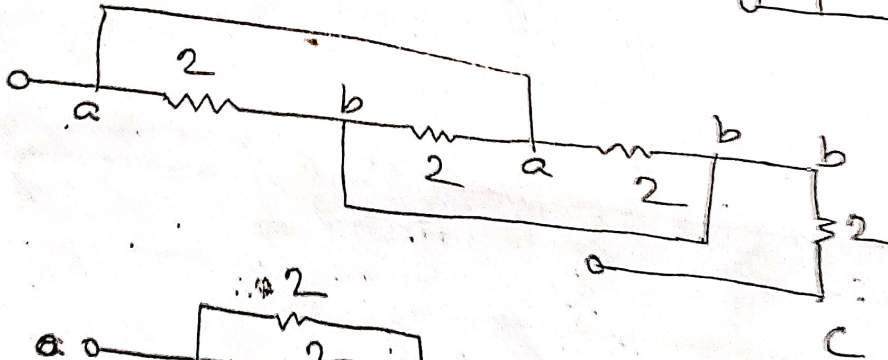


10.09.17
4c-SK8

**** Method of analysis:**

- i. Nodal analysis:
 - a. Find effective node
 - b. Apply KCL
 - c. The effective nodes are equal to the number of system equation.

ii. Mesh analysis.

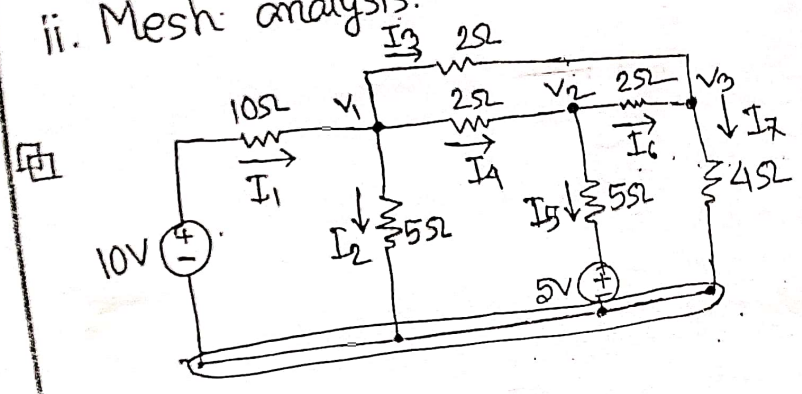

Apply KCL at node - 1,

$$I_1 = I_2 + I_3 + I_4$$

$$\Rightarrow \frac{10 - V_1}{10} = \frac{V_1 - 0}{5} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{2}$$

$$\Rightarrow \frac{10 - V_1}{10} = \frac{2V_1 + 5V_1 - 5V_2 - 5V_2 + 5V_1 - 5V_2}{10}$$

$$\Rightarrow 10 = 13V_1 - 5V_2 - 5V_3$$

$$\Rightarrow 13V_1 - 5V_2 - 5V_3 = 10 \quad \text{--- (1)}$$

Apply KCL at node 2,

$$I_4 = I_5 + I_6$$

$$\Rightarrow \frac{V_1 - V_2}{2} = \frac{V_2 - 5}{5} + \frac{V_2 - V_3}{2}$$

$$\Rightarrow 5V_1 - 5V_2 = 2V_2 - 10 + 5V_2 - 5V_3$$

$$\Rightarrow 5V_1 - 12V_2 + 5V_3 = -10 \quad \text{--- (iv)}$$

Apply KCL at node 3,

$$I_3 + I_6 = I_7$$

$$\Rightarrow \frac{V_1 - V_3}{2} + \frac{V_2 - V_3}{2} = \frac{V_3 - 0}{4}$$

$$\Rightarrow 2V_1 - 2V_3 + 2V_2 - 2V_3 = V_3$$

$$\Rightarrow 2V_1 + 2V_2 - 5V_3 = 0 \quad \text{--- (v)}$$


From equation (i), (ii) and (iii),

$$V_1 = 2.79 \text{ V}$$

$$V_2 = 2.95 \text{ V}$$

$$V_3 = 2.295 \text{ V}$$

(Ans)

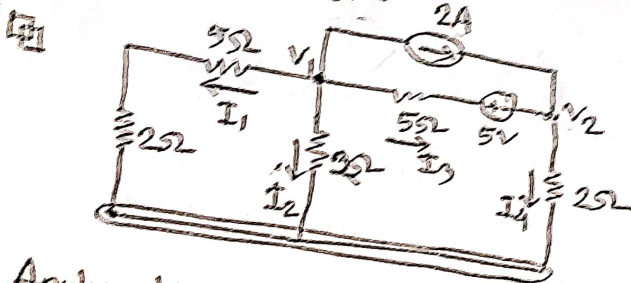

Apply KCL at node -1,

$$I_1 + I_2 + I_3 + 2 = 0$$

$$\Rightarrow \frac{V_1 - 0}{7} + \frac{V_1 - 0}{2} + \frac{V_1 - (5 + V_2)}{5} + 2 = 0$$

$$\Rightarrow 10V_1 - 55V_2 - 14V_1 - 30 - 17V_2 + 140 = 0$$

$$\Rightarrow 59V_1 - 14V_2 = -30 \quad \text{--- (i)}$$

Apply KCL at node-2,

$$I_3 + 2 = I_4$$

$$\Rightarrow \frac{V_1 - (5 - V_2)}{5} + 2 = \frac{V_2 - 0}{2}$$

$$\Rightarrow \frac{V_1 - 5 - V_2 + 10}{5} = \frac{V_2}{2}$$

$$\Rightarrow 2V_1 - 10 - 2V_2 + 20 = 5V_2$$

$$\Rightarrow 2V_1 - 3V_2 = -10 \quad \text{--- (ii)}$$

From equation (i) and (ii),


$$\left. \begin{aligned} V_1 &= -0.9 \text{ V} \\ V_2 &= 1.16 \text{ V} \end{aligned} \right\} \text{ (Ans)}$$

* Super nodes: If a voltage source exist between two nodes then it is called super node.

22 Sub:

EEE-1201
 13.09.17
 5A-SA

□ Nodal analysis with voltage source

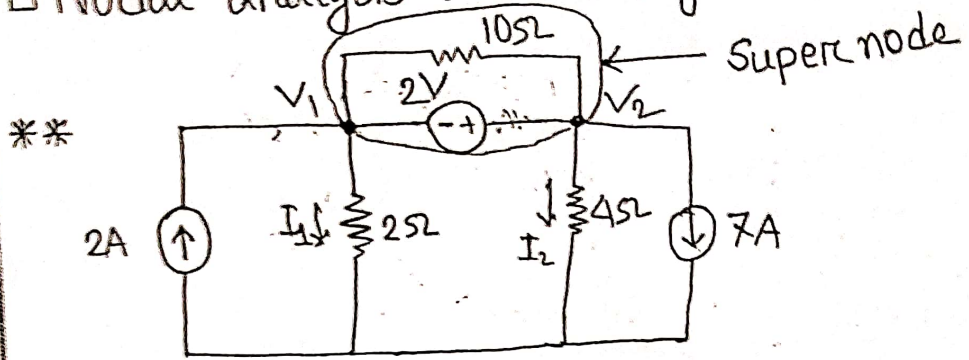

Solve:

Apply KCL at super node,

$$2 = I_1 + I_2 + 7$$

$$\Rightarrow 2 = \frac{V_1 - 0}{2} + \frac{V_2 - 0}{4} + 7$$

$$\Rightarrow 8 = 2V_1 + V_2 + 28$$

$$\Rightarrow 2V_1 + V_2 = -20 \quad \text{--- (i)}$$

Apply KVL for super node,

$$V_1 - V_2 = -2 \quad \text{--- (ii)}$$


from equation (i) & (ii),

$$V_1 = -7.33V$$

$$V_2 = -5.33V.$$

11/11/2020
 18/09/17
 5N-6N

SUN
 Time: _____
 Date: 7/7

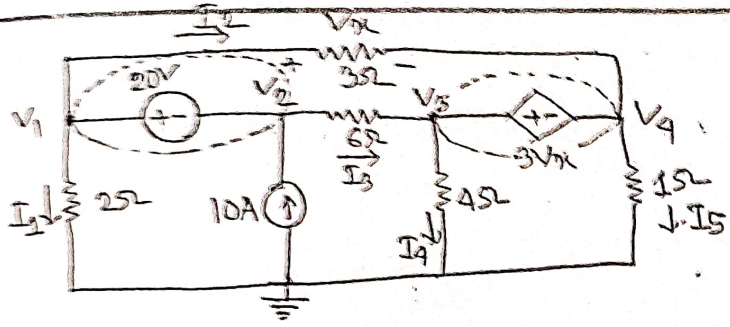

Solve:

Apply KCL at super node (1):

$$I_1 + I_2 + I_3 = 10$$

$$\Rightarrow \frac{V_1}{25} + \frac{V_1 - V_4}{3} + \frac{V_2 - V_3}{3} = 10$$

$$\Rightarrow 5V_1 + V_2 - V_3 - 2V_4 = 60 \quad \text{--- (I)}$$

Apply KCL at super node (2)

$$I_3 + I_2 = I_4 + I_5$$

$$\Rightarrow \frac{V_1 - V_4}{3} + \frac{V_2 - V_3}{3} = \frac{V_3}{4} + \frac{V_4}{15}$$

$$\Rightarrow 8V_1 + 4V_2 - 4V_3 - 8V_4 = 6V_3 + 24V_4$$

$$\Rightarrow 4V_1 + 2V_2 - 5V_3 - 16V_4 = 0 \quad \text{--- (II)}$$

From equation (III) $\Rightarrow V_1 = V_2 + 20$

$$\text{(I)} \Rightarrow 6V_2 - V_3 - 2V_4 = -40 \quad \text{--- (V)}$$

$$\text{(II)} \Rightarrow 6V_2 - 5V_3 - 16V_4 = -80 \quad \text{--- (VI)}$$

$$\text{(IV)} \Rightarrow 3V_2 - V_3 - 2V_4 = -60 \quad \text{--- (VII)}$$

from super node (1)

$$V_1 - V_2 = 20 \quad \text{--- (III)}$$

$$V_1 - V_4 = V_x$$

from super node (2)

$$V_3 - V_4 = 3V_x$$

$$\Rightarrow V_3 - V_4 = 3(V_1 - V_4)$$

$$\Rightarrow 3V_1 - V_3 - 2V_4 = 0 \quad \text{--- (IV)}$$

24

Sub: _____

SAT SUN MON TUE WED THU FRI

Time: _____

Date: / /


From equation (V), (VI), (VII) ;

$$V_2 = 6.67V, V_3 = 173.33V, V_4 = -46.67V.$$

$$\therefore V_1 = 6.67 + 20 = 26.67V.$$

(Ans:)

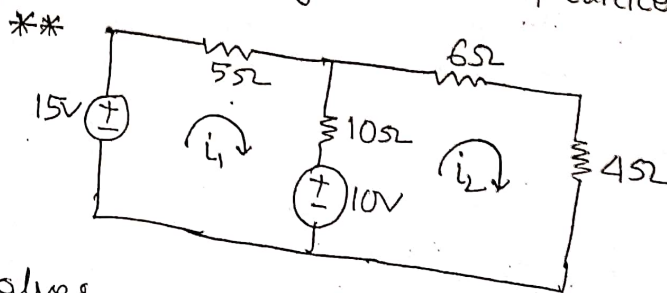Mesh analysis: loop current \neq Branch current



Solve:

Apply KVL at loop - ①

$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

$$\Rightarrow 15i_1 - 10i_2 = 5$$

$$\Rightarrow 3i_1 - 2i_2 = 1 \quad \text{--- ①}$$

Apply KVL at loop - ②

$$6i_2 + 4i_2 - 10 + 10(i_2 - i_1) = 0$$

$$\Rightarrow 20i_2 - 10i_1 = 10$$

$$\Rightarrow 2i_2 - i_1 = 1 \quad \text{--- ②}$$


from equation ① & ②

$$i_1 = 1A, i_2 = 4$$

Ans

Sub:

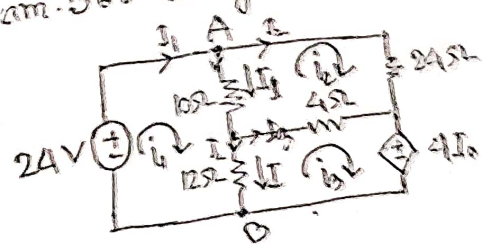Exam. 56: Using mesh analysis find out i_1, i_2, i_3, I_0 / 16.09.17
 50. PEE



loop current = i
 Branch " = I

Apply KVL at loop-①
 $-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$
 $\Rightarrow 22i_1 + 10i_2 - 12i_3 = 24$ ——— ①

Apply KVL at loop-②
 $24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$
 $\Rightarrow -10i_1 + 38i_2 - 4i_3 = 0$
 $\Rightarrow 10i_1 - 38i_2 + 4i_3 = 0$ ——— ②

Apply KVL at loop ③
 $4i_3 + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$
 $\Rightarrow 4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$
 $\Rightarrow -8i_1 - 8i_2 + 16i_3 = 0$
 $\Rightarrow i_1 + i_2 - 2i_3 = 0$ ——— ③

from ①, ② & ③
 $i_1 = 0.77A, i_2 = 0.15A, i_3 = -0.46A$

$P_{12} = I \times 12^2$
 $= 1.29 \times 12^2$
 $= 177.12 \text{ watt}$

Apply KCL at node A.
 $i_1 = I_0 + i_2$
 $\Rightarrow I_0 = i_1 - i_2$
 $\Rightarrow I_0 = 0.77 - 0.15$
 $= 0.62A$


$$P = I^2 R$$

$$= \frac{V^2}{R}$$

Apply KCL at node B
 $I + i_3 = i_1$
 $I = 1.23A$

** Super mesh:

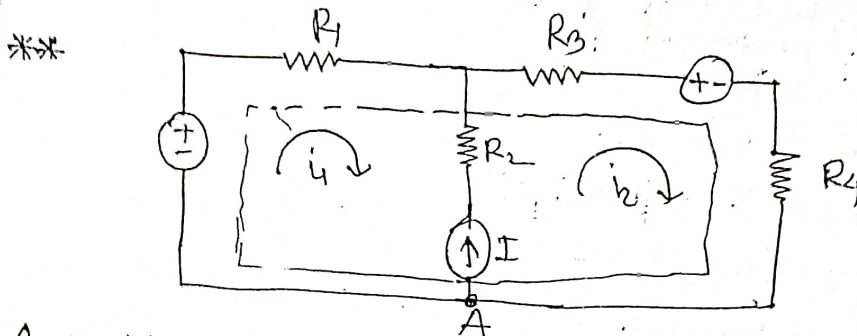If a current source and a resistor in series exist between two loop then that is called super mesh.



Apply KVL at super mesh


$$-V_1 + i_1 R_1 + i_2 R_3 + V_2 + i_2 R_4 = 0 \quad \text{--- (I)}$$

KCL at node A,

$$I + i_1 = i_2$$

$$\Rightarrow I = i_2 - i_1 \quad \text{--- (II)}$$

$$i_1, i_2 = ?$$

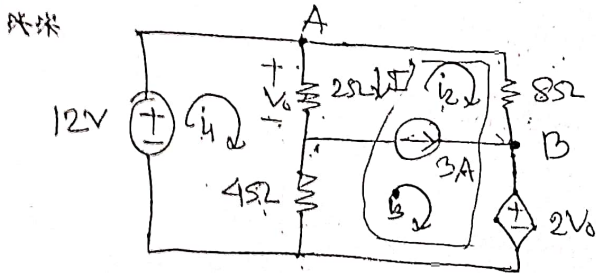

Apply KVL at super mesh (I) loop (I)

$$-12 + 2(i_1 - i_2) + 4(i_1 - i_2) = 0$$

$$\Rightarrow 6i_1 - 6i_2 - 4i_3 = 12 \quad \text{--- (I)}$$

Apply KVL at super mesh

$$8i_2 + 2(i_2 - i_1) + 2V_0 + 4(i_3 - i_1) = 0 \quad \text{--- (I)}$$

Apply KCL at node A

$$i_1 = I + i_2$$

$$\Rightarrow I = i_1 - i_2$$

$$V_0 = 2I = 2(i_1 - i_2)$$

$$\text{From (I)} \Rightarrow 8i_2 + 2i_2 - 2i_1 + 4i_1 - 4i_2 + 4i_3 - 4i_1 = 0$$

$$\Rightarrow -2i_1 + 6i_2 + 4i_3 = 0$$

$$\Rightarrow i_1 - 3i_2 - 2i_3 = 0 \quad \text{--- (II)}$$

Apply KCL at node B.

$$i_2 + 3 = i_1$$

$$\text{(II)} \Rightarrow i_2 + 3 - 3i_2 - 2i_3 = 0$$

$$\Rightarrow 2i_2 + 2i_3 = 3 \quad \text{--- (IV)}$$

$$\text{(I)} \Rightarrow 6(i_2 + 3) - 2i_2 - 4i_3 = 12$$

$$\Rightarrow 4i_2 - 4i_3 = -6 \quad \text{--- (V)}$$

from equation (IV) and (V)

$$i_2 = 0A, i_3 = 1.5A$$

$$i_1 = 0 + 3 = 3A$$

(Ans!)

Chapter 4.

17.09.17

SC - EEE

Theorem for circuit:

130 page

- i. Superposition theorem ✓
- ii. Source transformation theorem
- iii. Norton's theorem
- iv. Thevenin's theorem
- v. Maximum power transfer theorem.

*A linear circuit is one whose output is linearly related (or directly proportional) to its input.


[A] Superposition:

The superposition principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.

See example from book.

To apply the superposition principle, we must keep two things in mind:

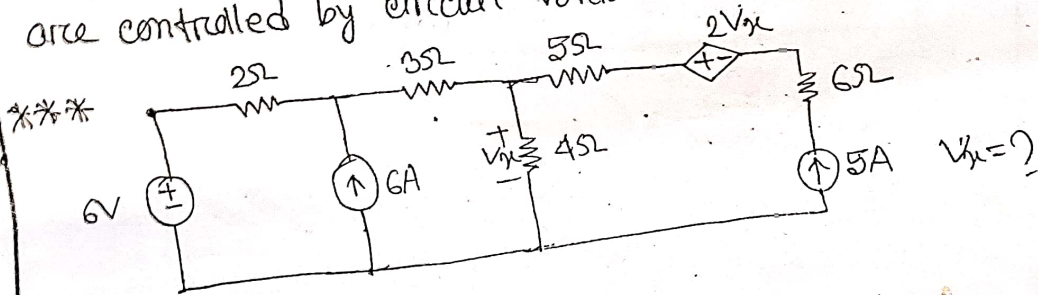1. We consider one independent source at a time while all other independent source are turned off. This implies that we replace every voltage source by 0V (or a short circuit), and every current source by 0A (or an open circuit). This way we obtain a simpler and more manageable circuit.
2. Dependent sources are left intact, because they are controlled by circuit variables.




$$V_x = V_{x_1} + V_{x_2} + V_{x_3}$$

Where, V_{x_1} , V_{x_2} , V_{x_3} are due to the 6V, 6A, 5A source respectively.

To obtain V_{x_1} , we turn off the 6A and 5A source.

On the other hand, Dependent source is short/open as follows

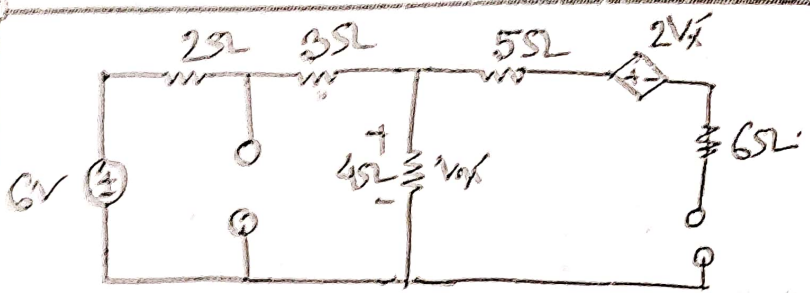NOTE: Independent source is voltage source is short
 2. Current source is open.




$V = \frac{\text{resistance of passage}}{\text{total resistance}} \times \text{source}$

$I = \frac{\text{Parallel resistance}}{\text{flowing and parallel resistance}} \times \text{source}$

$$V_{x1} = \frac{4}{2+3+4} \times 6 = \frac{4}{9} \times 6 = \frac{8}{3}$$

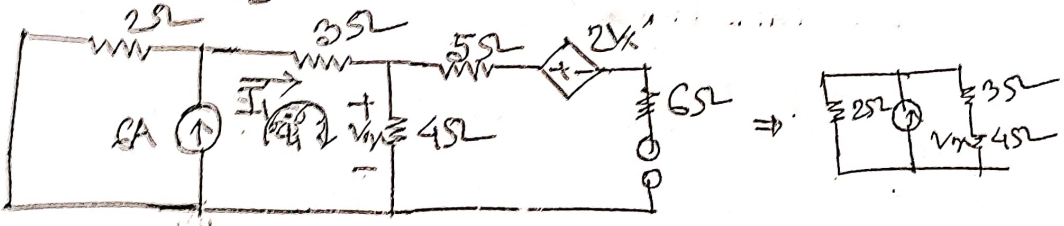To obtain V_{x2} turn off 6V and 5A source.




$$I = \frac{2}{2+3+4} \times 6 = \frac{4}{3}$$

$$V_{x2} = 4 \times \frac{4}{3} = \frac{16}{3} \text{ V}$$

DC source frequency zero

To obtain V_{x3} active 5A source

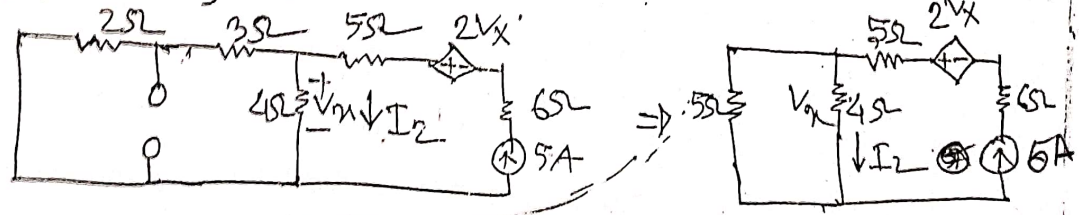

$$I_2 = \frac{5}{5+4} \times 5 = \frac{25}{9}$$

$$V_{x3} = 4 \times \frac{25}{9} = \frac{100}{9}$$



$$V_x = V_{x1} + V_{x2} + V_{x3} = \frac{8}{3} + \frac{16}{3} + \frac{100}{9} = 19.11 \text{ V}$$

Sub:
 * Source Transf



Sub:

20-09-17
 GA-EEE

* Source transformation method:

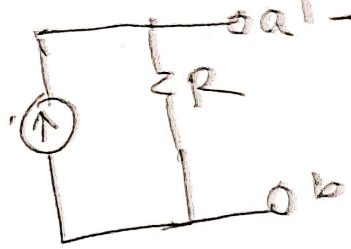
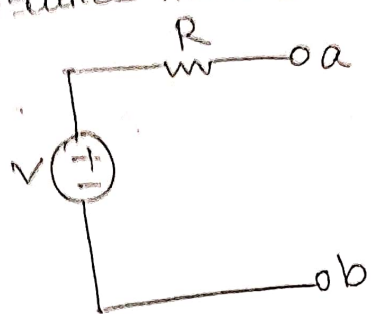



$V = IR, I = \frac{V}{R}$

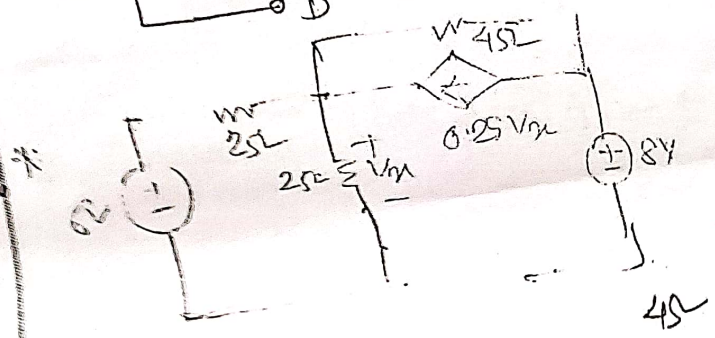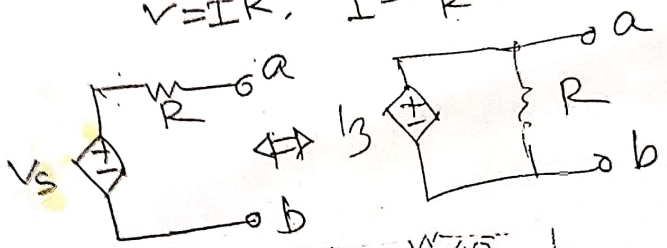

find V_x using source transfer technique.

$i = \frac{6}{2} = 3A$

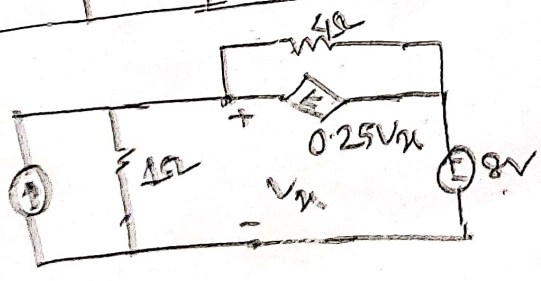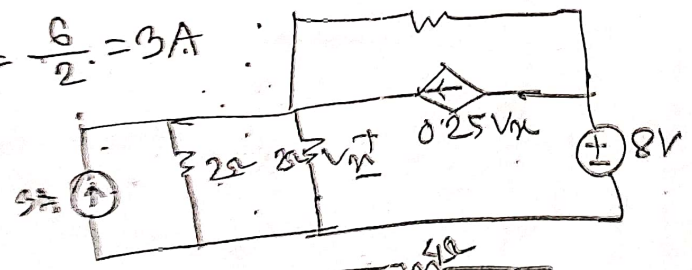

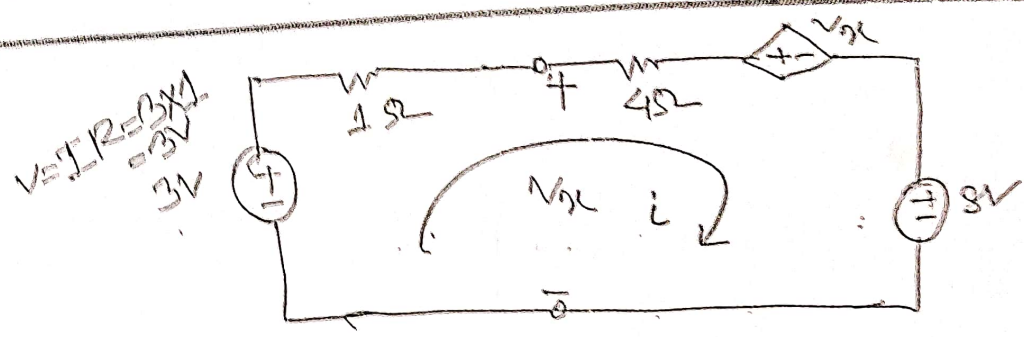


Apply KVL

$$-3 + i \times 1 + 4i + V_x + 8 = 0$$

$$\Rightarrow -3 + i + V_x = 0$$

$$\Rightarrow V_x = 3 - i$$

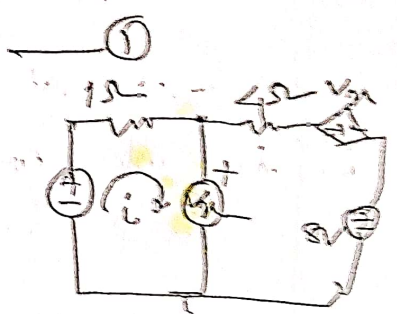


from (1)


$$-3 + i + 4i + 3 - i + 8 = 0$$

$$\Rightarrow 4i = -8$$

$$i = -2 \quad (\text{Ans})$$

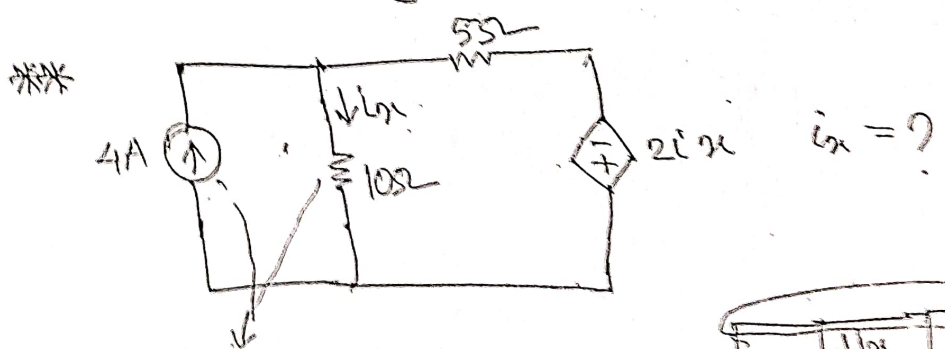

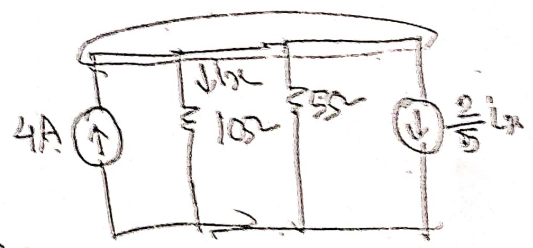Change করা যায় না।
কারণ resistence ছাড়া
current transfer হতে পারত না।



53

Apply KCL at node

$$4 = i_{10} + i_1 + \frac{2}{5} i_{10}$$

$$i_{10} = \frac{V_1}{10}$$


$$\Rightarrow 4 = \frac{V_1}{10} + \frac{V_1}{5} + \frac{2}{5} \cdot \frac{V_1}{10}$$

$$\Rightarrow 4 = \frac{3V_1}{10} + \frac{2}{5} \cdot \frac{V_1}{10} = \frac{3V_1}{10} + \frac{2V_1}{50}$$


$$\Rightarrow 4 = \frac{17V_1}{50}$$

$$\Rightarrow V_1 = \frac{4 \times 50}{17} = 11.76 \text{ V}$$

□ Thevenin's theorem:

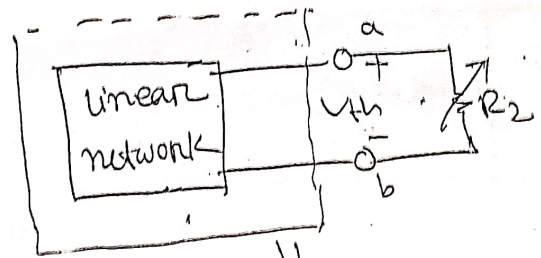


$V_{th} = V_{open}$
 circuit

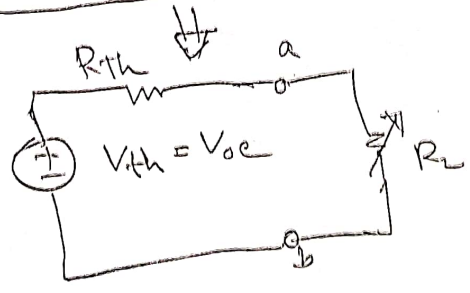

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{1V}{I} = R_{th}$$

Voltage short $V=0$
Current open $I=0$



dependent source start →

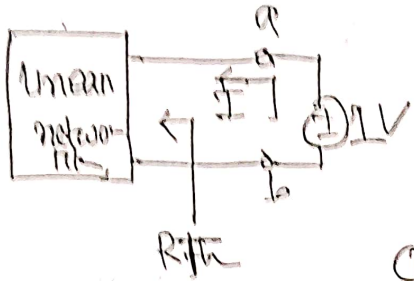



Application of thevenin's theorem.
Maximum power transfer.

Example 4.8:



HW: 4.9

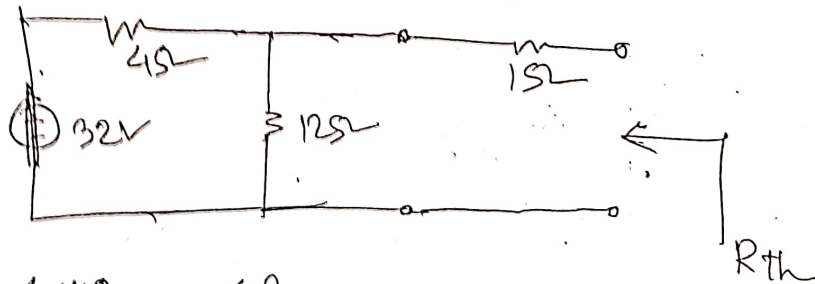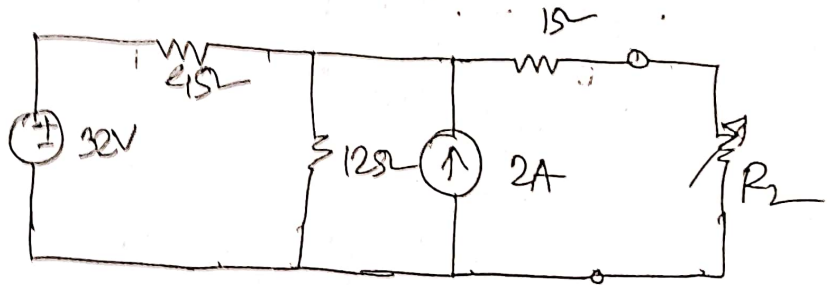
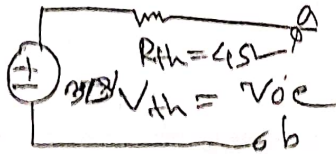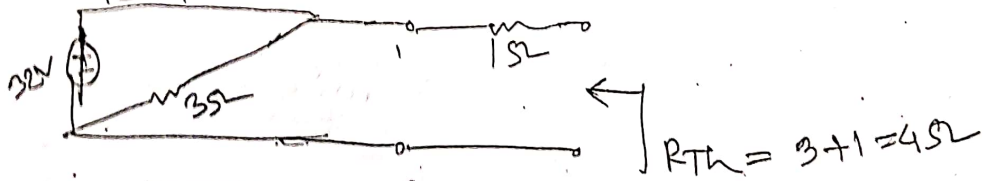
$$R_p = \frac{4 \times 12}{12 + 4} = \frac{48}{16} = 3\Omega$$




Sub: _____

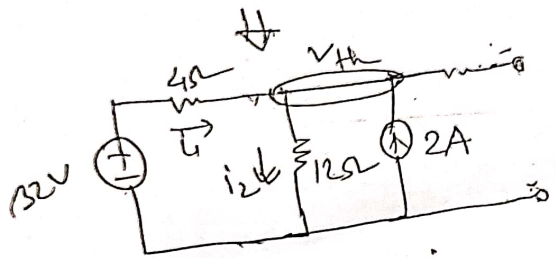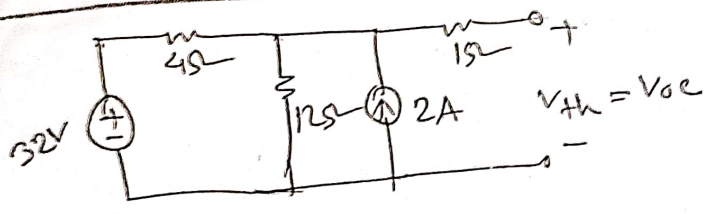

$$\begin{aligned}
 \cancel{i_1} &= i_1 + 2 = i_2 \\
 \Rightarrow \frac{32 - V_{th}}{4} + 2 &= \frac{V_{th}}{12} \\
 \Rightarrow \frac{40 - V_{th}}{4} &= \frac{V_{th}}{12} \\
 \Rightarrow 480 - 12V_{th} &= 4V_{th} \\
 \Rightarrow 16V_{th} &= 480 \\
 \Rightarrow V_{th} &= 30V
 \end{aligned}$$

* Source transformation theorems


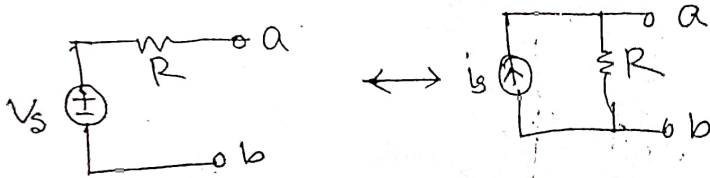
A source transformation is the process of replacing a voltage source V_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa.



$$V_s = i_s R, \text{ or } i_s = \frac{V_s}{R}$$


* Thevenin's theorem

A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{th} in terminals and R_{th} is the input or equivalent resistance in series with a resistor R_{th} .

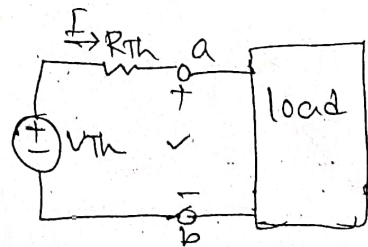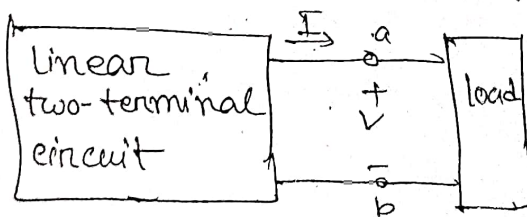


Exm 4.9: Find the thevenin circuit:

23.09.17
GB-EEE

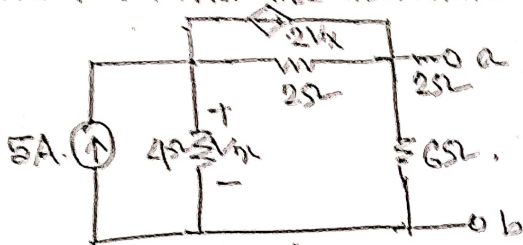

Solve:

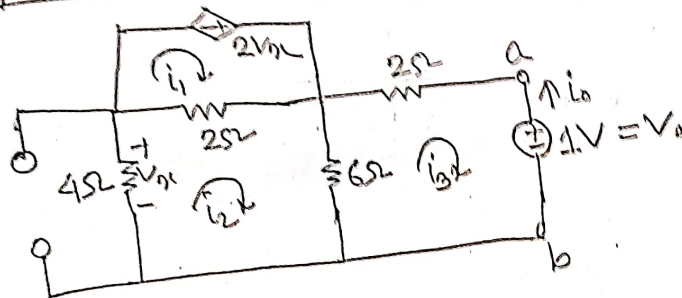

$R_{TH} = ?$
 $V_{TH} = ?$

Applying mesh analysis to loop 1 \Rightarrow

$$-2V_{0x} + 2(i_1 - i_2) = 0$$

$$\Rightarrow V_{0x} = i_1 - i_2$$

$$\Rightarrow -4i_2 = i_1 - i_2$$

$$\Rightarrow i_1 = -3i_2 \quad \text{--- (I)}$$

$$V_{0x} = -4i_2$$

Apply KVL at loop 2 $\Rightarrow 4i_2 + 2(i_2 - i_1) + 6(i_2 - i_3) = 0$ --- (II)

Apply KVL at loop 3 $\Rightarrow 6(i_3 - i_2) + 2i_3 + 1 = 0$ --- (III)

from (I), $4i_2 + 2(i_2 + 3i_2) + 6(i_2 - i_3) = 0$

$$\Rightarrow 4i_2 + 8i_2 + 6i_2 - 6i_3 = 0$$

$$\Rightarrow 18i_2 - 6i_3 = 0 \quad \text{--- (IV)}$$


$$\text{From (III)} \Rightarrow -6i_2 + 8i_3 = -1 \quad \text{--- (V)}$$

$$\text{(IV) and (V)} \Rightarrow i_2 = -\frac{1}{18} \text{ A} \quad i_3 = -\frac{1}{6} \text{ A}$$

$$i_0 = -i_3 = \frac{1}{6} \text{ A}$$

$$\therefore R_{th} = \frac{1 \text{ V}}{\frac{1}{6}} = 6 \Omega$$

To get V_{th} , we find V_{oc} in the circuit.

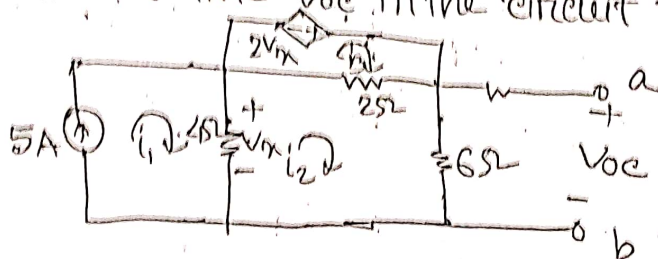

Loop 1

$$i_1 = 5 \text{ A}$$

Loop 2

$$-2V_x + 2(i_3 - i_2) = 0$$

$$\Rightarrow V_x = i_3 - i_2 \quad \text{--- (I)}$$

Loop 2

$$4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0$$

$$\Rightarrow 12i_2 - 4i_1 - 2i_3 = 0$$

$$\Rightarrow 12i_2 - 2i_3 = 20 \quad [\because i_1 = 5 \text{ A}] \quad \text{--- (II)}$$

$$\text{again, } V_x = 4(i_1 - i_2)$$

$$\Rightarrow i_3 - i_2 = 4(5 - i_2)$$

$$\Rightarrow i_3 - i_2 = 20 - 4i_2$$

$$\Rightarrow 3i_2 + i_3 = 20 \quad \text{--- (III)}$$


Sub: _____

Time: _____ Date: / /

From (i) and (ii) $i_2 = \frac{10}{3} A$, $i_3 = 10 A$.

$$V_{oc} = V_{Th} = 6 i_2 = 20 V.$$


∴ The thevenin equivalent is shown :

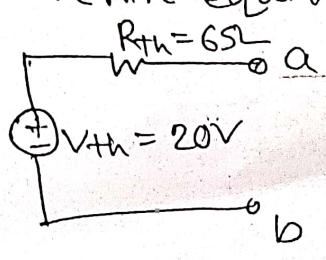

$$R_{Th} = \frac{V_{Th}}{I_N} = R_N$$


Northon's theorem:

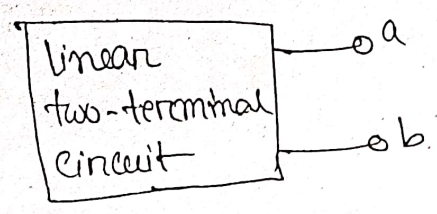Northon's theorem states that a linear two terminal circuit can be replaced by an equivalent circuit consisting of a current source I_N in parallel with a resistor R_N .



Where,
 I_N = short circuit current.

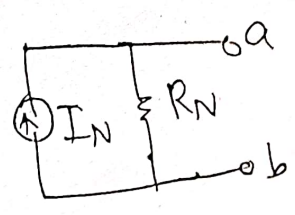R_N = input or equivalent resistance when independent source are turned off.




$$R_{Th} = \frac{V_{oc}}{I_{sc}} = R_N$$

$$R_N = R_{Th} \quad I_N = I_{sc}$$

Sub: _____

** Maximum power transfer theorem

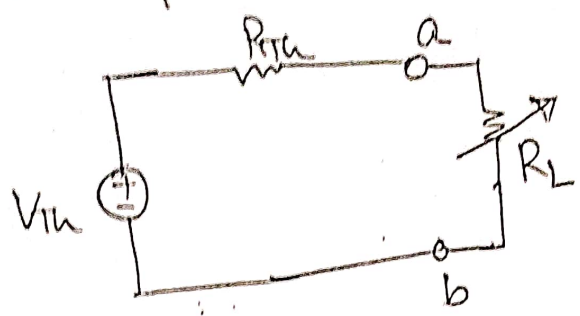

The thevenin equivalent is useful in finding the maximum power a linear circuit can deliver to a load. We assume that we can adjust the load resistance R_L . If the entire circuit is replaced by its thevenin equivalent except for the load, as shown in the figure, the power delivered to the load is,

$$P = i^2 R_L \qquad i = \frac{V_{Th}}{R_{Th} + R_L}$$

$$\Rightarrow P = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 \cdot R_L \quad \text{--- (1)}$$

$$\frac{dP}{dR_L} = 0$$

$$\Rightarrow V_{Th}^2 \left[\frac{(R_{Th} + R_L)^{-2} - 2R_L(R_{Th} + R_L)^{-3}}{(R_{Th} + R_L)^4} \right] = 0$$

$$\Rightarrow V_{Th}^2 \left[\frac{R_{Th} + R_L - 2R_L}{(R_{Th} + R_L)^3} \right] = 0$$

$$\Rightarrow R_{Th} + R_L - 2R_L = 0$$

$$\Rightarrow R_{Th} - R_L = 0$$

$$\Rightarrow R_{Th} = R_L$$

∴ Maximum power is transfer to the load when the load resistance equals the thevenin resistance as seen from the load ($R_L = R_{Th}$).

∴ from ① ⇒

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

Chapter - 9

Sinusoids and phasors

24.09.17

6C-EEE

A sinusoid is a signal that has the form of the sine or cosine function.

Consider the sinusoidal voltage

$$v(t) = V_m \sin \omega t$$



Where, V_m = the amplitude of the sinusoid

ω = the angular frequency in radians/s

ωt = the argument of the sinusoid.

$$T = \frac{2\pi}{\omega}$$

$$f = \frac{1}{T}$$

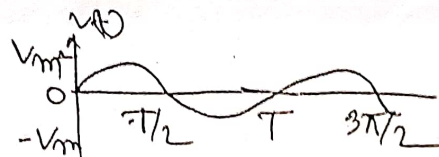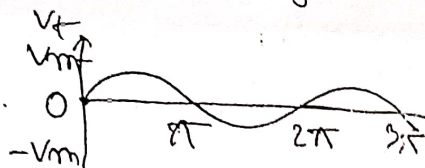

$$50 \text{ Hz}; \quad T = \frac{1}{50} = 20 \text{ ms}$$

Phasors:

A phasor is a complex number that represents the amplitude and phase of a sinusoid.

A complex number z can be written in rectangular form as, $z = x + jy$; $j = \sqrt{-1}$

Where, x = real part. y = imaginary part.

Sub: _____

SAT SUN MON TUE WED THU FRI
Time: _____ Date: / /

The complex number z can be also be written in polar or exponential form as.

$$z = r \angle \phi = r e^{j\phi}$$

Where r is the magnitude of z , and ϕ is the phase of z . We notice that z can be represented in three ways.

$$z = x + jy \quad \text{Rectangular form}$$

$$z = r \angle \phi \quad \text{Polar form}$$


$$z = r e^{j\phi} \quad \text{Exponential form}$$

$$r = \sqrt{x^2 + y^2}, \quad \phi = \tan^{-1} \frac{y}{x}$$

$$\text{and, } x = r \cos \phi, \quad y = r \sin \phi$$

z may be written as,
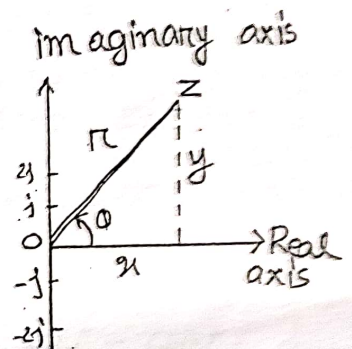
$$z = x + jy = r \angle \phi = r (\cos \phi + j \sin \phi)$$



Sub: _____

Kirchhoff's Laws in the frequency domain:

For KVL, let v_1, v_2, \dots, v_n be the voltages around a closed loop. Then,

$$v_1 + v_2 + \dots + v_n = 0$$

In the sinusoidal steady state, each voltage may be written ~~a closed loop~~ in cosine form, so that Equation becomes.

$$V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \dots + V_{mn} \cos(\omega t + \theta_n) = 0 \quad \text{①}$$

| Time domain | Phasor |
|---|---|
| $V_1(t) = V_{m1} \cos(\omega t + \theta_1)$ | $V_1 = V_{m1} \angle \theta_1$ class |
| $V_2(t) = V_{m2} \cos(\omega t + \theta_2)$ | $V_2 = V_{m2} \angle \theta_2$ <u>lecture</u> |
| $V_n(t) = V_{mn} \cos(\omega t + \theta_n)$ | $V_n = V_{mn} \angle \theta_n$ |

From equation ①

$$V_{m1} \angle \theta_1 + V_{m2} \angle \theta_2 + \dots + V_{mn} \angle \theta_n = 0$$

This can be written as.

$$\text{Re}(V_{m1} e^{j\theta_1} e^{j\omega t}) + \text{Re}(V_{m2} e^{j\theta_2} e^{j\omega t}) + \dots + \text{Re}(V_{mn} e^{j\theta_n} e^{j\omega t}) = 0$$

$$\text{or, } \text{Re}[(V_{m1} e^{j\theta_1} + V_{m2} e^{j\theta_2} + \dots + V_{mn} e^{j\theta_n}) e^{j\omega t}] = 0$$

Sub: _____

SAT SUN MON TUE WED THU FRI

Time: _____ Date: / /

If we let, $V_k = V_{mk} e^{j\omega_k t}$, then
$$\text{Re}[(V_1 + V_2 + \dots + V_n) e^{j\omega t}] = 0$$

Since $e^{j\omega t} \neq 0$,
$$V_1 + V_2 + \dots + V_n = 0.$$

indicating that Kirchhoff's voltage law holds for phasors.

By following a similar procedure, we can show that Kirchhoff's current law holds for phasors. If we let i_1, i_2, \dots, i_n be the current leaving or entering a closed surface in a network at time t , then

$$i_1 + i_2 + \dots + i_n = 0$$


If I_1, I_2, \dots, I_n are the phasor forms of the sinusoids i_1, i_2, \dots, i_n then

$$I_1 + I_2 + \dots + I_n = 0.$$

which is Kirchhoff's current law ~~forms of the sinusoids~~ in the frequency domain.

| Time domain | Phasor |
|---|--------------------------------|
| $i_1 = I_{m1} \cos(\omega t + \theta_1)$ | $I_1 = I_{m1} \angle \theta_1$ |
| $i_2 = I_{m2} \cos(\omega t + \theta_2)$ | $I_2 = I_{m2} \angle \theta_2$ |
| $i_3 = I_{m3} \cos(\omega t + \theta_3)$ | $I_3 = I_{m3} \angle \theta_3$ |
| $\therefore i_1(t) + i_2(t) + \dots + i_n(t) = 0$ | |
| $I_1 + I_2 + \dots + I_n = 0$ | |

* Impedance combinations:

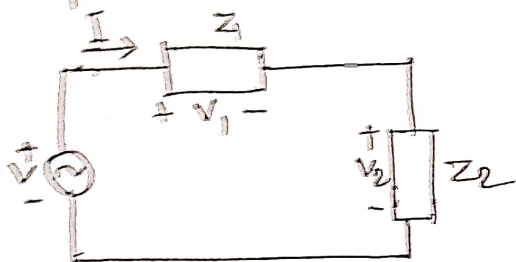


$$I = \frac{V}{Z_1 + Z_2}$$

$$V_1 = Z_1 I \text{ and } V_2 = Z_2 I$$

$$V_1 = \frac{Z_1}{Z_1 + Z_2} \times V, \quad V_2 = \frac{Z_2}{Z_1 + Z_2} \times V.$$

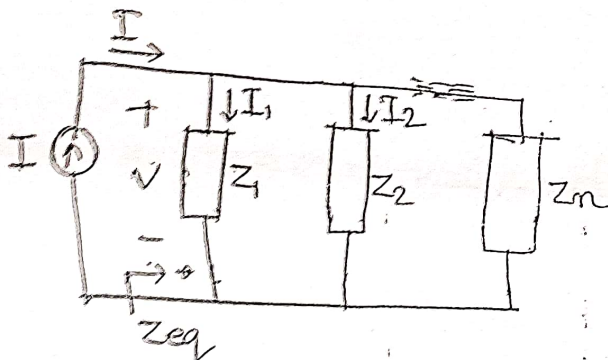
$$\therefore V_n = \frac{Z_n}{Z_1 + Z_2 + \dots + Z_n} \times V$$



$$I_1 = \frac{Z_2}{Z_1 + Z_2} \times I \quad I_2 = \frac{Z_1}{Z_1 + Z_2} \times I$$

Sub: CE-1600

031017
7A-EEE


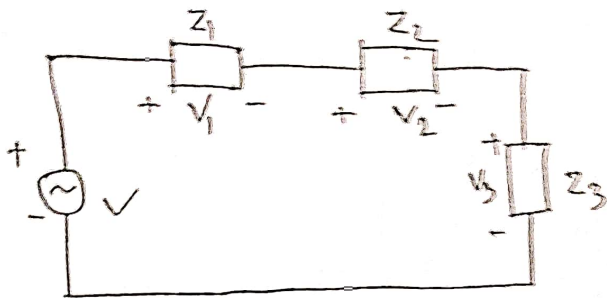


$$V = V_m \sin(\omega t + \theta) \text{ V}$$

$$= V_m \angle \theta$$

Voltage divider rule:
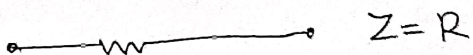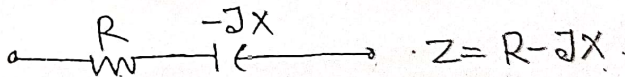
$$V_3 = \frac{Z_3}{Z_1 + Z_2 + Z_3} \times V$$



If can be,

$$Z = R + jX$$

$$= R$$

$$= -jX$$


$$= +jX$$

$$Z = R + jX_L$$

$$Z = R - jX_C$$

Current divider rule:

একটি সোর্স parallel- থাকতে হয়।

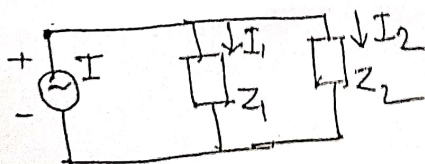

$$V = IZ$$

Sub: _____


Time: _____

Date: / /

Sub: _____



**Example 9.10:

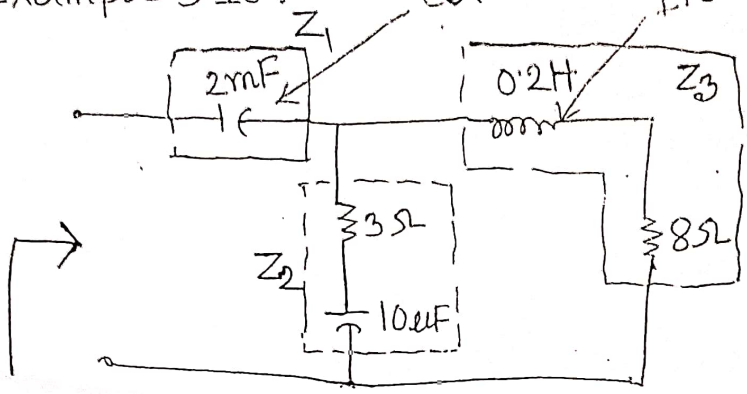

X_C Capacitor

X_L Inductor

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

Z_{in}
 $\omega = 50 \text{ rad/s}$. $Z_{in} = ?$

$$X_{C1} = \frac{1}{\omega C} = \frac{1}{50 \times 2 \times 10^{-3}} = 10 \Omega$$

$$X_L = \omega L = 50 \times 0.2 = 10 \Omega$$

$$Z_1 = -jX_{C1} = -j10 \Omega$$

$$Z_2 = R - jX_{C2}$$

$$= 3 - j \cdot \frac{1}{50 \times 10 \times 10^{-3}}$$

$$= (3 - j2) \Omega$$

$$Z_3 = R + jX_L = (8 + j10) \Omega$$

$$Z_{in} = Z_1 + Z_2 \parallel Z_3$$

$$= Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3}$$


$$= -j10 + \frac{(3 - j2)(8 + j10)}{3 - j2 + 8 + j10} = 11.52 \angle -78.3^\circ \text{ } \Omega$$


A_2

Sub: _____

SAT SUN MON TUE WED THU FRI
Time _____ Date: / /

* *

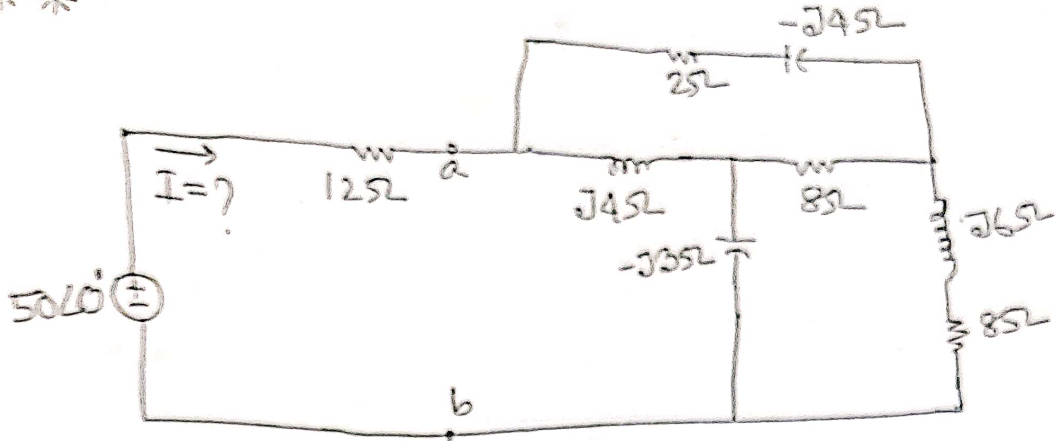

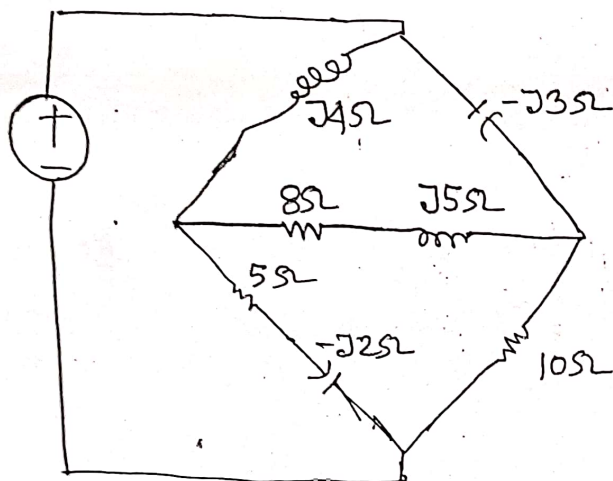

Sub: _____


SAT SUN MON TUE WED THU FRI

Time: _____ Date: / /

Chapter 10

Sinusoidal steady-state Analysis

Example 10.2: Find i_x from the figure.

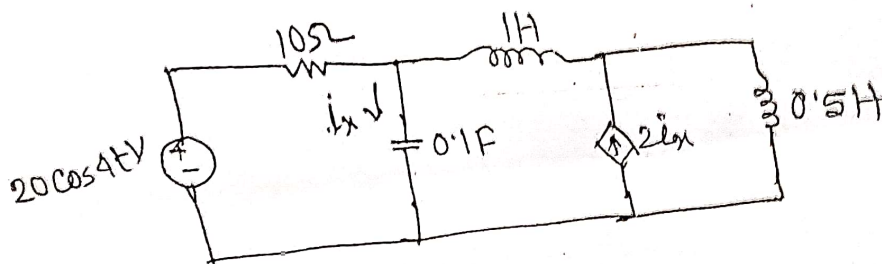

Solve:


We first convert the circuit to the frequency domain:

$$20 \cos 4t \Rightarrow 20 \angle 0^\circ, \quad \omega = 4 \text{ rad/s}$$

$$1 \text{ H} \Rightarrow j\omega L = j4$$

$$0.5 \text{ H} \Rightarrow j\omega L = j2$$
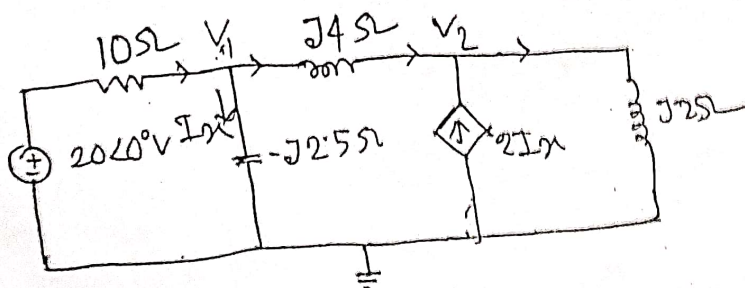
$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega C} = -j2.5$$



Sub: _____

SAT SUN MON TUE WED THU FRI

Time: _____ Date: / /

Apply KCL at node 1.

$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

$$\text{OR, } (1 + j1.5)V_1 + j2.5V_2 = 20 \quad \text{--- (1)}$$

Apply KCL at node 2

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

But, $I_x = V_1 / -j2.5$. substituting this gives

$$\frac{2V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

By simplifying we get

$$11V_1 + 15V_2 = 0 \quad \text{--- (2)}$$

Equation (1) and (2) can be put in matrix form as

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

We obtain the determinants as.

$$\Delta = \begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix} = 15 - j35 \quad \Delta_2 = \begin{vmatrix} 1 + j1.5 & 20 \\ 11 & 0 \end{vmatrix} = -220$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300$$

Sub: _____

SAT SUN MON TUE WED THU FRI

Time: _____ Date: / /

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{300}{15 - j5} = 18.97 \angle 18.43^\circ \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-220}{15 - j5} = 13.91 \angle 98.3^\circ \text{ V}$$

The current I_x is given by,


$$I_x = \frac{V_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} = 7.59 \angle 108.4^\circ \text{ A}$$

Transforming this to the time domain,

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

(Ans)

*** Example 10.4

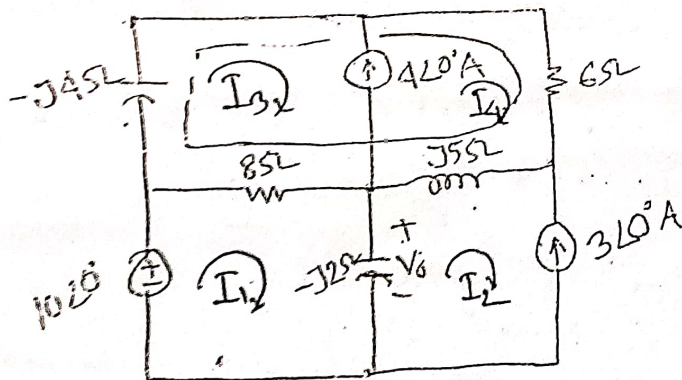

$V_0 = ?$

Solve:

Apply KVL at supermesh.

$$-10 + 8(I_1 - I_2) - 72(I_4 - I_4) = 0$$

$$\Rightarrow (8 - j2)I_1 + j2I_4$$

Sub: _____

SAT SUN MON TUE WED THU FRI

Time: _____ Date: / /

As shown in fig meshes 3 and 4 from a supermesh due to the current source between the meshes. For mesh 1.

$$-10 + (8 - j2)I_1 - (-j2)I_2 - 8I_3 = 0$$

$$\Rightarrow (8 - j2)I_1 + j2I_2 - 8I_3 = 10 \quad \text{--- (1)}$$

For mesh 2, $I_2 = -3$ --- (2)

For the supermesh,

$$(8 - j4)I_3 - 8I_1 + (6 + j5)I_4 - j5I_2 = 0 \quad \text{--- (11)}$$

Due to the current source between meshes 3 and 4 at node A.

$$I_4 = I_3 + 4 \quad \text{--- (12)}$$

from equation (1) and (2).

$$(8 - j2)I_1 - 8I_3 = 10 + j6 \quad \text{--- (13)}$$

from (11) and (12).

$$-8I_1 + (14 + j)I_3 = -24 - j35 \quad \text{--- (14)}$$

Sub: _____

SAT SUN MON TUE WED THU FRI

Time: _____ Date: / /

From (v) and (vi)

$$\begin{bmatrix} 8-j2 & -8 \\ -8 & 14+j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10+j6 \\ -24-j35 \end{bmatrix}$$

We obtain the following determinants,

$$\Delta = \begin{vmatrix} 8-j2 & -8 \\ -8 & 14+j \end{vmatrix} = 112 + j8 - j28 + 2 - 64 = 50 - j20$$

$$\Delta_1 = \begin{vmatrix} 10+j6 & -8 \\ -24-j35 & 14+j \end{vmatrix} = 140 + j10 + j84 - 6 - 192 - j280 = -58 - j186$$

Current I_1 is obtained as,

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-58 - j186}{50 - j20} = 3.618 \angle 274.5^\circ \text{ A}$$

The required voltage V_0 is,

$$\begin{aligned} V_0 &= -j2(I_1 - I_2) = -j2(3.618 \angle 274.5^\circ + 3) \\ &= -j7.234 - j6.568 = 9.756 \angle 222.32^\circ \text{ V} \end{aligned}$$

A2

Sub: _____


SAT SUN MON TUE WED THU FRI

Time: _____ Date: / /

Alternating current (Ac) and voltage

10.10.17
8A. EEE

⇒ Average value and rms value.

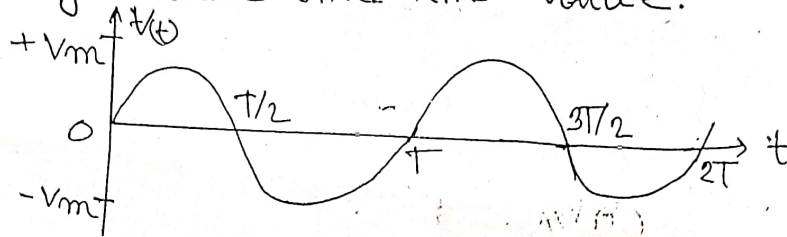

We know, $v(t) = V_m \sin \omega t$

$$V_{\text{average}} = \frac{1}{T} \int_0^T v(t) dt$$

$$= \frac{1}{T} \left[\int_0^{T/2} V_m \sin \omega t dt + \int_{T/2}^T V_m \sin \omega t dt \right]$$

$$= \frac{V_m}{T} \left[\frac{-\cos \omega t}{\omega} \right]_0^{T/2} + \frac{V_m}{T} \left[\frac{-\cos \omega t}{\omega} \right]_{T/2}^T$$

$$= \frac{V_m}{T} \left[-\cos \omega T/2 + \cos 0 - \cos \omega T + \cos \omega T/2 \right]$$

$$= \frac{V_m}{T} [1 - \cos \omega T]$$


$$= \frac{V_m}{T} (1 - \cos 2\pi)$$

$$= 0$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T V_m^2 \sin^2 \omega t dt}$$

**

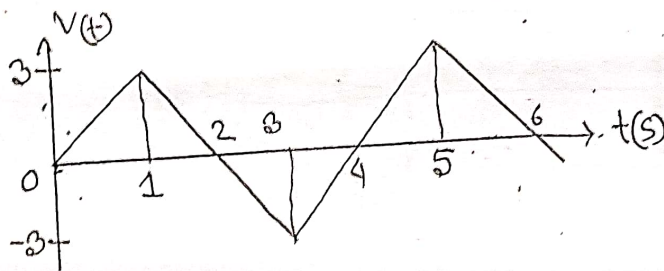

$$\frac{y - y_1}{y_1 - y_2} = \frac{x - x_1}{x_1 - x_2}$$

$$\Rightarrow \frac{v - 3}{3 - (-3)} = \frac{t - 1}{1 - 3}$$

$$\Rightarrow v_t = \left(6 \times \frac{t - 1}{-2} \right) + 3$$


$$= -3t + 3 + 3$$

$$= -3t + 6$$

Sub: _____

$$\begin{aligned}
 V_{rms} &= \sqrt{\frac{2}{4} \int_0^{T/2} v(t)^2 dt} \\
 &= \sqrt{\frac{1}{2} \int_0^3 (-3t+6)^2 dt} \\
 &= \sqrt{\frac{1}{2} \int_0^3 (9t^2 - 36t + 36) dt} \\
 &= \frac{1}{\sqrt{2}} \left[\frac{9t^3}{3} - \frac{36t^2}{2} + \frac{36t}{1} \right]_0^3 \\
 &= \dots \\
 &= \dots
 \end{aligned}$$

$$R = \frac{V_{rms}}{R}$$

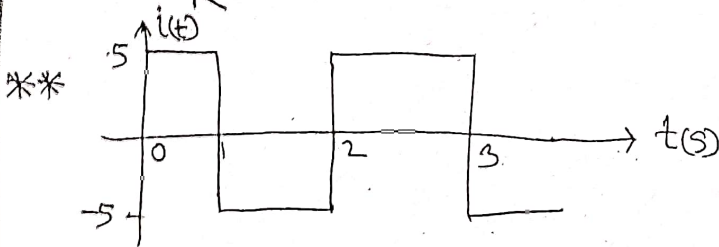


$$i(t) = 5 \quad ; 0 < t < 1$$

$$i(t) = -5 \quad ; 1 < t < 2$$

$$\begin{aligned}
 I_{rms} &= \sqrt{\frac{2}{2} \int_0^1 25 dt} \\
 &= \sqrt{25} = 5.
 \end{aligned}$$

Prob:

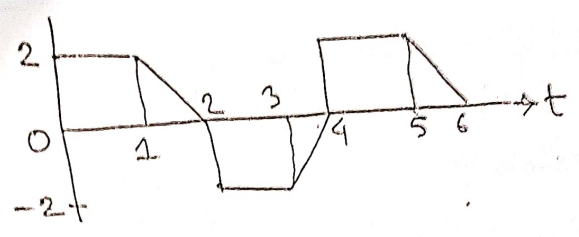

$$0 < t < 1 : v_1(t) = 2$$

$$1 < t < 2 : \frac{v_2(t) - 2}{2 - 0} = \frac{t - 1}{1 - 2}$$

$$\Rightarrow v_2(t) = \left(\frac{t-1}{-1}\right) \times 2 + 2$$

$$= -2t + 2 + 2$$

$$= -2t + 4$$

$$v_t = v_1(t) + v_2(t) = 2 - 2t + 4 = -2t + 6$$

$$v_t = \sqrt{\frac{2}{4}} \int_0^1 4 dt + \int_1^2 (-2t + 6) dt$$

Sub: _____


Time: _____ Date: / /

AC power / instantaneous power

□

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

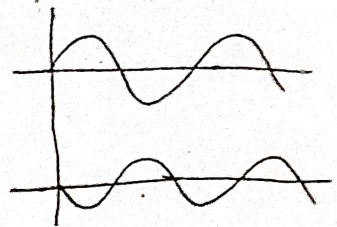

$$P(t) = v(t) i(t)$$

$$= V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$


$$= \frac{V_m I_m}{2} \cdot 2 \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$= \frac{V_m I_m}{2} \left[\cos(\omega t + \theta_v + \omega t + \theta_i) + \cos(\omega t + \theta_v - \omega t - \theta_i) \right]$$


$$= \frac{1}{2} V_m I_m \left[\cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i) \right]$$

Time independent part = $\cos(\theta_v - \theta_i)$

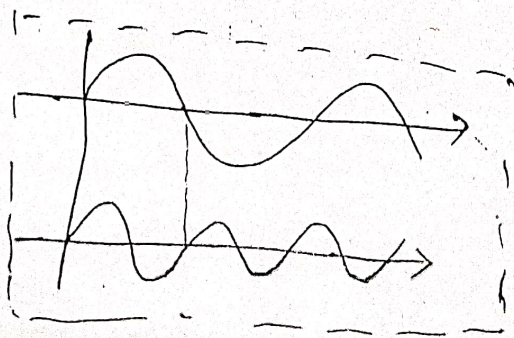Time dependent part = $\cos(2\omega t + \theta_v + \theta_i)$



Sub: _____

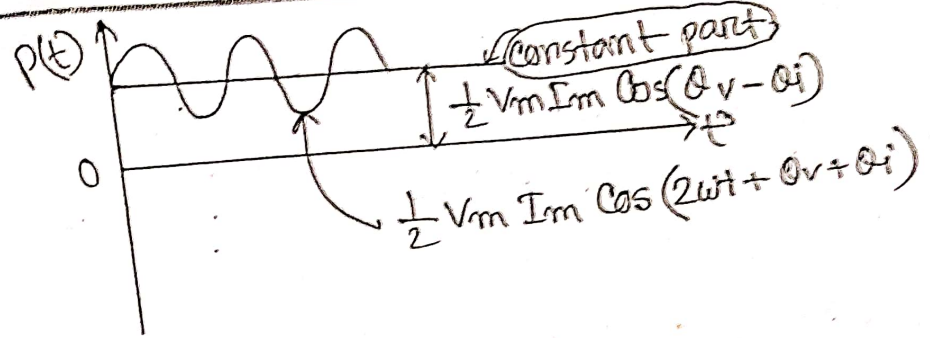

Average power

$$\begin{aligned}
 P_{\text{average}} &= \frac{1}{T} \int_0^T P(t) dt \\
 &= \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \left[\cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i) \right] dt \\
 &= \frac{V_m I_m}{2T} \int_0^T \cos(\theta_v - \theta_i) dt + \frac{V_m I_m}{2T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt \\
 &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + 0 \\
 &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)
 \end{aligned}$$

Power factor = $\cos(\theta_v - \theta_i)$

Chapter (11)

Sub: _____

SAT SUN MON TUE WED THU FRI

Time: _____

Date: _____

Power for ac circuit:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad \left[\begin{array}{l} \text{real power /} \\ \text{average power} \end{array} \right]$$
$$= V_{\text{rms}} \cdot I_{\text{rms}} \cos(\theta_v - \theta_i)$$

11.10.17
8B. EEE

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

V.V.I Complex power:

$$S = \frac{1}{2} V I^* \quad * = \text{conjugate.}$$

$$= \frac{1}{2} V_m \angle \theta_v \cdot I_m \angle -\theta_i$$

$$= \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + j \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$

$$V(t) = V_m \sin(\omega t + \theta_v)$$

$$V = V_m \angle \theta_v$$

$$\therefore S = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) + j V_m I_m \sin(\theta_v - \theta_i)$$

$$S = P \pm jQ$$

P = real power / average power


Q = reactive power.

For pure resistive resistive, $S = P$.

If it will pure inductive or capacitive
 $S = Q$ or $-Q$.


magnatude of capacitor complex power is equal
 to apparant power $= \frac{1}{2} V_m I_m$.

$$S = P \pm jQ$$

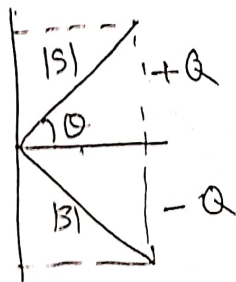

power triangle

$$Z = R \pm jX$$

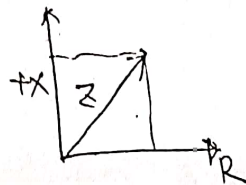


Impedance
 power triangle.




Sub:

Three phase / Poly phase system

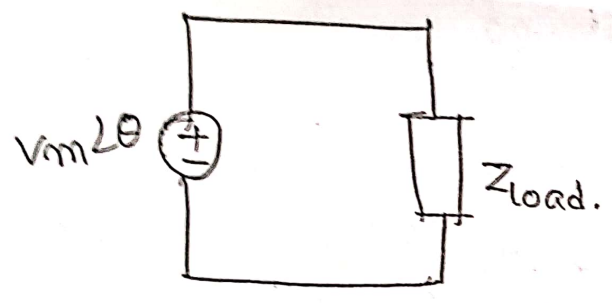If two or more than two voltage source operate at the same frequency are ~~called~~ called polyphase system.




Single phase two wire system.

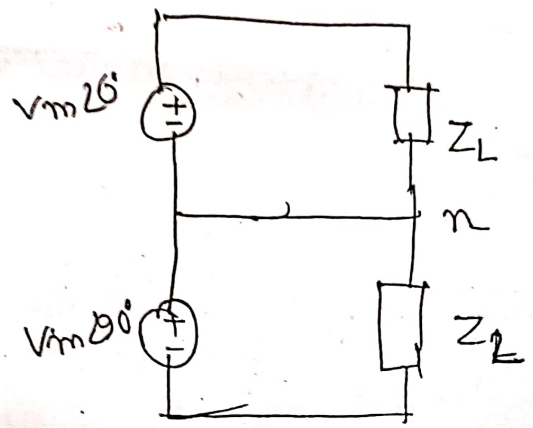

two phase three wire system.

Three phase system are two types:

- ① γ - connection.
- ② Δ - connection.

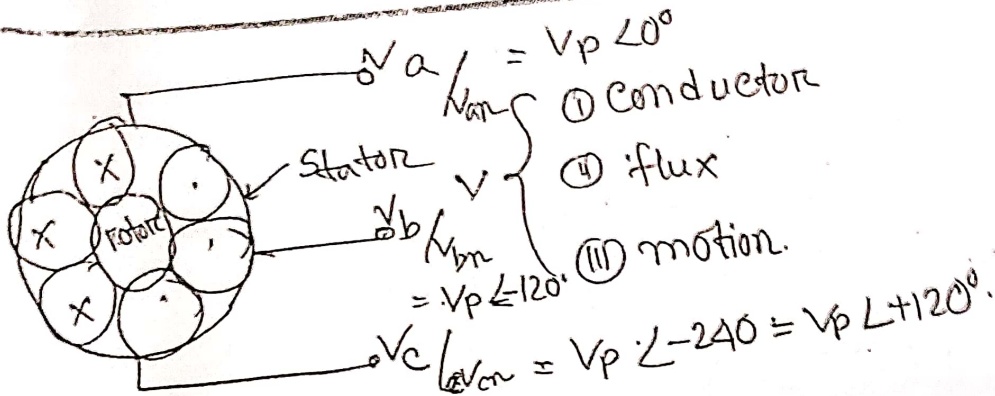


$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle 120^\circ$$

$$V_{cn} = V_p \angle +120^\circ = V_p \angle -240^\circ$$

$$|V_{an}| = |V_{bn}| = |V_{cn}|$$


120° out of phase.

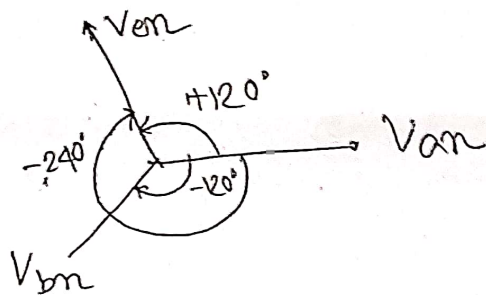

The condition of three phase system:

Every phase is differ from 120° angle.



Sub:

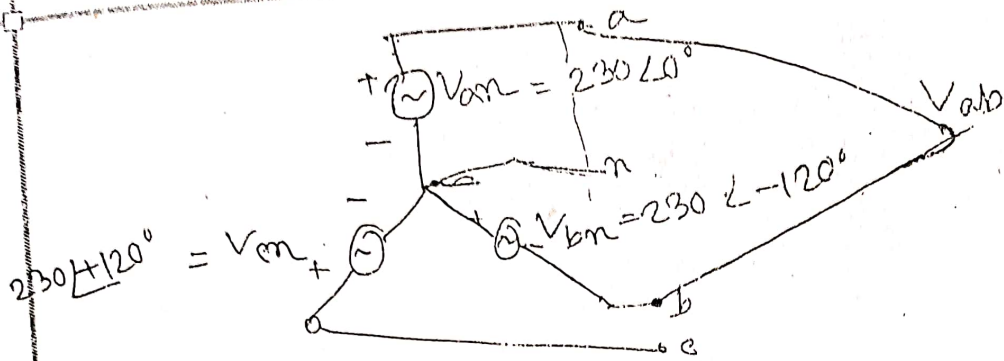

a-b-c sequence (positive) V_{an}, V_{bn}, V_{cn}

a-c-b sequence (negative) $V_{an} = V_p \angle 0^\circ$
 $V_{cn} = V_p \angle -120^\circ$
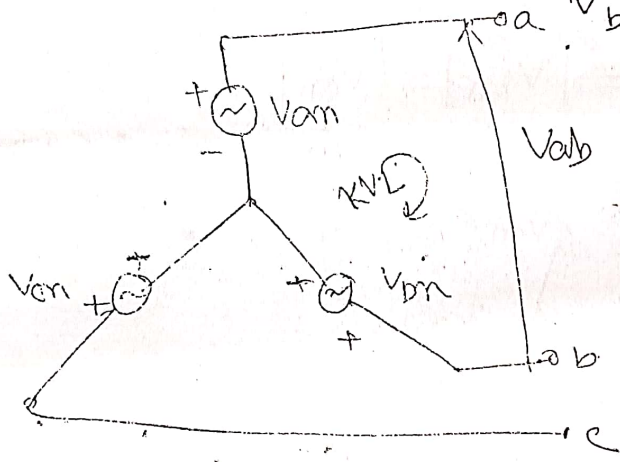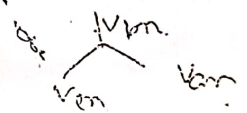
$$V_{bn} = V_p \angle -240^\circ = V_p \angle 120^\circ$$



$$\rightarrow V_{an} + V_{ab} + V_{bn} = 0$$

$$\begin{aligned} \Rightarrow V_{ab} &= V_{an} - V_{bn} \\ &= V_p \angle 0^\circ - V_p \angle -120^\circ \\ &= V_p (1 \angle 0^\circ - 1 \angle -120^\circ) \\ &= \sqrt{3} V_p \angle -30^\circ \end{aligned}$$