

2-11-19


3-phase circuit

Single phase (1- ϕ): A single phase system consists of a generator connected to a pair of wire to load.

Three phase system (3- ϕ): A 3-phase system is produced by a generator consisting of 3-voltage sources having equal in magnitude and frequency but out of phase by 120° ^{from} one each other

γ -connected 3 phase source

Phase 3π a_n, b_n, c_n

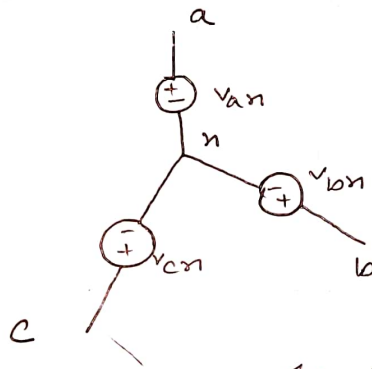

$2\pi/3$ difference 120°

$$V_{an} = V_m \sin(\omega t + \theta)$$



$$V_{bn} = V_m \sin(\omega t + \theta - 120^\circ)$$

$$V_{cn} = V_m \sin(\omega t + \theta + 120^\circ)$$

$2\pi/3$ distance -240° or 120°

3 π phasors
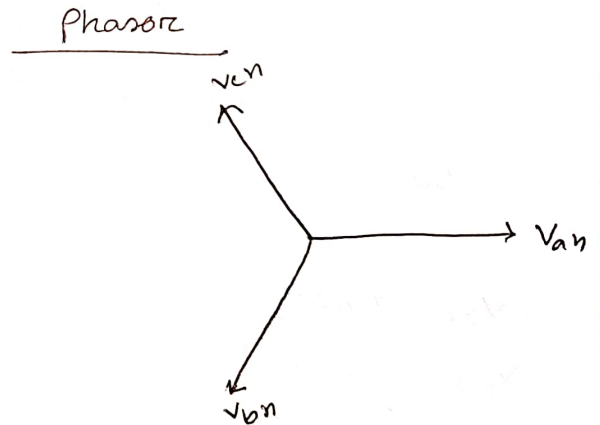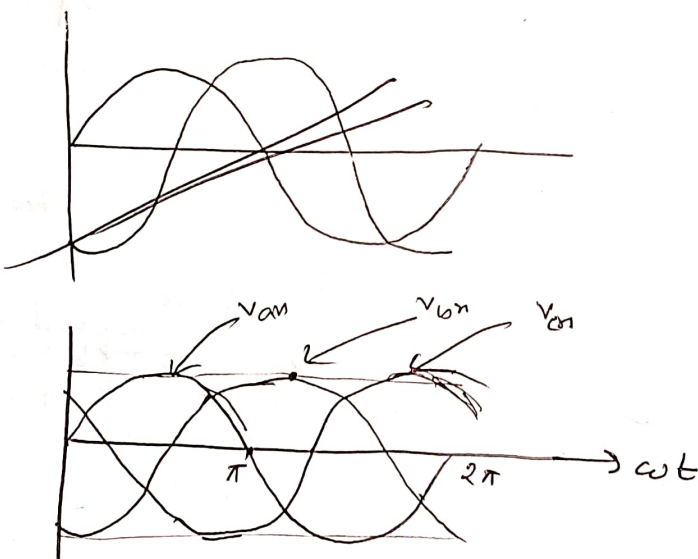
$$\begin{cases} V_{an} = V_m \angle \theta \\ V_{bn} = V_m \angle \theta - 120^\circ \\ V_{cn} = V_m \angle \theta + 120^\circ \end{cases}$$




Advantages

- (1) The instantaneous power of a 3-phase system is constant and for single phase system, it is time varying or depends on time
- (2) 3-phase system is ^{more} economical than single phase system. To transmit same amount of power over same distance the equal power of 3-phase system is less than required copper single phase system.
- (3) All the generated power are in 3-phase system
- (4) The efficiency of 3-phase system is more than the single phase
- (5) 3-phase induction motors are self-starting but single " " " " not "

Balanced 3-phase system: A 3-phase system is called to " it the voltage sources are equal in magnitude and frequency but out of phase in one each other by 120° and the loads are equal


$V_{an} = V_m \angle 0^\circ$
 $V_{bn} = V_m \angle -120^\circ$
 $V_{cn} = V_m \angle 120^\circ$

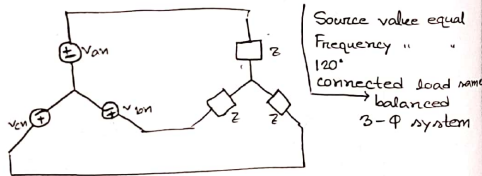

Balance 3-φ system

Phase sequence: A B C
 " " of a 3-phase system is the time order in which the voltage sources pass through their respective maxima

Positive sequence

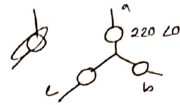

$0 \rightarrow 0 - 120^\circ \rightarrow 0 + 120^\circ$


(-)ve/a-c-b sequence
 (+ve)/a-b-c

$V_{an} = V_m \angle 0^\circ$
 $V_{bn} = V_m \angle +120^\circ$
 $V_{cn} = V_m \angle -120^\circ$

* a leads b, b leads c, c leads a then it is called a-b-c sequence or positive sequence
 * a leads c, c leads b, b leads a, then it is called a-c-b sequence/negative sequence.


3-phase
2 types of sources

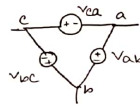- (i) Y-connected
- (ii) Δ - " (starts natural point n)




2 types of load

- (i) Y-connected
- (ii) Δ - "

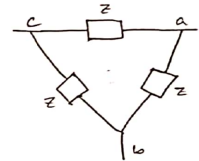

03-10-2019

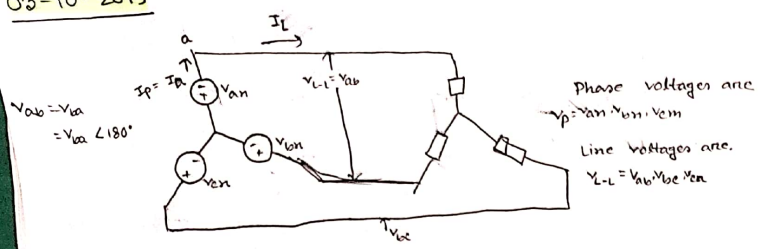


Phase voltages are
 $V_p = V_{an}, V_{bn}, V_{cn}$
 Line voltages are
 $V_{L-L} = V_{ab}, V_{bc}, V_{ca}$

Line and
 For Y-connected circuit, line current and phase current are in same phase, line voltages and line current are not equal

* abc sequence, positive

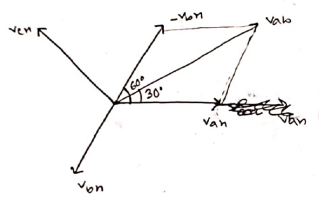
$V_{ab} = V_{an} - V_{bn}$
 Let, $V_{an} = V_m \angle 0^\circ$
 and for abc sequence
 $V_{bn} = V_m \angle -120^\circ$
 $V_{ab} = V_{an} + (-V_{bn})$
 $= V_m \angle 0^\circ - V_m \angle -120^\circ$
 $= \sqrt{3} V_m \angle 30^\circ - \sqrt{3} V_m \angle 0^\circ \cdot 1 \angle 180^\circ$
 $= \sqrt{3} V_m \angle 30^\circ$



$V_{L-L} = \sqrt{3} V \angle 30^\circ$
 $V_{ab} = |V_{an}| \cos 30^\circ + |V_{bn}| \cos 30^\circ = 2 |V_{bn}| \cos 30^\circ = \sqrt{3} V_m$

So for wye circuit,
 phase current and line current are equal but voltage leads phase voltage by 30° and the magnitude of line

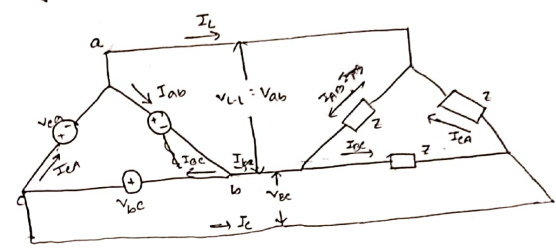
voltage is $\sqrt{3}$ times by phase voltage



For delta connected circuit, line and phase voltage are same.

$I_{ca} = I_a + I_{ab} \Rightarrow I_a = I_{ca} - I_{ab}$ Let,
 $I_{ab} = I_m \angle 0^\circ$
 $I_{bc} = I_m \angle -120^\circ$
 $I_{ca} = I_m \angle 120^\circ$

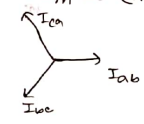$I_a = I_m \angle 0 + 120^\circ - I_m \angle 0$
 $= I_m \angle 0 \cdot 1 \angle 120^\circ - I_m \angle 0 \cdot 1 \angle 0^\circ$
 $= I_m \angle 0 (\sqrt{3}, 150^\circ) = \sqrt{3} I_{ab} \angle 150^\circ$



For delta circuit line current is $\sqrt{3}$ times of phase current

For source, the line current leads phase current by 15°


At load terminal

$$\begin{aligned}
 I_a &= I_{AB} - I_{CA} \\
 &= I_{AB} - I_{AB} \angle 120^\circ \\
 &= I_{AB} (1 - \angle 120^\circ) \\
 &= \sqrt{3} I_{AB} \angle -30^\circ
 \end{aligned}$$

the line current is $\sqrt{3}$ times I_p
phase current

In case of load terminal, the line current lags phase current by 30° and

Y-Y Y-Δ Δ-Y Δ-Δ

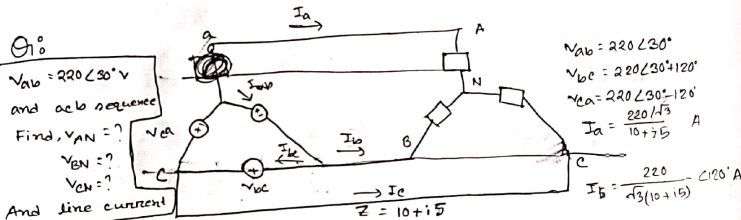

$$V_{L-L} = \sqrt{3} V_p \angle 30^\circ \Rightarrow V_p = \frac{V_{L-L}}{\sqrt{3} \angle 30^\circ}$$

$$V_p = \frac{V_{AB}}{\sqrt{3}} \angle -30^\circ$$

$$\therefore V_{AN} = \frac{V_{AB}}{\sqrt{3}} \angle -30^\circ$$

$$= \frac{220 \angle 30^\circ}{\sqrt{3}} \angle -30^\circ = \frac{220}{\sqrt{3}} \angle 0^\circ \text{ V}$$


$$V_{BN} = V_{AN} \angle +120^\circ = \frac{220}{\sqrt{3}} \angle 30^\circ \text{ V}$$

$$V_{CN} = V_{AN} \angle -120^\circ = \frac{220}{\sqrt{3}} \angle -120^\circ \text{ V}$$

23-11-19

$$I_L = \sqrt{3} I_p$$

$$V_L = I_p$$

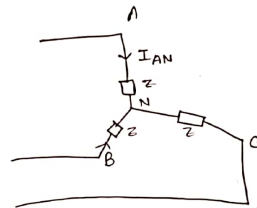

$$\text{Let, } V_{AN} = V_m \cos(\omega t + \theta)$$

$$V_{BN} = V_m \cos(\omega t + \theta - 120^\circ)$$

$$V_{CN} = V_m \cos(\omega t + \theta + 120^\circ)$$

$$\text{Let, } i_{AN} = I_m \cos(\omega t)$$

$$i_{BN} = I_m \cos(\omega t - 120^\circ)$$

$$i_{CN} = I_m \cos(\omega t + 120^\circ)$$

instantaneous power.

$$P(t) = V_{AN} i_{AN} + V_{BN} i_{BN} + V_{CN} i_{CN}$$


$$= V_m I_m \cos(\omega t + \theta) \cos(\omega t) + V_m I_m \cos(\omega t + \theta - 120^\circ) \cos(\omega t - 120^\circ)$$

$$+ V_m I_m \cos(\omega t + \theta + 120^\circ) \cos(\omega t + 120^\circ)$$

$$= \frac{1}{2} V_m I_m [\cos \theta + \cos(2\omega t + \theta) + \cos \theta + \cos(2\omega t + \theta - 240^\circ) + \cos \theta + \cos(2\omega t + \theta + 240^\circ)]$$

Measurement of power of 3- ϕ system :

2 wattmeter power

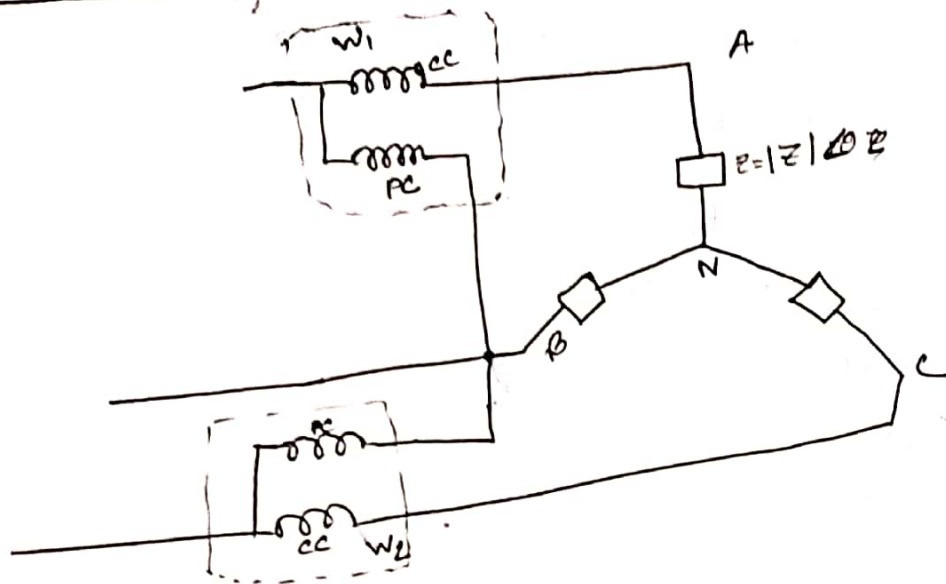

$$P = V_{AB} i_{AN} + V_{CB} i_{CN}$$

Let, $V_{AB} = V_{mL} \cos(\omega t + \theta)$ \rightarrow $V_{BC} = V_{mL} \cos(\omega t + \theta - 120^\circ)$
 $i_{AN} = I_{mL} \cos(\omega t)$ \rightarrow $V_{CB} = V_{mL} \cos(\omega t + \theta - 120^\circ + 180^\circ)$
 a-b-c sequence

$$P = V_{mL} \cos(\omega t + \theta) I_{mL} \cos(\omega t) + V_{mL} \cos(\omega t + \theta + 60^\circ) I_{mL} \cos(\omega t + 120^\circ)$$

$$= \frac{1}{2} V_{mL} I_{mL} [\cos \theta + \cos(2\omega t + \theta)] + \frac{1}{2} V_{mL} I_{mL} [\cos(\theta - 60^\circ) + \cos(2\omega t + \theta + 180^\circ)]$$

$$= \frac{1}{2} V_{mL} I_{mL} [\cos \theta + \cos(2\omega t + \theta) + \cos(\theta - 60^\circ) - \cos(2\omega t + \theta)]$$

$$= \frac{1}{2} V_{mL} I_{mL} \left[2 \cos \frac{2\theta - 60^\circ}{2} \cos \frac{60^\circ}{2} \right]$$

$$= \frac{\sqrt{3}}{2} V_{mL} I_{mL} \cos(\theta - 30^\circ)$$

///

$$P = P_1 + P_2$$

$$P_1 = \text{Re} [V_{AB} I_{AN}^*]$$

$$P_2 = \text{Re} [V_{CB} I_{CN}^*]$$

$$\begin{aligned} V_{AB} &= V_{AN} - V_{BN} \\ &= V_{AN} + (-V_{BN}) \end{aligned}$$

$$V_{CB} = V_{CN} - V_{BN}$$

$$\begin{aligned} P_1 &= \text{Re} [V_{AB} I_{AN}^*] \\ &= \text{Re} [V_{AB} \angle 30^\circ \cdot I_{AN} \angle +\theta] \\ &= V_{AB} I_{AN} \cos(30^\circ + \theta) \\ &= V_L I_L \cos(30^\circ + \theta) \end{aligned}$$

$$\begin{aligned} P_2 &= \text{Re} [V_{CB} I_{CN}^*] = V_{CB} I_{CN} \cos(30^\circ - \theta) \\ &= V_L I_L \cos(30^\circ - \theta) \end{aligned}$$


$$\begin{aligned} \text{Two wattmeter, } P &= P_1 + P_2 \\ &= V_L I_L \cos(30^\circ + \theta) + V_L I_L \cos(30^\circ - \theta) \\ &= V_L I_L [2 \cos 30^\circ \cos \theta] \\ &= V_L I_L 2 \cdot \frac{\sqrt{3}}{2} \cos \theta = \sqrt{3} V_L I_L \cos \theta \end{aligned}$$

Electronics

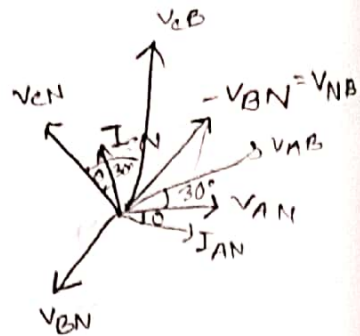V. K. Mehtab

Electronics is the branch of engineering which deals with the conduction of currents through semi-conductors and gases

$$\begin{aligned} r \angle \theta &= r \cos \theta + j r \sin \theta \end{aligned}$$



Semi-conductor

A " " is a material whose conductivity can be controlled by using proper doping.

Characteristics:

- 1) It's conductivity is in betⁿ conductor and insulator
- 2) It is magnetic temperature coefficient i.e with the increase of " " , the resistivity of semi-conductor materials is decreased.
- 3) The no. of valence electron is four.
- 4) It's conductivity can be controlled by using doping
- 5) ~~It's conduction band~~
- 6) The no. e⁻ in the conduction band of a semi-conductor material is depend on doping.

Difference among conductor, semi-conductor and insulator.

Intrinsic semi-conductor

The semi conductor material in pure form is called Intrinsic semi-conductor.

Extrinsic semi-conductor:


The semi conductor material in which penta-valent or tri-valent atom is added is called extrinsic semi-conductor.

- 2 types :
- | | |
|---|------------|
| 1) N-type | 2) P-type |
| ↓ | ↓ |
| penta valent | tri-valent |
| like As is added to a pure semi-conductor | |

For Si Ge diode




$$V_D > 0.3$$

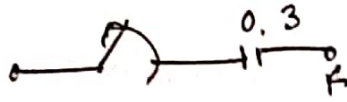


$$V_D < 0.3$$

Problem


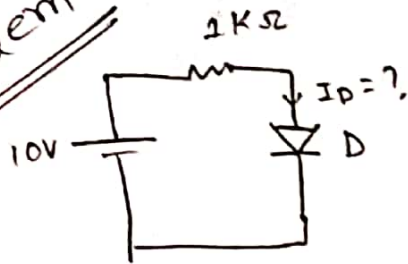


$$I_D = \frac{10 - 0.7}{1K} = 9.3$$

\Rightarrow

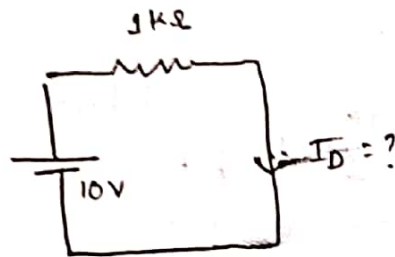

$$I_D = \frac{10}{1K} = 10 \text{ mA}$$

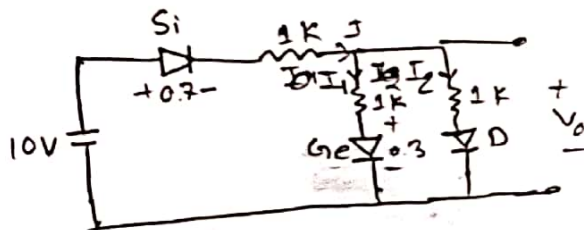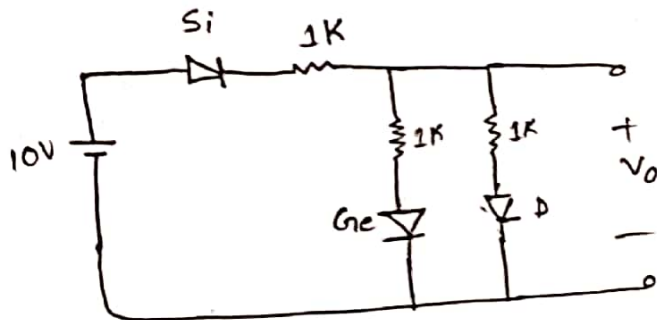

$$I = I_1 + I_2$$

$$\Rightarrow \frac{9.3 - V}{1} = \frac{V - 0.3}{1} + \frac{V}{1}$$

$$\therefore V = 3.2 \text{ V}$$

$$I_1 = \frac{3.2 - 0.3}{1} = 2.9 \mu\text{A}$$


$$I_0 = 3.2 \times 10^{-3} \text{ A}$$

03-12-2019


Rectifiers:

2 types \Rightarrow i) Half wave ii) Full wave
 - Bridge rectifier
 - Rectifier using centre tap transformer



Half wave rectifier:

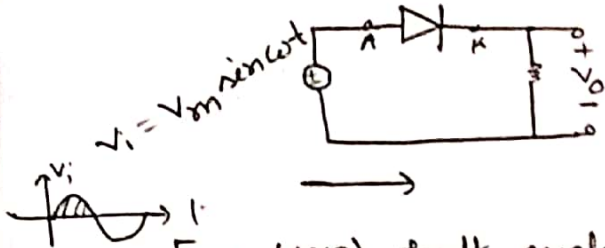

For (+ve) half cycle of input

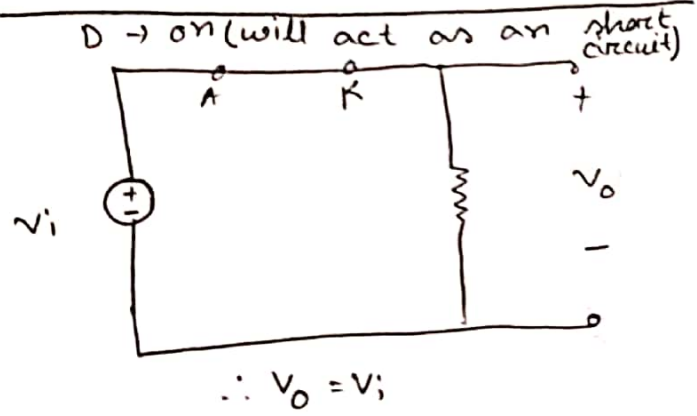


For (-ve) half cycle of input

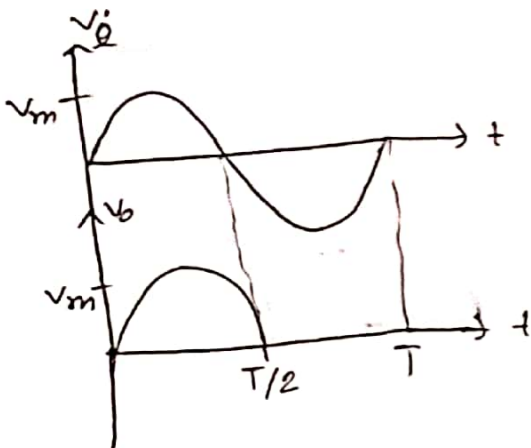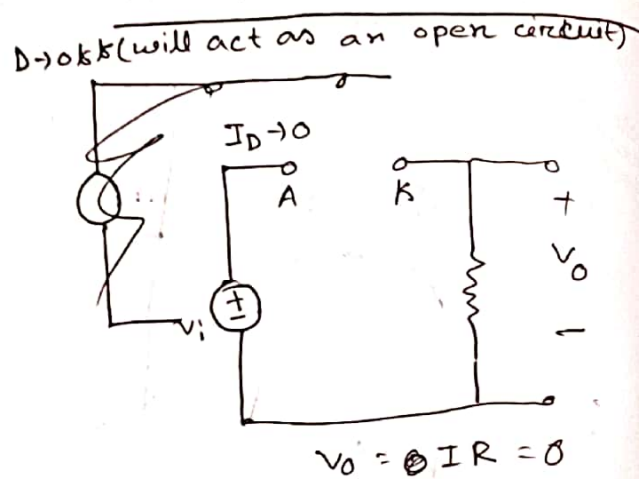

$$\begin{aligned}
 V_{AVG} &= \frac{1}{T} \int_0^T v_o dt \\
 &= \frac{1}{T} \left[\int_0^{T/2} v_i dt + \int_{T/2}^T 0 \cdot dt \right] \\
 &= \frac{1}{T} \int_0^{T/2} V_m \sin \omega t dt = \frac{V_m}{T} \left[-\frac{\cos \omega t}{\omega} \right]_0^{T/2}
 \end{aligned}$$

Forz (+ve) half cycle

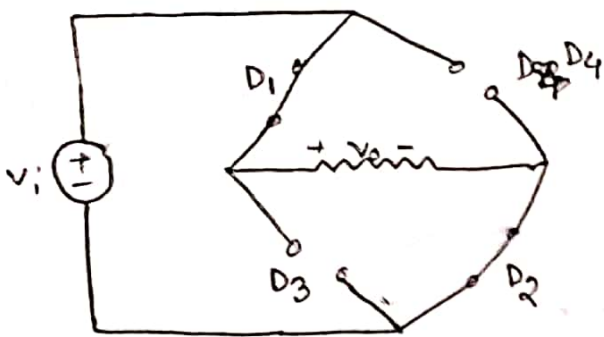
$D_1 \rightarrow \text{on}, D_4 \rightarrow \text{off}, D_3 \rightarrow \text{off}, D_2 \rightarrow \text{on}$




$v_o = v_i$

Forz (-ve) half cycle

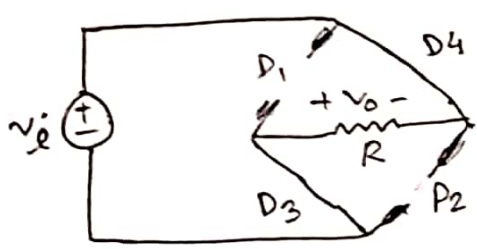$D_1, D_2 \rightarrow \text{off}, D_3, D_4 \rightarrow \text{on}$



$v_o = -v_i$

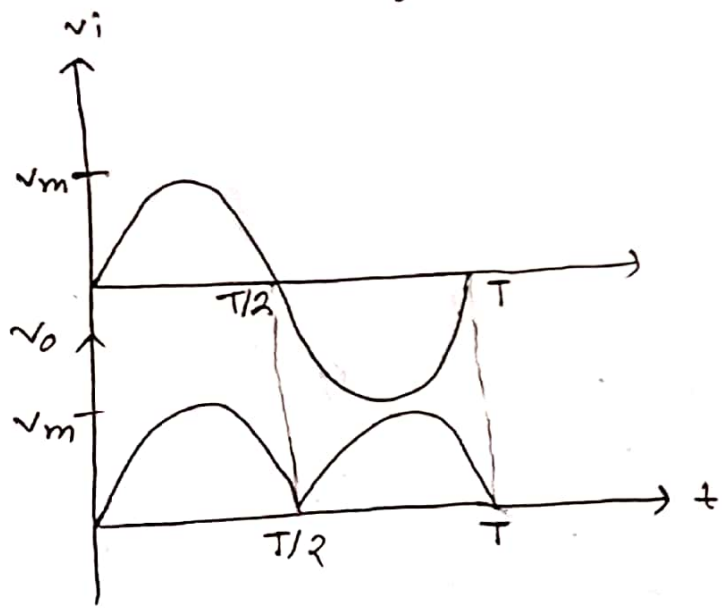

Machine

- (1) Faraday's laws of electromagnetic
- (2) Right hand rule for generator and left hand rule for ^{mot}
- (3) Working ^{loop} principle of simple loop DC generator
- (4) " " " motor
- (5) ~~Why~~ Why does the rotor of an induction motor rotate?
- (6) Why the ~~left~~ of a DC motor should never left open

Electronic machine ~~2 sets~~ 1 set or ~~2 sets~~

Electronics \rightarrow 1 set

DC \rightarrow 3 set

12 \rightarrow 1 set

9, 11 \rightarrow 2 set

Practice Problem
Example