

5(C) Sy 21-09-19

AC circuits

$$V(t) = V_m \cos(\omega t + \phi)$$

ഒരു AC signal

ഒരു sinusoidal signal ആണ്.


Sinusoidal : The signal sine or cosine is called sinusoidal signal.

$V_m \rightarrow$ peak value

$\omega \rightarrow$ Angular frequency

$\phi \rightarrow$ phase angle

$$\omega = \frac{2\pi}{T} = 2\pi f$$

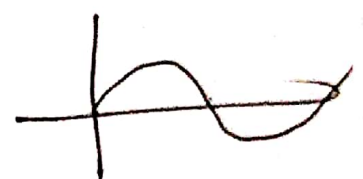

$$V_1 = 10 \cos(10t + 30^\circ)$$

$$V_2 = 10 \cos(10t + 50^\circ)$$

$$V_T = 10 [\cos(10t + 30^\circ) + \cos(10t + 50^\circ)]$$

Time domain

Time to

ഇതിനെ ടൈം ഡോമൈൻ ആണ് പറയുന്നത്. 2π ന്റെ ഫേസ് ആണ്.

phasor: phasor is complex number

representation of a sinusoidal signal that represents the peak value and phase angle of a sinusoidal signal.

In time domain:

$$v(t) = v_m \cos(\omega t + \phi)$$

In phasor

$$V = v_m \angle \phi$$

→ complex number (polar form)

phasor

$$V_1 = 10 \angle 30^\circ$$

$$V_2 = 10 \angle 50^\circ$$

$$V_{\text{total}} = V_1 + V_2 = 10 \angle 30^\circ + 10 \angle 50^\circ$$

$$= 15.088$$

$$= 19.69 \angle 40^\circ$$

$x + iy$

→ polar rectangular

$$\begin{aligned} x &= r \cos \theta \\ y &= r \sin \theta \\ \sqrt{(10 \cos 30^\circ + 10 \cos 50^\circ)^2 + (10 \sin 30^\circ + 10 \sin 50^\circ)^2} \\ &= 19.69 \end{aligned}$$

$$X + jY = \sqrt{X^2 + Y^2} \angle \tan^{-1} \frac{Y}{X}$$

$$\begin{aligned} \theta &= \tan^{-1} \frac{10 \sin 30^\circ + 10 \sin 50^\circ}{10 \cos 30^\circ + 10 \cos 50^\circ} \\ &= 40^\circ \end{aligned}$$

$$\begin{aligned} 10 \angle 30^\circ &= 8.66 + 5j \\ 10 \angle 50^\circ &= 6.42 + 7.66j \\ \therefore x &= 8.66 + 6.42 = 15.08 \\ \therefore y &= 5 + 7.66 = 12.66 \\ \therefore \sqrt{x^2 + y^2} &= 19.69 \\ \therefore \theta &= \tan^{-1} \frac{12.66}{15.08} \\ &= 40^\circ \end{aligned}$$

time domain

$$\therefore V_f(t) = 19.69 \cos(10t + 40)$$

$$t = 2 \text{ sec}$$

$$\omega = 10 \text{ (rad/sec)}$$

radian ७ 20 मिनट

वर्क degree को नोट कर

ω का मूल्य इस वही मूल्य पार ना

दूरे से निकले (same मूल्य)

$$\begin{aligned} V_f(t) &= 19.69 \cos(10t + 40) \\ &= 19.69 \cos(10 \times 2 + 40) \\ &= 19.69 \cos(20 \times \frac{180}{\pi} + 40) \\ &= -5.40 \end{aligned}$$


अथवा,

$$\begin{aligned} V_f &= 10 [\cos(10t + 30) + \cos(10t + 50)] \\ &= 10 [\cos(10 \times 2 + 30) + \cos(10 \times 2 + 50)] \\ &= 10 [\cos(20 \times \frac{180}{\pi} + 30) + \cos(20 \times \frac{180}{\pi} + 50)] \\ &= -5.40 \end{aligned}$$

Complex number

$$z = x + jy \quad | \quad i \text{ (दशम शक्ति ना)}$$

↓
rectangular form

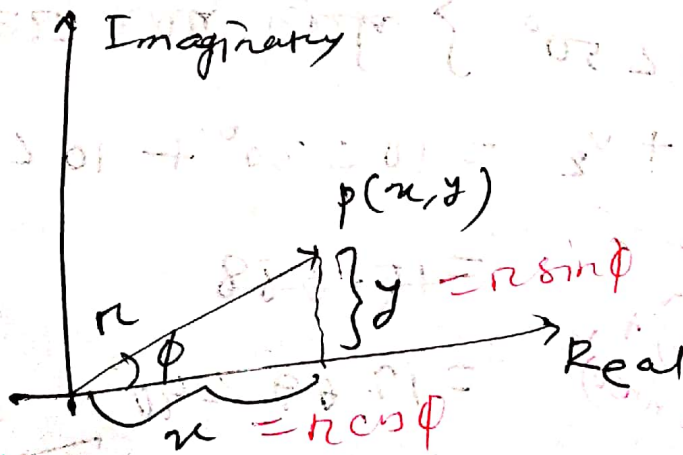

$$\begin{aligned} z &= x + jy \\ &= r \cdot \angle \phi \end{aligned}$$

where, $r = \sqrt{x^2 + y^2}$
 $\phi = \tan^{-1} \frac{y}{x}$

$$\begin{aligned} \therefore z &= x + jy \\ &= r \cos \phi + j r \sin \phi \\ &= r (\cos \phi + j \sin \phi) \\ &= r \cdot e^{j\phi} \end{aligned}$$

$j\phi = \angle$

$$\cos \theta = \text{Re} [e^{j\theta}]$$

$$\sin \theta = \text{Im} [e^{j\theta}]$$

$$\begin{aligned} \# \quad v(t) &= V_m \cos(\omega t + \phi) = \text{Re} [V_m \cos(\omega t + \phi) + j V_m \sin(\omega t + \phi)] \\ &= \text{Re} [V_m e^{j(\omega t + \phi)}] \end{aligned}$$

$$= \text{Re} [V_m e^{j\omega t} \cdot e^{j\phi}]$$

$$= \text{Re} [V_m e^{j\phi} \cdot e^{j\omega t}]$$

$$= \text{Re} [V \cdot e^{j\omega t}]$$

$$\text{where } V = V_m e^{j\phi} = V_m \angle \phi$$

$j\phi = \angle$

phasor

$$v_1(t) = V_{m1} \cos(\omega t + \phi_1)$$

$$v_2(t) = V_{m2} \cos(\omega t + \phi_2)$$

$$v_1(t) + v_2(t)$$

$$= V_{m1} \cos(\omega t + \phi_1) + V_{m2} \cos(\omega t + \phi_2)$$

$$= \text{Re} [V_{m1} e^{j(\omega t + \phi_1)}] + \text{Re} [V_{m2} e^{j(\omega t + \phi_2)}]$$

$$= \operatorname{Re} [v_{m1} e^{j(\omega t + \phi_1)} + v_{m2} e^{j(\omega t + \phi_2)}]$$

$$= \operatorname{Re} [v_{m1} e^{j\omega t} \cdot e^{j\phi_1} + v_{m2} e^{j\omega t} \cdot e^{j\phi_2}]$$

$$= \operatorname{Re} [\{ v_{m1} e^{j\phi_1} + v_{m2} e^{j\phi_2} \} e^{j\omega t}]$$

$$= \operatorname{Re} [v_T e^{j\phi_T} e^{j\omega t}]$$

$$= \operatorname{Re} [v_T e^{j(\omega t + \phi_T)}]$$

$$= v_T \cos(\omega t + \phi_T)$$


Handwritten note in red: $\frac{1}{\sqrt{2}}$ constant

(5) d. 22-9-19

$$v(t) = v_m \cos(\omega t + \phi) \implies v_m \angle \phi$$

phasor

$$j1 = 1 \angle 90^\circ$$

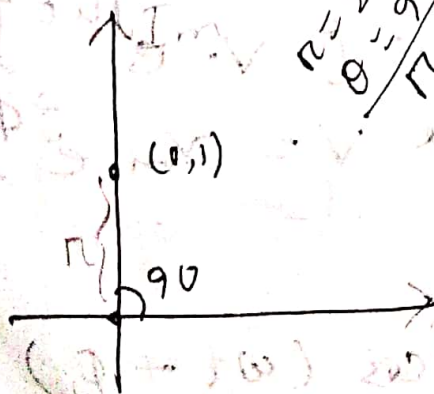

Handwritten notes: $\theta = 90^\circ$, $\theta = 90^\circ$, $\theta = 90^\circ$

$$j^2 = -1$$

$$\frac{1}{j} = \frac{j}{j^2} = -j$$

$$z_1 \pm z_2 = (r_1 + jy_1) \pm (r_2 + jy_2) \\ = (r_1 \pm r_2) + j(y_1 \pm y_2)$$

$$z_1 * z_2 = r_1 \angle \phi_1 \times r_2 \angle \phi_2 \quad r_1 e^{j\phi_1} \quad r_2 e^{j\phi_2} \\ = r_1 r_2 \angle \phi_1 + \phi_2$$

$$\frac{z_1}{z_2} = \frac{r_1 \angle \phi_1}{r_2 \angle \phi_2} = \frac{r_1 e^{j\phi_1}}{r_2 e^{j\phi_2}} \\ = \frac{r_1}{r_2} e^{j(\phi_1 - \phi_2)}$$

$$= \frac{r_1}{r_2} \angle \phi_1 - \phi_2 \quad \text{polar form}$$

$$\# 4 \angle 50 \text{ (कर्ककककक)} \frac{1}{2} \text{ पावर सत} \\ = 2 \angle 25 \quad \rightarrow \text{power}$$

$$\# \text{ square करककक} \quad 2 \text{ पावर सत सत} \\ \rightarrow \text{power}$$

$$\# \sqrt{z} = \sqrt{r \angle \phi} \\ = \sqrt{r} e^{j\phi} \\ = \sqrt{r} e^{j\phi/2} \\ = \sqrt{r} \angle \phi/2$$

conjugate \rightarrow argument $\tan^{-1} \frac{y}{x}$

$$(z)^* = (x + jy)^* = x - jy \quad \rightarrow \text{argument} = \tan^{-1} \frac{-y}{x}$$

$$= (r \angle \phi)^* = r \angle -\phi$$

$x(t) = X_m \cos(\omega t + \phi)$

In phasor $X = X_m \angle \phi$

$$\int x(t) dt = \int X_m \cos(\omega t + \phi) dt$$

$$= X_m \frac{\sin(\omega t + \phi)}{\omega}$$

$$= \frac{X_m}{\omega} \cos(\omega t + \phi - 90^\circ)$$

\therefore phasor representation of




$$\int x(t) dt$$

$$\frac{X_m}{\omega} \angle \phi - 90^\circ$$

$$= \frac{X_m}{\omega} e^{j(\phi - 90^\circ)}$$

$$= \frac{X_m}{\omega} e^{j\phi} \cdot e^{j(-90^\circ)}$$
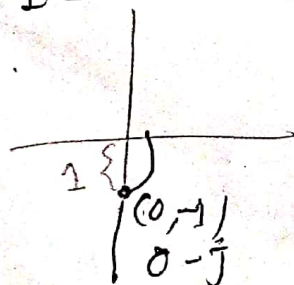
$$= \frac{X_m}{\omega} e^{j\phi} \cdot 1 \angle -90^\circ$$



$$\cos(90 - \theta) = \sin \theta$$

$$\cos(90 - \theta) = \sin \theta$$

$$\cos(\theta - 90) = \sin \theta$$

$$\cos(-\theta) = \cos \theta$$

$e^{j\omega t} r = 1$

$r e^{j\phi} = r \angle \phi$

$$e^{j\phi} = 1 \angle \phi$$

$$r \angle \phi = r e^{j\phi}$$

$r=1$

$$e^{j\phi} = \cos\phi + j\sin\phi$$

$$= -j \frac{X_m}{\omega} e^{j\phi}$$

$$= \text{---} -j^2 \times \frac{1}{j\omega} \angle X_m \angle \phi \quad \text{B}$$

$$= \boxed{\frac{X}{j\omega}} ; \text{ where } X \text{ is the phasor of } x(t)$$

QTV $\frac{1}{s}$ integration to phasor.

Again,

$$\frac{dx(t)}{dt} = -\omega X_m \sin(\omega t + \phi)$$

↓
অভিকলন

$$= \omega X_m \cos(90 + \omega t + \phi) \quad \left[\begin{array}{l} \cos\phi \text{ নিয়} \\ \text{২য়} \\ \text{কোণ}$$

∴ phasor representation of

$$\frac{dx(t)}{dt}$$

$x(t)$ এর মান $\cos\phi$ এর $\frac{1}{\omega X_m}$

$$= \omega X_m \angle 90 + \phi$$

$$= \omega X_m e^{j(90 + \phi)}$$

$$= \omega X_m e^{j90} \cdot e^{j\phi}$$

$$= j\omega X_m e^{j\phi}$$

$$= j\omega X_m \angle \phi$$

$$= \boxed{j\omega X} ; \text{ where } \angle X \text{ is the phasor of } x(t)$$

For AC circuit

3 - loads

(i) Resistor

(ii) Inductor

(iii) Capacitor

voltage current relationship: (time domain)
for resistor:

$$V(t) = i(t)R \Rightarrow i(t) = \frac{1}{R} V(t)$$

→ resistance

for inductor:

$$V_L(t) = L \frac{di_L(t)}{dt} \Rightarrow i_L(t) = \frac{1}{L} \int V_L(t) dt$$

→ inductance

for capacitor:

$$V_C(t) = \frac{1}{C} \int i_C(t) dt \Rightarrow i_C(t) = C \frac{dV_C}{dt}$$



voltage current relationship (in phasor domain)

if, $i(t) = I_m \cos(\omega t + \phi)$

then, $\underline{I} = I_m \angle \phi$

for resistor:

$$V = IR$$

for inductor:

$$V_L = L \cdot j\omega I$$

$$= j\omega L I$$

for capacitor:

$$V_C = \frac{1}{j\omega} \cdot \frac{1}{C} \cdot I$$

$$= \frac{I}{j\omega C}$$

Impedance: ^(resistor, capacitor, inductor) $(5)E-23-09-18$

Impedance is the ratio of voltage phasor and current phasor. ~~is called~~

$$\text{Impedance} = \frac{\text{voltage phasor}}{\text{current phasor}}$$

For Resistive load:

$$Z = \frac{V}{I} = R \rightarrow \text{impedance}$$

Impedance is denoted by Z and expressed in ohm measured in ohm.

For inductive load:

$$Z_L = \frac{V}{I} = j\omega L (\Omega)$$

L = Inductance
 $\omega = 2\pi f$
 impedance change 2π frequency change 2π

For capacitive load:



$$Z_C = \frac{V}{I} = \frac{1}{j\omega C} (\Omega)$$



$$V_1 = V_{m1} \cos(\omega t + 10^\circ)$$

$$V_2 = V_{m2} \cos(\omega t - 40^\circ)$$

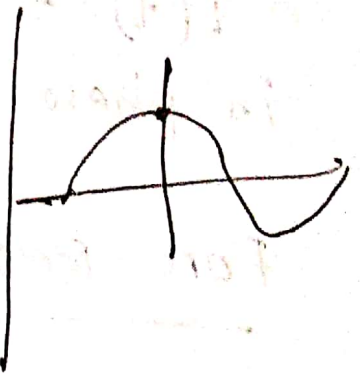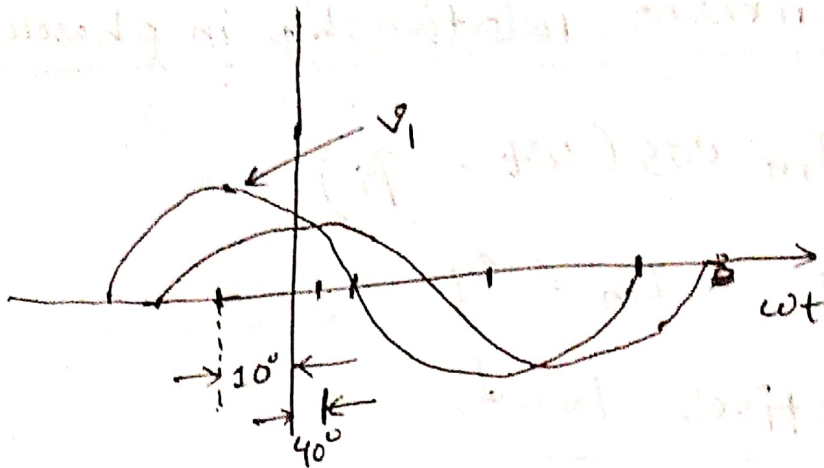$\omega t = -10^\circ$ at
 maximum
 value of V_1
 $\cos 0^\circ = 1$
 maximum




V_1 — leading
 V_2 — lagging

V_1 leads V_2 by 50°

V_2 lags V_1 by 50°

Phasor diagram of V_1 and V_2

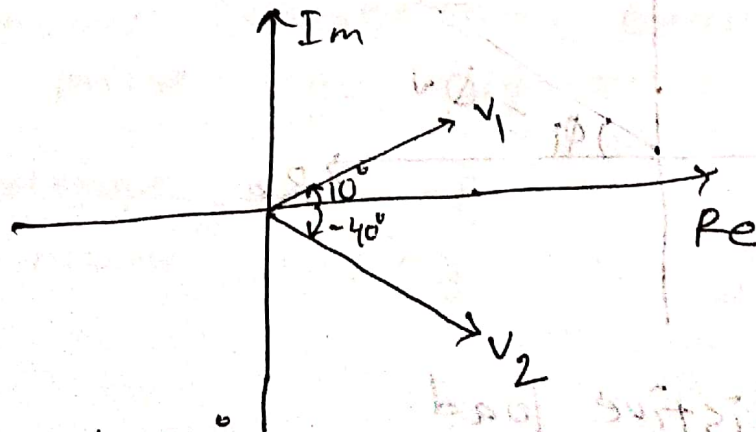

V_1 length = V_{m1}
 $\theta = 10^\circ$

anticlockwise
 V_1 — lead
 V_2 — lag

$V_1 = V_{m1} \angle 10^\circ$
 $V_2 = V_{m2} \angle -40^\circ$

V_1 leads V_2 by 50°

V_2 lags V_1 by 50°

anticlockwise is ^{not} lead
clockwise is lag

voltage current relationship in phasor diagram:

~~for~~

$$i(t) = I_m \cos(\omega t + \phi_i)$$

in phasor,

$$I = I_m \angle \phi_i$$


For Resistive load,

$$V = IR = R I_m \angle \phi_i$$

$$= V_m \angle \phi_v$$

where, $V_m = I_m R$


$$\phi_v = \phi_i$$

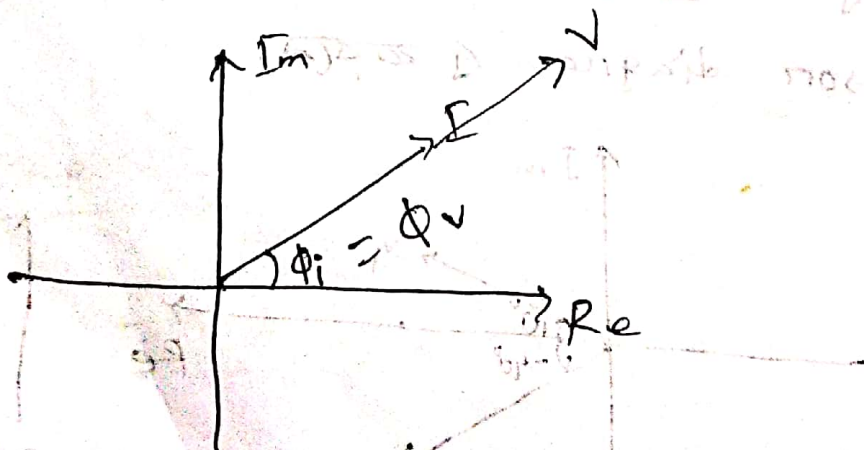

For resistive load

the phase angle of voltage and current are equal.

time dependent

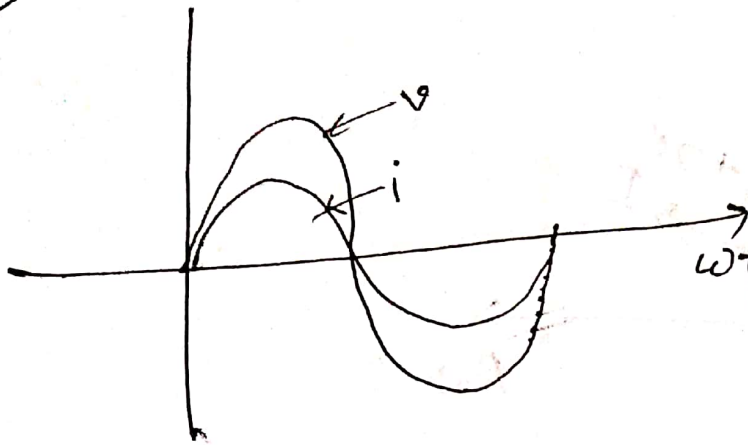

wt phase angle ϕ
amplitude v_m

For Inductive load :

$$V_L = j\omega L I$$

$$= j\omega L I_m \angle \phi_i$$

$$= 1 \angle 90^\circ \omega L I_m \angle \phi_i$$

$$= \omega L I_m \angle \phi_i + 90$$

$$= V_m \angle \phi_v$$


$$j = 1 \angle 90^\circ$$

where, $V_m = \omega L I_m$

$$\phi_v = \phi_i + 90$$


voltage phase angle ϕ_v
current phase angle ϕ_i

voltage leading
current lagging

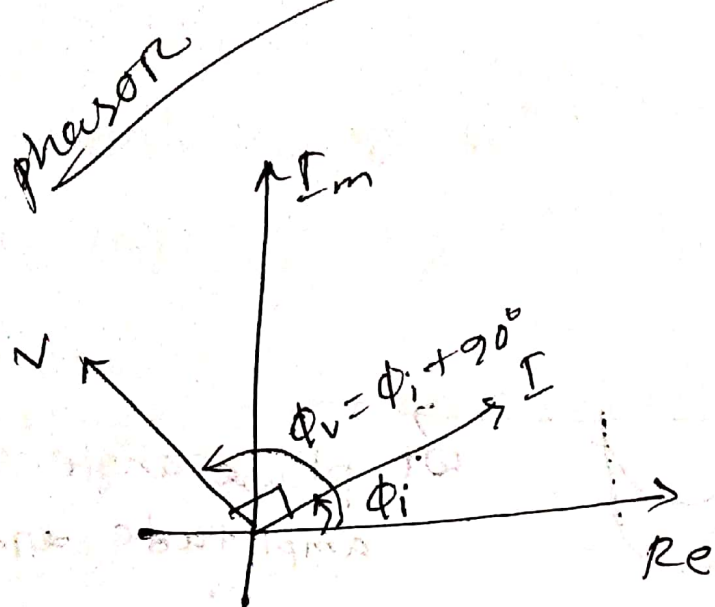

anticlockwise,
 For Inductive load voltage leads
 current by 90° or current lags
 voltage by 90°

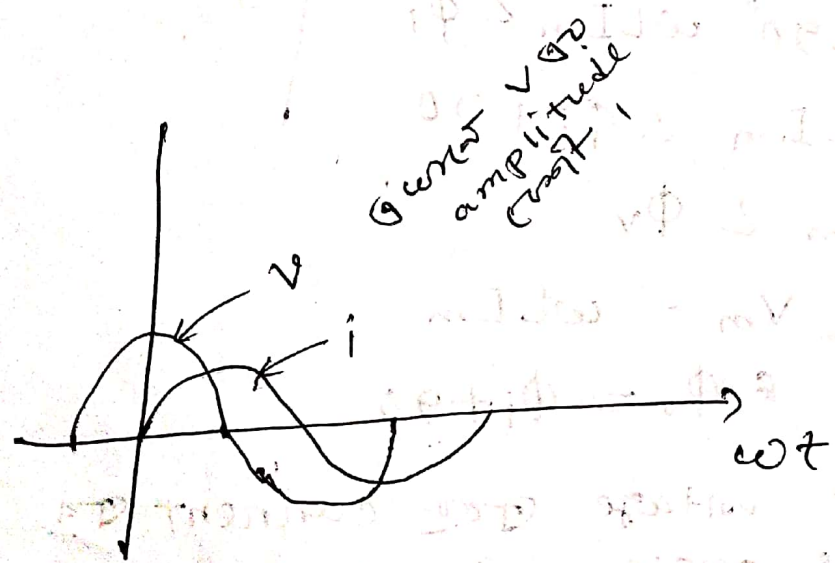anticlockwise
 volt leads
 current lags
 = lead



voltage 90° ahead of current



For capacitive load:

$$\begin{aligned}
 V_c &= \frac{I}{j\omega C} \\
 &= \frac{I_m \angle \phi_i}{j\omega C} \\
 &= \frac{I_m \angle \phi_i}{1 \angle 90^\circ \omega C} \\
 &= \frac{I_m}{\omega C} \angle \phi_i - 90^\circ \\
 &= V_m \angle \phi_v
 \end{aligned}$$


$$\begin{aligned}
 \frac{1}{j} &= -j \\
 -j &= 1 \angle -90^\circ
 \end{aligned}$$

where, $V_m = \frac{I_m}{\omega C}$ → Peak value
 $\phi_v = \phi_i - 90^\circ$

phasor

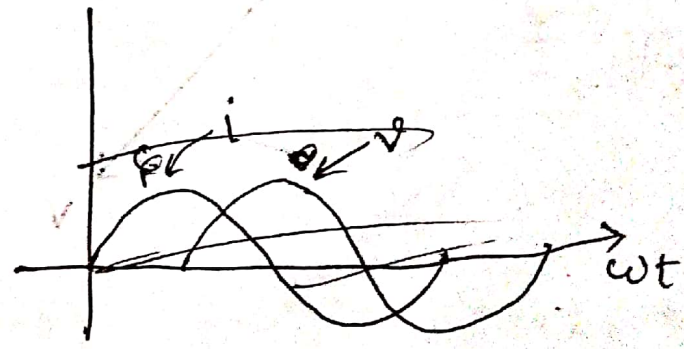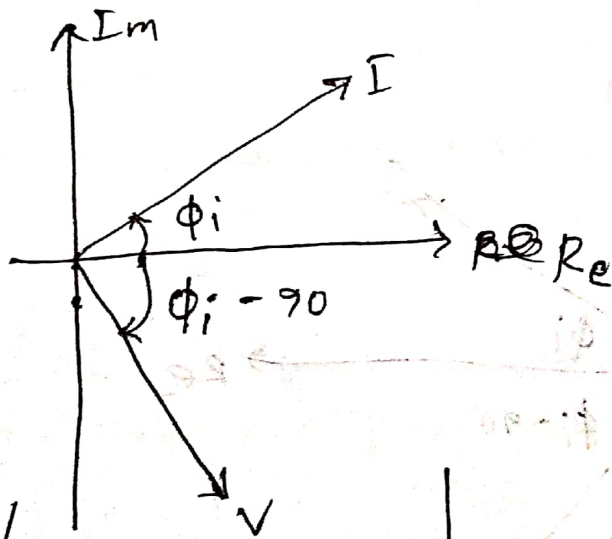

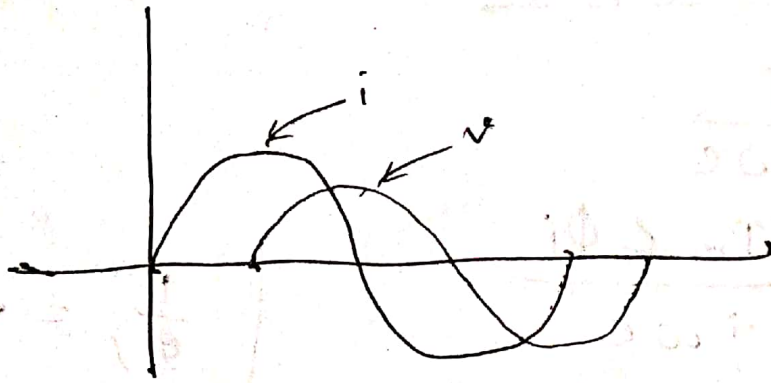ଦେଖା ଉପରା anticlockwise
 I ଉପରା ଉପରା ଉପରା
 ଉପରା I ଉପରା leading




ବିଦ୍ୟୁତ୍ i ଏବଂ
amplitude ଶକ୍ତି


For capacitive load :

$$V = \frac{I_m}{\omega C} \angle \phi_i - 90^\circ$$

$$= V_m \angle \phi_v$$

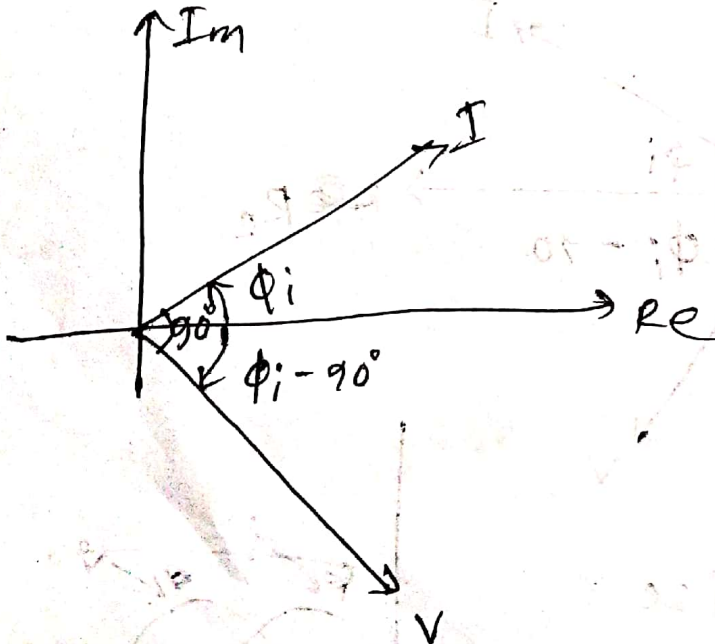
$$\text{where, } \phi_v = \phi_i - 90^\circ$$



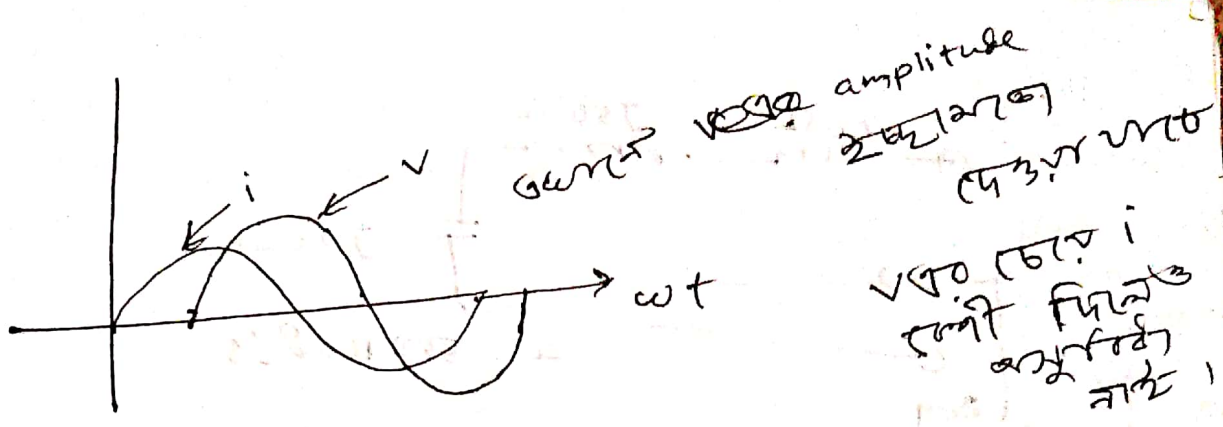

G(D)-day 9-09-19

Equivalent Impedance

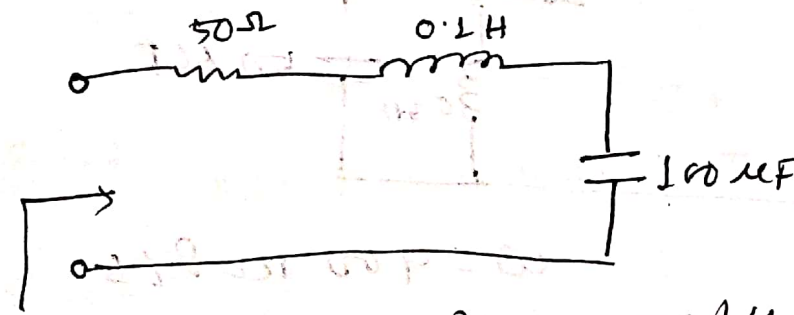

$\omega = 500 \text{ rad/s}$


$0.1 \text{ H} \Rightarrow j\omega L$
 $= j \times 500 \times 0.1$
 $= j 50 \Omega$

Inductor & capacitor depend on angular velocity

$100 \mu\text{F} \Rightarrow \frac{1}{j\omega C}$
 $= \frac{1}{j \times 500 \times 100 \times 10^{-6}}$
 $= -j 20 \Omega$


$\frac{1}{j} = -j = 1\angle -90^\circ$

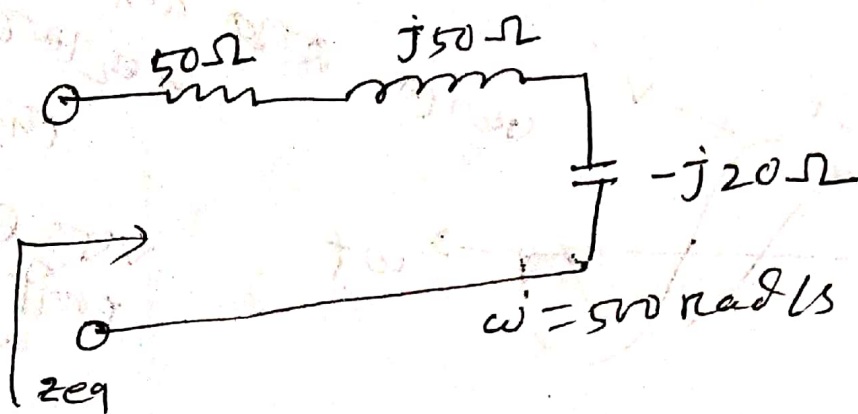Impedance
Inductor
 $j\omega L = \text{impedance}$
For resistor,
 $\frac{V}{I} = R \Omega$
Inductor,
 $\frac{V}{I} = j\omega L$
Capacitor,
 $\frac{V}{I} = \frac{1}{j\omega C}$



$$\therefore z_{eq} = 50 + j50 - j20$$

$$= 50 + j30 \Omega$$

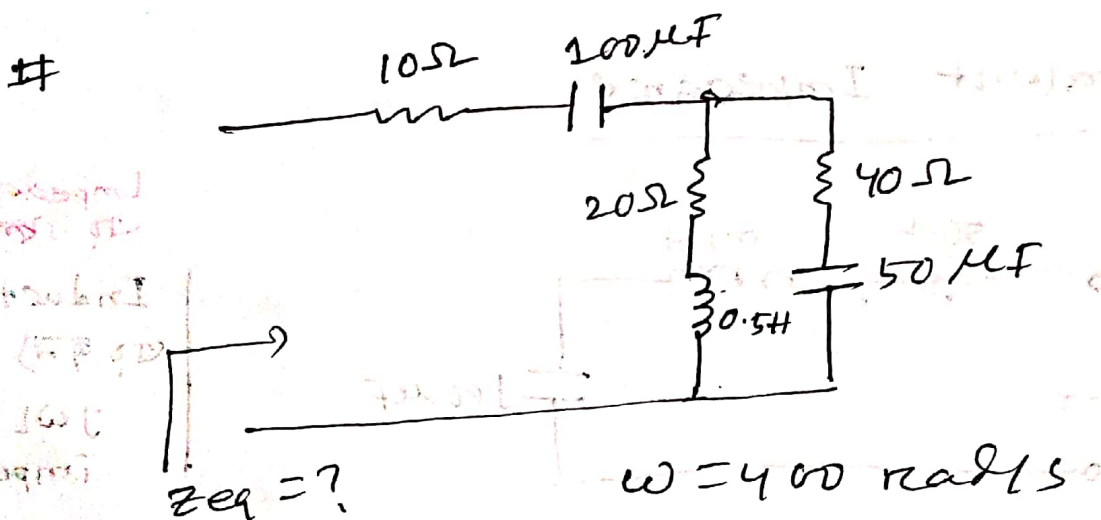

equivalent impedance = ?

$$100 \mu F \Rightarrow \frac{1}{j\omega C}$$

$$= \frac{1}{j \times 400 \times 100 \times 10^{-6}}$$

$$= -j25 \Omega$$

$$50 \mu F \Rightarrow$$

$$\frac{1}{j \times 400 \times 50 \times 10^{-6}}$$

$$= -j50 \Omega$$

$$0.5 \text{ H} \Rightarrow j\omega L$$


$$= j \times 400 \times 0.5$$

$$= j200 \Omega$$

$$\therefore 40 + (-j50)$$

$$= 40 - j50$$

$$\therefore 20 + j200$$

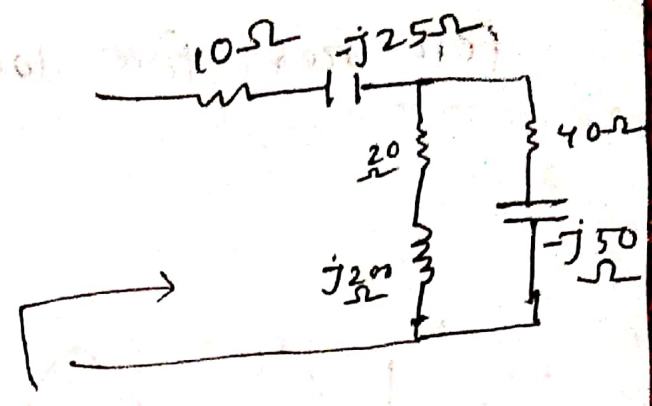

$$z_{eq} = 10 - j25 + (20 + j200) \parallel (40 - j50)$$

$$\therefore \frac{1}{20 + j200} + \frac{1}{40 - j50}$$

$$10 - j25 + \frac{(20 + j200)(40 - j50)}{20 + j200 + 40 - j50}$$

$$= 75.05 - j70.97 \Omega$$

shift (b) to
wavy equal
b) to 2 (d)

Instantaneous power


$$v(t) = V_m \cos(\omega t + \phi_v)$$

$$i(t) = I_m \cos(\omega t + \phi_i)$$

$$p(t) = v(t) \cdot i(t)$$

$$= V_m I_m \cos(\omega t + \phi_v) \cos(\omega t + \phi_i)$$
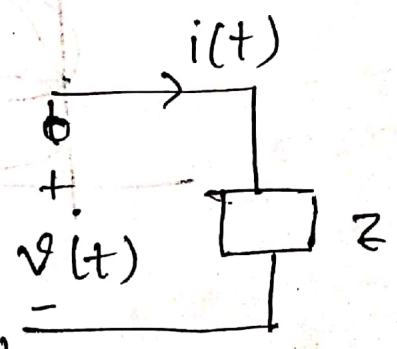
$$= \frac{1}{2} V_m I_m [\cos(\phi_v - \phi_i) + \cos(2\omega t + \phi_v + \phi_i)]$$




$$\cos A \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

$$= \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) + \frac{1}{2} V_m I_m \cos(2\omega t + (\phi_v + \phi_i))$$

For resistive load

angular frequency 2ω (first)


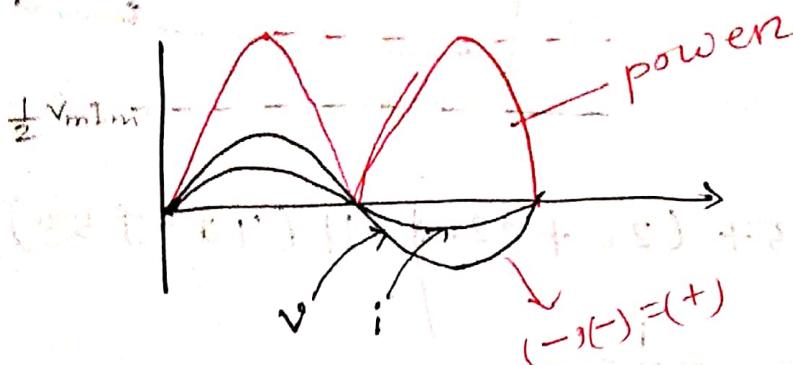


power \propto frequency
voltage \propto current
 $\propto f^2$

v and i ~~one~~ ~~cycle~~ = power \propto 2 cycle

For resistive load $(\phi_v - \phi_i) = 0$

$$v = 5 + (5) \sin \omega t$$

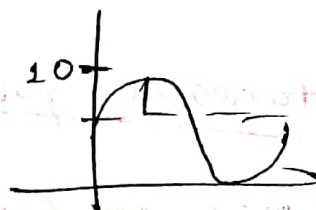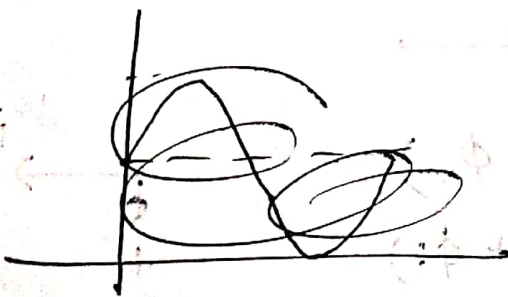

7(c)-day
12-10-19

Instantaneous power:

$$P(t) = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \phi_v + \phi_i)$$

$$\begin{aligned} P_{av} &= \frac{1}{T} \int_0^T P(t) dt \\ &= \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) dt + \\ &\quad \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \phi_v + \phi_i) dt \\ &= \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) + 0 \\ &= \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) \end{aligned}$$

∴ Average power,

$$P_{av} = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i)$$

where,

V_m → peak value of voltage



I_m → peak value of current

ϕ_v = phase angle of voltage

ϕ_i = phase angle of current

or

$\cos(\phi_v - \phi_i)$ → power factor

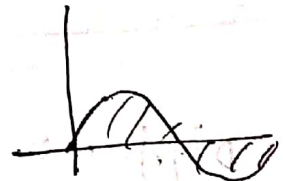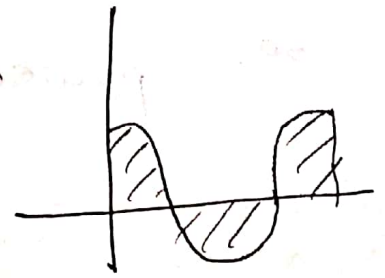

एक चक्र के क्षेत्रों का
निकालना
area निकालना
एक चक्र का
(integrate) $\int_0^T P(t) dt$
260

Power factor is the cosine of the difference between phase angle of the voltage and current.

power factor to minimum value 2π , zero.

" " " " maximum " " 1.

power factor negative 2π to π ,

For resistive load:

$$\phi_v = \phi_i$$

$$\text{So, power factor} = \cos 0^\circ = 1 \quad \left| \begin{array}{l} \text{phase angle} \\ \text{is } 0 \end{array} \right.$$


For capacitive and inductive load:

Difference between the phase angle of voltage and current is 90° .

$$\phi_v \sim \phi_i = 90^\circ$$

$$\therefore \text{power factor} = \cos 90^\circ = 0$$

#

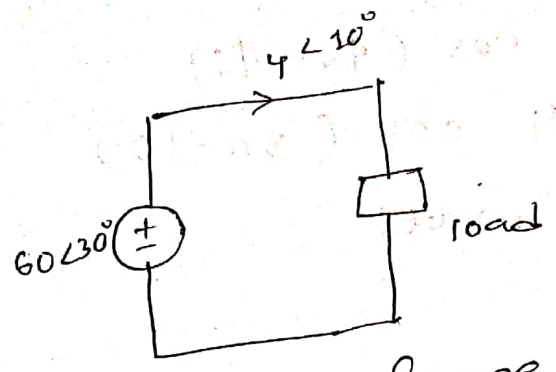

find i) load impedance
 ii) power absorbed by load

Ans
 load impedance, $Z = \frac{V}{I}$
 $= \frac{60\angle 30^\circ}{4\angle 10^\circ}$
 $= 15\angle 20^\circ$
 $= 14.09 + j5.13 \Omega$


impedance \rightarrow rectangular $(a + jb)$
 # current \rightarrow voltage \rightarrow polar $(r\angle\theta)$

power absorbed \rightarrow average power
 $P_{avg} = I_{rms}^2 R$

ii)
 $\phi_v = 30^\circ$
 $\phi_i = 10^\circ$

$$\begin{aligned}
 P_{av} &= \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) \\
 &= \frac{1}{2} \times 60 \times 4 \cos(30 - 10) \\
 &= 112.76 \text{ watt}
 \end{aligned}$$

#

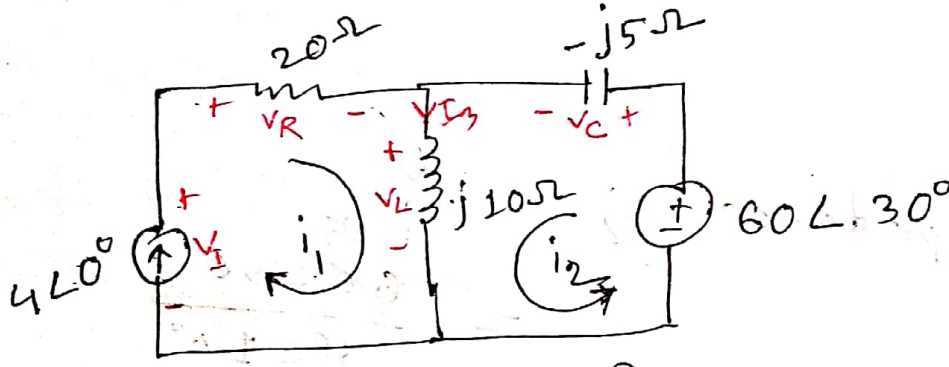

ଏକକ element ଥିବୁଥିବୁ power absorbs
କରାଏ ତାର ୧୦୦ ୨୦ ୧

୧) voltage ଏବଂ current ଦିଆଯାଇ ୨୦ ୧

KVL [mesh analysis] କରାଯାଉ ୨୦ ୧

$$I_1 = 4\angle 0^\circ$$

$$-60\angle 30^\circ - j5I_2 + j10(I_2 + I_1) = 0$$

$$\Rightarrow -60\angle 30^\circ + j5I_2 + j10I_1 = 0$$

$$\Rightarrow j5I_2 = 60\angle 30^\circ - j10I_1$$

$$\Rightarrow \cancel{I_2 = 11.93 \angle -99.04^\circ}$$

$$\Rightarrow I_2 = 10.58 \angle -100.89^\circ$$

$$I_3 = I_1 + I_2 = 4 \angle 0^\circ + 10.58 \angle -100.89^\circ$$

$$= \cancel{14.58 \angle -100.89^\circ}$$

$$= 10.58 \angle -79.11^\circ$$

Inductor, capacitor & resistors are called passive element.

voltage and current sources are called active element.

$$V_R = 20 I_1$$

$$= 20 \times 4 \angle 0^\circ$$

$$= 80 \angle 0^\circ$$

$$V_C = -j5 I_2$$

$$= -j5 \times 10.58 \angle -100.89^\circ$$

$$= 52.9 \angle 169.11^\circ$$

$$V_L = j10 I_3$$

$$= j10 \times 10.58 \angle -79.11^\circ$$

$$= 105.8 \angle 10.9^\circ$$

$$V_I = V_R + V_L$$

$$V_I = V_R - V_C + V_L = 60 \angle 30^\circ$$

voltage 100
 200 (अस्य)
 पदिक दिष्ट
 current 100
 200 (+ve)
 (-) मान्यकर ।
 (-) मान्यकर ।

Applying KVL at Mesh-1

current source
 voltage source

$$= 80 + 105.8 \angle 10.9^\circ$$

$$= 184.97 \angle 6.21^\circ$$

$$P_R = \frac{1}{2} \times 80 \times 4 \cos(0^\circ - 0^\circ)$$

$$= 160 \text{ W}$$

$$P_L = \frac{1}{2} \times 105.8 \times 10.58 \cos(10.9 + 79.11^\circ)$$

$$= 0$$

$$P_C = \frac{1}{2} \times 52.9 \times 10.58 \times \cos(169.11 + 100.89^\circ)$$

$$= 0$$

$$P_V = \left(- \frac{1}{2} \times 60 \times 10.58 \cos(30 + 100.89^\circ) \right) P_V = \text{Power absorbed by voltage source}$$

$$= 207.77 \text{ W}$$

current (I_2)
(-) $\overline{P_V}$

$$P_I = \left(- \frac{1}{2} \times 184.97 \times 4 \cos(6.21 - 0^\circ) \right)$$

$$= -367.77 \text{ W}$$

current
(-) $\overline{P_I}$
power supply $\overline{P_I}$

voltage source power absorbed
current supply

power absorb \rightarrow power supply
 ସମାନ ଥାଏ ।

13-10-19
 7(0) day


Average power / real power \rightarrow normally power
 ବ୍ୟୟ ବୁଝାଏ

AC ଓ DC ଗଠା Node ଓ Mesh Analysis ଗଠାଏ
 ଗଠାଏ କରା ଥାଏ ।

EX-10.1-10.4

Practice problem - 10.1-10.4
 ନୂଆ node Analysis ଓ
 Mesh Analysis (ନୂଆ) ଗଠାଏ

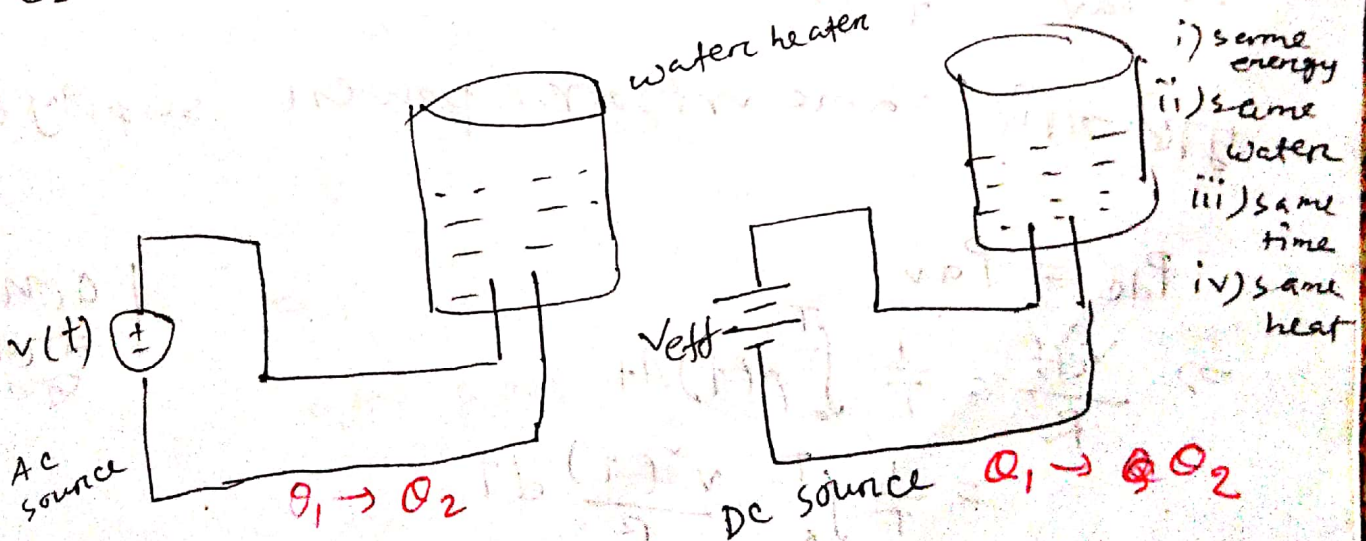RMS value: Root Mean square (effective value)
 ଗଠାଏ signal ଗଠାଏ RMS value ଗଠାଏ ବୁଝାଏ
 ଗଠାଏ signal DC equivalent value.



ଶୁଣିବେ ଚାହୁଁ ଚାହୁଁ ଥାଏ

ଶିକ୍ଷା + ନୀତି

ତାପମାତ୍ରା $20^{\circ}\text{C} \rightarrow 100^{\circ}\text{C}$ ରେ

ଏହା ଉପରେ ଉପଯୋଗୀ energy supply ଦିଆଯାଏ source ଦ୍ୱାରା

\therefore DC ଓ AC ଉଭୟ equivalent (ସମ) DC source ଓ AC source ଉଭୟ effective

AC signal ଓ DC equivalent ଉଭୟ V_{eff} value.

For DC source,

$$P_{\text{DC}} = \frac{V_{\text{eff}}^2}{R}$$

For AC source,

$$P(t) = \frac{v^2(t)}{R}$$

↓
Instantaneous power

AC ଉପରେ (ଅନୁସ୍ଥାପନ) power ଉପରେ ବ୍ୟବହାର Average power

$$\therefore P_{\text{AV}} = \frac{1}{T} \int_0^T P(t) dt$$

ଯଦି ଉଭୟ same amount power supply (ହୁଏ)

$$P_{\text{DC}} = P_{\text{AV}}$$

$$\Rightarrow \frac{V_{\text{eff}}^2}{R} = \frac{1}{T} \int_0^T P(t) dt$$

0 (ଅନୁସ୍ଥାପନ) ଉପରେ ବ୍ୟବହାର cycle

$$= \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt$$

$$\Rightarrow v_{eff} = \frac{1}{T} \int_0^T v(t) dt$$

$$\Rightarrow v_{eff} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

\rightarrow AC signal $\{v(t)\}$ effective value

value (effective value) process.

v_{eff} value is DC equivalent

So, the RMS value of $x(t)$

$$X_{rms} = X_{eff} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

we generalise expression.

Let, $x(t) = X_m \sin \omega t$

$$X_{eff} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T X_m^2 \sin^2 \omega t dt}$$

$$= \sqrt{\frac{X_m^2}{2T} \int_0^T 2 \sin^2 \omega t dt}$$

$$= \sqrt{\frac{X_m^2}{2T} \int_0^T (1 - \cos 2\omega t) dt}$$

$$= \sqrt{\frac{X_m^2}{2T} (T - 0)}$$

$$= \frac{X_m}{\sqrt{2}}$$


(we) RMS value is effective value.

sin or cos
 take 2
 cycle of
 integrate
 zero
 in

(DC source)

AC source is DC source

II

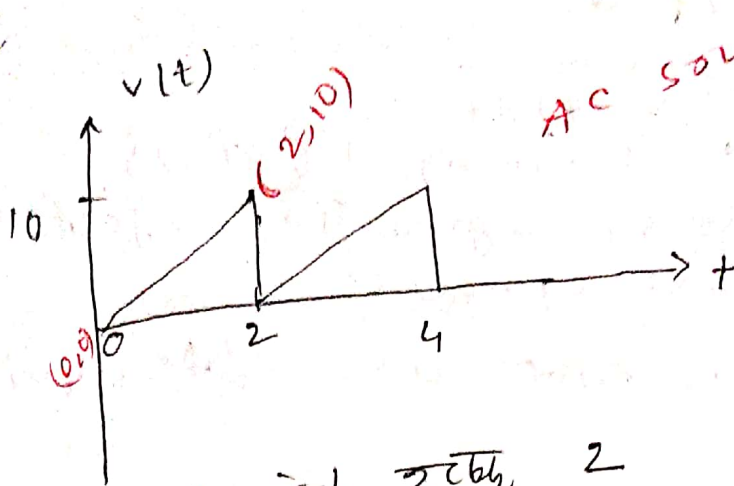

AC source

$$y = \frac{y_1 - y_2}{x_1 - x_2}$$

$$= \frac{0 - 10}{0 - 2}$$

$$= 5$$

period 2T, 2

Find the RMS value of the given signal
 Give expression in form of wave
 form (4.5V) or expression
 in form of cycle of 2π

$v_{rms} = \frac{V_m}{\sqrt{2}}$

$v = V_m$

$$v(t) = 5t \quad 0 < t < 2$$

cycle of 2π
2π

use the formula
V rms

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$= \sqrt{\frac{1}{2} \int_0^2 25t^2 dt}$$

$$= \sqrt{\frac{25}{2} \left[t \frac{t^3}{3} \right]_0^2}$$


$$= \sqrt{\frac{25}{2} \times \frac{8}{3}}$$

$$= 5.773$$

(DC source)

5.773 ATQ DC source or power supply
 (4.5V, AC source or power supply)

A

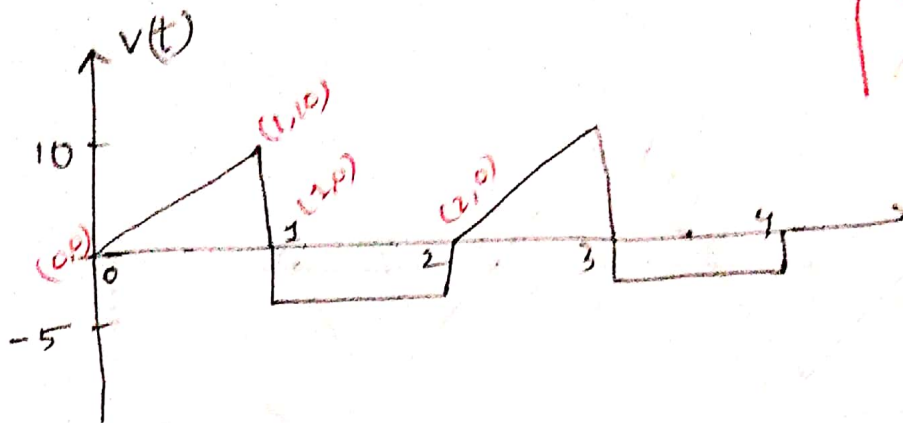

$0 < t < 1$
 $y = mt$
 $y - 0 = \frac{10 - 0}{1 - 0} (t - 0)$
 $\Rightarrow y = 10t$
 $1 < t < 2$
 $y = b$
 $y - 10 = \frac{10 - 10}{2 - 1} (t - 1)$
 $\Rightarrow y = 10$

Period 2 (0 to 2 and 2 to 4)

$$v(t) = 10t \quad 0 < t < 1$$

$$= -5 \quad 1 < t < 2$$

2T/2 cycle to find expression.


$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$= \sqrt{\frac{1}{2} \int_0^2 v^2(t) dt}$$

$$= \sqrt{\frac{1}{2} \left[\int_0^1 (10t)^2 dt + \int_1^2 (-5)^2 dt \right]}$$

$$= \sqrt{\frac{1}{2} \left[100 \frac{t^3}{3} \Big|_0^1 + [25T]_1^2 \right]}$$
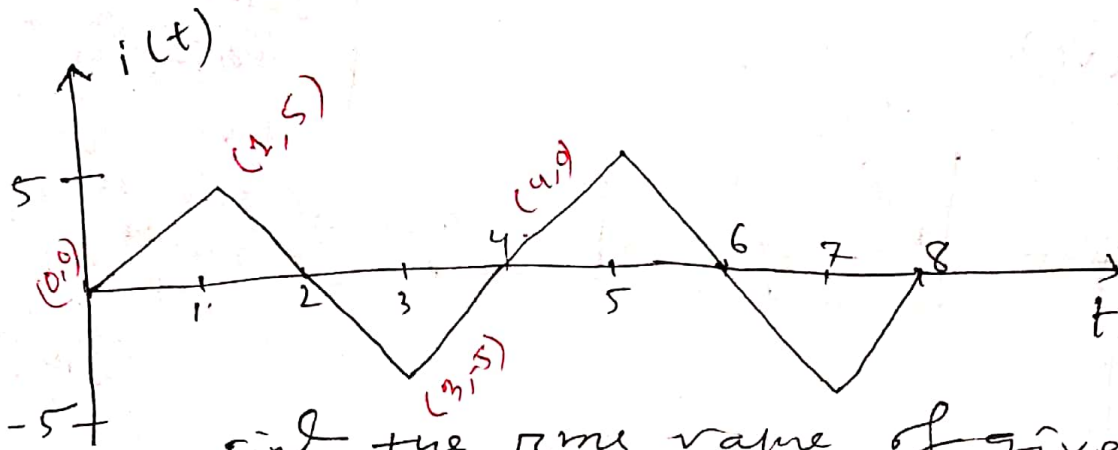
$$= \sqrt{\frac{1}{2} \left[100 \frac{1^3}{3} + 25(2-1) \right]}$$



Find the rms value of given signal
 given period is 4 units

$$\therefore T = 4$$

Given 0 < t < 1

$$i(t) = 5t \quad 0 < t < 1$$

$$= -5t + 10 \quad 1 < t < 3$$

$$= 5t - 20 \quad 3 < t < 4$$

$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$= \sqrt{\frac{1}{4} \left[\int_0^1 (5t)^2 dt + \int_1^3 (-5t+10)^2 dt + \int_3^4 (5t-20)^2 dt \right]}$$

$$-5t + 10$$

$$\downarrow$$

$$t = 2$$

$$t = 0$$

$$t = 4$$

$$t = 1$$

$$t = 3$$

$$t = 4$$

$$t = 0$$

$$t = 1$$

$$t = 3$$

$$t = 4$$

$$t = 0$$



$$t = 1$$

$$t = 3$$

$$t = 4$$

7(E)-Day

14-10-19

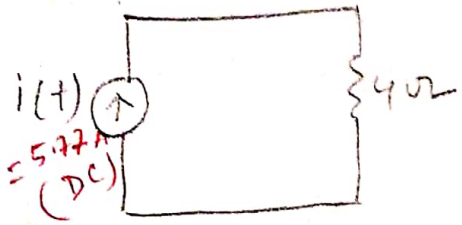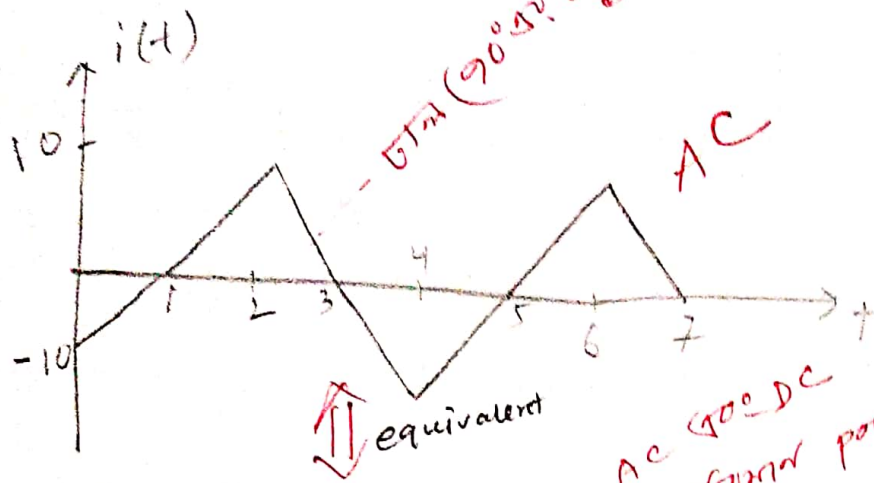

AC & DC
Same reference power supply

4Ω resistor
absorb power
power supply

I_{rms} value of current

$T = 4$

$$i(t) = 10t - 10 \quad 0 < t < 2$$

$$= -10t + 30 \quad 2 < t < 4$$

$$\begin{cases} t = 1 \\ i = 0 \end{cases}$$

2nd part
 $y - (-10) = \frac{-10 - 10}{0 - 2} (x - 0)$
 $\Rightarrow y + 10 = 10x$
 $\Rightarrow y = 10x - 10$
 $\Rightarrow i(t) = 10t - 10$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$= \sqrt{\frac{1}{4} \left[\int_0^2 (10t - 10)^2 dt + \int_2^4 (-10t + 30)^2 dt \right]}$$

$$= \sqrt{\frac{1}{4} (66.67 + 66.67)}$$

$$= 5.77 \text{ A}$$

~~P = I_{rms}^2 R~~

$$P = I_{rms}^2 R$$

$$= 5.77^2 \times 4$$

$$= 133.1 \text{ W}$$

$$P = \frac{V^2}{R}$$

voltage (V) \rightarrow $\frac{V^2}{R}$

Q2 related pb at (2017-2018) 25d1

Power in AC circuit
chapter - 11

Apparent power:

$$S = \frac{1}{2} V_m I_m$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

Apparent power:

if, $v(t) = V_m \sin(\omega t + \phi_v)$
 $i(t) = I_m \sin(\omega t + \phi_i)$

then Apparent power, $S = \frac{1}{2} V_m I_m$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}}$$

$$= V_{rms} I_{rms}$$

Unit of apparent power is VA

V_{rms} (voltage) \times I_{rms} (current) \rightarrow product \rightarrow Apparent power

power factor, $pf = \cos(\phi_v - \phi_i)$

power factor \rightarrow maximum value 1
minimum " 0

resistive load \rightarrow power factor

capa \rightarrow Induc

Average power or Real power,

$$P = P_{av} = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i)$$

$$\Rightarrow P = S \times pf$$

$$\Rightarrow pf = \frac{P}{S}$$

ϕ for \cos , \rightarrow Apparent power
or real power \rightarrow convert \rightarrow \rightarrow

complex power

$$\underline{S} = \frac{1}{2} V I^*$$

I^* = current
 \rightarrow complex
conjugate

The product of the
phasor of voltage and complex
conjugate of current is complex power.

$$= \frac{1}{2} V_m \angle \phi_v \cdot I_m \angle -\phi_i$$

$$= \frac{1}{2} V_m I_m \angle \phi_v - \phi_i$$

$$= \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) + j \frac{1}{2} V_m I_m \sin(\phi_v - \phi_i)$$

$$= P + jQ$$

↓
real power

where, $P \rightarrow$ Real power / average power
 $Q \rightarrow$ Reactive power

for resistive load,

$$\phi_v - \phi_i = 0^\circ$$

इसलिए reactive power शून्य है।
 inductive or capacitive load,

$$\phi_v - \phi_i = 90^\circ$$

इसलिए reactive power शून्य है।

unit of Real power = watt

u Reactive power = VAR

u u complex " = VA

→ volt ampere reactive

Impedance:

$$\text{Impedance, } Z = \frac{V}{I}$$

$$= \frac{V_m \angle \phi_v}{I_m \angle \phi_i}$$

$$= \frac{V_m}{I_m} \angle \phi_v - \phi_i$$


$$= \frac{V_m/\sqrt{2}}{I_m/\sqrt{2}} \angle \phi_v - \phi_i$$

$$= \frac{V_{rms}}{I_{rms}} \angle \phi_v - \phi_i \ \Omega$$

$$\Rightarrow Z = \frac{V_m}{I_m} \angle \phi_v - \phi_i = \frac{V_{rms}}{I_{rms}} \angle \phi_v - \phi_i$$

\downarrow peak value
 \downarrow rms value

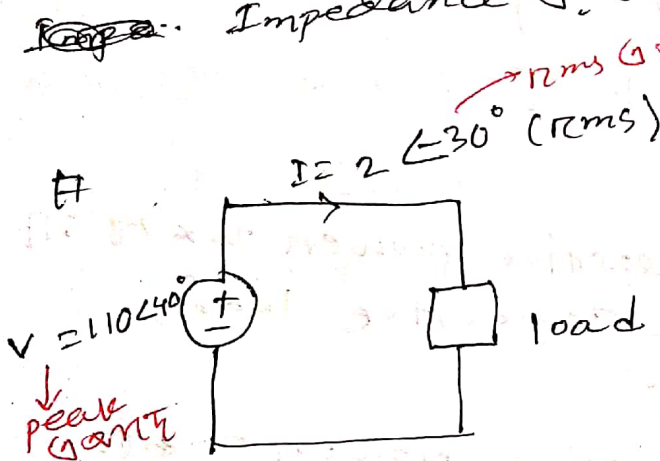~~Impedance~~ Impedance $Z = \frac{V}{I} \angle \phi_v - \phi_i$



find, (i) load impedance, Z

(ii) Apparent power

(iii) Real and reactive power

(iv) complex power

(v) power factor, pf

दिए गये Z rms / दिए गये Z peak value के साथ मिलान करें, Z के value rectangular format में

निम्न Z (Ans 9)

~~i) $Z = \frac{V}{I} = 55.67$~~

i) $13.30 + j 36.92 \Omega$

Apparent power = $\frac{1}{2} V_m I_m$
or $V_{rms} \cdot I_{rms}$

~~153~~

i) $V_{rms} = \frac{110}{\sqrt{2}} \angle 40^\circ$

$Z = \frac{110 \angle 40 + 30^\circ}{\sqrt{2}}$

$= 38.89 \angle 70$ — polar

$= 13.30 + j 36.92$ — rectangular

Example 11.9 - 11.12
practice pb

11.9 - 11.12
15.10 270

related
pb 270
271

ii) Apparent power = $\frac{1}{2} V_m I_m$
 $= \frac{1}{2} \times 110 \times 2\sqrt{2}$
 $= 155.56$

Syllabus: AC (rms) \angle \angle \angle

8(c)-day

19-10-19

(तारा का सत्या प्रोजेक्ट क्लास)

power factor correction:

Power factor correction is a process, the process by which the power factor of the system can be improved without changing the original load current or voltage.

$$P_{av} = S \times pf$$

$$S = \frac{P_{av}}{pf}$$

$$pf = \cos(\phi_v - \phi_i)$$

s = apparent

$$L_1 = 100 \text{ W}, pf = 0.9$$

$$L_2 = 100 \text{ W}, pf = 0.5$$

Real power same

Supply voltage = 220 V (rms)

$$P = V_{rms} I_{rms} \cos(\phi_v - \phi_i)$$

$$= V_{rms} I_{rms} pf$$

$$I_{rms1} = \frac{100}{220 \times 0.9} = 0.505 \text{ A (rms)} \quad (\text{rms})$$

$$I_{rms2} = \frac{100}{220 \times 0.5} = 0.91 \text{ A (rms)} \quad (\text{rms})$$

$i^2 R$ loss 20

power factor correction का मतलब है (power factor correction का मतलब है)

original pf = $\cos \phi_1$

new pf = $\cos \phi_2$

power factor correction value $\cos \phi_2$

Inductor Z_0 (ms),



$$R + j\omega L = R \angle \phi$$

$$Z = \sqrt{R^2 + (\omega L)^2}$$

$$\phi = \tan^{-1} \frac{\omega L}{R}$$

If, $R=0$, $\phi = 90^\circ$

for $R=0$, $\phi = 90^\circ$ to 180°

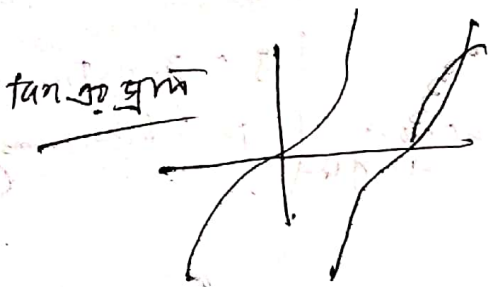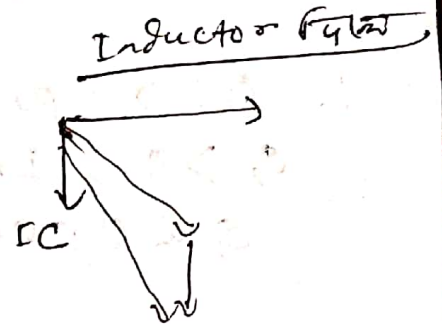

Reactive power:

$$Q = V_{rms} I_{rms} \sin(\phi_v - \phi_i)$$

$$= S \sin(\phi_v - \phi_i)$$

$$\frac{1}{2} V_m I_m$$

for resistive load,
 $Q = 0$

for resistive load,
 $\phi_v - \phi_i = 0$
 $\sin 0 = 0$

$V_{rms} I_{rms}$
Power

for inductive load,

$$Q = S$$

for capacitive load,


$$Q = -S$$

- $\therefore Q = 0$, resistive
- $Q > 0$, inductive
- $Q < 0$, capacitive

complex power,

$$\underline{S} = P + jQ$$

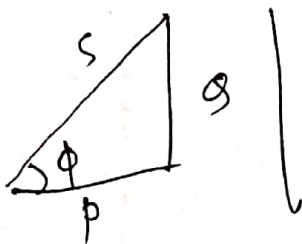apparent power, $S = V_{rms} I_{rms} = \sqrt{P^2 + Q^2}$ complex $P = P_{rms} \cos(\phi_v - \phi_i)$



$\phi =$ power factor angle


$$Q = P_{rms} I_{rms} \sin(\phi_v - \phi_i)$$

$$P = P_{rms} I_{rms} \cos(\phi_v - \phi_i)$$

$$P = S \cos \phi$$

$$Q = S \sin \phi$$

ϕ wrt $\phi_v - \phi_i$

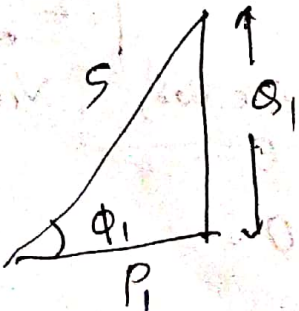


figure

$$Q_1 = P_1 \tan \phi_1$$

Inductive
angle ϕ_1

2nd figure

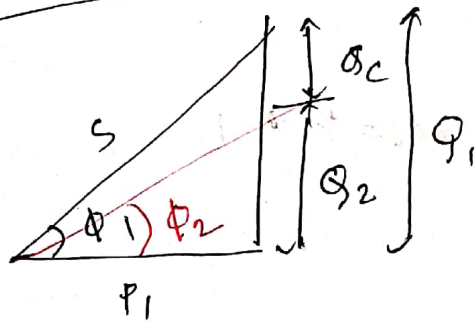

real power same as
reactive " " " " " "
apparent power =

$$Q_2 = P_1 \tan \phi_2$$

$$Q_c = Q_1 - Q_2 = P_1 (\tan \phi_1 - \tan \phi_2)$$

error

$$Q_c = \frac{V_{rms}^2}{X_c}$$

reactive power in VAR
mainly = $\frac{V^2}{R}$

$$= \frac{V_{rms}^2}{\frac{1}{\omega C}}$$

$$= \omega C V_{rms}^2$$

$$\therefore \omega C V_{rms}^2 = P_1 (\tan \phi_1 - \tan \phi_2)$$

$$C = \frac{P_1 (\tan \phi_1 - \tan \phi_2)}{\omega V_{rms}^2}$$

power factor
PF, power
factor or
angle

(for capacitance calculation)

$$f = 50 \text{ Hz}$$

Chapter 11

for AC topic

1st Example practice
2nd Example practice

AC circuit is based

node and mesh and Kirchhoff's equations

and also other circuit

analysis and synthesis

