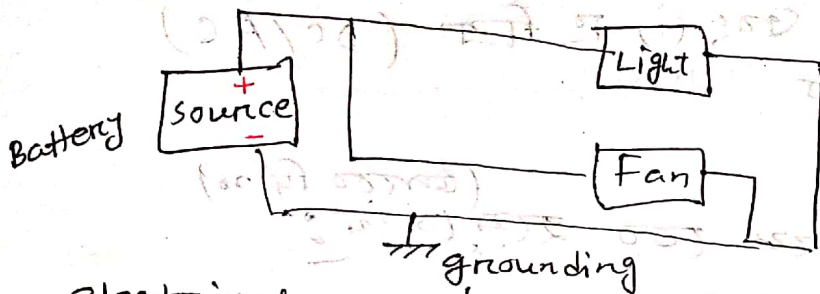


(1) c-day (20-8-19) (revised)

EEE



electrical circuit: definition

source: Battery, generator

source 2 प्रकार 1



- i) voltage source
- ii) current "

* source एक Active element.


* source power supply करा

* याका power receive करा (active element (उत्तर) कात passive element, such as light, fan etc.

voltage source:

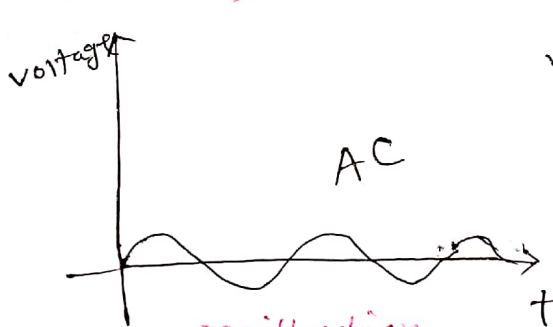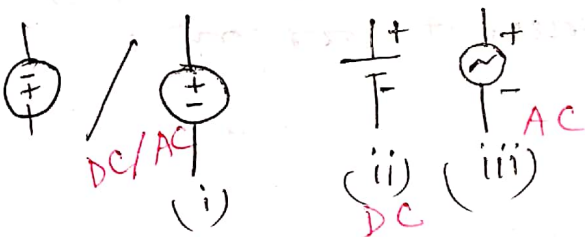

oscillation
क्या करता है (2)

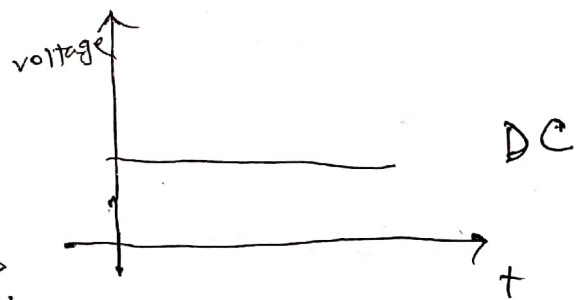

Current source

Battery - DC (ii) नं चित्र

generator - AC वयं (i) नं चित्र (DC/AC)
(iii) नं चित्र

current source :

current source लवळ लळ शयें (जायें) (कलळ दिळ)




निळे दिळे (जायें, source व current प्रवळण)



passive element :



resistor

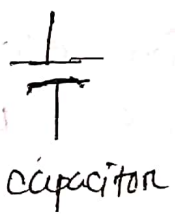


capacitor




Inductor

सकल passive element लळ वयें दिळ represent करुण

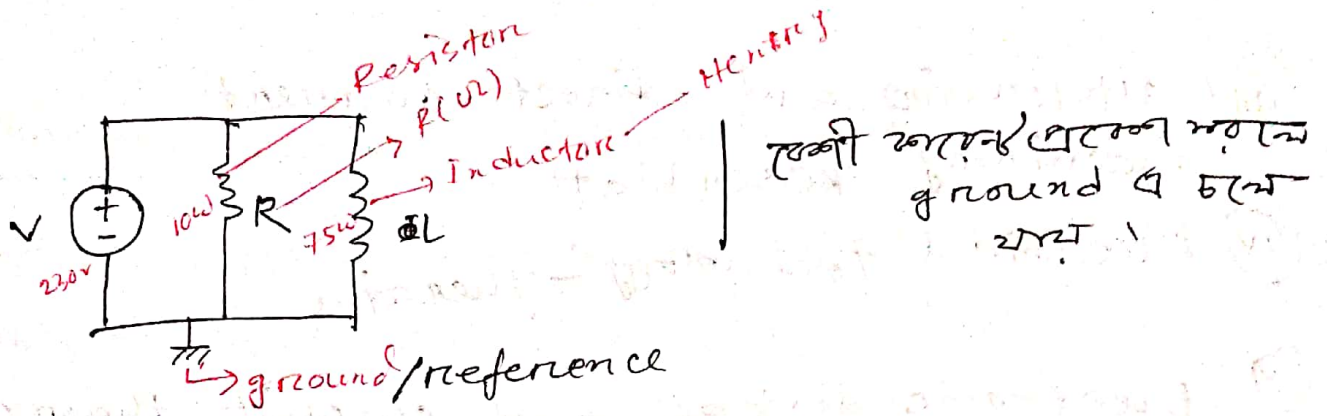- * light लळ resistor
- * Fan लळ inductor



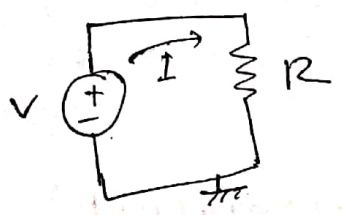उत्तर है:
At definite temperature, $V \propto I$




voltage बढ़ाना, current बढ़ाना

$V \propto I$

$\Rightarrow V = IR$ \rightarrow proportionality constant

$\therefore R = \frac{V}{I}$

वास्तव में constant fixed value है।

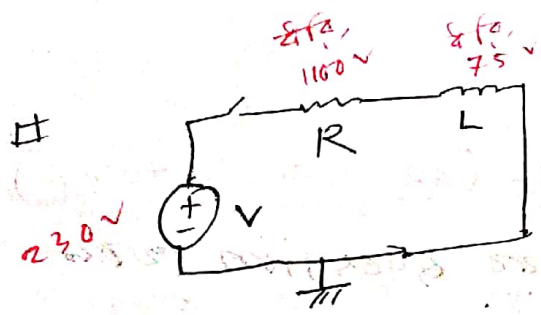

series
एक ही धारा बहने (जो कि एक ही धारा बहने)

इ समानता (voltage same value)

Electrical circuit (60-70%)

- Book - \rightarrow main book
- (i) Fundamentals of Electronic circuits - Alexander
 - (ii) Introductory circuit Analysis - Boylstad

machine

- (iii) Alternating and direct current machinery - Rosenblatt
- (iv) Electrical Technology - Theraja
- (v) Electronic devices and circuit theory - Boylestad

(1) D-day - (21-08-19) 5/10

Md. Farhamdur REZA

COURSE NAME: Basic electrical circuit

COURSE NO: EEE-1241

part

- 1. circuit - 6 marks question
- 2. machine } 2 marks "
- 3. Electronics }

BOOK:

Electronic circuit - Alexander (বই + class lecture)

অধিকার বই এবং বিজ্ঞান বইয়ের question থেকে
কিছু common করতে গা।

charge: charge is an electrical property of an atomic particle of which material consists, measured in C (Coulomb)

atom = electron + proton + neutron
 ↓ ↓ ↓
 (-ve charged) (+ve) charge chargeless

e is the smallest unit of positively charge. proton has maximum e and electron has $-e$.

Charge is denoted as q (denoted as q)

current: The rate

$$dt \rightarrow dq$$

$$I \rightarrow \frac{dq}{dt}$$

$$I = \frac{dq}{dt}$$

dt समय प्रवाहित चार्ज मात्रा $\frac{dq}{dt}$

$$I = \frac{dq}{dt}$$


The amount of charge flows through a wire/conductor per unit time is called current.

The rate of change of charge is called current.

$$i = \frac{dq}{dt}$$

$$\Rightarrow Q = \int i dt$$

চার্স flow

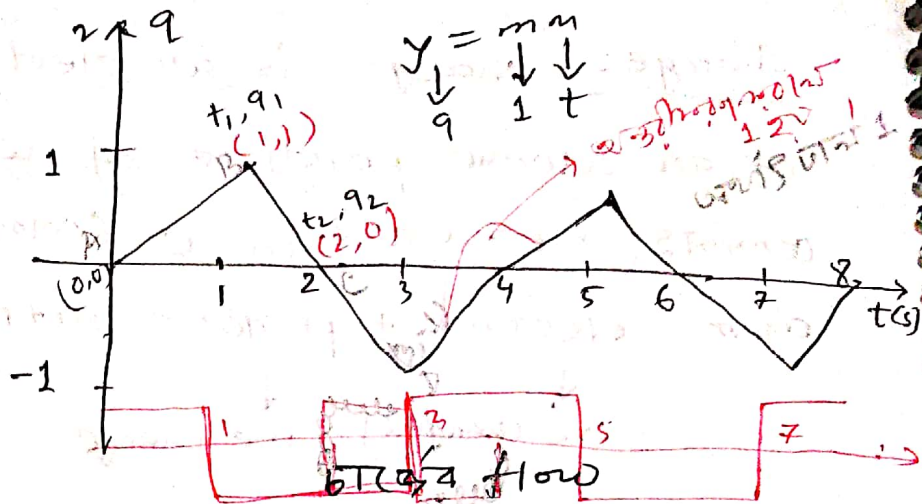

$$q(t) = \begin{cases} t & 0 < t < 1 \\ -t+2 & 1 < t < 3 \end{cases}$$

$$\text{slope} = \frac{y_1 - y_2}{x_1 - x_2}$$

$$AB \text{ এর ঢাল} = \frac{1-0}{1-0} = 1$$

$$BC \text{ এর ঢাল} = -1$$

সিদ্ধান্ত:

$$y - y_1 = \frac{y_1 - y_2}{x_1 - x_2} (x - x_1)$$

$$\Rightarrow y - y_1 = \frac{0-1}{2-1} (x - x_1)$$

$$\therefore i(t) = \begin{cases} 1 & 0 < t < 1 \\ -1 & 1 < t < 3 \end{cases}$$

$$\Rightarrow q - 1 = \frac{1-0}{1-2} (t-1)$$

$$\Rightarrow q = -t + 2$$

$$\therefore i(t) = \begin{cases} 1 & 0 < t < 1 \\ -1 & 1 < t < 3 \end{cases}$$

The current flowing through an element

$$i(t) = \begin{cases} 2A & 0 < t < 1 \\ 2t^2 A & t > 1 \end{cases}$$

find the amount of charge from $t=0$ to $t=2$

Ans $q = \int_0^2 i dt$


$$= \int_0^1 2 dt + \int_1^2 2t^2 dt$$

$$= 2 + \left[\frac{2}{3} t^3 \right]_1^2$$



$$= 2 + \frac{2}{3}(8-1)$$

$$= 2 + 4.667$$

$$= 6.667 \text{ C}$$



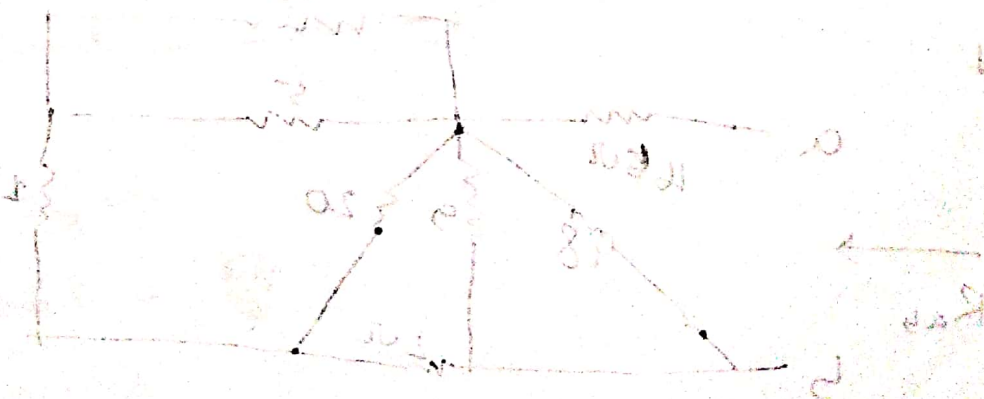


(1) E-day (24-08-19)

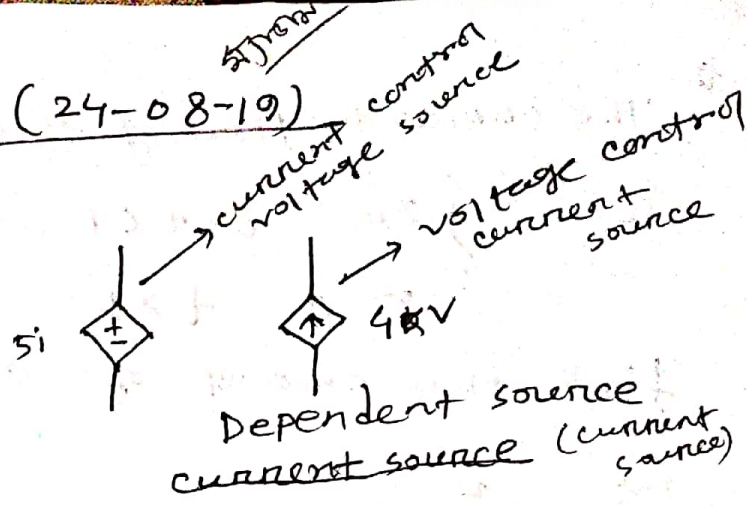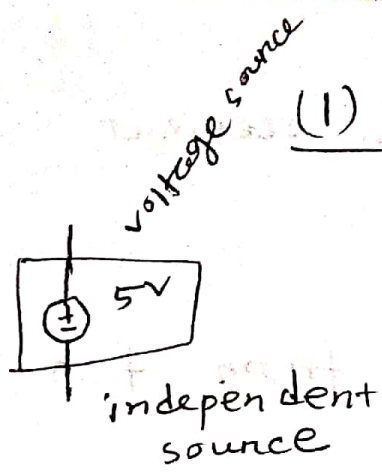

voltage & current flow direction

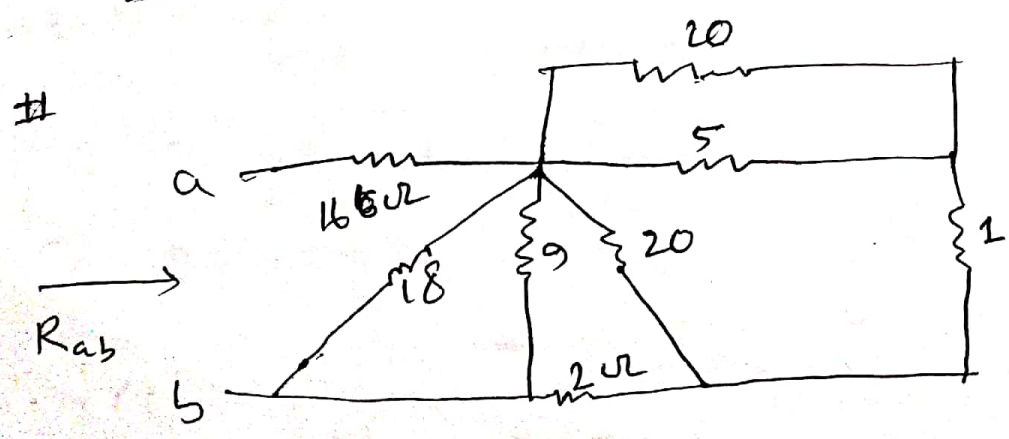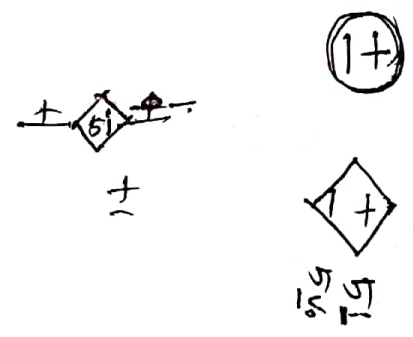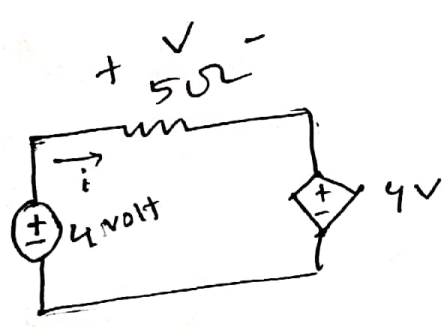- (i) voltage controlled voltage source / voltage current source
- (ii) current u u u
- (iii) voltage u current u
- (iv) current u u u



Find the equivalent resistance / R_{ab} / R_{eq}

$$5 \parallel 20 = \frac{5 \times 20}{5 + 20} = 4 \Omega$$

$$4 + 1 = 5 \Omega$$


$$5 \parallel 20 = 4 \Omega$$

$$4 + 2 = 6 \Omega$$

$$18 \parallel 9 \parallel 6 = \frac{1}{\frac{1}{18} + \frac{1}{9} + \frac{1}{6}} = 3 \Omega$$

$$\therefore R_{eq} = 16 + 3 = 19 \Omega$$

#

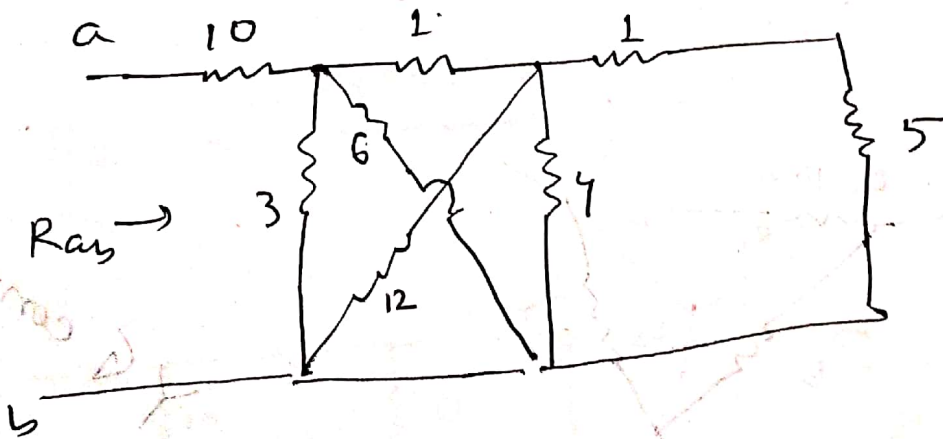

$$5 + 1 = 6 \Omega$$

$$6 \parallel 4 \parallel 12 = 2 \Omega$$


$$2 + 1 = 3 \Omega$$

$$3 \parallel 6 \parallel 3 = \frac{6}{5} \Omega$$

$$\therefore R_{eq} = \frac{6}{5} + 10$$

$$=$$

Et

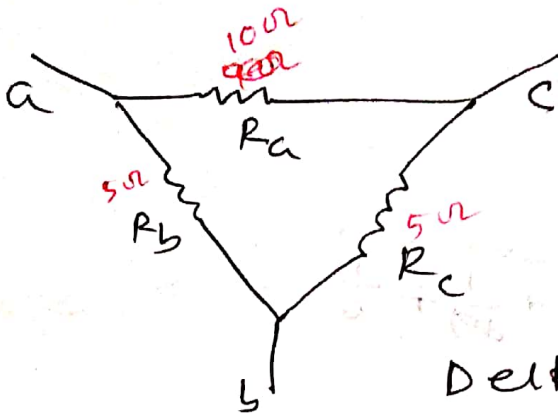


Delta network




wye network

#

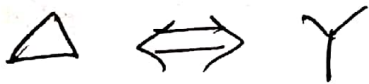

convert Δ to Y

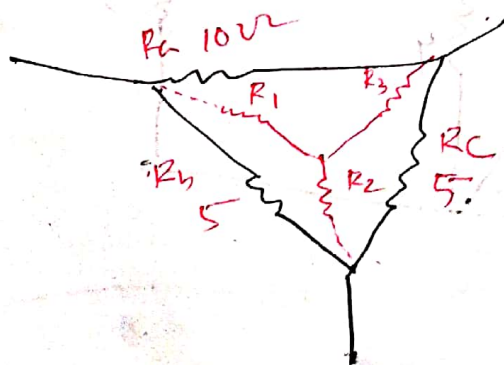


$Y \rightarrow \Delta$ convert

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{10 \times 5}{10 + 5 + 5}$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$
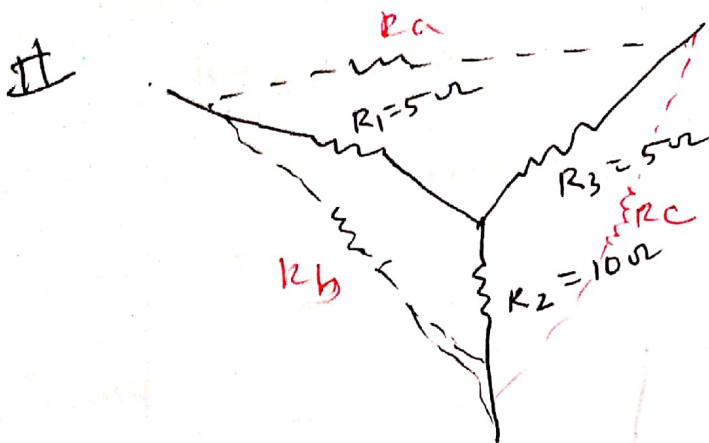
$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$




wye to ~~delta~~ delta


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$
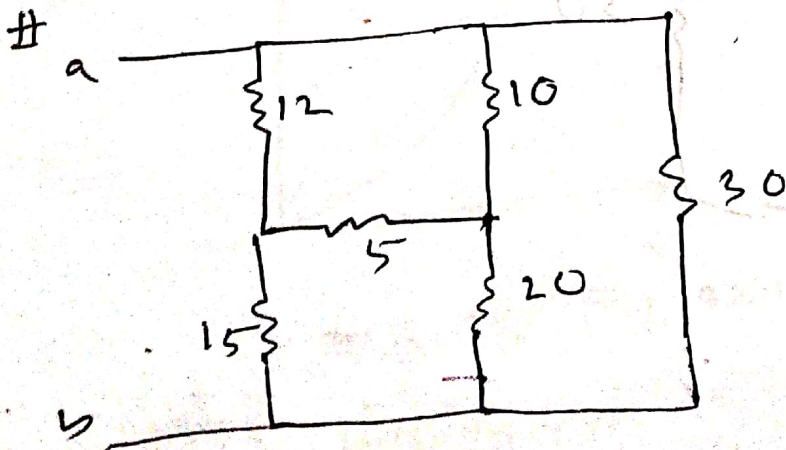
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$



⇒ Ray

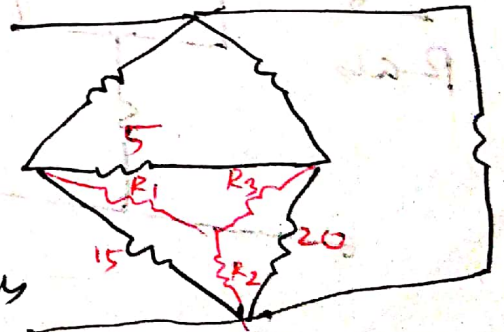


$$R_1 = \frac{5 \times 15}{5 + 15 + 20}$$

$$R_2 = \frac{15 \times 20}{5 + 15 + 20}$$


$$R_3 = \frac{5 \times 20}{5 + 15 + 20}$$

⇒

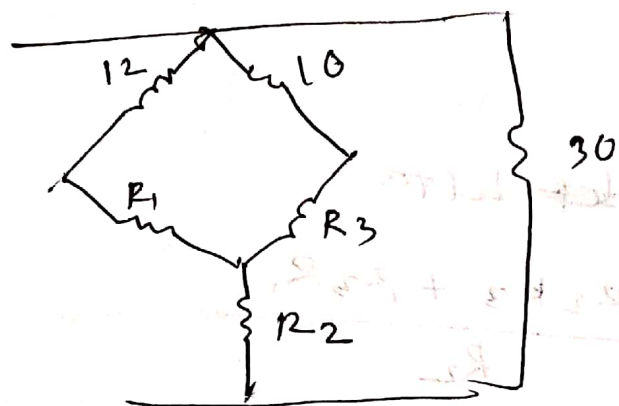

12Ω u R1 in series


10 u R3 u R2

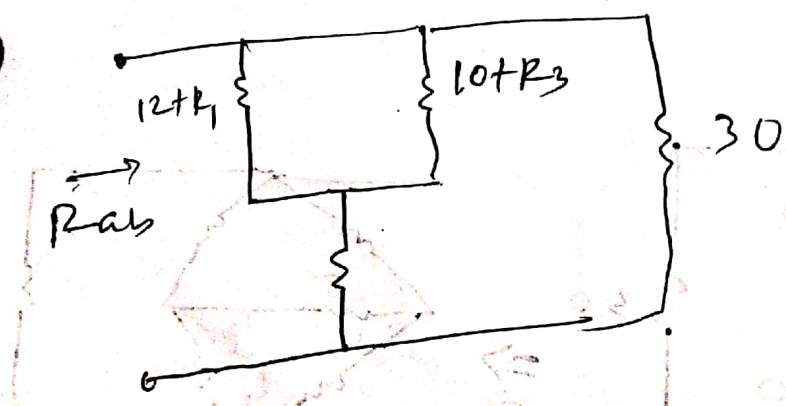

problem


Alexander: 2.57, 2.53, 2.45, 2.46

Homework

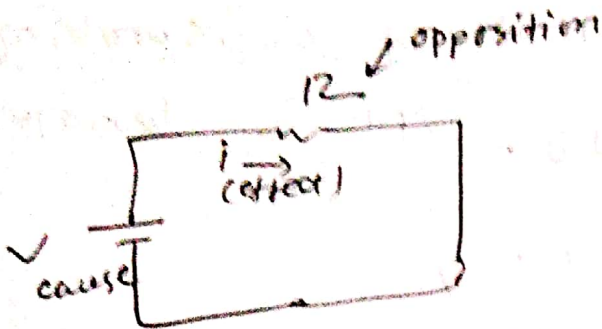


$$\text{effect} = \frac{\text{cause}}{\text{opposition}}$$

$$i = \frac{V}{R}$$

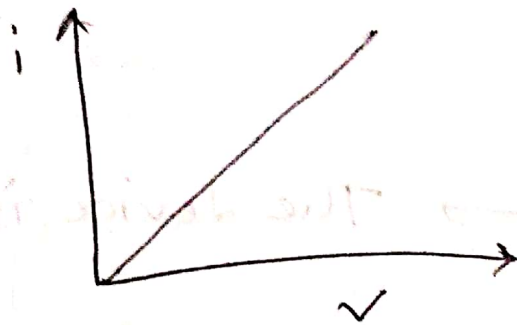

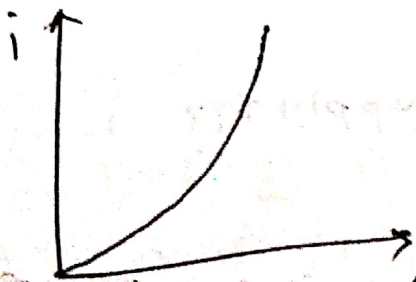voltage R is independent
 current is dependent
 R is independent
 i is dependent



कारण (वोल्टेज) का अभाव

वोल्टेज limitation

कारण temperature vary करेगा ।

2(c) - Day

27-08-19

power: rate at which work is done or energy is transferred

power is the time rate of absorbing or supplying energy. It is denoted as P , measured in watt (W).

$$P = \frac{dW}{dt} \quad W \rightarrow \text{energy}$$

$$= \frac{dq}{dt} \cdot \frac{dW}{dq}$$

$$= iV$$


$$= Vi$$

If, $P \Rightarrow (+ve)$ \rightarrow The device is absorbing power


→ mechanical energy to convert

generator power supply

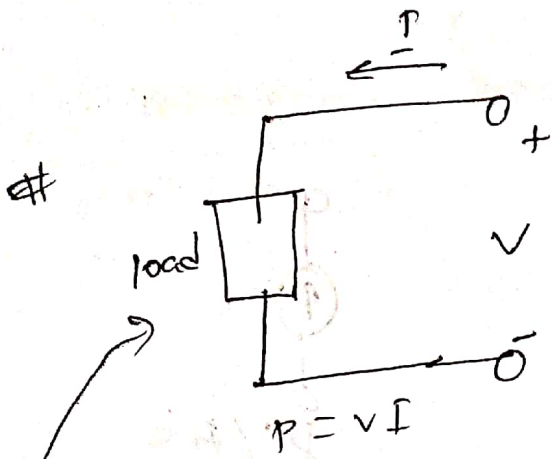If, $P \rightarrow (-ve)$ \rightarrow supplying power





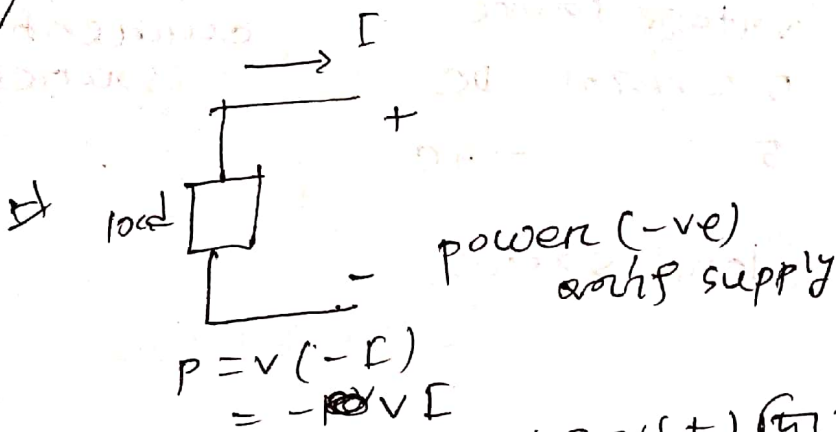+ दि.प. प्राप्त, (-) दि.प. लो
 शत, power (+ve)
 लो अक्षर्य



power (-ve)
 लो supply


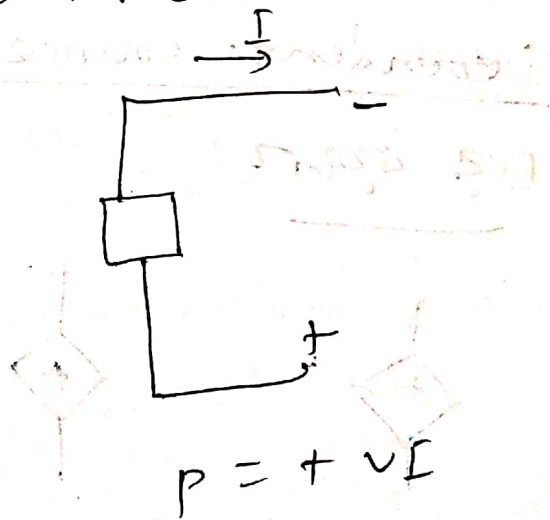
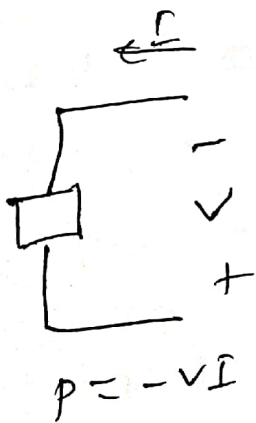
current लो लो (+) दि.प. शत, (-) दि.प. लो शत



Energy: Energy is the capacity to do work and it is measured in joule.

$$W = \int_0^t P dt$$



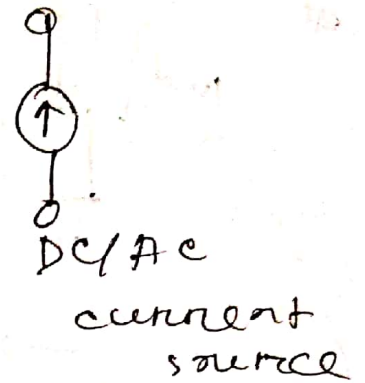
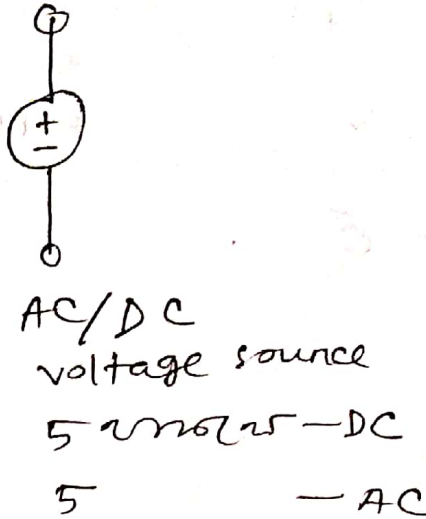
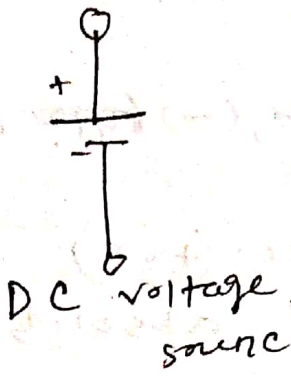
$$= Pt \quad [\text{power constant शत}]$$




स्रोत, independent source

Dependent source:

दो प्रकार:

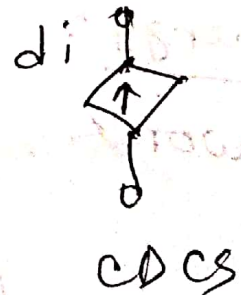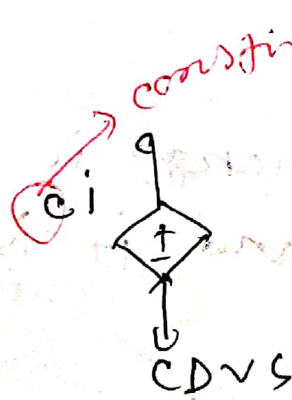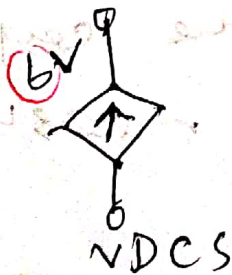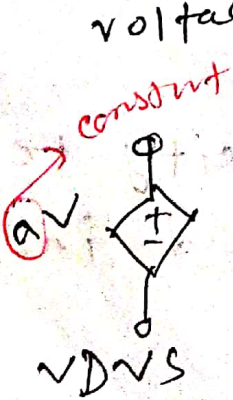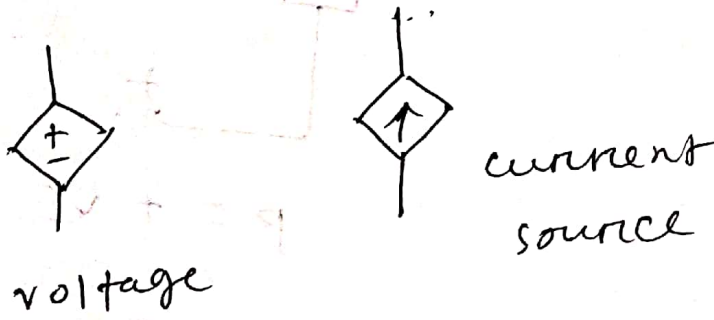

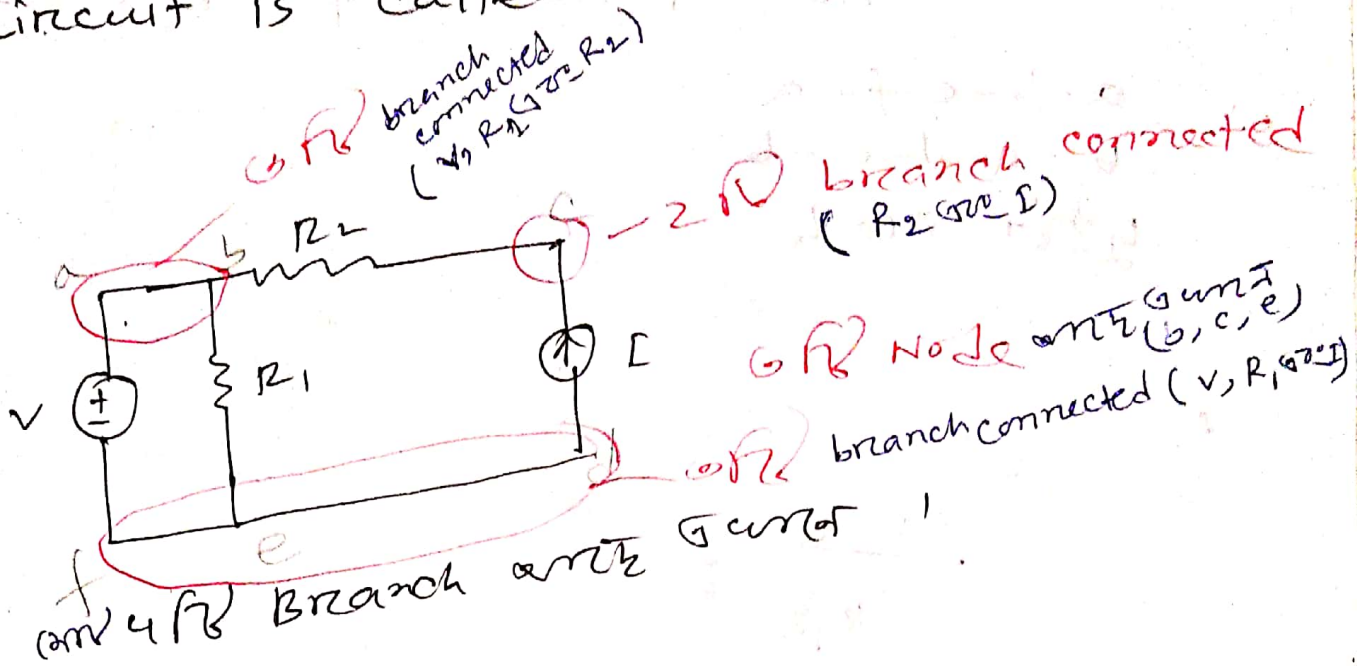(I) Branch: Each element of an electrical circuit is called Branch.



(II) Node: Point in circuit where two or more branches are connected.

Node is a point where two or more branches are connected.



(III) Loop: Loop is a closed path in a circuit.

- a-b-e-f-a
- b-c-d-e-b
- a-b-c-d-e-f-a

(iv) Mesh: Mesh is also a close path where no other loop is exist.


a-b-e-f-a
 b-c-d-e-b
 2 mesh

#

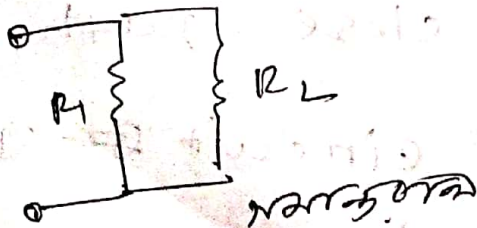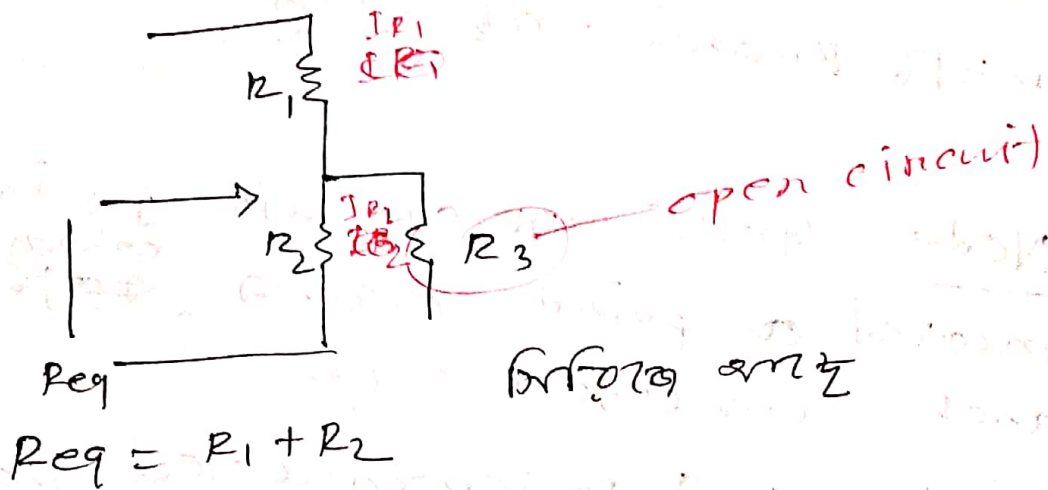

voltage divider Rule
(series connection)

ଅନୁପାତ ଗୁଣିତ ଭାବେ
ପ୍ରୟୋଗ କରାଯାଏ

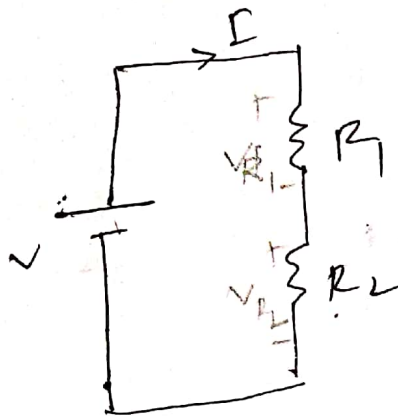

$$I = \frac{V}{R_1 + R_2}$$

$$V_{R_1} = I R_1$$

$$= \frac{V}{R_1 + R_2} \cdot R_1$$

$$= \frac{R_1}{R_1 + R_2} \cdot V$$

$$V_{R_2} = I R_2$$

$$= \frac{V}{R_1 + R_2} \cdot R_2$$

$$= \frac{R_2}{R_1 + R_2} V$$

If, N resistors are connected in series,


then, voltage across

the resistor

$$R_m, V_{R_m} = \frac{R_m}{R_1 + R_2 + \dots + R_N} \times \text{applied voltage}$$

where, $m = 1, 2, \dots, N$

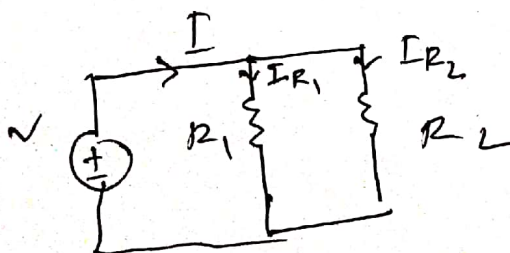current divider rule: (ଅନୁପାତ ଗୁଣିତ ଭାବେ ପ୍ରୟୋଗ କରାଯାଏ)



ଅନୁପାତ ଗୁଣିତ ଭାବେ

$$R_{eq} = \frac{V}{I}$$

$$I_{R_1} = \frac{V}{R_1}$$

$$I_{R_2} = \frac{V}{R_2}$$

$$I = I_{R_1} + I_{R_2}$$

$$\Rightarrow \frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\Rightarrow \frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$$

$$\Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


Req for parallel connection
current divider

$$I_{R_1} = \frac{V}{R_1} = \frac{I R_{eq}}{R_1} = \frac{I}{R_1} \times \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{R_2}{R_1 + R_2} I$$

$$I_{R_2} = \frac{R_1}{R_1 + R_2} I$$



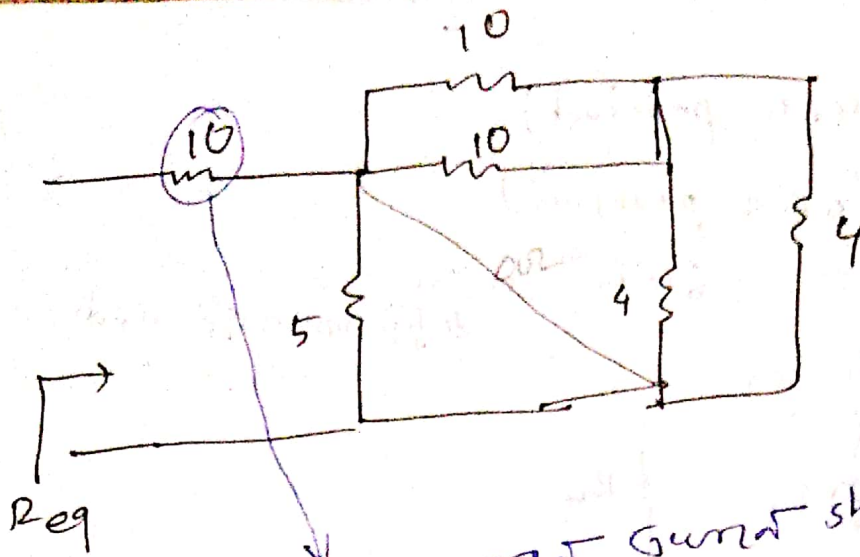

Ans: 10 Ω (short circuit)

ans 1


calculation also (ans),

$$10 \parallel 10 \Rightarrow 5 \Omega$$

$$4 \parallel 4 \Rightarrow 2 \Omega$$

5 Ω & 2 Ω are in series,


$$5 + 2 = 7 \Omega$$

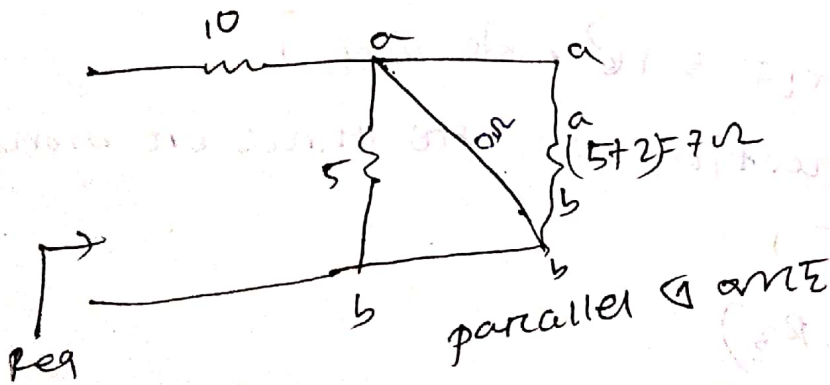

E-day (4th period)

C-day (5th period)

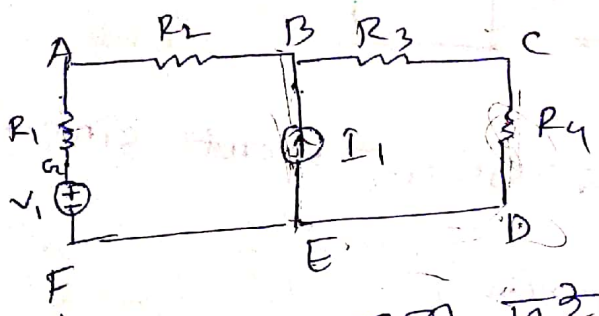From YouTube: (6 Feb 2020) definition of node



Node: दो वा दो से अधिक एक branch मिलने वाला जो node है

कुल node 5 है,

- A (R₁, R₂)
- B (R₂, I₁, R₃)
- C (R₃, R₄)
- E (V₁, I₁, R₄)
- G (R₁, V₁)

कुल 5 है node का

Junction: connection of three or more element का जो है

- B (R₂, I₁, R₃)
 - E (V₁, I₁, R₄)
- दो junction

Branches

कुल 4 दो junction का है

- BACFE
- BCDE
- BE

~~2~~ Branch
6 Branch

Loop

ABEFGA
BCDEB
ABCDEF A
font Loop




Mesh

ABEFGA
BCDEB
2 for Mesh



(2) D-day


28-08-19

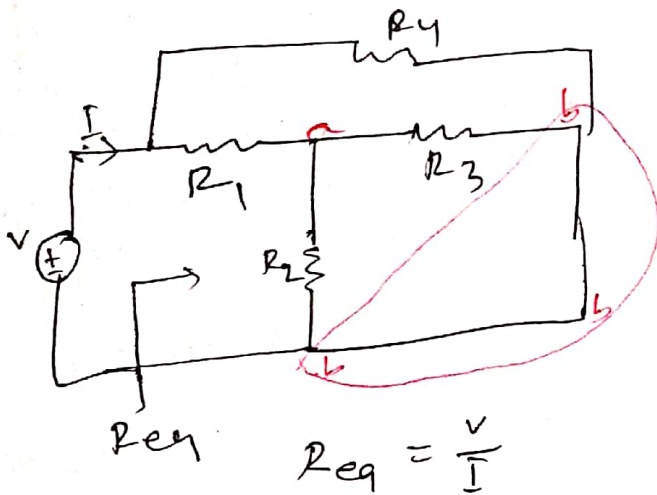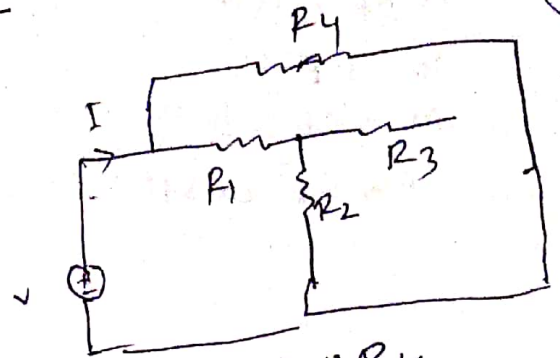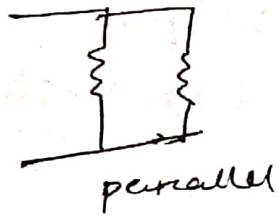

$(R_1 + R_2) \parallel R_4$
 R_3 (ground) first current
 into it 1 into open circuit
 R_2 and R_3 parallel
 R_1 and $(R_2 \parallel R_3)$ and

$R_{eq} = (R_1 + R_2 \parallel R_3) \parallel R_4$

open circuit current (no current)

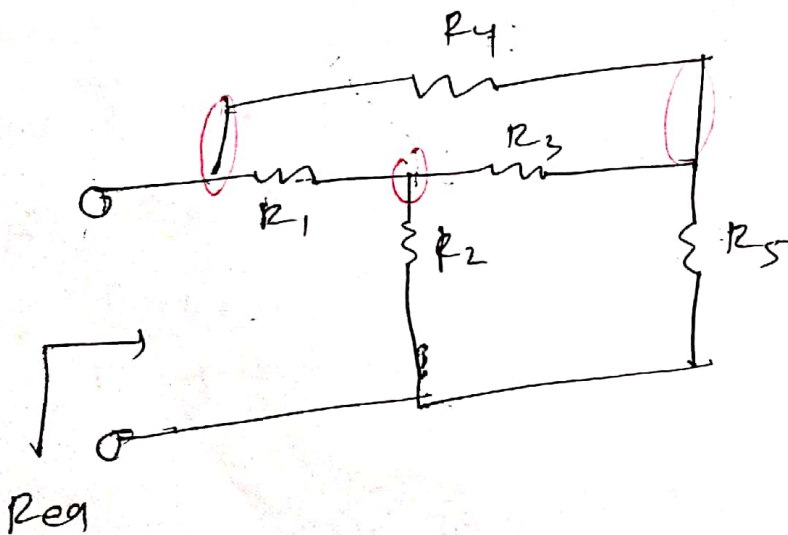


resistors are
 first of
 parallel &
 connect it

$R_1 R_4 R_3 - \Delta$
 $R_1 R_3 R_2 - \gamma$
 $R_2 R_3 R_5 - \Delta$
 $R_3 R_5 R_4 - \gamma$


resistors are parallel
 it means that
 into Y or (delta)
 and

Wye-connected

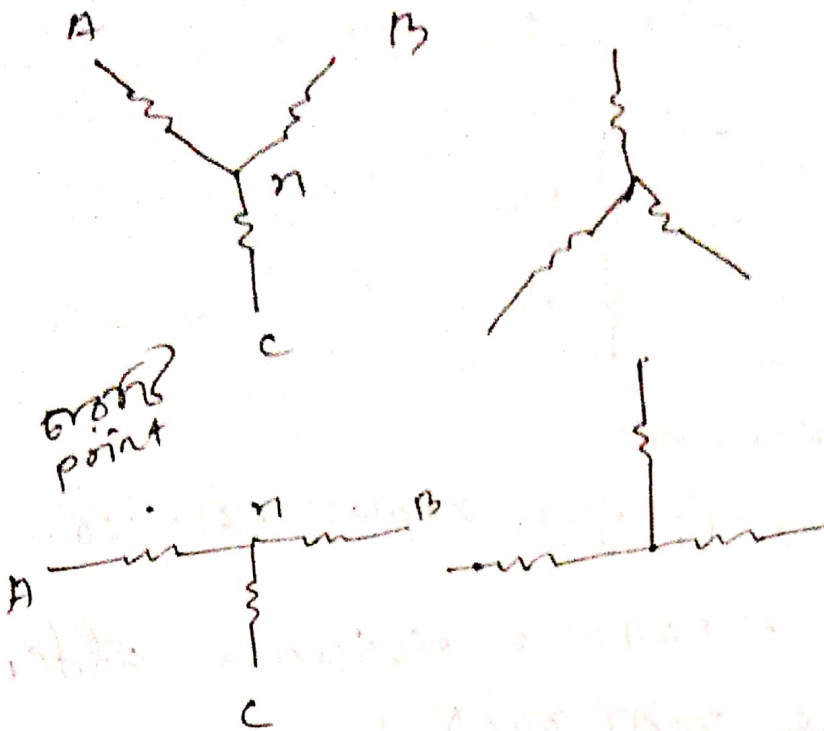



center point


Del-connected

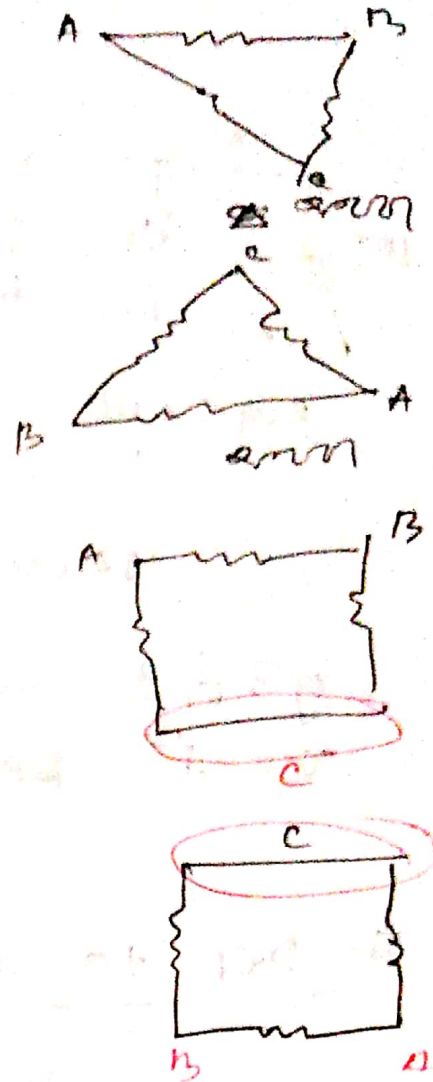

for resistance to the common point (n) is

II

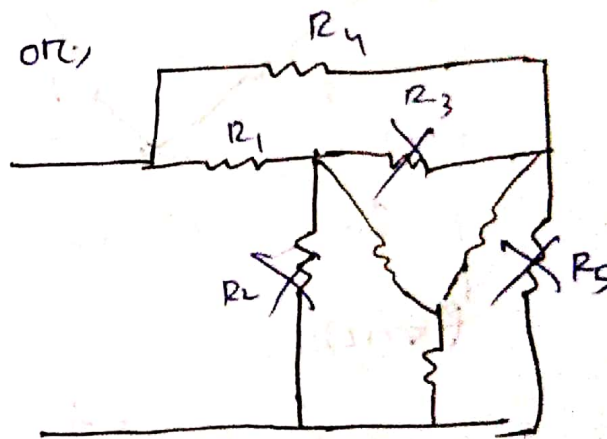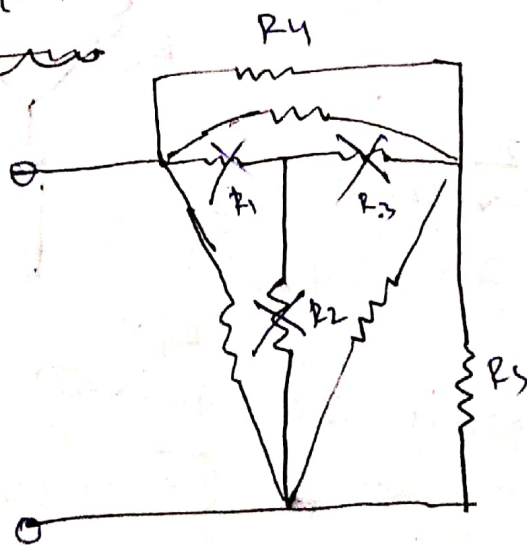


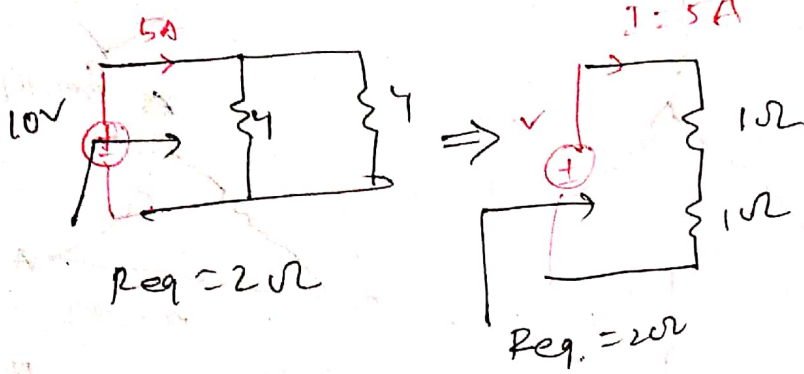

1 ओम का प्रतिरोध जोड़ें और 10V का प्रतिरोध बदलें


दोनों प्रतिरोधों का समान प्रतिरोध देना
 1 ओम का प्रतिरोध जोड़ें और 10V का प्रतिरोध बदलें

Δ to wye conversion:

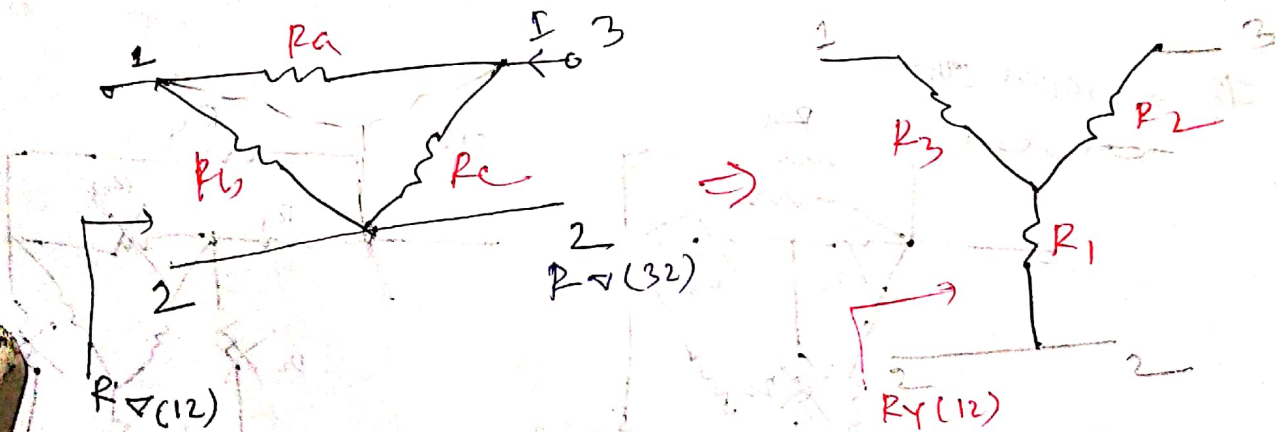

दोनों circuitों में equivalent resistance का ही replace करना

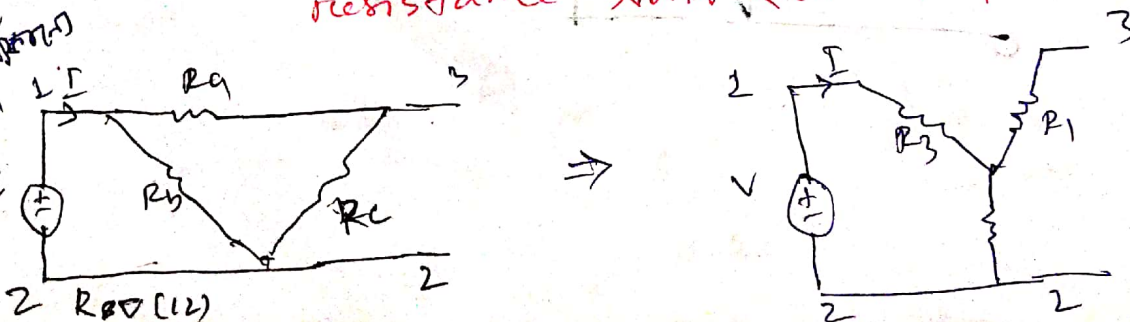10V का प्रतिरोध जोड़ें और 10V का प्रतिरोध बदलें



10V का प्रतिरोध जोड़ें और 10V का प्रतिरोध बदलें

$$R_{\Delta}(12) = R_b \parallel (R_a + R_c)$$

$$R_Y(12) = R_3 + R_1$$

$$\cancel{R_{\Delta}(12)} = R$$

$$R_Y(12) = R_{\Delta}(12)$$

$$\Rightarrow R_3 + R_1 = \frac{R_b(R_c + R_a)}{R_a + R_b + R_c} \quad \text{--- (i)}$$

now,

$$R_{\Delta}(32) = R_c \parallel (R_a + R_b)$$

$$R_Y(32) = R_1 + R_2$$

$$\therefore R_Y(32) = R_{\Delta}(32)$$

$$\Rightarrow R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} \quad \text{--- (ii)}$$

similarly,

$$R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} \quad \text{--- (iii)}$$

$$\text{(i)} + \text{(ii)} + \text{(iii)}$$

$$2(R_1 + R_2 + R_3) = \frac{2(R_a R_b + R_b R_c + R_c R_a)}{R_a + R_b + R_c}$$

$$\Rightarrow R_1 + R_2 + R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a + R_b + R_c} \quad \text{--- (iv)}$$

R1 to R2 to R3 to R4

$$(IV) - (III)$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

similarly,

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Wye to Del conversion - Homework

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

II

If, $R_a = R_b = R_c = R_{\Delta}$

$$R_1 = \frac{R_{\Delta}}{3}$$
$$= \frac{R_{\Delta}}{3}$$

$$R_2 = \frac{R_{\Delta}}{3} \quad R_3 = \frac{R_{\Delta}}{3}$$

$$\therefore R_1 = R_2 = R_3 = R_Y \text{ (Let)}$$

$$R_Y = \frac{R_\Delta}{3}$$

$$R_\Delta = 3 R_Y$$

3rd element was not applicable


practice problem (assignment)

2.14, 2.15

2.51, 2.56


31-08-19 (2)-E-Day

Kirchhoff's laws:

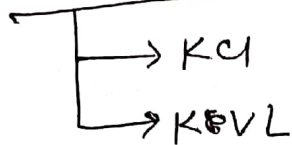

KVL

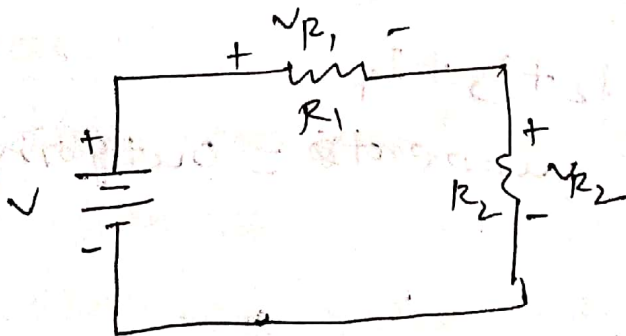
Kirchhoff's voltage law states that the algebraic sum of the voltages in a close path of a circuit is zero.



$$-V + V_{R1} + V_{R2} = 0$$

$$\Rightarrow V = V_{R1} + V_{R2}$$


supply voltage = voltage drop

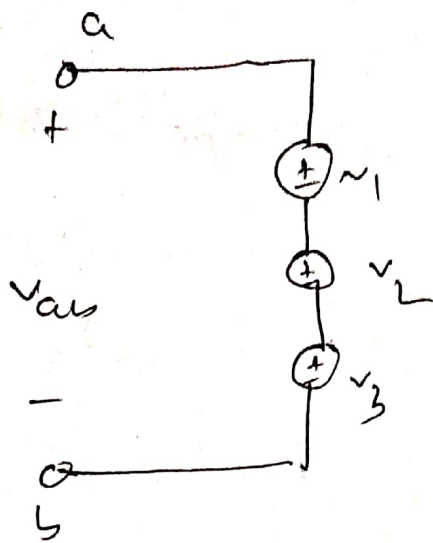

$$V_{ab} = V_1 + V_2 + V_3$$

$$-V_{ab} + V_1 + V_2 + V_3 = 0$$

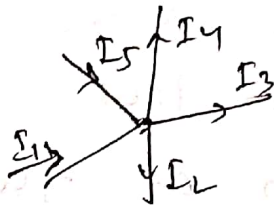
KCL: KCL states that the algebraic sum of the currents entering in a node or a closed boundary is equal to zero



$$I_1 + (-I_2) + (-I_3) + (-I_4) + I_5 = 0$$

$$\Rightarrow I_1 + I_5 = I_2 + I_3 + I_4$$

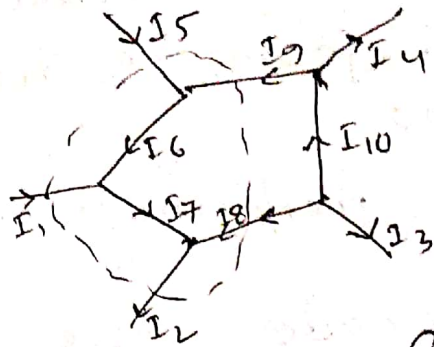\therefore Entering current = outgoing current



In the close boundary,

$$\begin{aligned}
 & I_1 + (-I_2) + I_8 + I_9 + I_5 \\
 \Rightarrow & (I_7 - I_6) - (I_7 + I_8) + I_8 + I_9 + (I_6 - I_9) \\
 = & I_7 - I_6 - I_7 - I_8 + I_8 + I_9 + I_6 - I_9 \\
 = & 0
 \end{aligned}$$

$$\begin{aligned}
 I_7 &= I_6 + I_9 \\
 I_5 &= I_6 - I_9 \\
 I_6 &= I_5 + I_9
 \end{aligned}$$

Methods of circuit Analysis:

① Nodal Analysis

② Mesh Analysis

① Nodal Analysis:

process:

- 1) First we need to determine the number of nodes in the circuit
- 2) Then we need to consider a node as a reference node

2) Generally we ~~can~~ consider the voltage of the reference node ~~is~~ ~~zero~~ equal to zero.

ground point (reference node) is

3) we need to denote the potential of each node with respect to reference node ~~and~~ except the reference node.

n nodes $(n-1)$ nodes

4) we need to apply KCL at each node.

5) Then we need to solve the expressions obtain from KVL KCL

~~to determine the~~ at each node to determine the potential of each node.

calculator use Σ solve equation solve

Interconnection ~~with~~ reference node



App KCL at node 2

$$2 + I_2 = I_3$$

$$\Rightarrow 2 + \frac{V_1 - V_2}{5} = \frac{V_2 - V_1}{2}$$


$$\Rightarrow \frac{10 + V_1 - V_2}{5} = \frac{V_2 - V_1}{2}$$

$$\Rightarrow 5V_2 - 5V_1 = 20 + 2V_1 - 2V_2$$

$$\Rightarrow 5V_2 + 2V_2 - 5V_1 - 2V_1 = 20$$

$$\Rightarrow 7V_2 - 7V_1 = 20$$

$$\Rightarrow 7V_1 - 7V_2 = -20$$

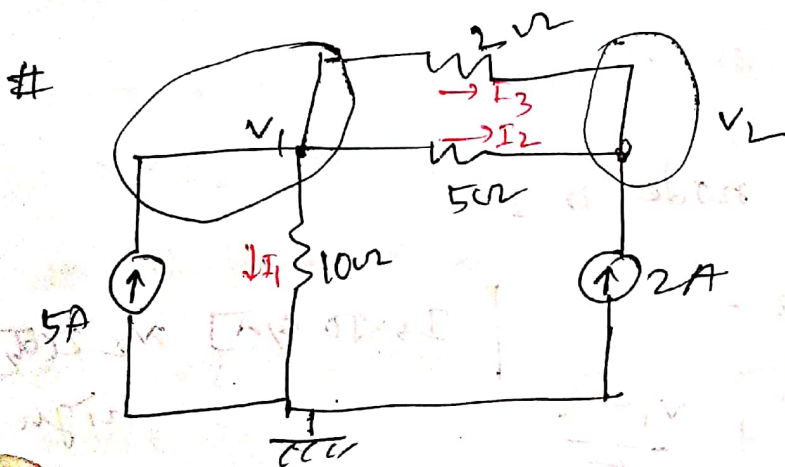

$$5 = I_3 + I_2 \quad I_1 + I_2 + I_3$$

$$\Rightarrow 5 = \frac{V_1 - 0}{10} + \frac{V_1 - V_2}{5} + \frac{V_2 - V_1}{2}$$

$$\Rightarrow 8V_1 - 7V_2 = 50$$

At node-2

$$2A + I_2 + I_3 = 0$$



$$\Rightarrow 2A + \frac{V_1 - V_2}{5} + \frac{V_1 - V_2}{2} = 0$$

$$\Rightarrow \frac{20 + 2(V_1 - V_2) + 5(V_1 - V_2)}{10} = 0$$

$$\Rightarrow 20 + 2V_1 - 2V_2 + 5V_1 - 5V_2 = 0$$

$$\Rightarrow 7V_1 - 7V_2 = -20$$

(3) D-Day
7-9-19

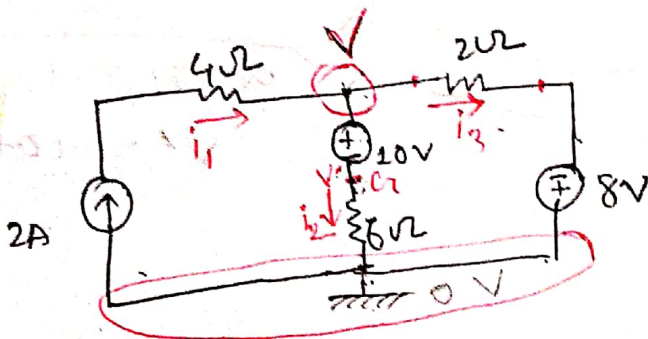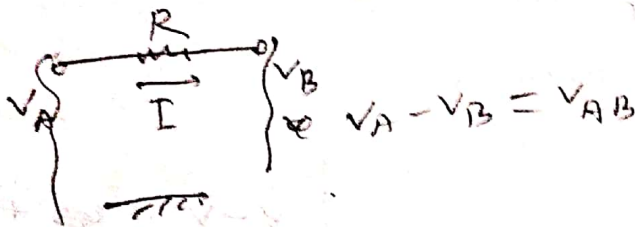

जिसे व. तारा सर्किट
connection (26 node)
देखा जाता

यदि किन्हीं दो नोड्स का मतलब होगा कि
जिसे व. तारा सर्किट Interconnection point (26
node) होगा।

v point current ground to potential.

KCL equation

$$i_1 = i_2 + i_3$$

$$i_1 = 2$$

$$i_2 = \frac{-10 + v}{6} - 0$$

$$i_3 = \frac{v - (-8)}{2} - 0$$

$$= \frac{v + 8}{2}$$

$$i_1 = i_2 + i_3$$

$$\therefore 2 = \frac{-10 + v}{6} + \frac{v + 8}{2}$$

वoltage

i_2, i_3 voltage

drop across all resistors

$$i_2 = \frac{-10 + v}{6}$$


$$i_3 = \frac{v + 8}{2}$$

Independent source

i_1 2A current supply

$$i_1 = 2$$

वoltage point to potential = -10

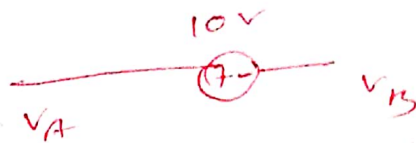

$$V_A - V_B = 10$$

$$V_B - V_A = -10$$


V' = voltage

$$V - V' = +10$$

$$\Rightarrow V' = V - 10$$

अतः,

$$V' = -10 + v$$

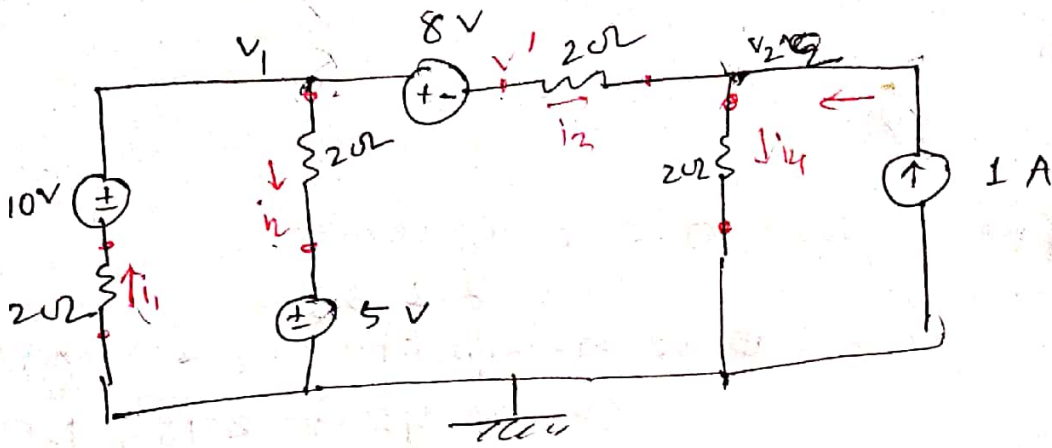

$$V_1 - V' = 10$$

$$\Rightarrow V' = V_1 - 10$$

$i_1 = i_2 + i_3$
Applying KCL at node 1,

i_3 is 2A (2Ω resistor) + 8V source + 2Ω resistor. All are on the same side.

$$i_1 = i_2 + i_3$$

$$\Rightarrow \frac{-10 - V_1}{2} = \frac{(V_1 - V' + 5) - 0}{2} + \frac{(8 - V_2) - 0}{2}$$

$$\Rightarrow \frac{0 - (-10 + V_1)}{2} = \frac{V_1 - 5}{2} + \frac{(-8 + V_1) - V_2}{2}$$

i_3 is 2A (2Ω resistor) + 8V source + 2Ω resistor. All are on the same side.

Applying KCL at node 2

$$1 + i_3 = i_4$$

$$\Rightarrow 1 + \frac{(-8 + V_1) - V_2}{2} = \frac{V_2 - 0}{2}$$

$$V_1 - V' = 8$$

$$\Rightarrow V' = V_1 - 8$$

$$V_1 = -8 + V_1$$

chapter - 3

example
3.1

assignment - practice problem -

3.1, 3.2, 3.3


অথবা অনুশীলনী থেকে যে
কোনো দুইটি সঠিক problem

অনুশীলনী
থেকে
কোনো
দুইটি
সঠিক
problem



3.17

(3)E - Jay
8-9-19

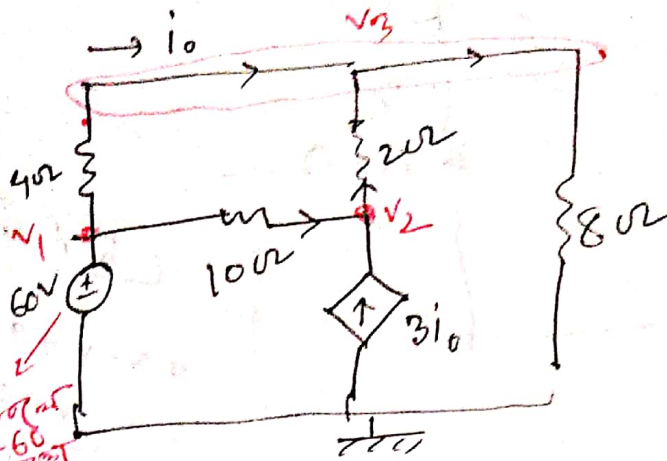

node-1
 $V_1 = 60 \text{ V}$

node-2
$$V_1 = \frac{V_2}{10} + 3i_0 = \frac{V_2 - V_3}{2}$$

node-3


$$\frac{V_1 - V_3}{4} + \frac{V_2 - V_3}{2} = \frac{V_3 - 0}{8}$$

super node

मदि पूर्ण node एक मात्रा खूब मात्रा
voltage source एक टाइटने पूर्ण
node एक एकमात्रे एकमात्रे node
consider करा शुभ ।

अथवा series 0 resistance एकमात्र

super node का एक न ।

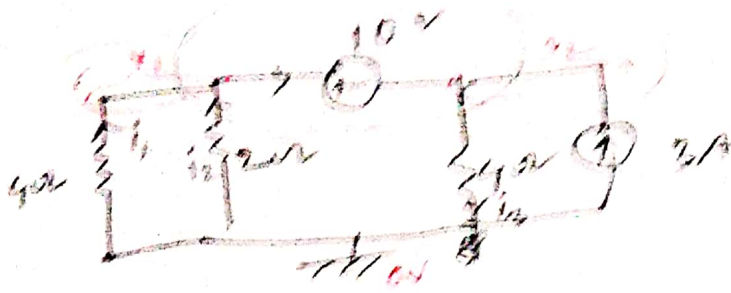


super node method
 directly use
 apply KCL
 boundary of
 node
 (KVL)
 solve

$$i_1 + i_2 + 3 = i_3$$

$$\Rightarrow \frac{0-v_1}{4} + \frac{0-v_1}{2} + 3 = \frac{v_2-0}{4} \quad \text{--- (1)}$$

$$v_1 - v_2 = 10 \quad \text{--- (2)}$$

#

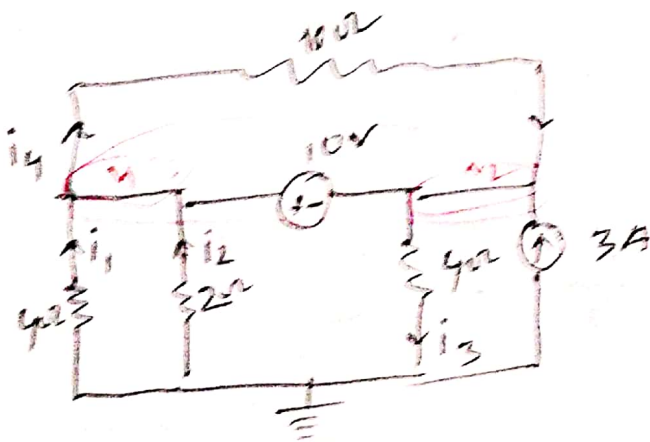


i_4 (current)
 through 4Ω

for super
 node (KCL)
 for super
 node (KVL)

$$i_1 + i_2 + 3 + i_4 = i_3 + i_4$$

$$\Rightarrow i_1 + i_2 + 3 = i_3$$

3.20

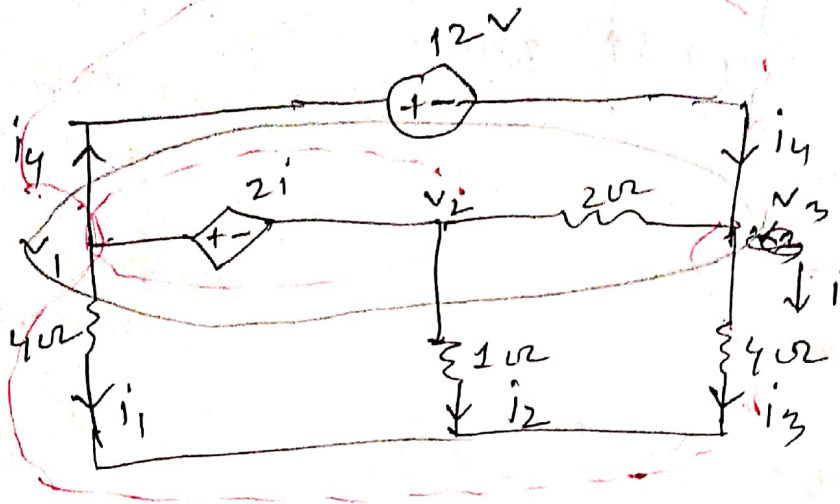

$$i_1 + i_2 + i_3 + i_4 = i_4$$


$$\Rightarrow i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{v_1}{4} + \frac{v_2}{1} + \frac{v_3}{4} = 0 \quad \text{--- (I)}$$

$$v_1 - v_3 = 12 \quad \text{--- (II)}$$

$$v_1 - v_2 = 2i$$
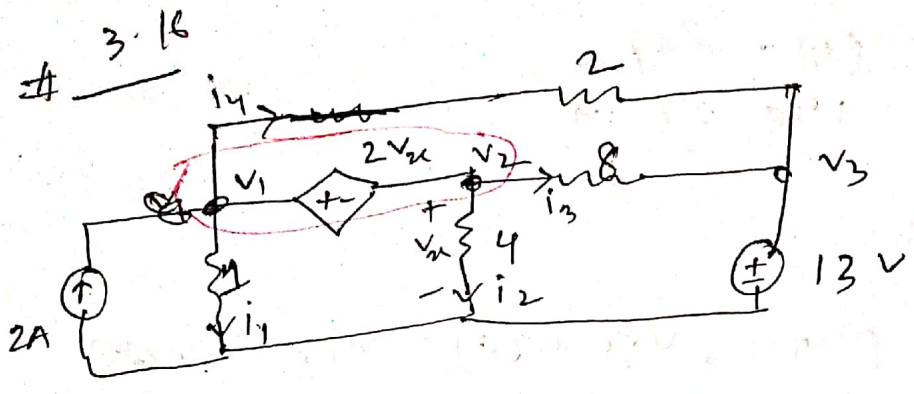
$$\Rightarrow \frac{v_1}{4} - v_2 = 2 \cdot \frac{v_3}{4} \quad \text{--- (III)}$$



বিভিন্ন বান্ডে
করে

৭ বান্ডে নড়ে
এক শর্ত দুই
না। তবে এক
neglect করা
করো না


$$2A = i_1 + i_2 + i_3 + i_4$$

$$\Rightarrow 2A = \frac{v_1 - 0}{1} + \frac{v_2 - 0}{4} + \frac{v_2 - v_3}{8} + \frac{v_1 - v_3}{2} \quad | \quad v_n = v_2$$

$$v_1 - v_2 = 2V_{2x} \quad \text{--- (I)}$$

$$v_3 = 13 \quad \text{--- (III)}$$

যদি দুই node এক করে

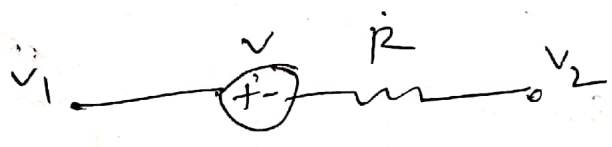

$$I = \frac{-v + v_1 - v_2}{R} \quad \text{এইটিই super node কমা করে}$$




$I = ?$
 The current I through the resistor is

(4) c-day
14-09-19

Mesh Analysis

Mesh is a closed path, where no other closed path exists.
 Mesh 1 is a loop.
 Mesh 2 is a loop.

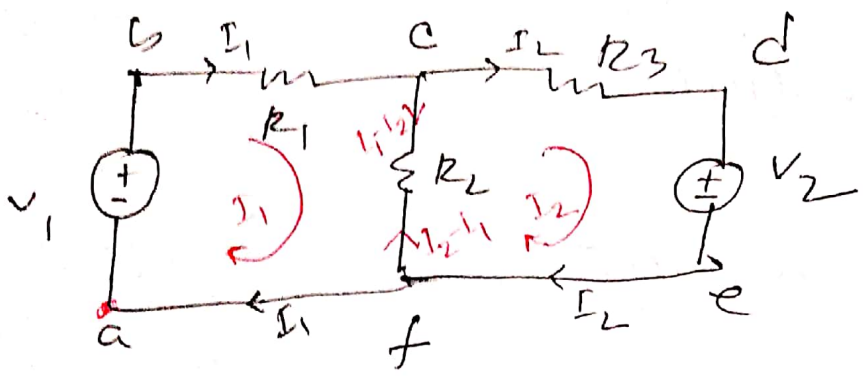Mesh is a closed path of a circuit where no other closed path exist.



I_2 mesh current direction
 I_1 mesh current direction
 Net current $(I_1 - I_2)$
 Net current $(I_2 - I_1)$

- ab cfa → Mesh 1
- cd efc → Mesh 2
- ab c d e f a → Mesh 3

Steps of Mesh Analysis:

1. we need to determine the number of meshes in a circuit.
2. Then we need to consider the direction of current in each mesh if it is not given.

3. After this, KVL is applied in each mesh

Then we need to solve the expressions obtained from KVL in each mesh.

node to voltage assignment
mesh to current assignment


Mesh-1:

$$-V_1 + I_1 R_1 + (I_1 - I_2) R_2$$

Mesh-2:

$$I_2 R_3 + V_2 + (I_2 - I_1) R_2 = 0$$
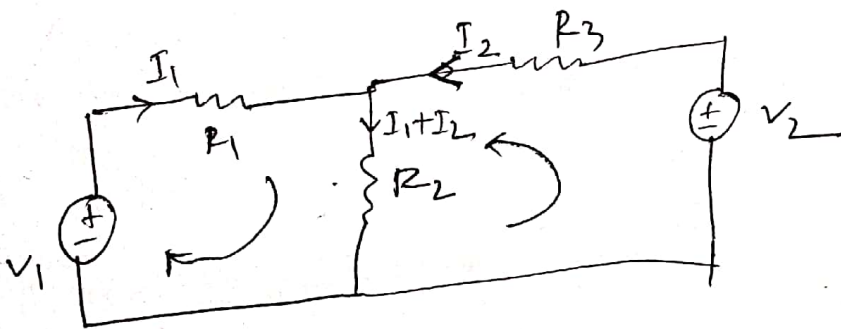
$$\Rightarrow I_2 R_3 + V_2 - (I_1 - I_2) R_2 = 0$$




Mesh-1:

$$-V_1 + I_1 R_1 + (I_1 + I_2) R_2 = 0$$

Mesh-2:

$$I_2 R_3 + V_2$$

$$-V_2 + I_2 R_3 + (I_1 + I_2) R_2 = 0$$

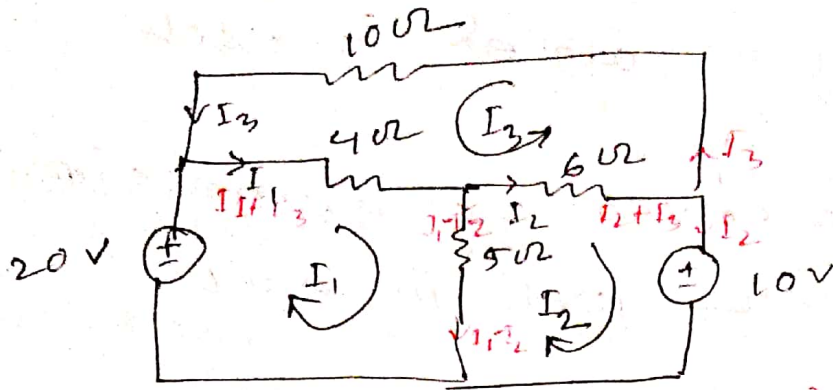

Mesh-1 (घड़ना घड़ना)

$$-20 + (I_1 + I_3)4 + (I_1 - I_2)5 = 0$$

Mesh-2 (घड़ना घड़ना)


$$(I_2 + I_3)6 + 10 + (I_2 - I_1)5 = 0$$

Mesh-3 (घड़ना घड़ना)

$$10I_3 + (I_1 + I_3)4 + (I_2 + I_3)6 = 0$$



#

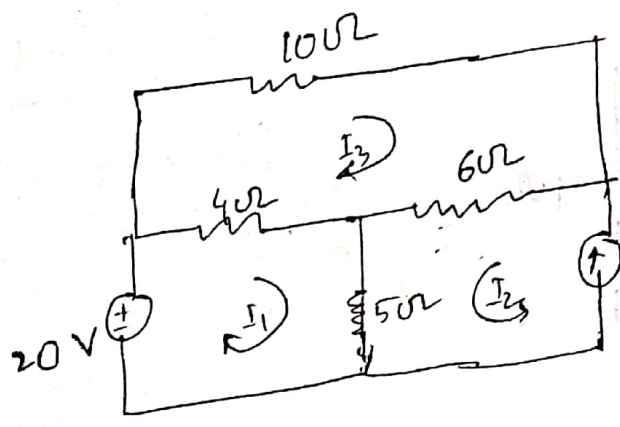

2A voltage source को 2A का current source में बदलें।
 2A current source को 4V के voltage source में बदलें।

$$I_2 = 2A$$

I_2 का 2A का current source में बदलें।
 2A current source को 4V के voltage source में बदलें।
 4V voltage source को 2A का current source में बदलें।

Mesh-1:

$$-20 + (I_1 - I_3)4 + (I_1 + 2)5 = 0$$


Mesh-2:

~~$$(2 + I_3)6 + (I_1 + 2)5 = 0$$~~

Mesh-3:

$$10I_3 + (2 + I_3)6 + (I_3 - I_1)4 = 0$$

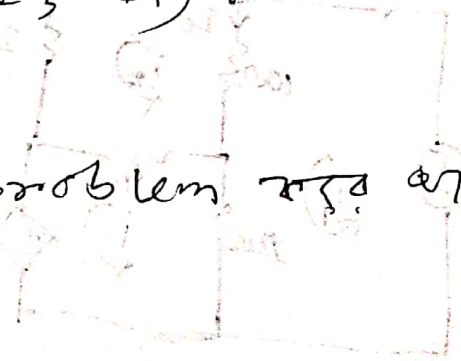
mesh Analysis का प्रश्न problem का answer है।



MESH-1:

$$0 = (i_1 - i_3)4 + (i_1 - i_2)10 + i_1 \cdot 20$$
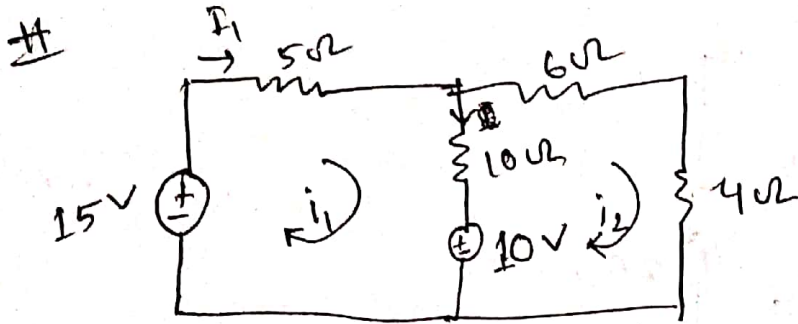
$$0 = 4i_1 - 4i_3 + 10i_1 - 10i_2 + 20i_1$$



Mesh-1


$$-15 + 5I_1 + 10(I_1 - I_2) + 10 = 0$$

Mesh-2:

$$-10 + 10(I_2 - I_1) + 6I_2 + 4I_2 = 0$$

$$I_1 = 1 \text{ A}$$

$$I_2 = 1$$

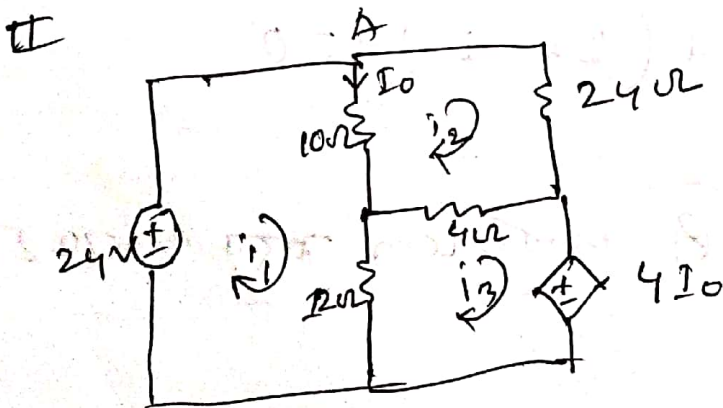

Mesh-1:

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$$

$$\Rightarrow 11i_1 - 5i_2 - 6i_3 = 12$$

Mesh-2:

$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$\Rightarrow -5i_1 + 19i_2 - 2i_3 = 0$$

Mesh-3:

$$4I_0 + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

But at node A, $I_0 = i_1 - i_2$, so that,

$$4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$\Rightarrow -i_1 - i_2 + 2i_3 = 0$$


$$\therefore i_1 = 2.25A$$

$$i_2 = 0.75A$$

$$i_3 = 1.5A$$

(4) D-Day

15-09-19

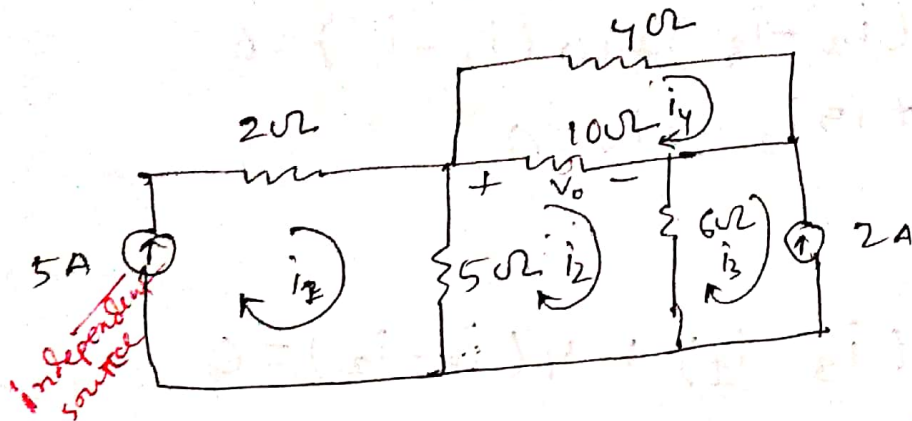

Mesh-1

$$i_1 = 5A$$

Mesh-1:

$$5(i_2 - i_1) + 10(i_2 - i_4) + 6(i_2 - i_3) = 0$$

$$i_3 = -2A$$

Mesh-2:

$$4i_4 + 10(i_4 - i_2) = 0$$

2A Branch (current source zero)
(KVL apply for zero A)

From mesh-1:

$$\begin{aligned} 5i_2 - 5i_1 + 10i_2 - 10i_4 + 6i_2 - 6i_3 &= 0 \\ \Rightarrow 5i_2 - 25 + 10i_2 - 10i_4 + 6i_2 + 12 &= 0 \\ \Rightarrow 21i_2 - 10i_4 + 3 &= 0 \end{aligned}$$

from mesh 2

$$\text{Eq} \quad -10i_2 + 14i_4 = 0$$

$$\therefore i_2 = 0.93$$


$$i_4 = 0.67$$

$$V_0 = 10(i_2 - i_4)$$

$$= 2.68 \text{ V}$$

super mesh:

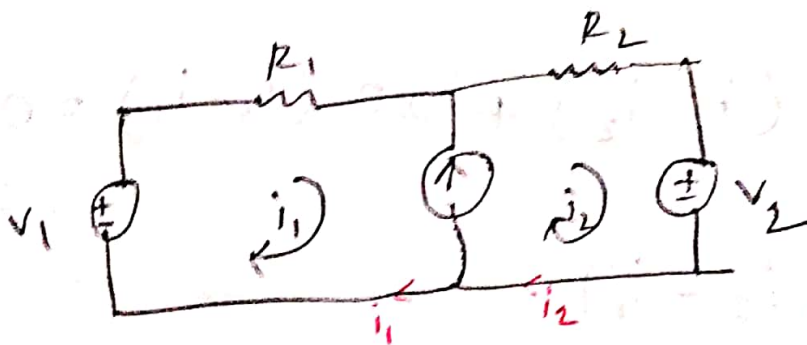
यदि दो mesh को common branch में
 कोई current source हो तो हम दो mesh
 को एक ही super mesh consider
 करेंगे।



$$-V_1 + i_1 R_1 + i_2 R_2 + V_2 = 0 \quad \text{--- (1)}$$

$$i_2 - i_1 = I$$

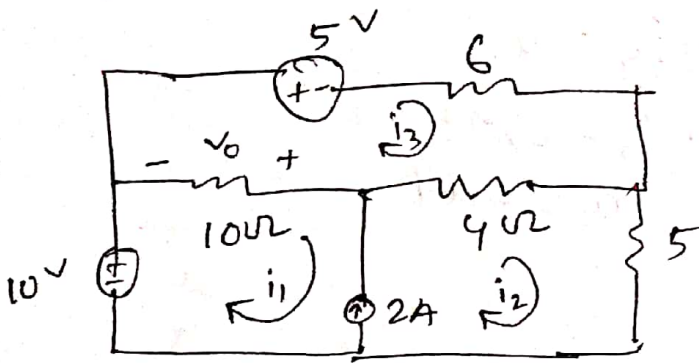Current source की तरफ
 flow रहे, अगर i_2 के
 साथ i_1 के i_2 के
 i_1 की तरफ i_2 के



$$V_0 = ?$$

* super mesh,

$$-10 + 10(i_1 - i_3) + 4(i_2 - i_3) + 5i_2 = 0$$


$$i_2 - i_1 = 2$$

Mesh-2:

$$5 + 6i_3 + 4(i_3 - i_2) + 10(i_3 - i_1) = 0$$

$$V_0 = 10(i_3 - i_1)$$



CT syllabus — Mesh, node analysis

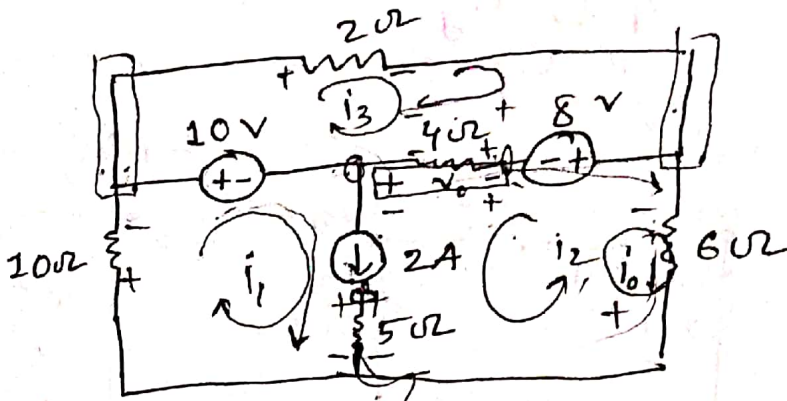

$V_o = ?$
 $i_o = ?$

Node mesh

① In de-branch current

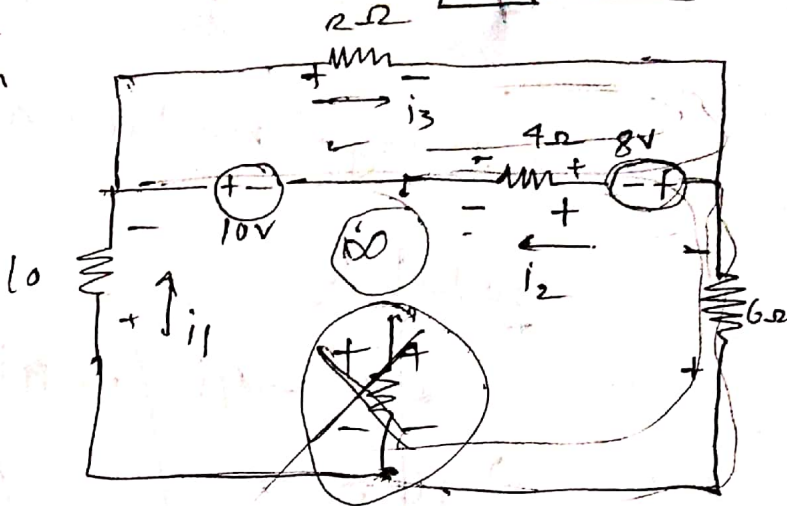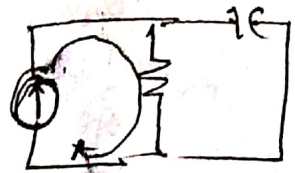

$i_1 =$
 $i_2 = +$
 $i_3 = -$


$+10 - (i_2 + i_3) \cdot 4 - 8 - (i_2 + i_3) \cdot 6 = 0$
 $10 i_1 = 0$

$+2i_3 + 8 + (i_2 + i_3) \cdot 4 - 10 = 0$

$i_1 + i_2 = 2$

current i_0 (20V)
 2Ω open circuit
 voltage i_0 (3V)
 2A short circuit

4(E)-day
16-09-19

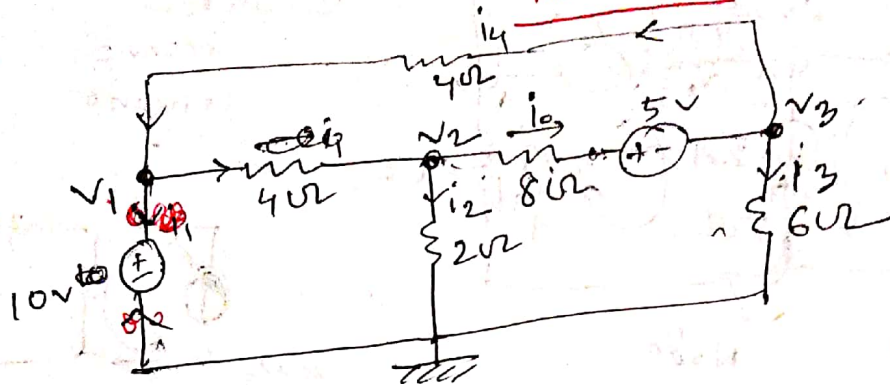


$5 + v_3$

$$\begin{aligned} v_1 - v_3 &= 5 \\ v_1 &= 5 + v_3 \\ v_2 - (5 + v_3) & \end{aligned}$$

using nodal Analysis find i_0

node-1:

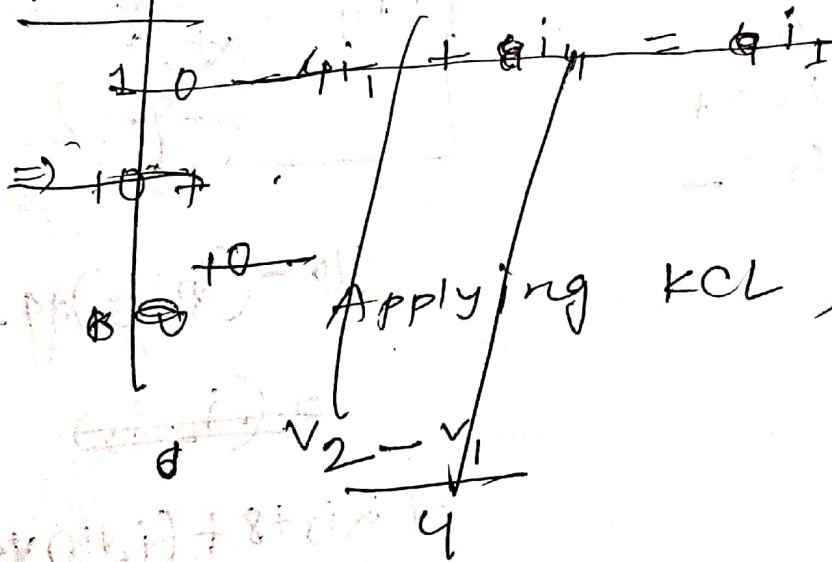

$v_2 - 5 = v_3$


node-1:

$$v_1 = 10V$$

node-2

$$\frac{v_2 - (5 + v_3)}{8} + \frac{v_2}{2} = \frac{v_1 - v_2}{4}$$
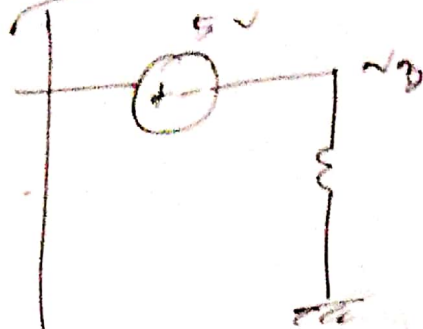
$$\Rightarrow 7v_2 - v_3 = 25 \quad \text{--- (1)}$$



5 + v₃, 2Ω, ground

node-3

$$v_2 - (5 + v_3) = \frac{v_3}{6} + \frac{v_3 - v_1}{4}$$

$$\Rightarrow 3v_2 - 13v_3 = -45$$


$$I_0 = \frac{v_2 - (5 + v_3)}{8}$$

$$v_2 = 4.2$$

$$v_3 = 4.43$$

$$\therefore I_0 = \frac{4.2 - 5 - 4.43}{8} = -0.65375 \text{ A}$$

Mesh

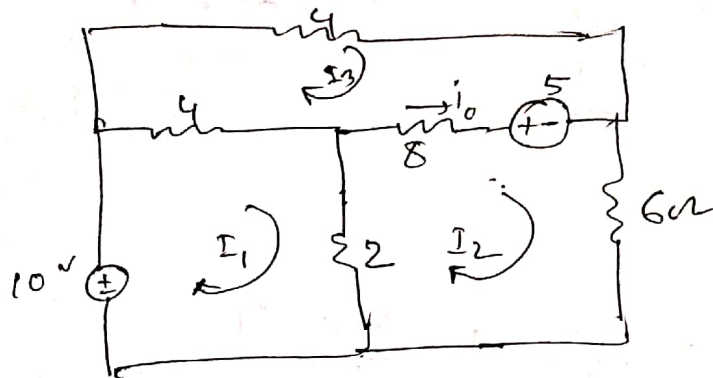

Mesh-1

$$-10 + 4(I_1 - I_3) + 2(I_1 - I_2) = 0$$
$$\Rightarrow 6I_1 - 2I_2 - 4I_3 = 10 \quad \text{--- (1)}$$

Mesh-2

$$8I_2 + 5 + 6I_2$$
$$8(I_2 - I_3) + 5 + 6I_2 + 2(I_2 - I_1) = 0$$
$$\Rightarrow -2I_1 + 16I_2 - 8I_3 = -5 \quad \text{--- (2)}$$

Mesh-3

$$4I_3 - 5 + 8(I_3 - I_2) + 4(I_3 - I_1) = 0$$
$$\Rightarrow -4I_1 - 8I_2 + 16I_3 = 5$$

$$i_0 = \cancel{8(I_2 - I_3)}$$

$$I_1 = 2.840$$

$$I_2 = 0.7938$$

$$I_3 = 1.392$$

$$\therefore i_0 = 8(I_2 - I_3)$$

$$= 8(0.79 - 1.39)$$

$$= -5.2$$

$$i_0 = (I_2 - I_3)$$

$$= 0.739 - 1.392$$

$$= -0.653$$



$$\left[\begin{matrix} (10 \cos(10t + 20)) + (10 \cos(10t + 20)) \\ (10 \cos(10t + 20)) + (10 \cos(10t + 20)) \end{matrix} \right]$$