

**EEE 1241**  
**Basic Electrical Engineering**


**Full Marks: 72**

**Time: 3 Hours**

- N.B.:-**
- (i) Answer any **SIX** questions, taking **THREE** from each section.
  - (ii) Figure in the margin indicate full marks.
  - (iii) Use separate answer script for each section.


**SECTION-A**

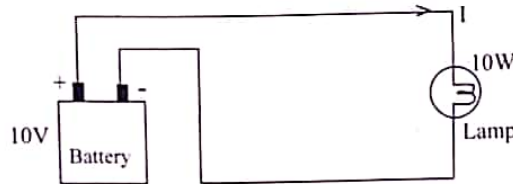- Q.1 (a) Define voltage source and current source. Also classify the dependent and independent sources with symbols. 4.0
- (b) Find out the current through the following circuit. 4.0




- (c) Prove that the source voltage is divided among the resistors is directly proportional to their resistances. 4.0

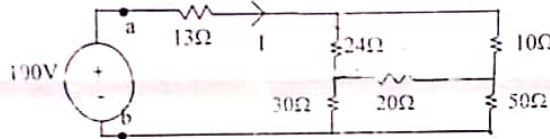
- Q.2 (a) For the bridge network in the figure shown below, find  $R_{ab}$  and  $I$ . 5.0



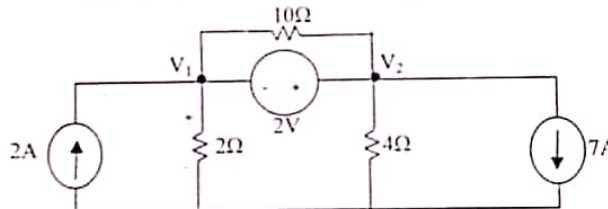
- (b) Define supernode. Write down the steps to determine the node voltages. 3.0
- (c) For the circuit shown below, find out the node voltages. 4.0



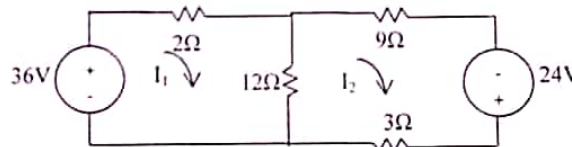- Q.3 (a) Calculate the mesh currents  $I_1$  and  $I_2$  for the following circuit shown below. 4.0



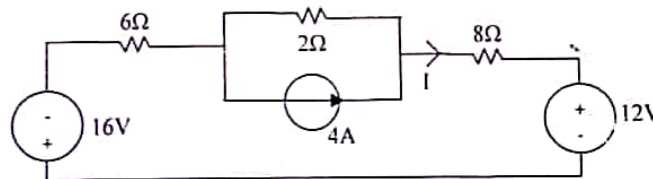- (b) State and explain the superposition theorem. 3.0
- (c) Find out the current  $I$  for the circuit shown below. 5.0




- Q.4 (a) For the following pair of sinusoids, determine which one leads and by how much. 4.0

- (i)  $v(t) = 10 \cos(4t - 60^\circ)$  and  $i(t) = 4 \sin(4t + 60^\circ)$
- (ii)  $v_1(t) = 4 \cos(377 + 10^\circ)$  and  $v_2(t) = -20 \cos 377t$


- (b) Define phasor. Find the phasors corresponding to the following signals. 4.0  
 (i)  $v(t) = 21 \cos(4t - 15^\circ) V$   
 (ii)  $i(t) = -8 \sin(10t + 70^\circ) mA$   
 (iii)  $v(t) = 120 \sin(10t - 50^\circ) V$   
 (c) For a pure capacitor and inductor prove that voltage and current are  $90^\circ$  out of phase. 4.0

SECTION-B

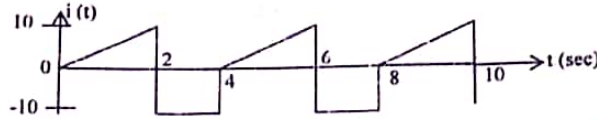
- Q.5 (a) Define RMS value. Determine the rms value of the current waveform shown in figure below. 6.0  
 If the current is passed through a  $2-\Omega$  resistor, find the average power absorbed by the resistor.



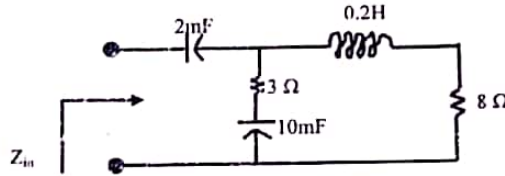
- (b) Find the input impedance of the circuit shown below. Assume that the circuit operates at  $\omega = 50 \text{ rad/s}$ . 3.0



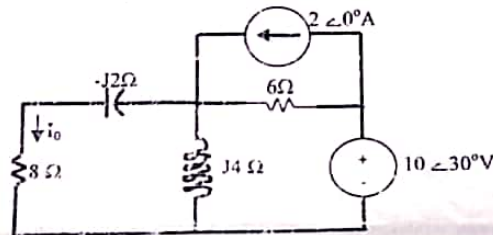- (c) Find  $I_0$  for the circuit shown in figure below using mesh analysis. 3.0




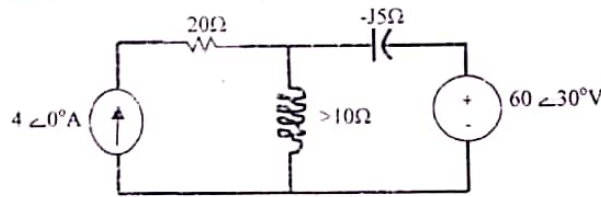- Q.6 (a) Determine the power generated by each source and the average power absorbed by each passive element in the circuit shown in figure below. 6.0



- (b) When connected to a 230-V (rms) 50-Hz power line, a load absorbs 4 kW at a lagging power factor of 0.8. Find the reactive power of the system. 2.0  
 (c) Define phase sequence. Write down the condition of three phase balanced and unbalanced system. 4.0

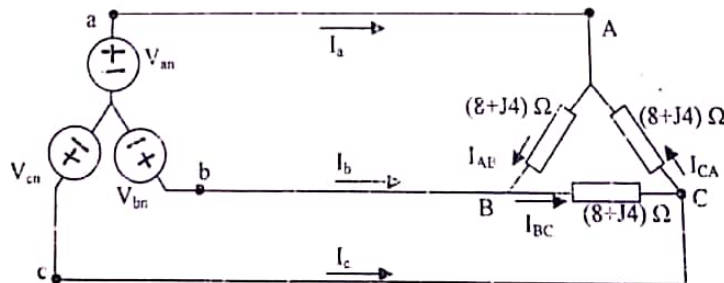- Q.7 (a) Mention the possible connections of the three phase source and the three phase load 2.0  
 (b) Derive the relationship between phase voltages and line voltages, phase currents and line currents for a three phase Y-Y system. Assume positive phase sequence. 4.0  
 (c) A balanced abc-sequence Y-connected source with  $V_{an} = 100 \angle 10^\circ V$  is connected to a  $\Delta$ -connected load  $(8 + j4) \Omega$  /phase. Calculate (i) phase voltages (ii) line voltages (iii) phase currents and (iv) line currents. The circuit is shown in Figure below. 6.0



- Q.8(a) Explain an operating principle of a half wave and full wave rectifier circuit with a suitable circuit diagram and output wave shape. 4.0  
 (b) Define generator, motor and transformer. Classify D.C. generator. 4.0  
 (c) Explain how voltage is induced across a conductor. 4.0


Full marks: 72

Time: 3 Hours


- N.B.:-**
- (i) Answer any SIX questions, taking THREE from each section.
  - (ii) Figures in the margin indicate full marks.
  - (iii) Use separate answer script for each section.
  - (iv) Assume reasonable value for any data missing.

**SECTION-A**

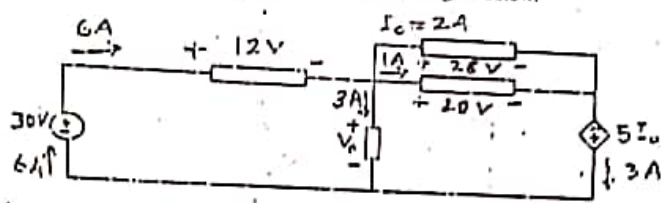
- Q.1 (a) Define active elements and passive elements. Classify ideal dependent source with appropriate symbols. 2.00  
 (b) Compute the power absorbed or supplied by each component of the circuit in figure below. 4.00



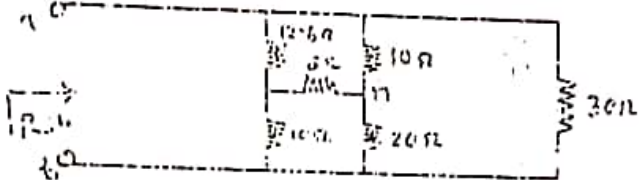
- (c) Show that if a voltage divider has  $N$  resistors ( $R_1, R_2, \dots, R_n$ ) in series with the source voltage  $v$ , the  $n$ th resistor ( $R_n$ ) will have a voltage drop of  $v_n = \frac{R_n}{R_1 + R_2 + \dots + R_n} v$ . 4.00  
 (d) Define the following terms: (i) Branch (ii) Node (iii) Loop (iv) Short circuit. 2.00
- Q.2 (a) State and explain KCL and KVL with examples. 3.00  
 (b) Obtain the equivalent resistance  $R_{ab}$  for the circuit in figure below. 5.00



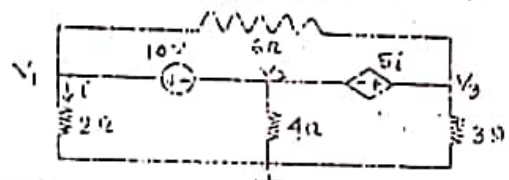
- (c) Find  $v_1$ ,  $v_2$ , and  $v_3$  in the circuit in figure below using nodal analysis. 4.00



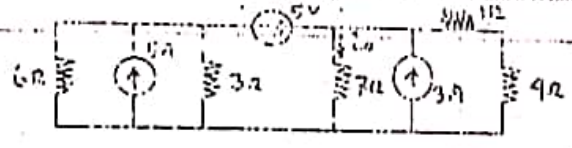- Q.3 (a) State and explain superposition theorem. 7.00  
 (b) Find  $I$  in the circuit of figure below using source transformation technique. 4.00




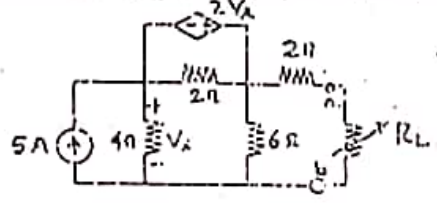- (c) Find the value of  $R_L$  for maximum power transfer in the circuit of the figure below. Find the maximum power. 4.00




- (d) State maximum power transfer theorem. 2.00

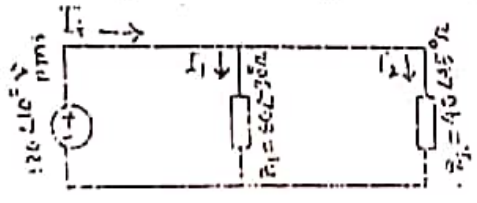- Q.4 (a) Define the following terms: (i) apparent power (ii) power factor angle (iii) complex power (iv) reactive power. 2.00  
 (b) In the circuit of the figure below, calculate (i) apparent power, (ii) real power (iii) reactive power (iv) power factor. 4.00



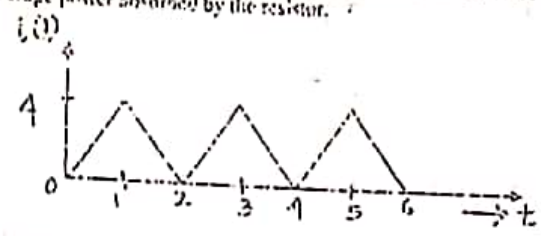
- (c) Find the rms value of the current waveform of figure below. If the current flows through a  $9\text{-}\Omega$  resistor, calculate the average power absorbed by the resistor.




- (d) Define power triangle. 1.00

SECTION-B

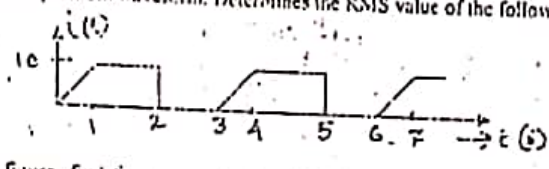- Q.5(a) Define RMS value of a periodic waveform. Determine the RMS value of the following waveform. 5.00




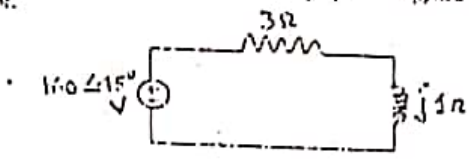- (b) For the following figure, find the average power supplied by source and power absorbed by inductor and resistor. 3.00



- (c) Prove that, the line current is  $\sqrt{3}$  times the magnitude  $I_p$  of the phase current for  $\Delta$ -connected load 4.00
- Q.6(a) Write the advantages of three phase system. Determine the relation between line currents and phase currents of a three phase  $\Delta$ -connected system. 4.00
- (b) Prove that, the instantaneous power of a balanced 3-phase system is constant. 4.00
- (c) A positive sequence, balanced  $\Delta$ -connected source supplies a balanced  $\Delta$ -connected load. If the impedance per phase of the load is  $18 + j12\Omega$  and  $I_L = 10\sqrt{2}\angle 15^\circ\text{A}$ , find line currents and line voltages. 4.00

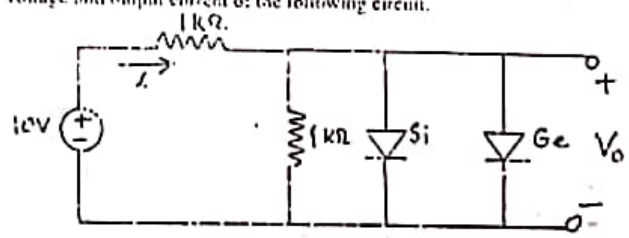- Q.7(a) Define diodes. Describe the importance of diodes. 3.00
- (b) Explain the operation of a full wave bridge rectifier circuit. Also derive expression of output voltage. 5.00
- (c) Determine the output voltage and output current of the following circuit. 4.00



- Q.8(a) Explain the no load magnetization curve of a DC generator. 4.00
- (b) The voltage induced in a DC generator is 220 V when the armature rotates at 1100 r/min. What will the voltage be if the speed is increased to 1200 r/min? 4.00
- (c) Explain the operating principle of a DC motor. 4.00

....

**EEE 1241**  
 Basic Electrical Engineering

Full marks: 72


Time: 3 Hours

- N.B.:-**
- (i) Answer any SIX questions, taking THREE from each section.
  - (ii) Figures in the margin indicate full marks.
  - (iii) Use separate answer script for each section.
  - (iv) Assume reasonable value for any data missing.

**SECTION-A**


- Q.1(a)** Define (i) active circuit element, (ii) passive circuit element, (iii) dependent source.  
**(b)** Find  $R_{eq}$  at terminals  $a$  and  $b$  for the network shown in figure below.

3.00  
4.00

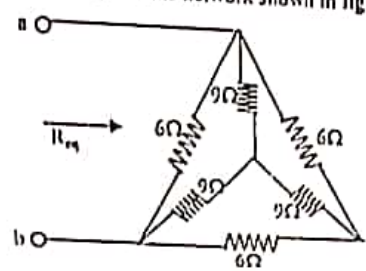


- (c)** What do you mean by a linear circuit? Write nodal equations for the network shown in figure below.

5.00

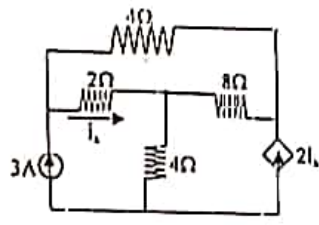


- Q.2(a)** Write down the properties of a super mesh. Find  $i_1$ ,  $i_2$ , and  $i_3$  shown in figure below using mesh analysis.

5.00

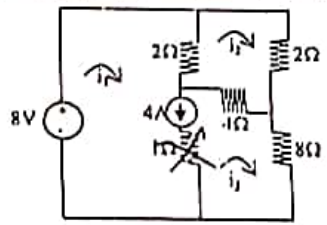


- (b)** State and explain Thevenin's theorem.  
**(c)** Find  $V_0$  in the circuit of figure using superposition theorem.

3.00  
4.00

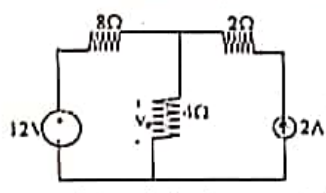


- Q.3(a)** Convert the voltage source shown in figure below into an equivalent current source.

2.00

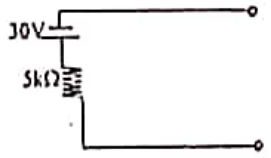


- (b)** Find the value of  $R_L$  for maximum power transfer in the circuit shown in figure. Find the maximum power.


4.00

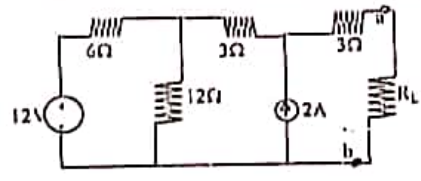

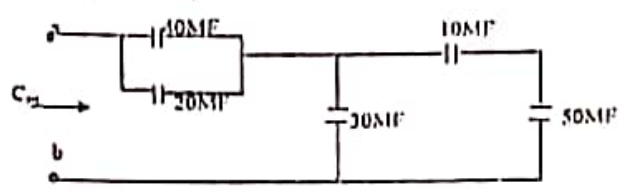
(d) Calculate the equivalent capacitance at the terminals of the circuit shown in figure below.



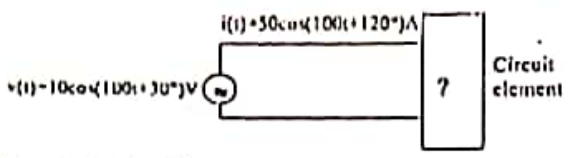- Q.5(a) What is phase sequence? Determine the phase sequence of the set of voltages  $v_{an} = 110 \cos(\omega t + 150^\circ) V$ ,  $v_{bn} = 110 \cos(\omega t + 30^\circ) V$ ,  $v_{cn} = 110 \cos(\omega t - 90^\circ) V$  4.00
- (b) A voltage  $v(t)$  is applied across a circuit element in figure. If current  $i(t)$  flows through that element, determine the circuit element whether it is inductor or capacitor by drawing phasor diagram. 4.00




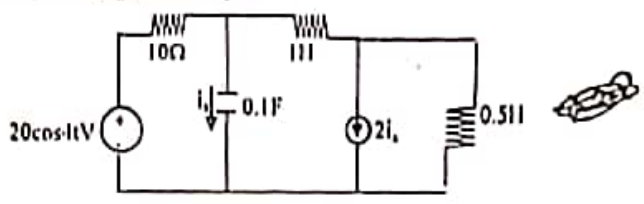- (c) Find  $I_0$  in the circuit of figure using nodal analysis. 4.00




SECTION-B

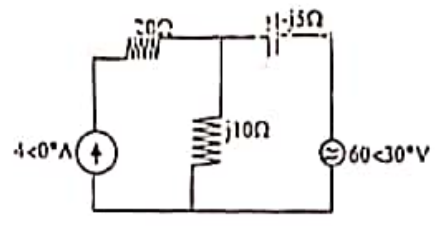- Q.6(a) "A resistive load absorbs power at all time, while a reactive load (L or C) absorbs zero average power", justify the statement. 4.00
- (b) Determine the average power generated by each source and the average power absorbed by each passive element in the circuit shown in figure. 4.00



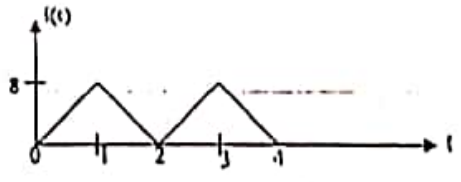- (c) What is meant by r.m.s. value of a periodic signal? Find the r.m.s. value of the current waveform shown in figure. 4.00



- Q.7(a) What are the advantages of 3-φ system over 1-φ system? Find the relationship between the line voltage and phase voltage of a y-y system. 4.00
- (b) Prove that the total instantaneous power in a balanced 3-φ system is constant. 4.00
- (c) One line voltage of a balanced Y-connected source is  $V_{AB} = 240 \angle -20^\circ V$ . If the source is connected to a Δ-corrected load of  $20 \angle 40^\circ \Omega$ , find the phase and line currents. Assume the abc sequence. 4.00
- Q.7(a) Define electronics. Discuss some importance of electronics. 4.00
- (b) Prove that, PIV of a full-wave rectifier using center-tapped transformer is twice than the PIV of a full-wave bridge rectifier circuit. 4.00
- (c) Draw the equivalent circuit of a transformer. What will happen, if dc voltage is applied across the primary of a transformer? 4.00
- Q.8(a) Describe the working principle of a simple loop dc generator. 4.00
- (b) What is the significance of back emf of a dc motor? Why field circuit of a dc motor never be opened? 4.00
- (c) Why does the rotor of an induction motor rotate? 4.00

12

**EEE 103**  
**Basic Electrical Engineering**


Full marks: 70

Time: 3 Hours

- N.B:-**
- (i) Answer any SIX questions, taking THREE from each section.
  - (ii) Figure in the margin indicate full marks.
  - (iii) Use separate answer script for each section.


**SECTION-A**

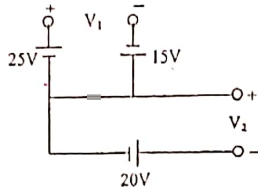- Q.1 (a) What is the main difference of maximum power transfer theorems in AC and DC circuits? Show that 5.67  
 $P_{max} = \frac{E_{Th}^2}{4R_L}$  in both AC and DC cases. Where the symbols have their usual meanings.
- (b) Find  $V_1$  and  $V_2$  for the following network. 4.00




$\frac{4 \times 63}{105}$

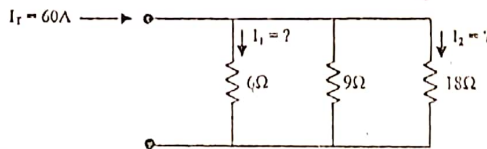- (c) Why ammeters are connected in series and voltmeters in parallel? 2.00
- Q.2 (a) State and explain any one of the following theorems. 5.67  
 (i) Kirchhoff's Voltage law (ii) Kirchhoff's Current law (iii) Voltage divider rule.
- (b) Calculate the currents  $I_1$  and  $I_2$  in the following circuit. 6.00




$\frac{2 \times 18 \times 6}{27} = 26$

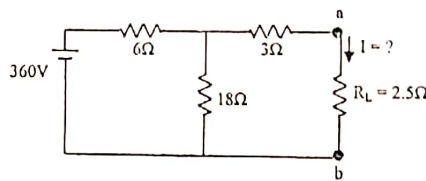- Q.3 (a) State and explain Thevenin's theorem. 5.67  
 (b) Calculate the current in load resistor  $R_L$  in the following circuit, by applying Thevenin's theorem. 6.00




$\frac{6 \times 18 \times 9}{27} = 3.67$   
 $\frac{4}{2} = 8.00$

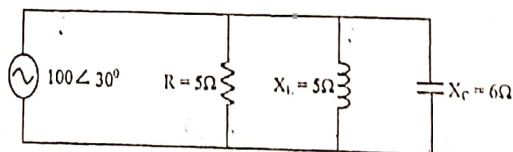- Q.4 (a) For ac circuit, prove that power  $P = VI \cos \theta$ , where the symbols has their usual significance. 3.67  
 (b) A single phase ac parallel circuit is shown below. 8.00



$24.5$

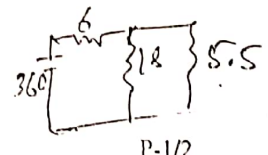
- (i) Calculate the individual currents drawn by each load elements.
- (ii) Calculate the total current supplied by the source.
- (iii) Calculate the power consumed/supplied by each elements.




P-17

SECTION-B

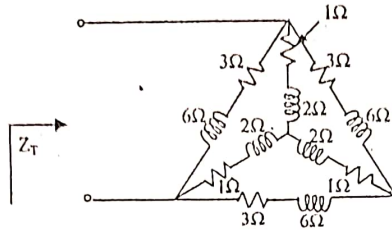- Q.5 (a) Discuss possible sources conversion process. 2.67  
 (b) Draw an electrical network which contains three nodes. Find the node voltages using nodal analysis. Assume suitable values of active and passive circuit elements. 4.00  
 (c) Find the total impedance  $Z_T$  for the following network using both  $\Delta$ -Y and Y- $\Delta$  conversion processes. 5.00



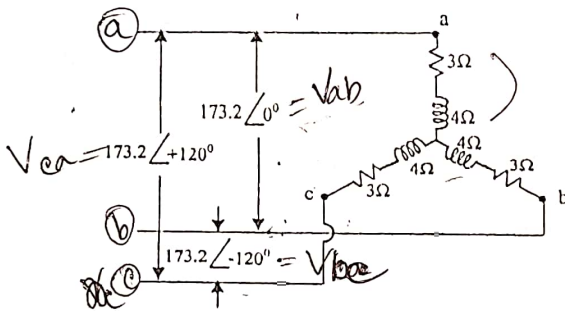- Q.6 (a) Define (i) phase sequence, (ii) balanced circuit, and (iii) unbalanced circuit. 2.67  
 (b) Show that in a Y-connected system  $E_L = \sqrt{3}E_{\phi}$ ; where the symbols have their usual meanings. 4.00  
 (c) Find real power, reactive power, apparent power, and power factor from the following network. 5.00



$3+4j$

$173.2 \angle 0^\circ$

$\sqrt{3} \times 100 \angle 0^\circ$

$V_{ab} = \sqrt{3} V_P \angle 0^\circ$   
 $V_P = 100 \angle 0^\circ$

- Q.7 (a) Discuss the relative advantages and disadvantages of DC generators and alternators. 2.67  
 (b) Define back emf in a dc motor. Derive the condition for maximum power developed by a dc motor. 4.00  
 (c) What are the losses in a transformer? How can we estimate these losses? Derive the condition for maximum efficiency of a transformer. 5.00

- Q.8 (a) Explain how a P-N junction is made. Draw the circuit diagram and explain the operation of a half wave rectifier using P-N junction diode. 5.67  
 (b) Draw neat sketch and explain how a d' Arsonval basic instrument is made. Explain how an ammeter can be made using it. 6.00

\*\*\*

$\cos \theta = P.F$

$P$

$Z = 3+4j$


Full Marks: 70

Time: 3 Hours


- N.B.:-
- (i) Answer SIX questions, taking THREE from each section.
  - (ii) Figure in the margin indicates full marks.
  - (iii) Use separate answer script for each section.
  - (iv) Assume reasonable value for any data not given.

SECTION - A

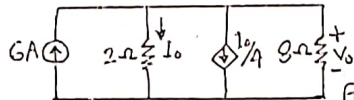
- Q.1 (a) Draw the equivalent circuit of a transformer. What do you mean by energizing current of a transformer? 3.00
- (b) Define - (i) *p-type* semiconductor, (ii) *n-type* semiconductor, (iii) intrinsic semi-conductor, (iv) extrinsic semi-conductor, (v) depletion layer. 5.00
- (c) What are the difference between BJT and FET? 3.67
- Q.2 (a) Find  $V_o$  and  $I_o$  in the circuit of Fig. 3. 3.00



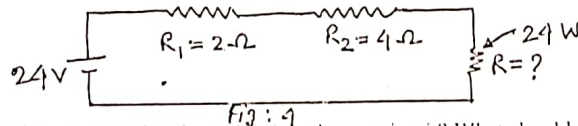
- (b) For the conditions specified in Fig. 4 determine unknown resistance. 3.00



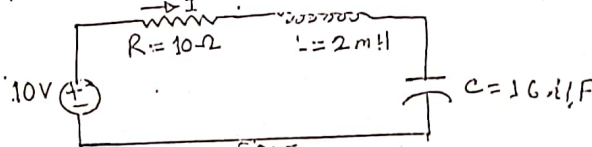
- (c) What do you mean by short circuit and open circuit? What should be done to inactive a voltage source and a current source? 3.67
- (d) Find the current  $I$  in the circuit of Fig. 5. 2.00



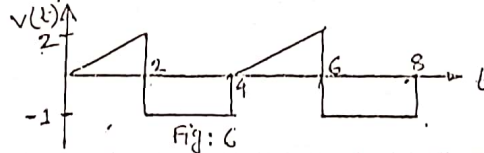
- Q.3 (a) Find the rms and average value of the following wave form in Fig. 6. 3.67



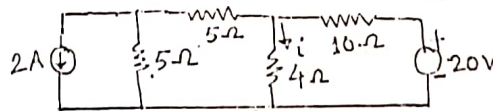
- (b) Use source transformation to find  $i$  for the circuit in Fig. 7. 3.00



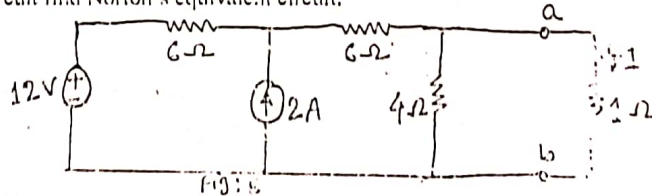
- (c) Find the Thevenin equivalent circuit for the following network and from this thevenin equivalent circuit find Norton's equivalent circuit. 5.00



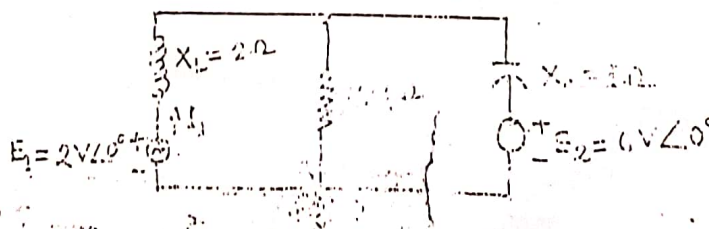- Q.4 (a) Using Mesh analysis, find the current  $I_1$  in Fig. 9. 5.00



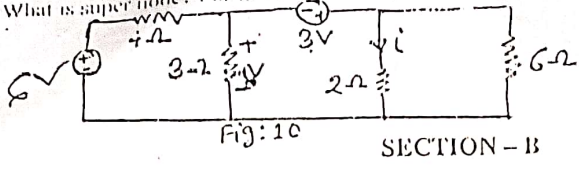(b) What is super node? For the circuit in Fig. 10, find  $V$  and  $i$  by using nodal method.




SECTION - B

4.00

Q.5 (a) For the following series, R-L-C circuit determine -

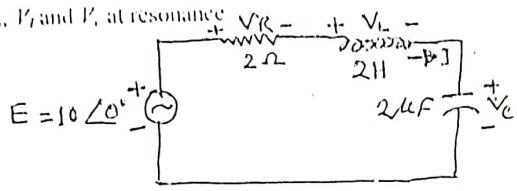- (i) the resonance frequency
- (ii) the quality factor  $Q$  at resonance
- (iii) the current  $I$  at resonance
- (iv)  $V_R$ ,  $V_L$  and  $V_C$  at resonance



3.00

(b) Write the advantages of 3-phase system.

4.67

(c) Prove that 3-phase system is more economical than equivalent single phase system.

3.00

Q.6 (a) Determine the power factor of resistor, inductor and capacitor.

4.67

(b) What is Faraday's law? Briefly describe the operating principle of dc generator.

4.00

(c) What is armature reaction? Discuss any one method that can minimize armature reaction.

3.00


Q.7 (a) Determine the phase relations between the signals of the following set:

- (i)  $V = 2 \cos(\omega t + 20^\circ)$ ,  $i = 1 \sin(\omega t + 10^\circ)$
- (ii)  $V = -3 \sin(\omega t + 10^\circ)$ ,  $i = 2 \cos(\omega t + 10^\circ)$
- (iii)  $V = 3 \sin(\omega t + 20^\circ)$ ,  $i = -2 \cos(\omega t + 10^\circ)$

4.00


(b) For the following network determine -

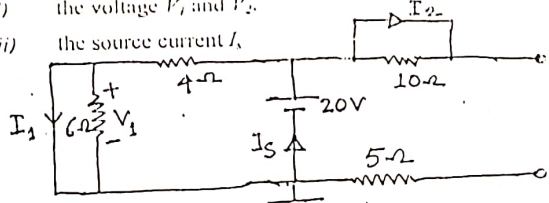- (i) the short circuit currents  $I_1$  and  $I_2$
- (ii) the voltage  $V_1$  and  $V_2$
- (iii) the source current  $I_s$



4.67

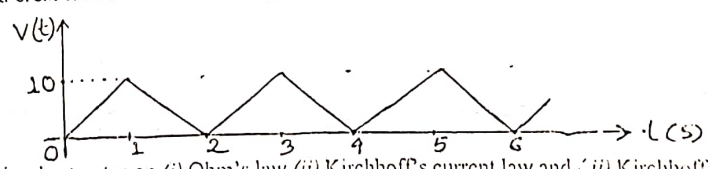(c) Find crest factor for the following wave form.




Q.8 (a) Write short notes on (i) Ohm's law (ii) Kirchhoff's current law and (iii) Kirchhoff's voltage law.

5.67


(b) Using Kirchhoff's current law, determine the unknown currents for the following network of

3.00

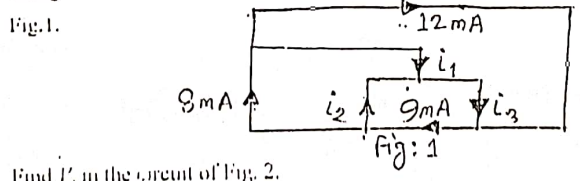

(c) Find  $V_1$  in the circuit of Fig. 2.

3.00

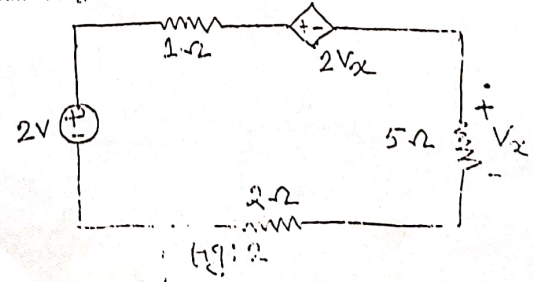


Full Marks: 70


- N.B.:-  
 (i) Answer SIX questions, taking THREE from each section.  
 (ii) Figure in the margin indicates full marks.  
 (iii) Use separate answer script for each section.  
 (iv) Assume reasonable value for any data missing.

SECTION-A

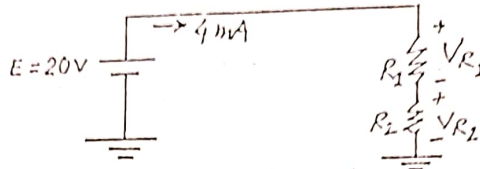
- Q.1(a) Define: (i) Ideal voltage source, (ii) Ideal current source, (iii) Dependent source, (iv) Active circuit element, and (v) Passive circuit element. 3.00  
 (b) Design the voltage divider such that  $V_{10} = 4 V_{10}$  3.67



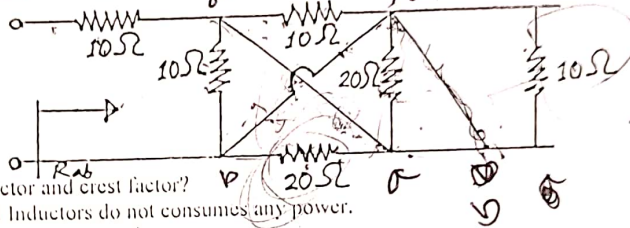
- (c) Calculate the equivalent resistance  $R_{ab}$  of the following circuit. 3.00



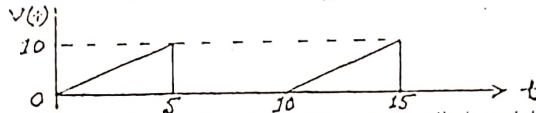
- Q.2(a) What is meant by form factor and crest factor? 3.00  
 (b) Prove that Capacitors and Inductors do not consume any power. 3.00  
 (c) Find form factor for the following waveform. 5.67



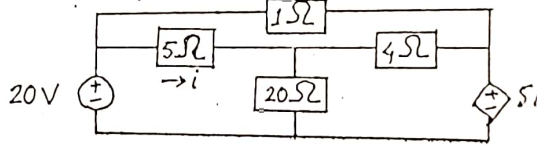- Q.3(a) Use mesh current method of circuit analysis to determine the power dissipated through the  $4\Omega$  resistor. 6.07



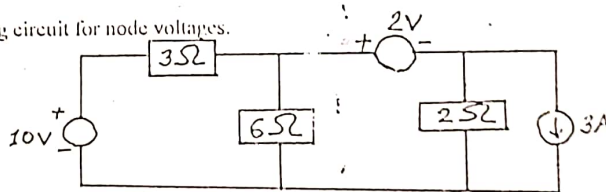
- (b) Solve the following circuit for node voltages. 3.00



- Q.4(a) "The superposition principle is not applicable to power effects" - Justify the statement. 3.00

- (b) Prove that  $P_{max} = \frac{E_{Th}^2}{4R_{Th}}$ , where symbols have their usual meaning. 3.00

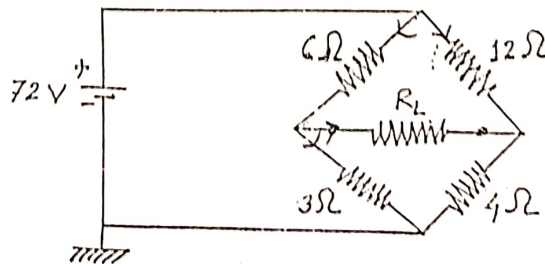- (c) Find the maximum power delivered to the load  $R_L$  of the following network. 5.67




Handwritten notes and scribbles at the bottom of the page, including the number '23.33'.


SECTION-B

Q.5(a) Determine whether the circuit element is R, L, or C for the following waveform.

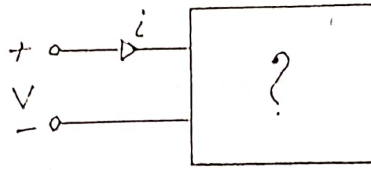- (i)  $v = 100 \sin(\omega t + 10^\circ)$   
 $i = 20 \sin(\omega t - 80^\circ)$
- (ii)  $v = 50 \cos(\omega t + 130^\circ)$   
 $i = 20 \sin(\omega t + 120^\circ)$
- (i)  $v = 10 \sin(\omega t + 50^\circ)$   
 $i = 5 \sin(\omega t + 50^\circ)$



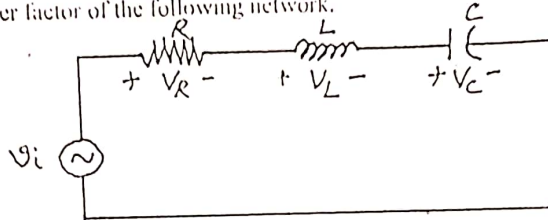(b) Calculate (i) Real power, (ii) Apparent power, (iii) Reactive power, (iv) Voltage drop across each circuit element, and (v) Power factor of the following network.



Given:  
 $v_i = 100 \sin(314t - 10^\circ)$   
 $R = 10 \Omega$   
 $L = 0.1 \text{ Henry}$   
 $C = 100 \mu F$


- Q.6(a) Show that at dc inductor acts as short circuit and capacitor acts as open circuit.
- (b) Derive the E.M.F. equation of transformer.
- (c) Derive the condition for which transformer efficiency is maximum.

Q.7(a) What is counter E.M.F? Why the counter E.M.F can never be equal to the applied voltage?  
 (b) What do you mean by balanced system? Derive the relationship between line voltage and phase voltage for a Y connected balanced 3-φ system.

(c) Show that balanced 3-φ power can be measured by using two wattmeter.

Q.8(a) Draw the characteristics (V-I) curve for ideal and practical diode.

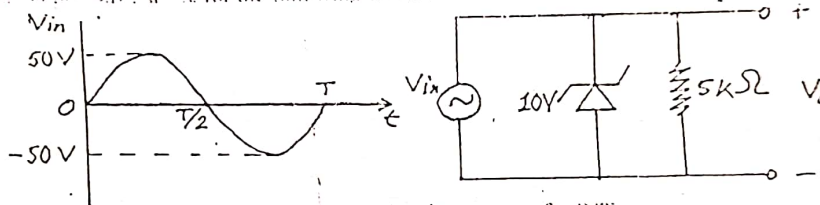(b) Draw the output wave form for the following circuit.



(c) Derive the relationship between base-current and emitter current for BJT.

**EEE 103**  
**Basic Electrical Engineering**


Full Marks: 70

Time: 3 Hours

- N.B.: (i) Answer SIX questions, taking THREE from each section.  
 (ii) Figure in the margin indicate full marks.  
 (iii) Use separate answer script for each section.  
 (iv) Assume reasonable value for any data missing.


SECTION-A

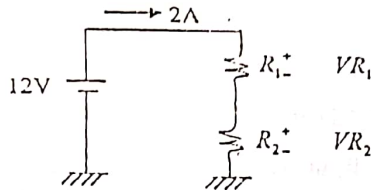- Q.1.(a) Define: (i) Linear circuit (ii) Bilateral circuit (iii) Ideal voltage source (iv) Short circuit. 4.00  
 (b) State voltage divider rule. Design the following voltage divider circuit such that  $V_{R_1} = 5V_{R_2}$ . 3.67




- (c) Define efficiency. What is the total cost of using the following at 10 Tk. per unit. 4.00  
 (i) A 300w dish washer for 60 min (ii) A 1000w heater for 30 min (iii) Five 100w fan for 45 min.

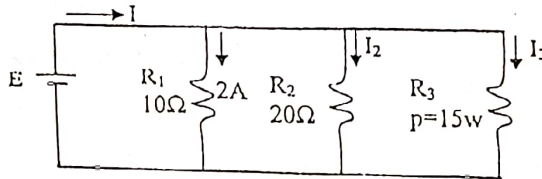
- Q.2.(a) Find the unknown quantities of the following circuit. 3.00



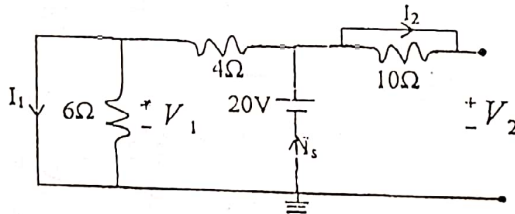
- (b) For the following network find  $I_s$ ,  $I_1$ ,  $I_2$ ,  $V_1$  and  $V_2$ . 4.00



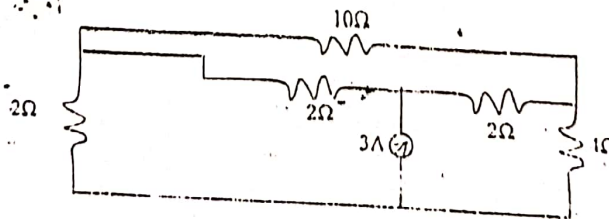- (c) Define node. Write down the node equations and also determine the voltage across the 10Ω resistor. 4.67




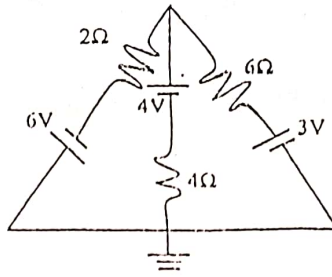Q.3.(a) Using mesh analysis find the branch currents in the following circuit:




(b) Using nodal analysis find the potential across 4Ω resistor:

6.00

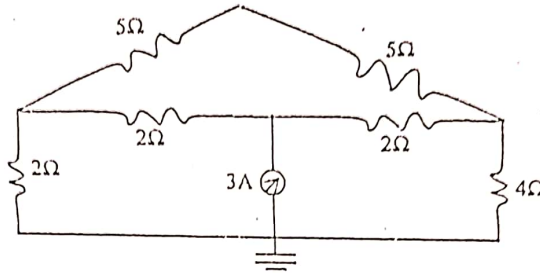


Q.4.(a) State super position theorem. Write down the limitation of this theorem. Prove that power delivered to  $R_L$  under maximum condition is  $P_{max} = \frac{E_{th}^2}{4R_{th}}$  4.00

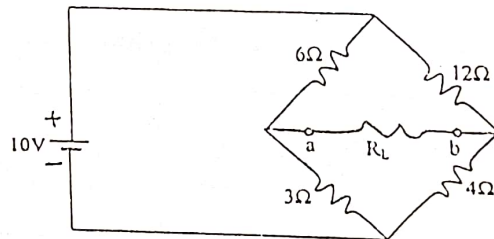(b) Determine the load resistance,  $R_L$  and maximum power delivered to the load under maximum power for the following network. 4.67



(c) Find  $R_{eq}$  and  $I_s$  for the following network.


3.00

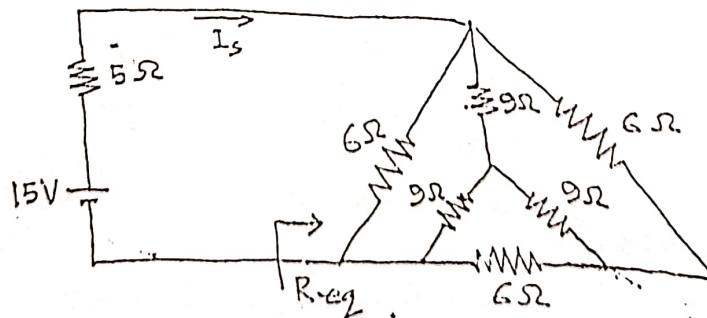

SECTION-B

Q.5.(a) Find the average power when  $v = V_m \sin(\omega t + \theta_v)$ ,  $i = I_m \sin(\omega t + \theta_i)$ . Show that power dissipated by ideal inductor is zero. 3.67

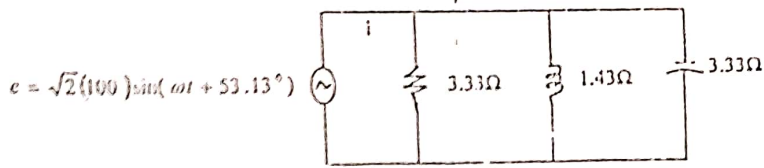(b) For the following circuit, find (i)  $Z_T$  (ii)  $I$  (iii)  $I_R, I_L, I_C$  (iv)  $P_R, P_L, P_C, P$  (v) PF. 8.00




Q.6.(a) Define (i) Form factor (ii) Crest factor. Find the form factor of the wave form shown in figure below. 4.67

$i^2 dt$

$$i = \sqrt{\frac{1}{6} \int_0^3 50t^2 dt}$$
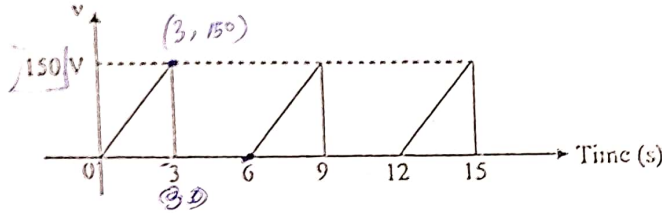
$$\frac{50t^2}{6} \left(\frac{t^3}{3}\right)_0^3$$



(b) Define RMS. Show that only resis or consumes power but inductor and capacitor do not consume any power. 4.00


1.24

(c) Find the rms value of the following wave form. 3.00

$V = 150$

$$F = \frac{V_{peak}}{V_{rms}}$$


$$= 2.45$$

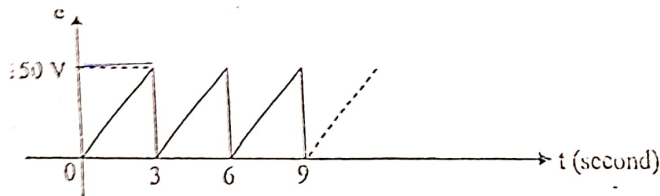

Q.7.(a) Why starters are necessary for motors? 2.00

(b) Define (i) Mutual inductance (ii) coefficient of coupling. 2.00

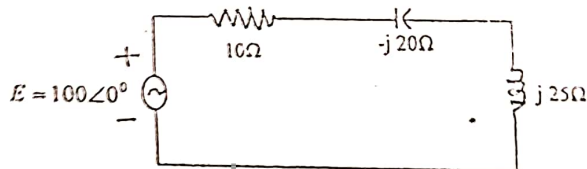(c) Find the (i) Real power (ii) Apparent power (iii) Reactive power (iv) Power factor,  $F_p$  for the following network. 4.67



(d) What is counter emf? Why the counter emf can never be equal to the applied voltage? 3.00

Q.8.(a) Define transformer. Determine the condition for maximum efficiency of a transformer. 3.67

(b) Show how a diode can be used as rectifier. Find the expression of PIV for a half wave diode rectifier. 4.00


(c) What are differences between BJT and FET? Show how BJT can be used as a switch. 4.00

-: The End:-


- N.B:- (i) Answer any SIX questions, taking THREE from each section.  
 (ii) Figure in the margin indicate full marks.  
 (iii) Use separate answer script for each section.

SECTION-A

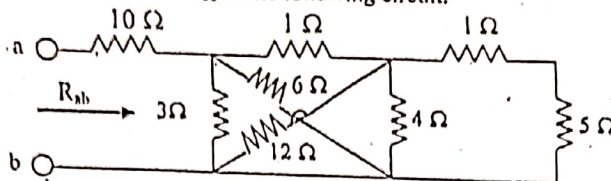
- Q.1 (a) Define (i) Practical voltage source (ii) Practical current source (iii) Linear circuit. 3.00  
 (b) Calculate the equivalent resistance  $R_{ab}$  in the following circuit. 4.00



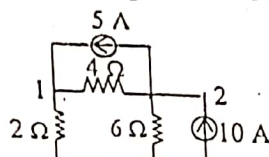
- (c) Using Nodal analysis, determine the node voltage in the following circuit. 4.67



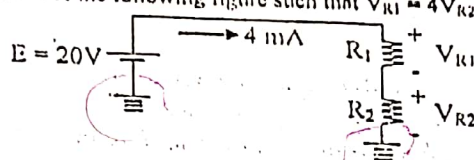
- Q.2 (a) State and explain the following terms:- (i) KVL (ii) KCL (iii) VDR (iv) CDR 6.00  
 (b) Design the voltage divider of the following figure such that  $V_{R1} = 4V_{R2}$  3.00



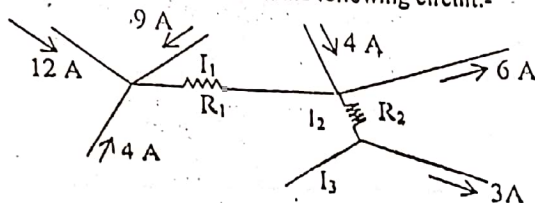
- (c) Find all unknown currents and their direction in the following circuit:- 2.67



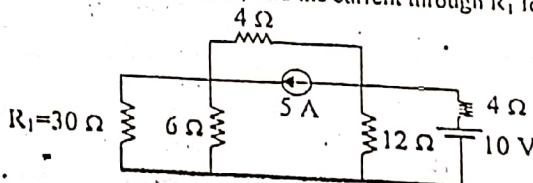
- Q.3 (a) State Superposition theorem. Using this theorem, find the current through  $R_1$  for the network. 4.67




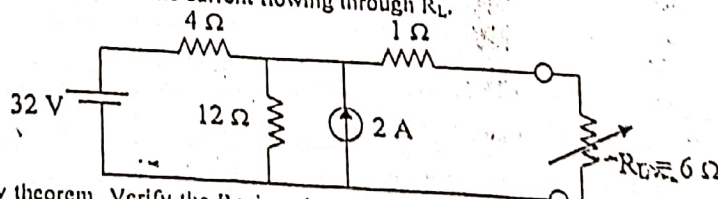- (b) Using Thevenin's theorem, find the current flowing through  $R_L$ . 3.00




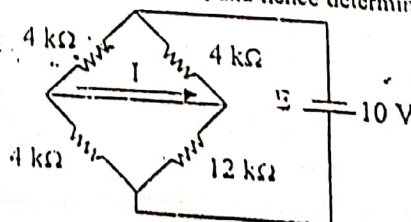- (c) State Reciprocity theorem. Verify the Reciprocity theorem and hence determine the current  $I$  for the following network. 4.00



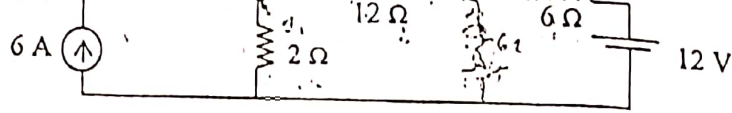

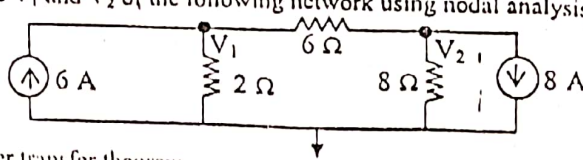(b) Determine the voltage  $V_1$  and  $V_2$  of the following network using nodal analysis:



6.00

(c) State maximum power transfer theorem.

1.67

SECTION-B

Q.5 (a) Define: (i) Oscillating current (ii) Periodic current (iii) Alternating current (iv) Phase sequence.

4.00

(b) Find the real power and reactive power when  $v = V_m \sin(\omega t + \theta)$  and  $i = I_m \sin \omega t$ .


3.67

(c) For a particular circuit, the supply voltage  $v = 100 \sin(157t - 150^\circ)$  and the supply current  $i = 10 \cos(157t + 30^\circ)$ . Find the nature and the magnitude of the circuit parameter.

4.00


Q.6 (a) Find the total resistance of the following network:

2.67

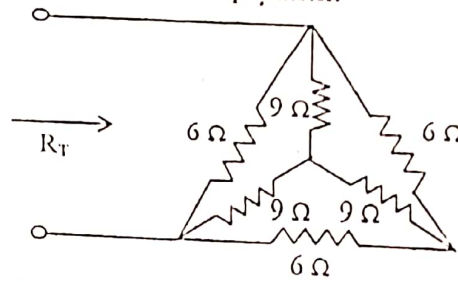


(b) Find the form factor of the following waveform:

4.00

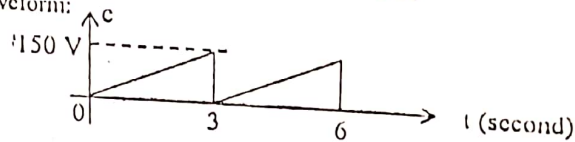



(c) Calculate the frequency, power factor, power and voltage drop across each part of the following circuit at resonance.

5.00

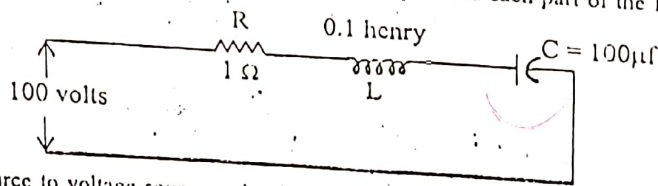

Q.7 (a) Convert current source to voltage source and voltage source to current source for the following networks.

3.00

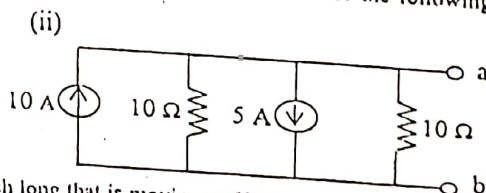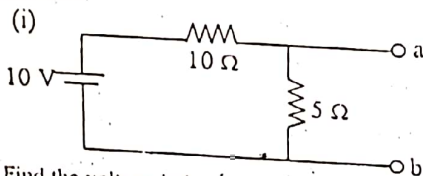

(b) Find the voltage induced in a conductor 12 inch long that is moving at  $60^\circ$  to the lines of flux in a uniform magnetic field of 30,000 lines per sq. inch. The length of the conductor in the magnetic field is 10 inch and the velocity of the conductor is 50 ft/sec.

4.00

(c) What is counter emf? Why the counter emf can never be equal to the applied voltage?


4.67

Q.8 (a) What is Zener diode? What are the necessities of starter for starting of a motor?

3.67

(b) Sketch the output  $v_o$  and determine the dc level of the output for the following network.

4.00

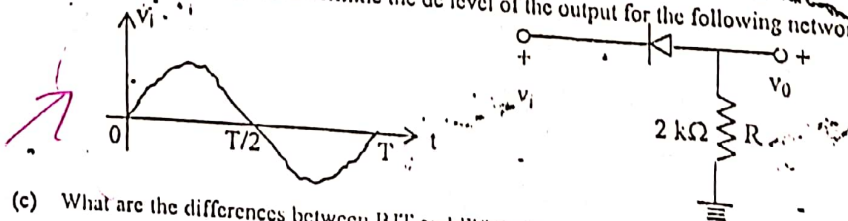

(c) What are the differences between BJT and FET? What do you mean by primary and secondary of a transformer?

4.00

06

EEE 103

BASIC ELECTRICAL ENGINEERING

Full Marks: 70

Time: 3 Hours

Q.B.: Answer SIX questions, taking THREE from each section.  
 Figure in the margin indicate full marks.  
 Use separate answer script for each section.  
 Assume reasonable value for any data missing.

$R = \frac{V}{I}$   
 $R = \frac{V}{I}$

SECTION - A

- Q.1.(a) Define resistance. Discuss the temperature effect on resistance of copper. 3.67  
 (b) Find the range in which a resistor having the following color bands must exist to satisfy the manufacturer tolerance: 3.00


1st band	2nd band	3rd band	4th band	5th band
Gray	Red	Black	Gold	Brown

What is the significance of the 5<sup>th</sup> band?

- (c) What is the total cost of using the following at 7 Tk. per unit?

- (i) a 860-W air conditioner for 24 hr.
- (ii) a 4800-W clothes dryer for 30 min.
- (iii) a 60-W tape recorder for 2 hr.
- (iv) a 1200-W dishwasher for 45 min.

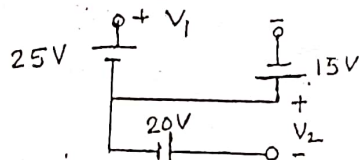- (d) Find  $V_1$  and  $V_2$  for the following network.




3.67  
 3.00  
 $R = \frac{V}{I}$   
 $R = \frac{V}{I}$   
 3.00  
 1h = 60min  
 60 min = 1h  
 2.00  
 $90 = \frac{1}{100}$


- Q.2.(a) Prove that the power delivered to the load resistance  $R_L$  under maximum condition is 3.67

$$P_{L,max} = \frac{E_{th}^2}{4R_{th}}$$

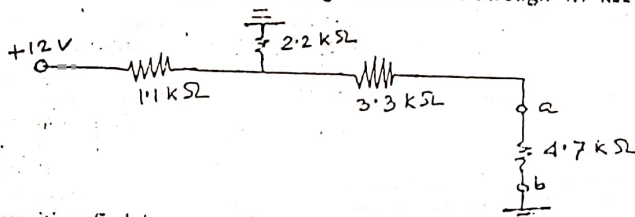- (b) Using Thevenin's theorem determine the voltage and current through 4.7 kΩ resistor connected across 'ab' 4.00




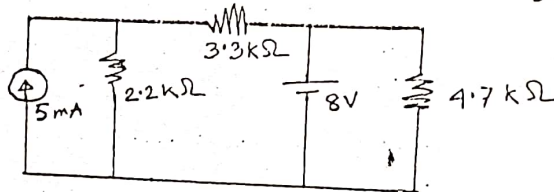- (c) Using superposition, find the current through 2.2 kΩ resistor for the following network. 4.00



- Q.3.(a) What is meant by form factor and peak factor?

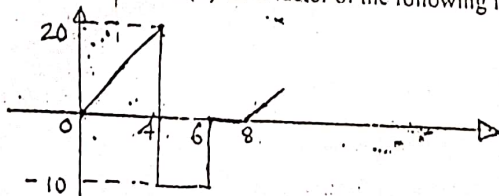- (b) Find the (i) Crest factor and (ii) form factor of the following figure. 3.00




3.00

5.67

- (c) Sketch the following signal and find the phase relationship between them

$$i = -5 \cos(\omega t - 30^\circ)$$


$$v = 25 \sin(\omega t - 60^\circ)$$

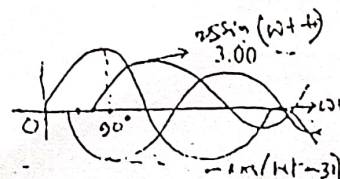


- Q.4.(a) What is the basic difference between series and parallel resonance? Mention some practical applications of series resonance circuit. 4.0
- (b) "Capacitor and inductor do not consume any power" - Explain. 4.0
- (c) For a balanced 3- $\phi$ , Y system, prove the relation between line voltage and phase voltage. 3.6

### SECTION - B

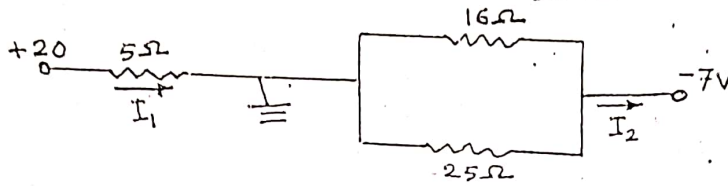
- Q.5.(a) Draw the characteristic (V - I) curves of ideal and practical diode. 3.67
- (b) What is meant by (i) PIV (ii) Breakdown voltage & (iii) Knee voltage? 3.00
- (c) Prove that the maximum efficiency of a half wave rectifier is 40.6%. 5.00
- Q.6.(a) Define real, reactive and apparent power. 2.67
- (b) What is meant by quality factor of a series resonant circuit? Draw the  $Z_T$  versus frequency curve of series resonant circuit (Both magnitude & phase plot). 6.00
- (c) Discuss selectivity & half power point of a series resonant circuit. 3.00
- Q.7.(a) State Superposition theorem. What are the limitations of this Theorem? 3.67
- (b) Determine the currents  $I_1$  and  $I_2$  for the following circuit. 4.00



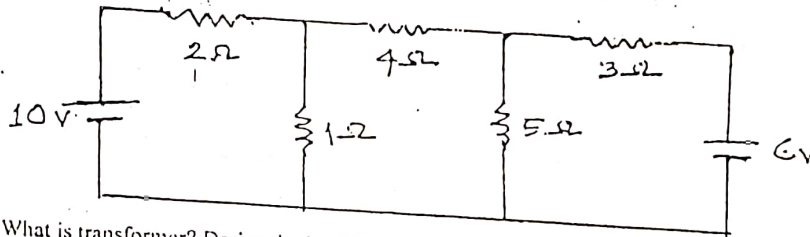- (c) Using mesh analysis, determine the current through the 6-volt battery for the following network. 4.00



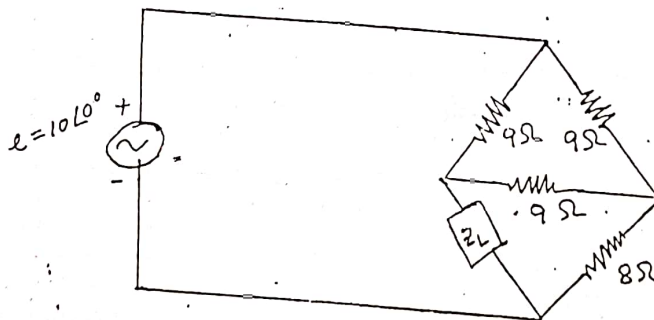- Q.8.(a) What is transformer? Derive the E.M.F equations of a transformer. 4.00
- (b) A shunt motor takes the total line current of 5 amp. Under full load condition, the field current is 1.5 amp. If the terminal voltage of the motor is 230 V, then determine the back e.m.f of the motor under full load condition. Consider armature resistance is  $0.2 \Omega$ . 3.67
- (c) Find the load impedance in the following figure for maximum power to the load and also find the maximum power. 4.00



Define rms value and average value of sinusoidal voltage wave.

3.67

(b) "Capacitor and inductor do not consume any power" - Explain.

4.00

(c) The current and voltage of a certain network are given, respectively as:

$$v(t) = 300 \cos(\omega t + 30^\circ)$$

$$i(t) = 50 \sin(\omega t + 30^\circ)$$




Calculate the real power consumed by the network.



(5) State (i) Superposition theorem (ii) Thevenin's theorem and (iii) Maximum Power Transfer theorem. 3.00

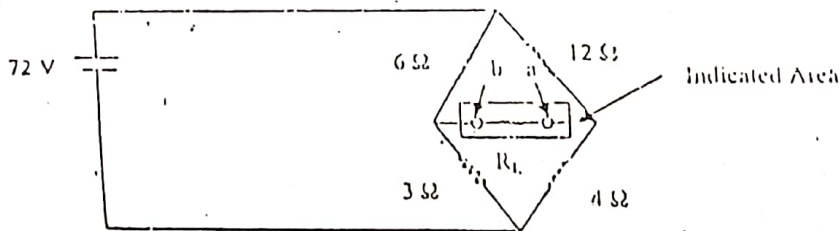(b) Find the Thevenin equivalent circuit for the network in the indicated area of the following bridge network. 4.33




(c) State Kirchhoff's Voltage Law. Design the following voltage divider circuit such that  $V_{R1} = 4V_{R2}$


$$\frac{500 \times 50}{2} = 4.67$$

SECTION - B

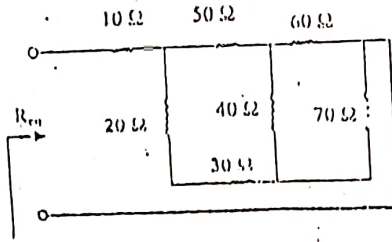Q.5(a) Draw the  $R_{in}$  of the following combination



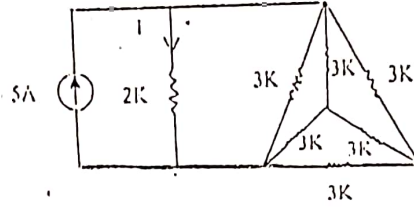(b) Determine the current  $I$  of the following network




(c) Define an ideal voltage source and ideal current source.

Q.6(a) Define (i) Oscillating current (ii) Periodic current and (iii) Alternating current

(i) Prove that the effective value of a sinusoidal wave is equal to 0.707 times the maximum value.

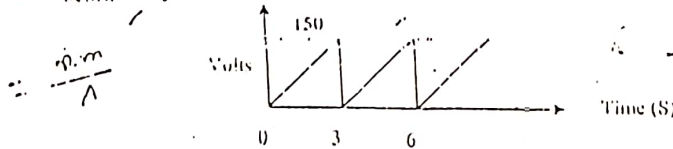(c) Find (i) the form factor and (ii) the crest factor of the saw tooth wave form as shown in Figure below



Q.7(a) State maximum power transfer theorem in a.c circuit.

(b) Compare series and parallel resonance.

A series circuit with resistance of  $10 \Omega$ , inductance of  $0.2 \text{ H}$  and capacitance of  $40 \mu\text{F}$  is supplied with a  $100 \text{ V}$  supply at variable frequency. Find the frequency at which resonance will take place. At resonance find the current, power and power factor. Also find the voltage across resistance, inductance and capacitance at that time.

(a) "DC" motor starts with a series resistance" - Explain.

(b) What is transformer? Derive the e.m.f equation of a single phase transformer.

A shunt motor takes the total line current of  $5 \text{ amp}$ . Under full load condition, the field current is  $1.5 \text{ amp}$ . If the terminal voltage of the motor is  $230 \text{ V}$ , then determine the back emf of the motor under full load condition. Consider armature resistance is  $0.2 \Omega$ .

$R = 10 \Omega$   
 $X_L = 2\pi f L$   
 $X_C = \frac{1}{2\pi f C}$

$I_s = \frac{1}{230 \text{ V}}$

$I = 1.05 \text{ A}$

05003

EEE 103

Basic Electrical Engineering


Full Marks: 70

Time: Three Hours


- N. B.: (i) Answer 5 questions, taking THREE from each section  
 (ii) Figures in the margin indicate full marks  
 (iii) Use separate answer script for each section  
 (iv) Assume reasonable value for any data missing

SECTION - A

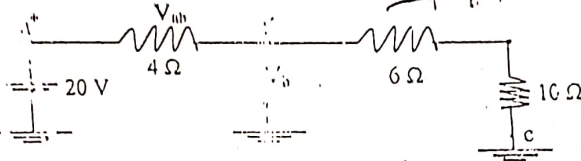
- Q. 1. (a) Explain Ohm's law. The resistance of a copper wire is  $0.76 \Omega$  at  $30^\circ\text{C}$ . What is its resistance at  $-40^\circ\text{C}$ ? 3.00  
 (b) State and explain Kirchoff's voltage law. 2.00  
 1.27 (c) Define efficiency. A 2 hp motor operates at an efficiency of 75%. What is the power input in watts? If the input current is 9.05 A, what is the input voltage? page-81 4.00  
 (d) Define voltage and current. What is meant by DC and AC? 2.67  
 Q. 2. (a) For the following network calculate  $V_{ab}$ ,  $V_b$  and  $V_c$ . 1.95 4.00



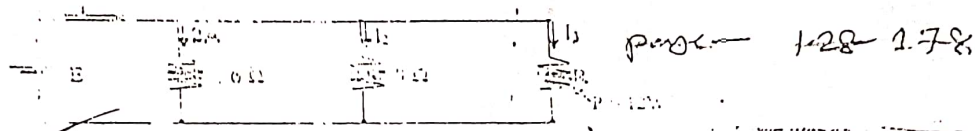
- (b) Find the unknown quantities for the following circuit. 4.00



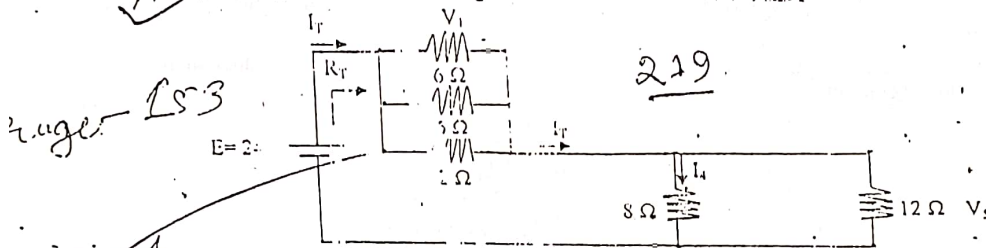
- (c) Find the indicated currents and voltages for the network. Find  $R_T$ ,  $I_1$ ,  $V_1$  and  $V_3$ . 3.67



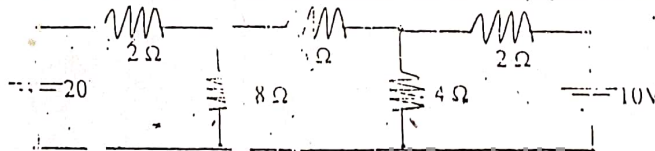- Q. 3. (a) Using mesh analysis determine the current through the 10V battery for the network. 5.00



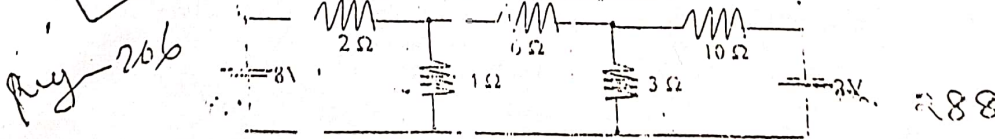- (b) Write down the nodal equations for the following circuit. 3.00



- (c) Explain Superposition theorem with an example. 3.67


- Q. 4. (a) Describe Lenz's law. Show that the voltage induced in the armature of a generator is  $E_g = \omega \Phi N$ ,  $\omega = \frac{d\theta}{dt}$ . 3.67

- (b) Draw the circuit diagram of a three-point starter and explain its operation. How does a four-point start overcome the objections of a three-point starter? 4.00

- (c) How is continuous rotation obtained for coil of DC motor? 2.00


SECTION - B

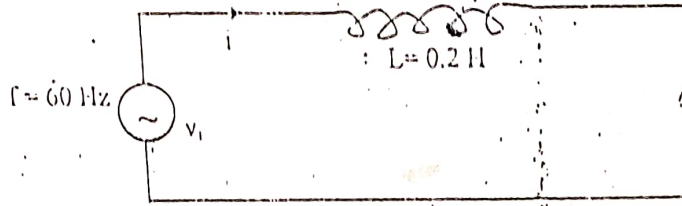- Q. 5. (a) Define phase, leading and amplitude. Why does sine wave in electrical power system? 3.67  
 (b) Derive the equation of alternating voltage and current. 4.00  
 (c) Define rms value. Show that the rms value of an alternating quantity is  $\frac{1}{\sqrt{2}}$ . 4.00
- Q. 6. (a) What is meant by form factor and peak factor? 2.00  
 (b) Deduce the equation of current for the following circuit. 3.67




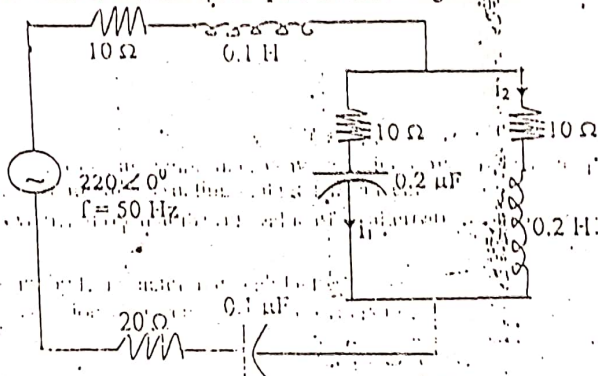(c) Determine the value of currents  $i_1$  and  $i_2$  for the following circuit. 6.00

$V_1 = 220 \angle 0^\circ$   
 $V_2 = 220 \angle 0^\circ$   
 $V_3 = 220 \angle 0^\circ$   
 $V_4 = 220 \angle 0^\circ$   
 $V_5 = 220 \angle 0^\circ$



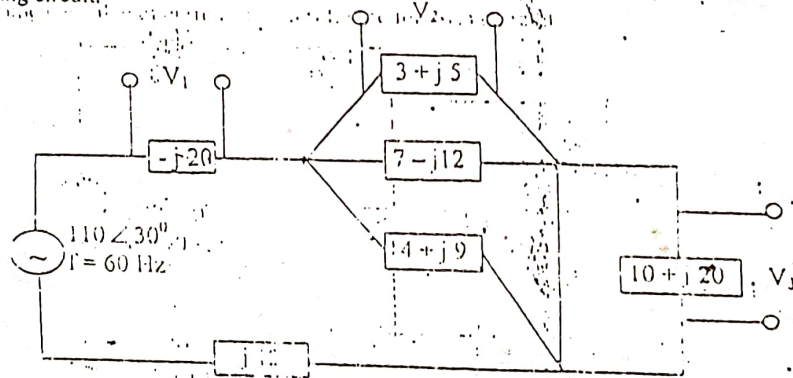- Q. 7. (a) What is phasor? Show that a pure capacitor does not consume any power. 2.67  
 (b) What is meant by balanced system? Show that in a balanced Y connection system  $V_L = \sqrt{3} V_p$ . 4.00  
 (c) Determine the voltage  $V_1$ ,  $V_2$  and  $V_3$  and also calculate the total power loss in the following circuit. 5.00



- Q. 8. (a) Define the term transformer. Write the principle of operation of a single-phase transformer. 3.67  
 (b) Derive the equation of torque of a three phase induction motor under running conditions and also determine the condition for maximum running torque. 5.00  
 (c) Why is transformer rating in KVA? 2.00  
 (d) Define primary and secondary of a transformer. 1.00

The End :