
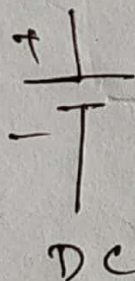


Electrical Circuit: Resistor, Capacitor, Inductor, ^{Source} these are the electrical components of circuit.

Arrangement of electrical components or elements is known as electrical circuit.

AC current → AC Generator
 AC source

DC current → DC source
 Battery.

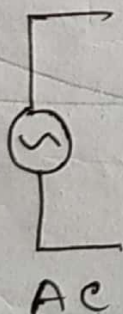


Some stored energy:
 Capacitor = $\frac{1}{2} CV^2$
 Inductor = $\frac{1}{2} LI^2$

Circuit Element:

- i) Active Circuit Element. [Delivers electrical Power on the circuit]
- ii) Passive C.E. [received energy and stored and dissipated energy].
 Capacitor, Inductor, Resistor

11.08.19
11.08.19

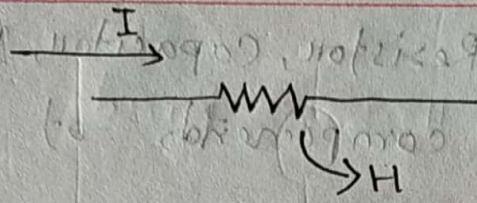


⊗ Resistor does not store any energy.


* Circuit Element:

i) Linear [if current is always proportional to voltage]

ii) Non-linear

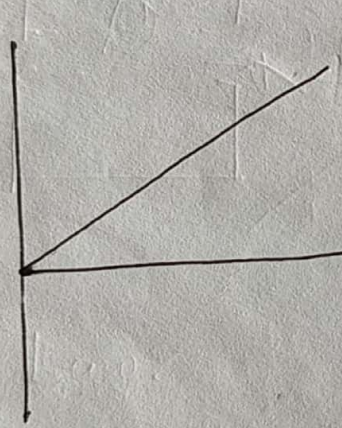

Linear

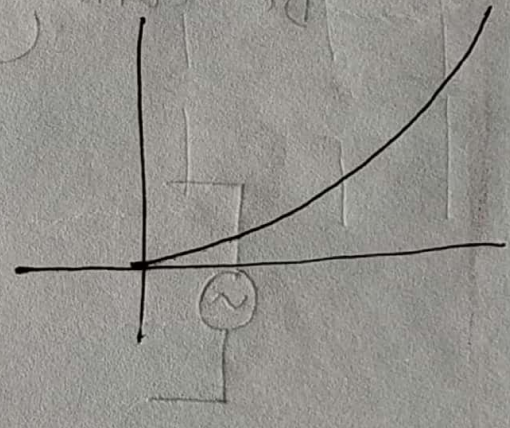

Non-linear

$I = \frac{V}{R}$

Homogeneous property:
 $V = IR$




$V = 1V, I = 1A, R = 1\Omega$ $kV = kIR$

$2V = 2V, I = 2A$
 $2 \times V = 2 \times 1$ linear

Circuit Element:


i) Bilateral. \rightarrow (যদি C.E. এর যোগে না দিলে
কারণের (যা হতে পারে, Resistor)

ii) Uni-lateral. (e. capacitor).

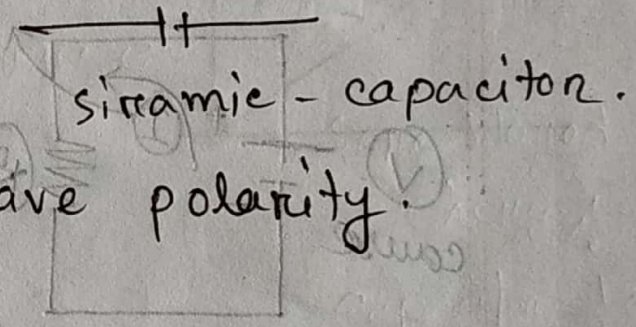
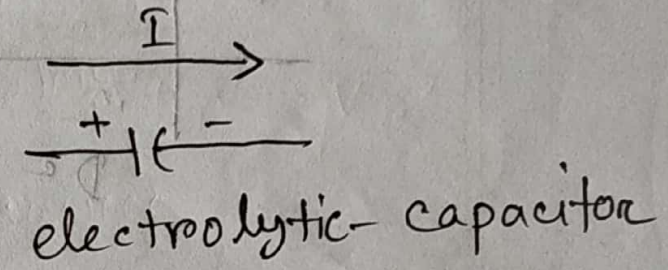
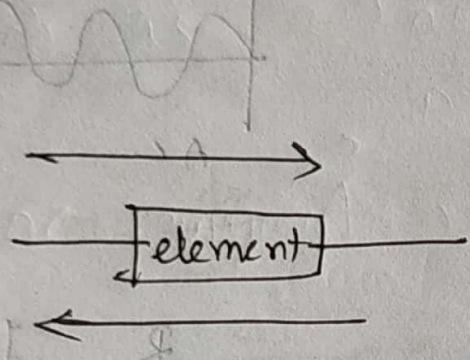


* electrolytic-capacitors have polarity.

24.08.19
1st E. Day

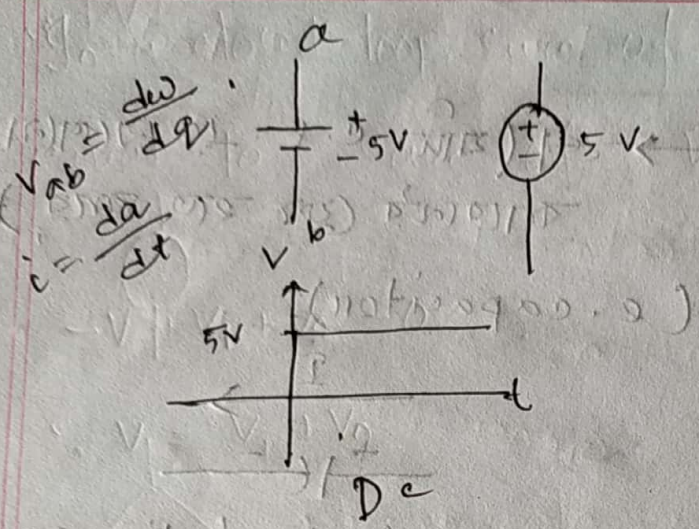


Form of AC

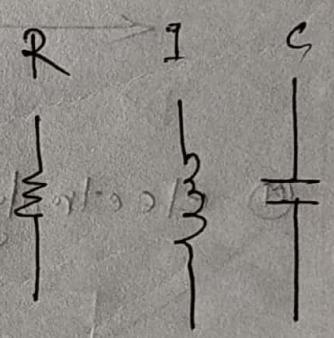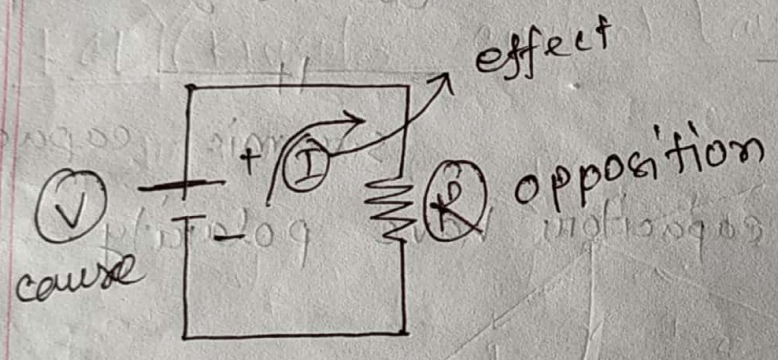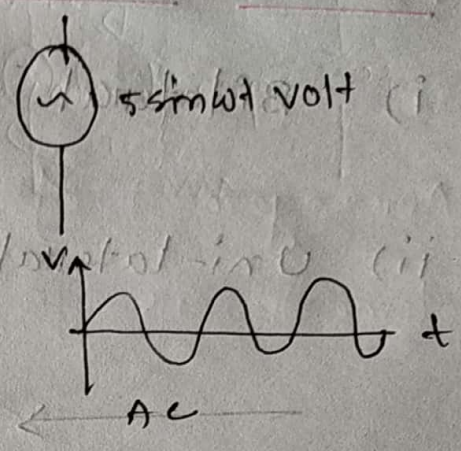

* Ohm's Law:


$$I \propto V$$

$$\Rightarrow I \propto \frac{V}{R}$$

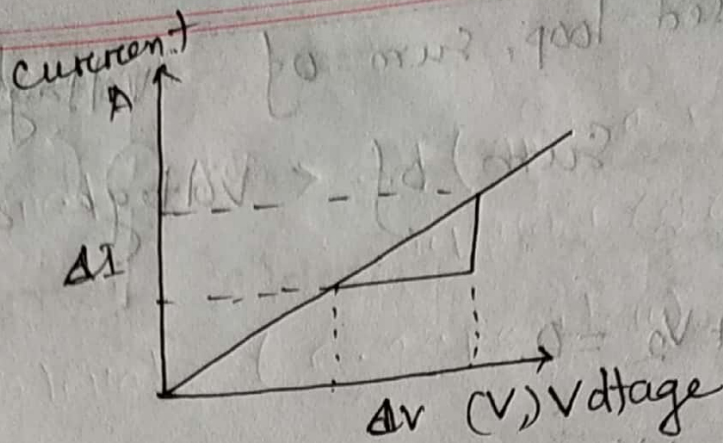

$$m = \frac{dy}{dx}$$

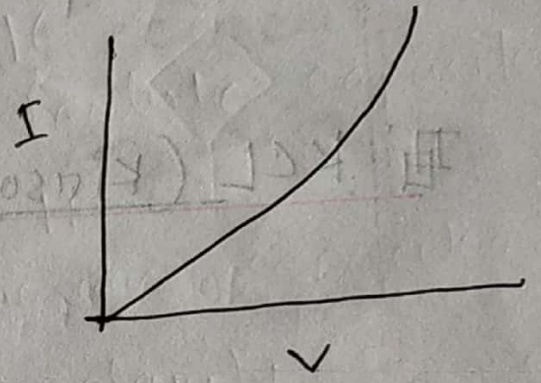
$$\Rightarrow \frac{\Delta I}{\Delta v} = \frac{1}{R}$$



Power, $P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt}$

$$= v_i = i^2 R = \frac{v^2}{R}$$

KVL (Kirchhoff's voltage law)

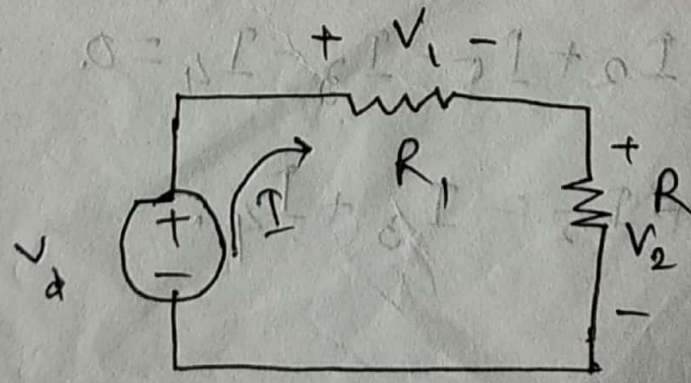


"In a closed loop, sum of voltage rises is equal to sum of voltage drops."

$$-V + V_1 + V_2 = 0.$$

$$\therefore V = V_1 + V_2$$

KCL (Kirchoff's Current Law):

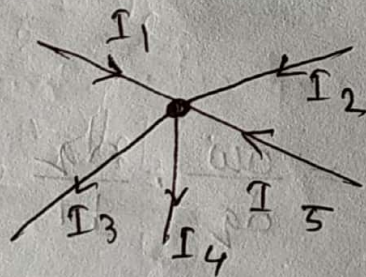

"sum of currents entering a node is equal to sum of current leaving that node."

$$I_1 + I_2 + I_5 - I_3 - I_4 = 0.$$

$$\therefore I_1 + I_2 + I_5 = I_3 + I_4$$

i. Fundamental of electric circuit. $\sum V = 0$

- Alexander.

ii. Introductory circuit Analysis. Boylestad.


iii) Electronic Devices and circuit. Boylestad.

iv)
- Rosenblatt
- Thereaja.

$$\sum_{n=1}^{\infty} V_n = 0$$

$$\sum_{n=1}^{\infty} V_n = 0$$



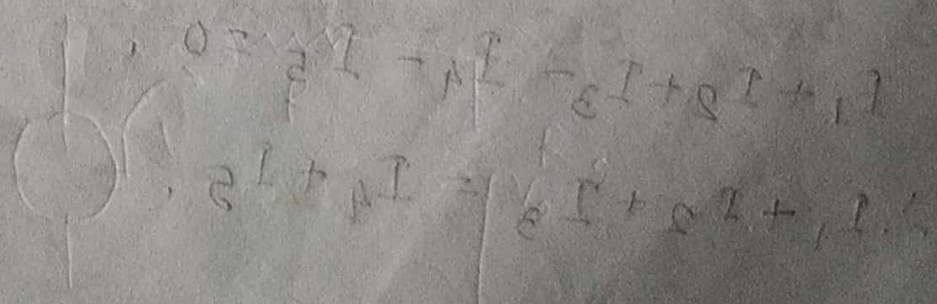
Node: Two or more branches which point is called node.



25.08.19
2nd - A Day

* KVL: Kirchhoff's Voltage Law

$$\sum V_n = 0$$

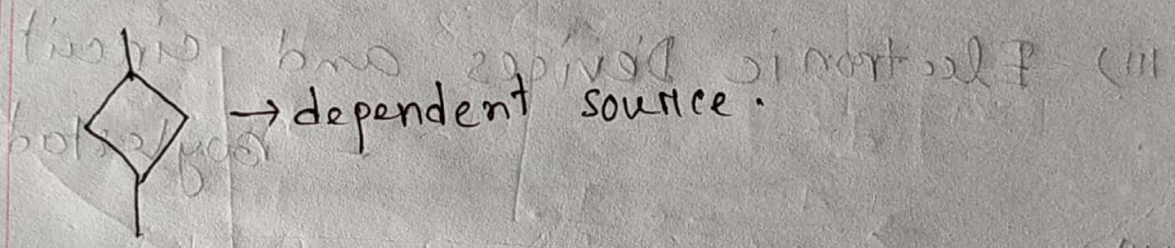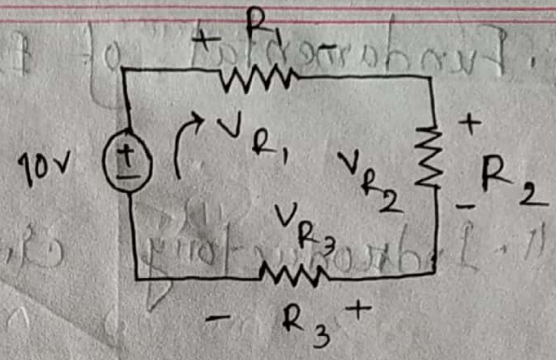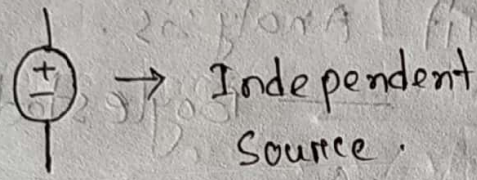

$$\Rightarrow -10 + V_{R1} + V_{R2} + V_{R3} = 0.$$

$$\Rightarrow 10 = V_{R1} + V_{R2} + V_{R3}$$

* KCL: Kirchhoff's Current Law

$$\sum_{n=1}^{\infty} I_n = 0.$$

Node: Two or more branches are connected which point is called node.

$$I_1 + I_2 + I_3 - I_4 - I_5 = 0.$$

$$\therefore I_1 + I_2 + I_3 = I_4 + I_5.$$

The charge flowing in a wire is plotted in

Fig 1.24. Sketch the corresponding current.

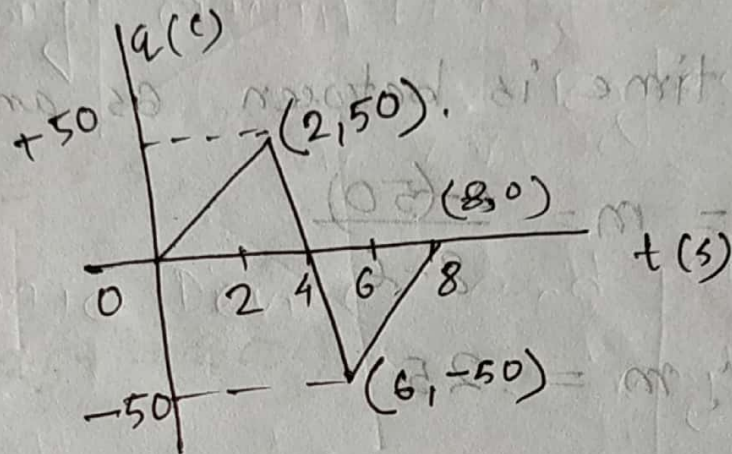


Fig. 1.24.

The line between (0,0) and (2,50)

$$\text{slope, } m = \frac{q_2 - q_1}{t_2 - t_1} = \frac{50 - 0}{2 - 0} = 25.$$

$$\therefore q = mt = 25t. \quad \text{--- (1)}$$

When, t is ind between 2s and 6s.

$$m = \frac{-50 - 50}{6 - 2} = -25.$$

$$\therefore q - 50 = -25(t - 2)$$

$$\therefore q = -25t + 100 \quad \text{--- (ii)}$$

When time is between 6s and 8s,

$$m = \frac{0 - 50}{8 - 6}$$

$$\therefore m = -25$$

$$\therefore q + 50 = 25(t - 6)$$

$$\Rightarrow q = 25t - 150 + 50$$

$$\therefore q = 25t - 100 \quad \text{--- (iii)}$$

Current, $I = \frac{dq}{dt}$

When, time is $0 \leq t \leq 2$,

$$I = \frac{d}{dt} (25t)$$

$$= 25$$

When $0 < t < 6$



$$i = \frac{d}{dt} (-25t + 100)$$

$$= -25$$


When $6 \leq t \leq 8$ s,

$$i = \frac{d}{dt} (25t - 200)$$


$$= 25$$

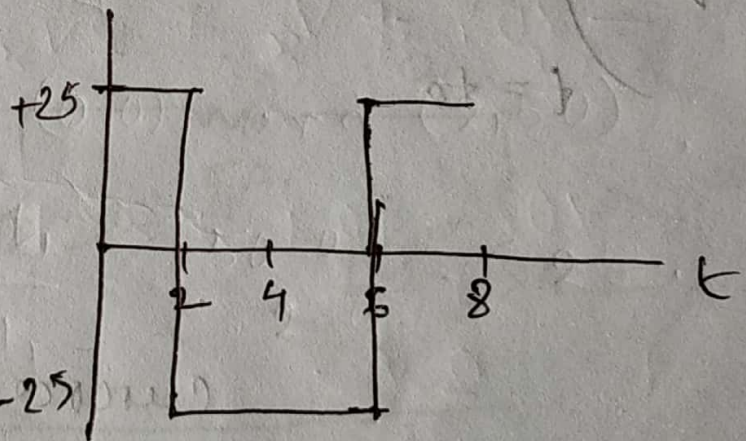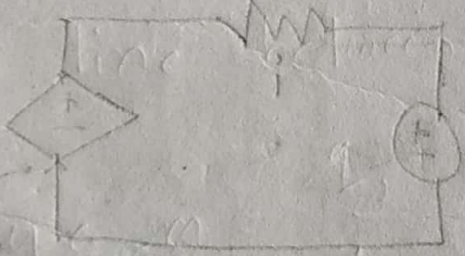

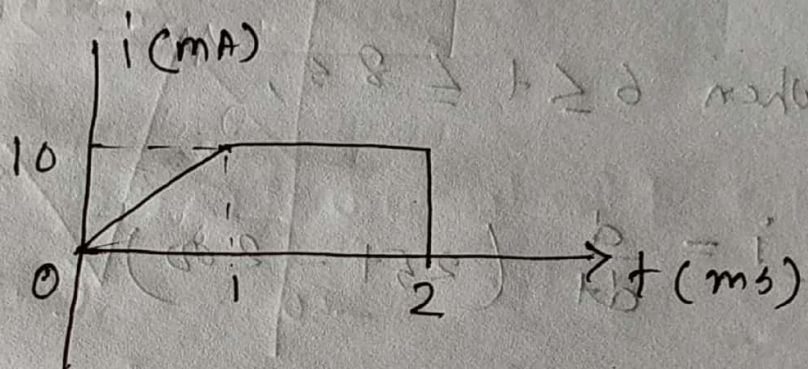
⊗ The current flowing past a point in a device is shown Fig 1.25. Calculate the total charge through the point.



$$q = \int_{t=t_0}^{t=t_1} i dt$$

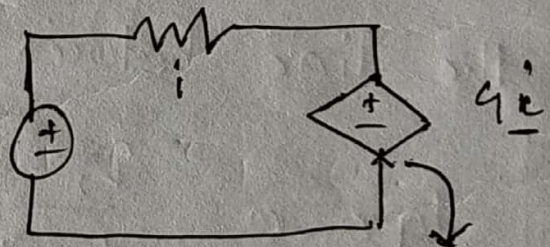


current control voltage source

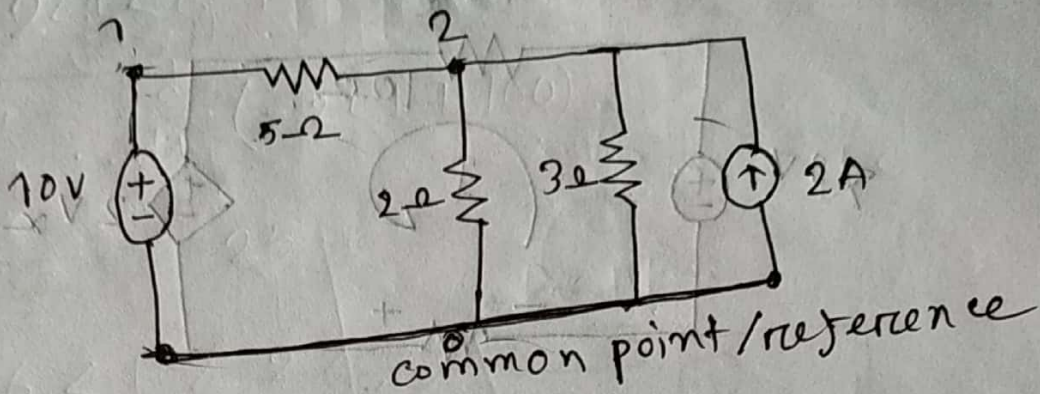

Number of branches = 5.


Number of nodes = 3.

Number of loops = 3.

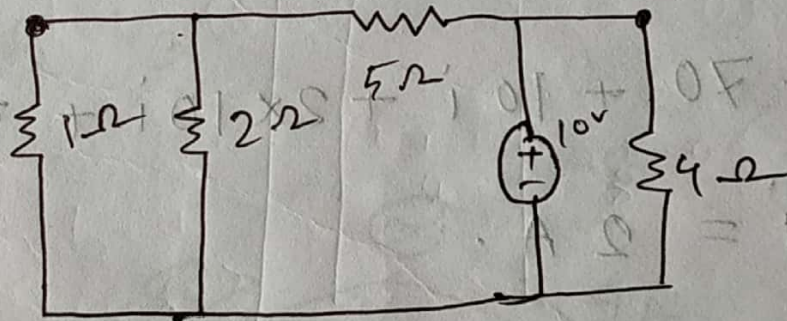

Nodes = 3.

loops = 3.

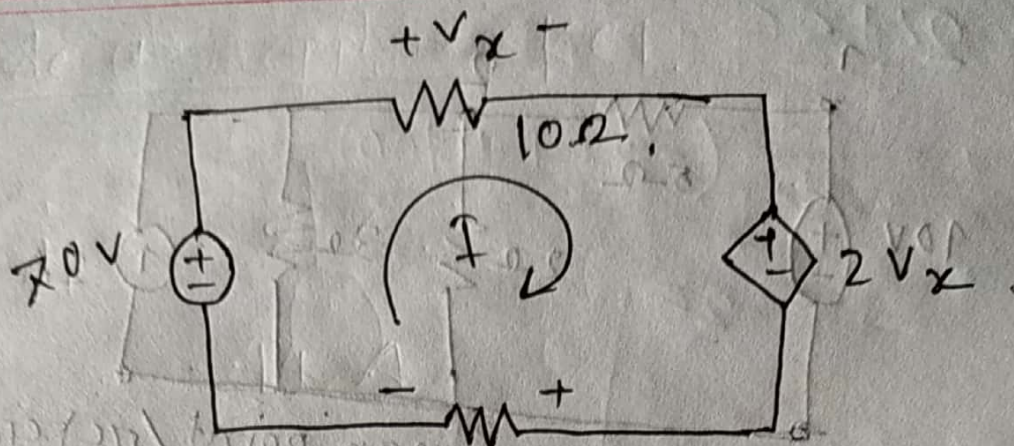

Find V_x ?

Applying KVL.

$$-70V + V_x + 2V_x + 5i = 0.$$

$$\Rightarrow -70 + 10i + 2 \times 10i + 5i = 0,$$

$$\Rightarrow i = 2A.$$

$$\therefore V_x = 10 \times 2 = 20V.$$


$$\therefore V_o = -5i.$$

$$= -5 \times 2.$$


$$= -10V.$$

Example - 2.6.1

Problem: 2.12

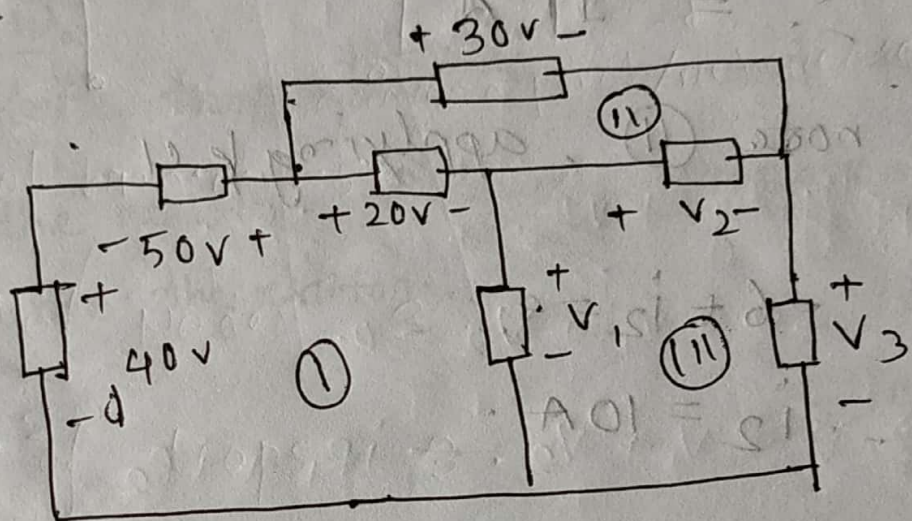

Find V_1, V_2, V_3 .

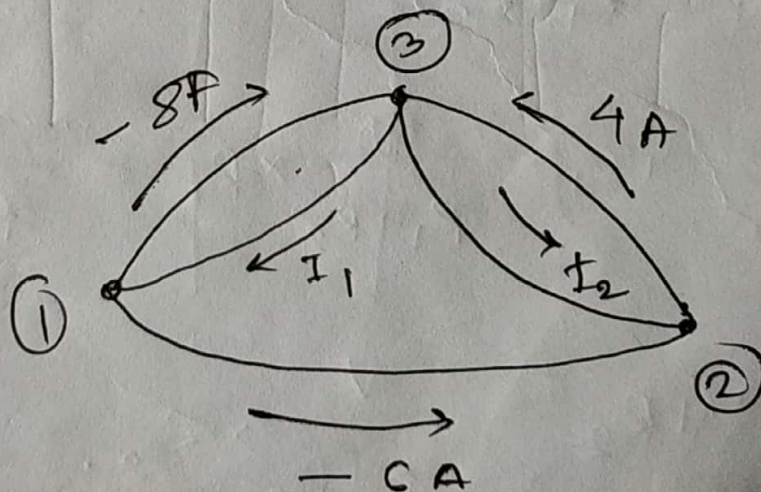

Find i_1, i_2

At node (i), applying KCL.

$$i_1 = -8 - 6.$$


$$\therefore i_1 = -14 \text{ A}$$

At node (ii), applying KCL


$$-6 + i_2 = 9.$$

$$\therefore i_2 = 10 \text{ A}$$

At node (iii),

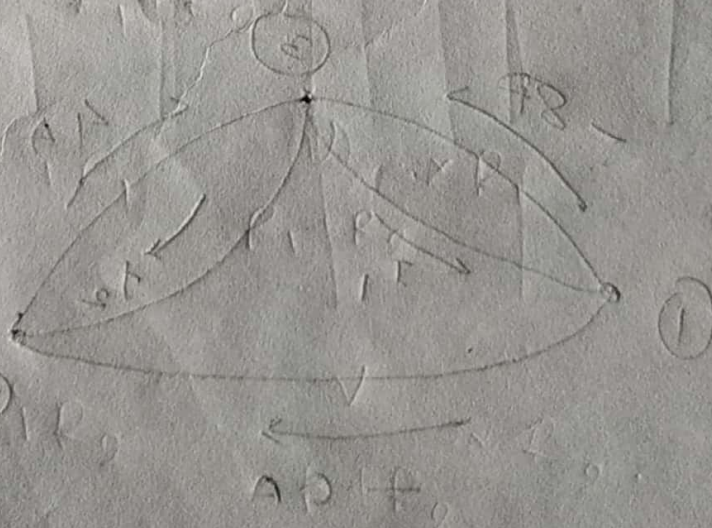

Problem: 2.7, 2.9, 2.11, 2.13

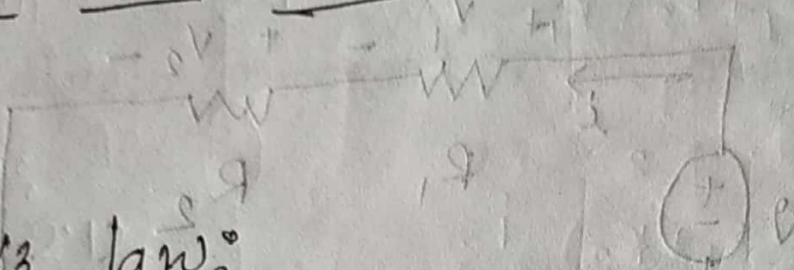

Ohm's law:

At definite temperature, the current flowing through the resistor is directly proportional to the voltage across the resistor.

$$iR_1 + iR_2 = V_1 + V_2 = V \Rightarrow$$

$$iR_1 + iR_2 = iR \Rightarrow$$


$$i = \frac{V}{R_1 + R_2}$$

$$V_1 = iR_1 = \frac{V}{R_1 + R_2} \times R_1$$

$$V_2 = iR_2 = \frac{V}{R_1 + R_2} \times R_2$$

31.08.19
2nd EET

Voltage divider rule

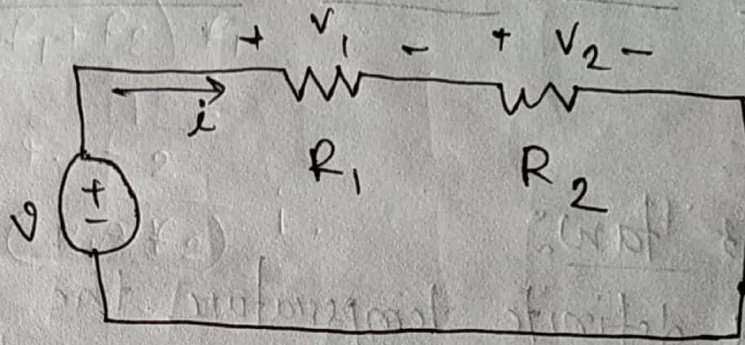

Applying KVL,

$$-V + V_1 + V_2 = 0.$$

$$\Rightarrow V = V_1 + V_2 = iR_1 + iR_2.$$

$$\Rightarrow iR_{eq} = iR_1 + iR_2$$

$$\Rightarrow i = \frac{V}{R_1 + R_2}$$


$$\therefore V_1 = iR_1 = \frac{V}{R_1 + R_2} \times R_1 = \frac{R_1}{R_1 + R_2} \times V$$

and,

$$V_2 = iR_2 = \frac{V}{R_1 + R_2} \times R_2 = \frac{R_2}{R_1 + R_2} \times V.$$

Source voltage V is divided among the resistors in direct proportion to their resistances.

Current divider rule

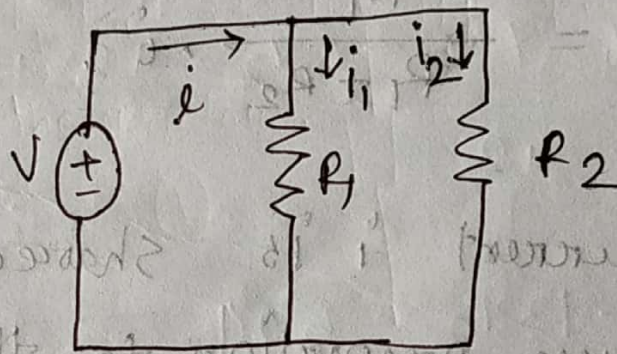

$$V = i_1 R_1 = i_2 R_2$$

Applying KCL,

$$i = i_1 + i_2$$


$$= \frac{V}{R_1} + \frac{V}{R_2} = \frac{V}{R_{eq}}$$

$$\Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


∴ $i_1 \Rightarrow \frac{R_2}{R_1 + R_2} i$ in direct proportion to their resistance

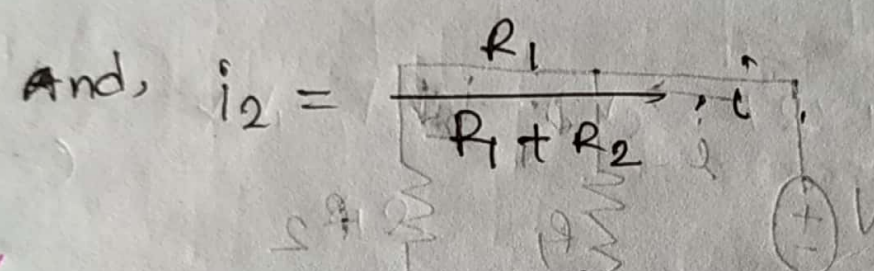∴ $i_1 = \frac{R_2}{R_1 + R_2} i$ in inverse proportion to their resistance



Total current i is shared by the resistors in inverse proportion to their resistance.

Nodal analysis:

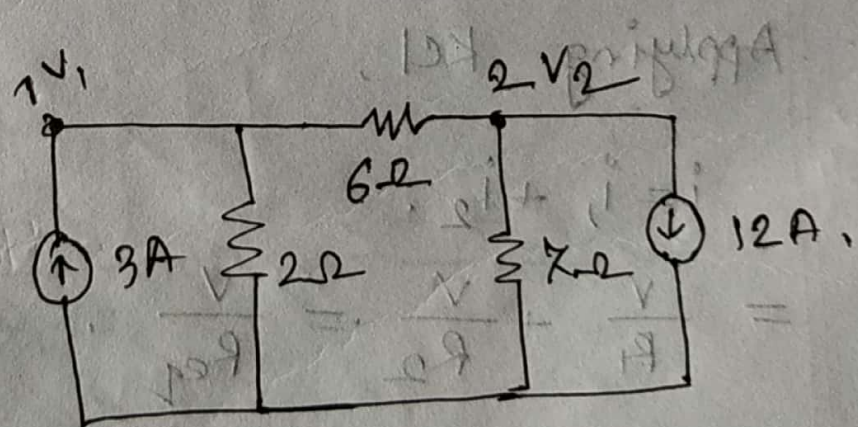

$$\frac{1}{2} + \frac{1}{6} = \frac{1}{7} + 12$$

$$\frac{6+2}{12} = \frac{1}{7} + 12$$

$$\frac{8}{12} = \frac{1}{7} + 12$$

$$\frac{2}{3} = \frac{1}{7} + 12$$

$$\frac{2}{3} - \frac{1}{7} = 12$$

$$\frac{14-3}{21} = 12$$

$$\frac{11}{21} = 12$$

$$11 = 252$$

* Steps:

(i) At first select a node as the reference. Assign voltage $v_1, v_2, \dots, v_{(n-1)}$ to the remaining $(n-1)$ nodes.

(ii) Apply KCL to each of $(n-1)$ non reference node.

(iii) Solve equation.

At node 1, applying KCL,

$$3A = I_{2\Omega} + I_{6\Omega}$$

$$\Rightarrow 3 = \frac{v_1 - 0}{2} + \frac{v_1 - v_2}{6}$$

$$\Rightarrow \frac{3v_1 + v_1 - v_2}{6} = 3$$

$$\Rightarrow 4v_1 - v_2 = 18 \quad \text{--- (1)}$$

At node L

$$I_{6\Omega} = I_{7\Omega} + 12 \text{ V}$$

$$\Rightarrow \frac{V_1 - V_2}{6} = \frac{V_2 - 0}{7} + 12$$

$$\Rightarrow \frac{7V_1 - 7V_2 - 6V_2 - 12 \times 42}{42} = 0$$


$$\Rightarrow 7V_1 - 13V_2 = 504 \quad \text{--- (i)}$$

By solving (i) & (ii)

$$V_1 = 6 \text{ Volt}$$

$$V_2 = 42 \text{ Volt}$$
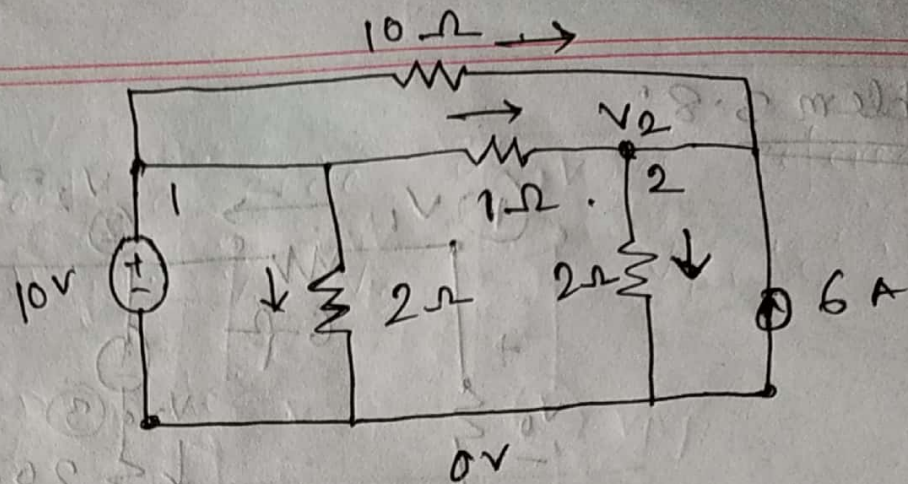
$$\text{(i)} \quad \text{--- } 81 = 5V - 12A \quad \text{---}$$



At node ②, applying KCL.

$$\frac{10 - V_2}{1} + \frac{10 - V_2}{10} + 6 = \frac{V_2 - 0}{2}$$

$$\Rightarrow \frac{150 - 10V_2 + 70 - V_2 + 60}{10} = \frac{V_2}{2}$$


$$\Rightarrow 5V_2 = \cancel{50 - 11V_2} + \cancel{160} + 170 - 11V_2$$

$$\Rightarrow 16V_2 = 170$$

$$V_2 =$$

3.7, 3.8, 3.11, 3.12.

Problem 3.8:

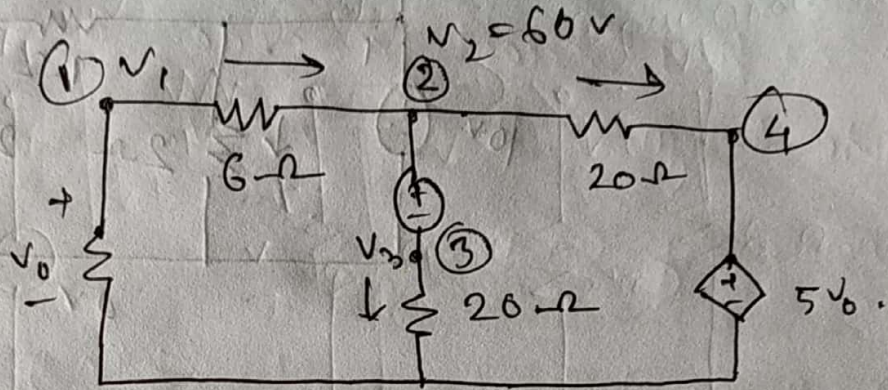

Super nodes: If there is a voltage source between two non-reference nodes.


$$100 - 10V_1 + 10V_2 + 10V_3 = 0$$

$$10V_1 - 10V_2 + 10V_3 = 0$$

$$10V_1 = 10V_2$$

$$3.8, 3.8, 3.8, 3.8$$

02.09.19
3rd A. Day

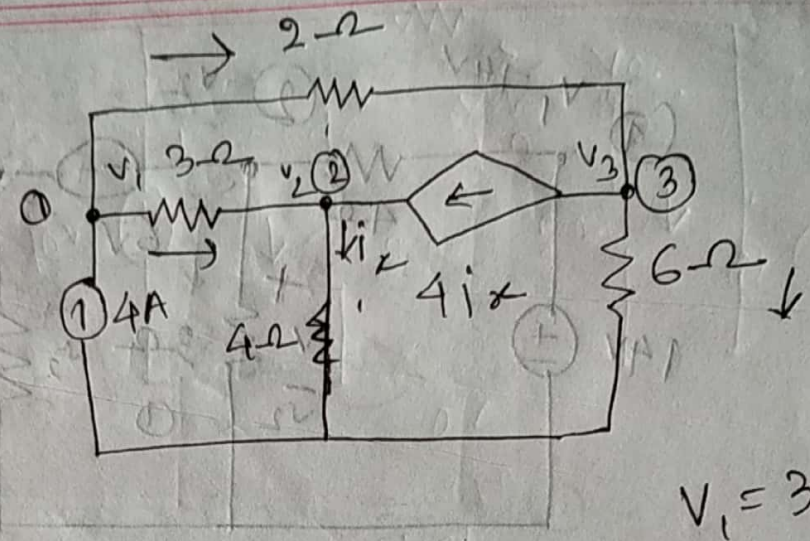

$v_1 = 32, v_2 = -25$
 $v_3 = 62.4$

$i_x = \frac{v_2}{4}$

At node (I),

$4 = \frac{v_1 - v_2}{3} + \frac{v_1 - v_3}{2}$ (I)


At node (II),

$\frac{v_1 - v_2}{3} + 4i_x = \frac{v_2}{4}$

$\Rightarrow \frac{v_1 - v_2}{3} + 4 \cdot \frac{v_2}{4} = \frac{v_2}{4}$ (II)

At node (III),

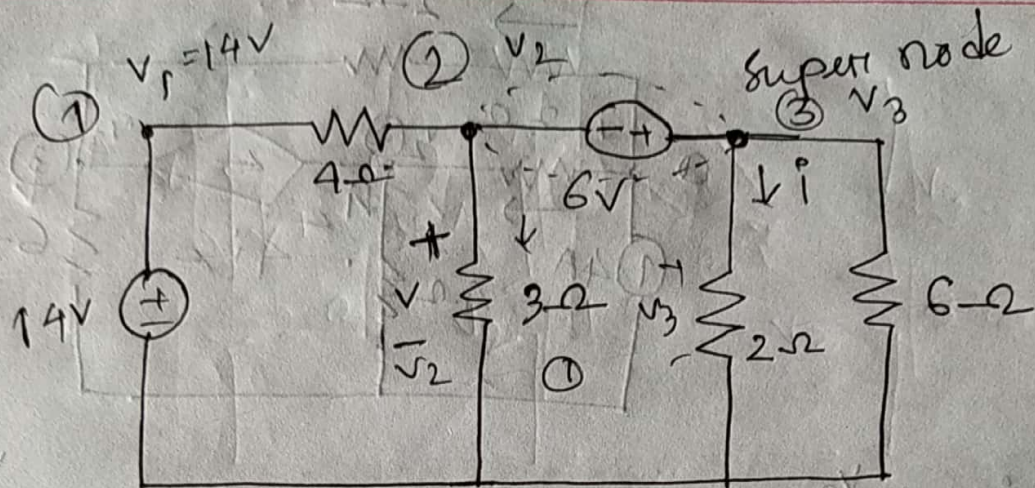$\frac{v_1 - v_3}{2} = \frac{v_3 - v_2}{4} + \frac{v_3}{6}$ (III)



Find v and i using nodal analysis.

When a super node exists we consider KCL on both the nodes and the voltage source do not consider.

Applying KCL at node ② and ③.

$$\frac{14 - v_2}{4} = \frac{v_2}{3} + \frac{v_3}{2} + \frac{v_3}{6}$$

$$\Rightarrow 14 \times 3 - 3v_2 = 4v_2 + 6v_3 + 2v_3$$

$$\Rightarrow -7v_2 - 8v_3 + 14 \times 3 = 0$$

$$\Rightarrow 7v_2 + 8v_3 = 42$$

Applying KVL in loop ①,

$$-V_2 - 6 + V_3 = 0$$

$$\Rightarrow -V_2 + V_3 = 6$$

By solving eqⁿ ① and ②.

$$V_2 =$$


$$V_3 =$$

Here, $V_2 = V =$


$$i = \frac{V_3}{2}$$

①

Assignment

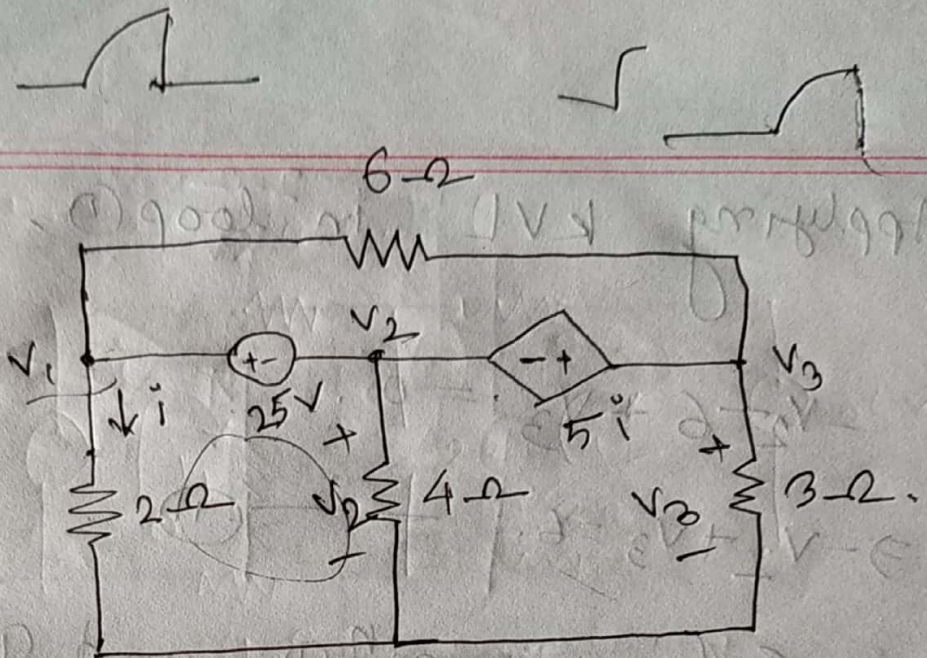


And 3.8.

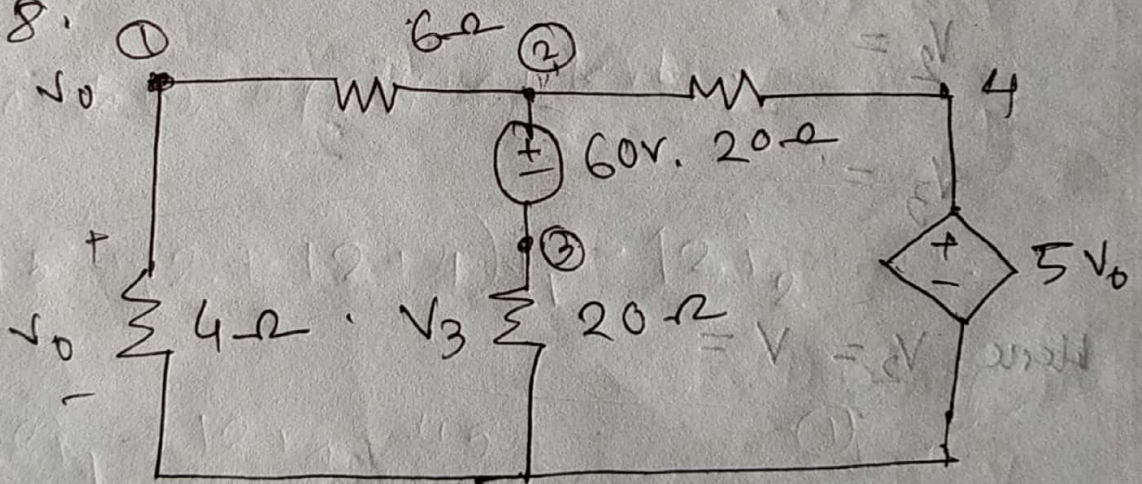

Mesh analysis : [Applying KVL]

P.T. 3.2.2

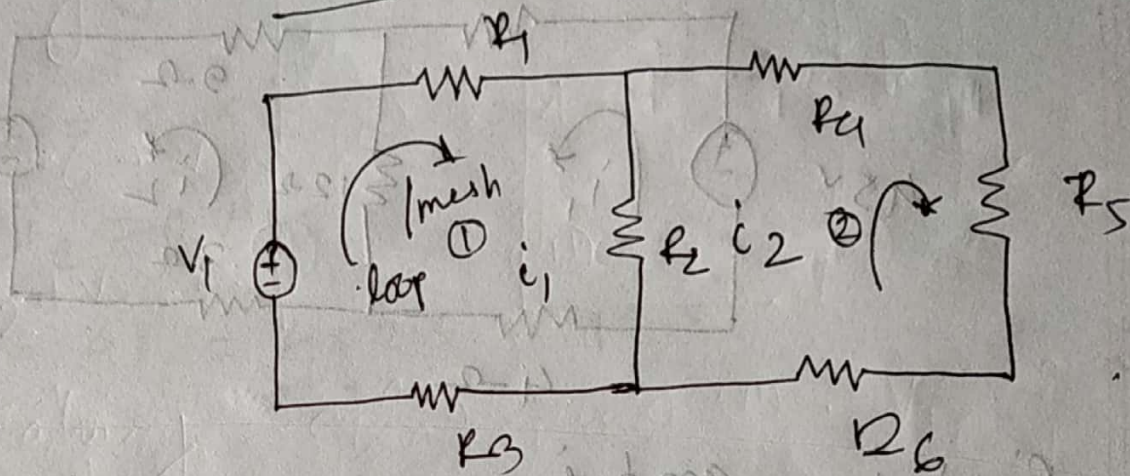

1. Assign mesh current $i_1, i_2, i_3, \dots, i_n$ for n meshes.

2. Apply KVL.

3. Solve the equations.

Apply in planned circuit.


For mesh (I), apply KVL

$$-V_1 + (R_1 + R_2 + R_3) \cdot i_1 - i_2 R_2 = 0 \quad \text{--- (I)}$$

For mesh (II), apply KVL,

$$(R_2 + R_4 + R_5 + R_6) i_2 - i_1 R_2 = 0 \quad \text{--- (II)}$$

P.P-3.5:

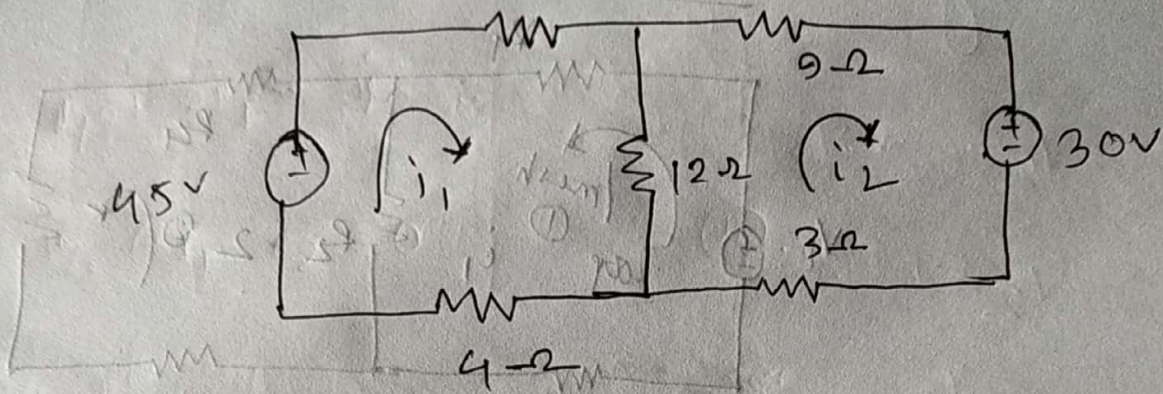

Find i_1 and i_2 .

For mesh ①, applying KVL.

$$-45 + (2 + 12 + 4)i_1 - 12i_2 = 0$$

$$\Rightarrow 18i_1 - 12i_2 = 45 \quad \text{--- ①}$$

For mesh ②,

$$(12 + 9 + 3)i_2 + 30 - 12i_1 = 0$$

$$\Rightarrow 24i_2 - 12i_1 = -30 \quad \text{--- ②}$$

$$\text{--- ③}$$


By solving the eqⁿ ① and ②

$$i_1 = 2.5 \text{ A}$$

$$i_2 = 0 \text{ A}$$

$$V_{4\Omega} = 4i_1 = 4 \times 2.5 = 10 \text{ V}$$

Super mesh:

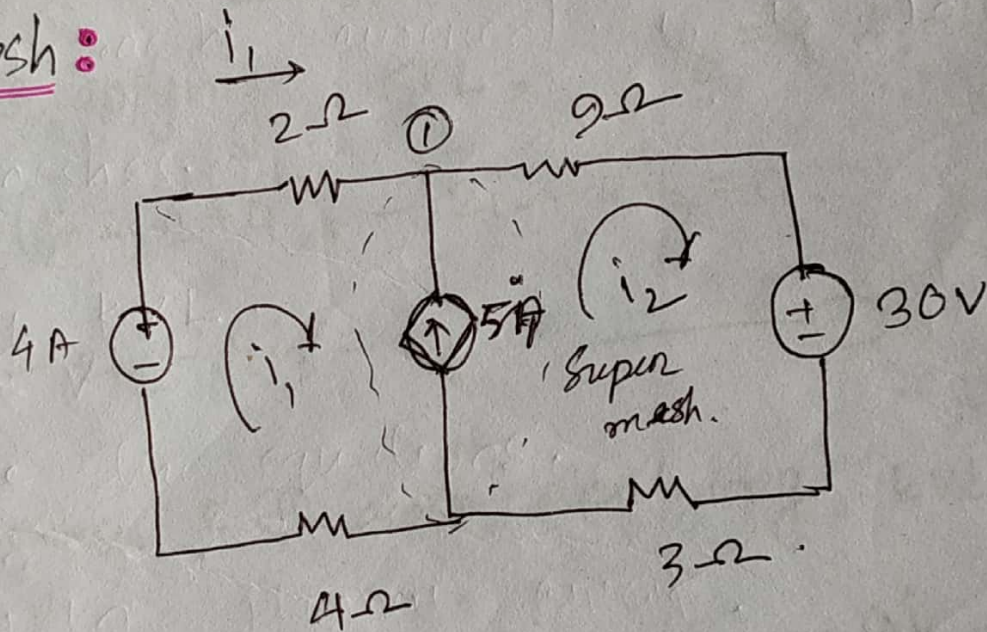

applying KVL in mesh ① and ②,

$$\cancel{2i_1 + 4i_1} + (2+4)i_1 + (9+3)i_2 + 30 = 0$$


$$\therefore 6i_1 + 12i_2 = -30 \quad \text{--- ①}$$

At node ①, applying KCL

$$i_1 + 5i_1 = i_2$$

$$\therefore 6i_1 - i_2 = 0 \quad \text{--- (1)}$$

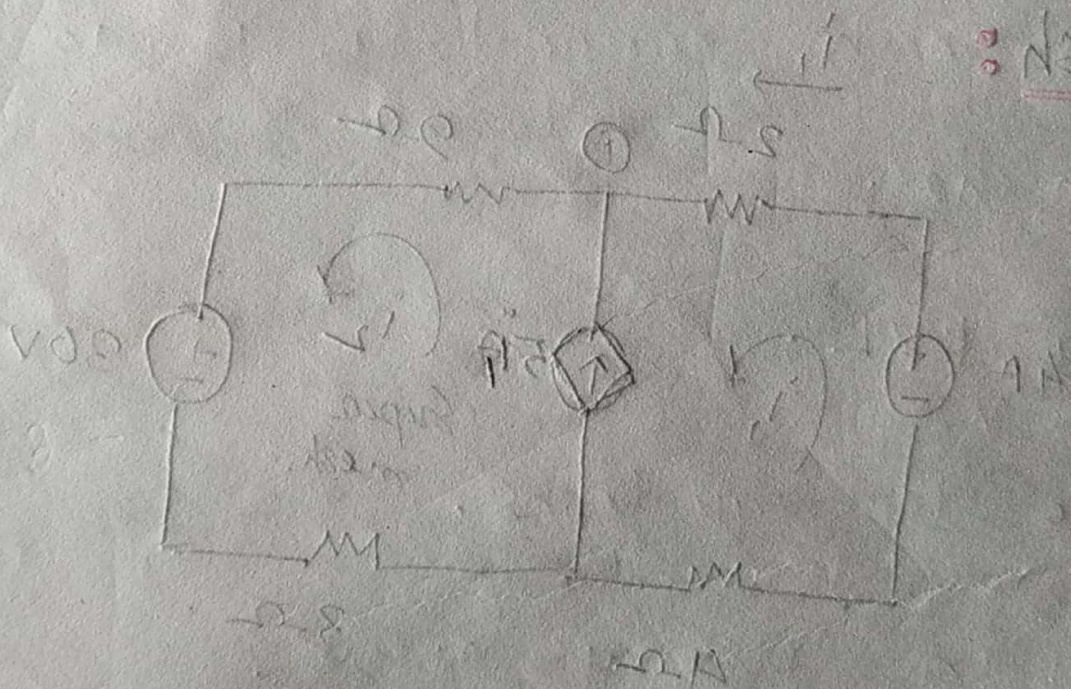
$$V_{01} = 2.0 \times 10^{-3} = 1 \mu V = 0.1 \mu V$$



Applying KVL in loop 1

$$0 = 0.5 + (5+5)i_1 + (5+5)i_2 + 30 = 0$$

Find V_0 using mesh analysis.

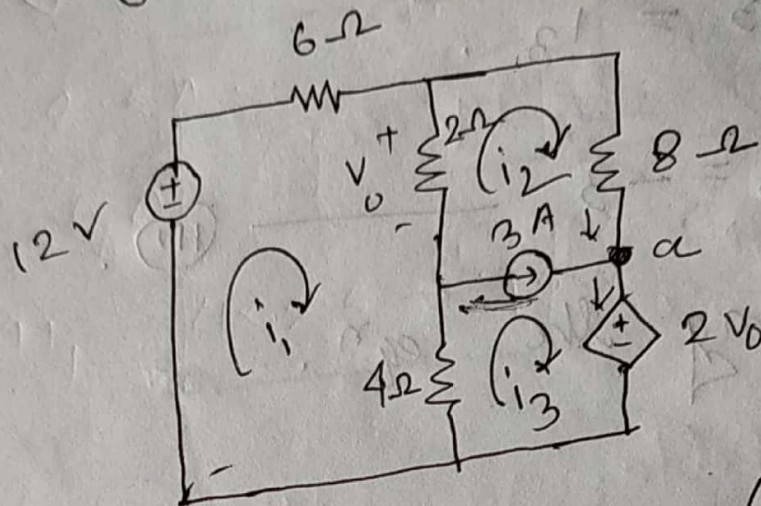

For mesh ①, applying KVL, $V_0 = (i_1 - i_2) 2$

$$-12 + (6 + 2 + 4)i_1 - 2i_2 - 4i_3 = 0.$$

$$\Rightarrow 12i_1 - 2i_2 - 4i_3 = 12 \quad \text{--- ①}$$

For meshes ② and ③ applying KVL,

$$(2 + 8)i_2 - 2i_1 + 4i_3 + 2V_0 - 4i_1 = 0.$$

$$\Rightarrow 10i_2 - 2i_1 + 4i_3 + 4(i_1 - i_2) - 4i_1 = 0.$$


$$\Rightarrow 6i_2 - 2i_1 + 4i_3 = 0 \quad \text{--- ②}$$

at node a,

$$i_2 + 3 = i_3$$

$$\therefore i_2 - i_3 = -3$$



By solving the eqⁿ.

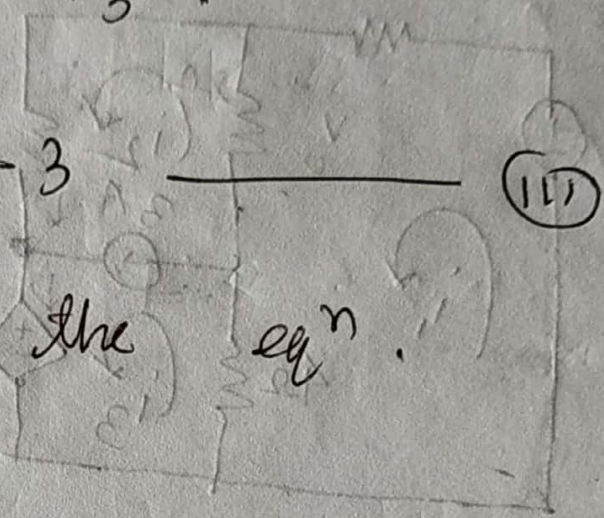

$$i_1 =$$

$$i_2 =$$


$$i_3 =$$

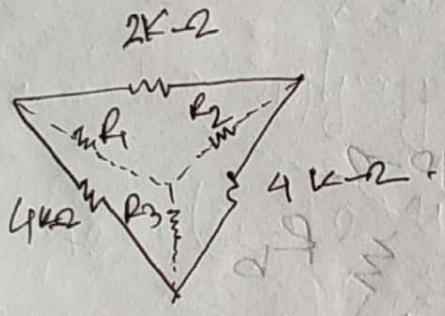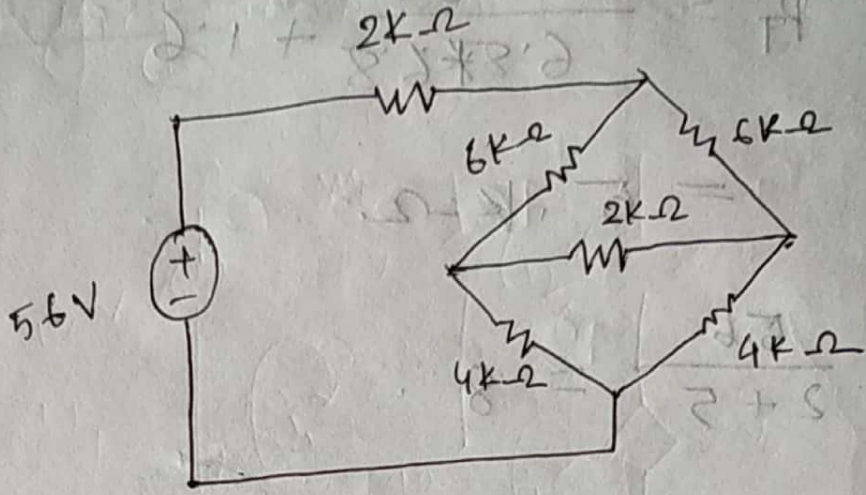

$$R_1 = \frac{4 \times 2}{4 + 2 + 4} = \frac{4}{5} \text{ k}\Omega = 0.8 \text{ k}\Omega$$

$$R_2 = \frac{4 \times 2}{4 + 2 + 4} = \frac{4}{5} \text{ k}\Omega = 0.8 \text{ k}\Omega$$
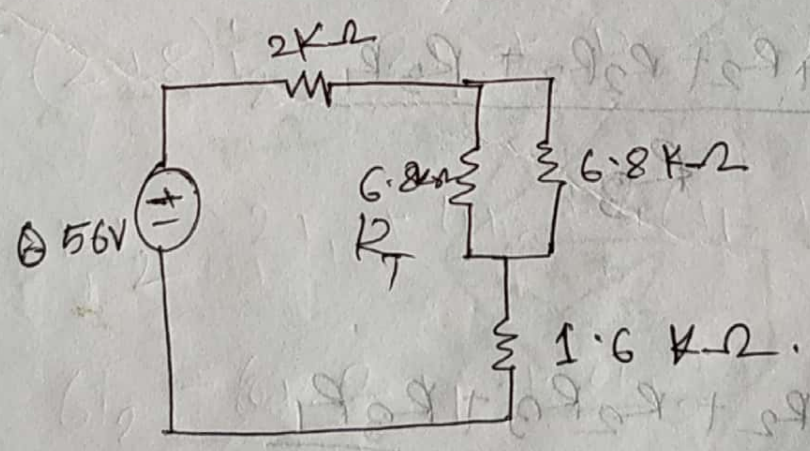
$$R_3 = \frac{4 \times 4}{4 + 4 + 2} = \frac{8}{5} \Omega = 1.6 \Omega$$




$$R_T = \frac{6.8 \times 6.8}{6.8 + 6.8} + 1.6$$

$$= 5.1 \text{ k}\Omega$$

$$i_o = \frac{56}{2 + 5} = 8$$

way to Delta:


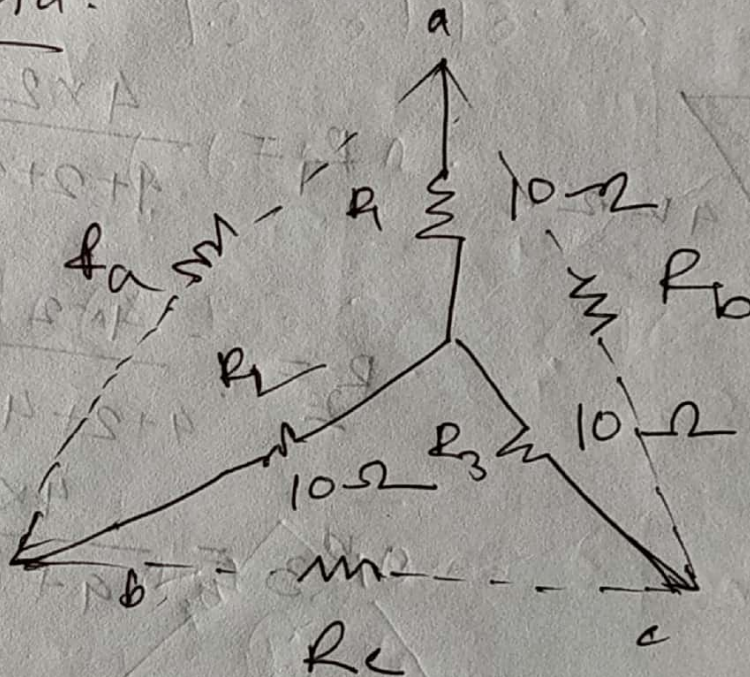


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

=

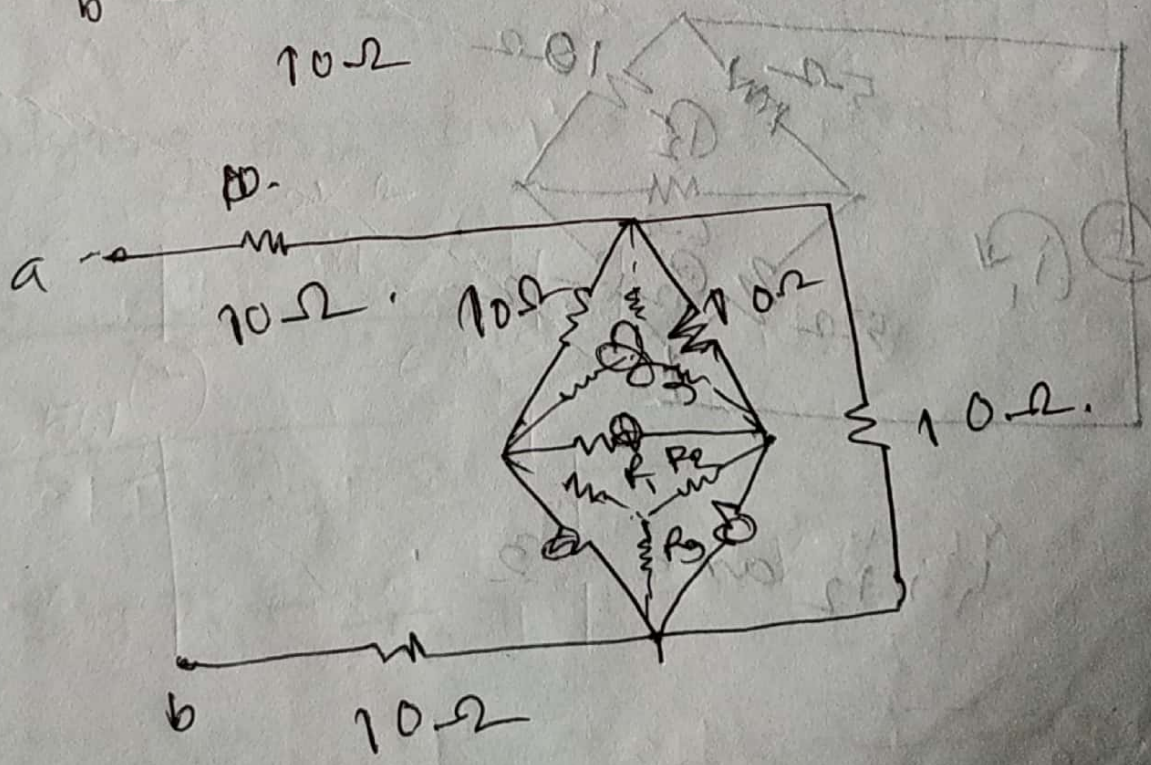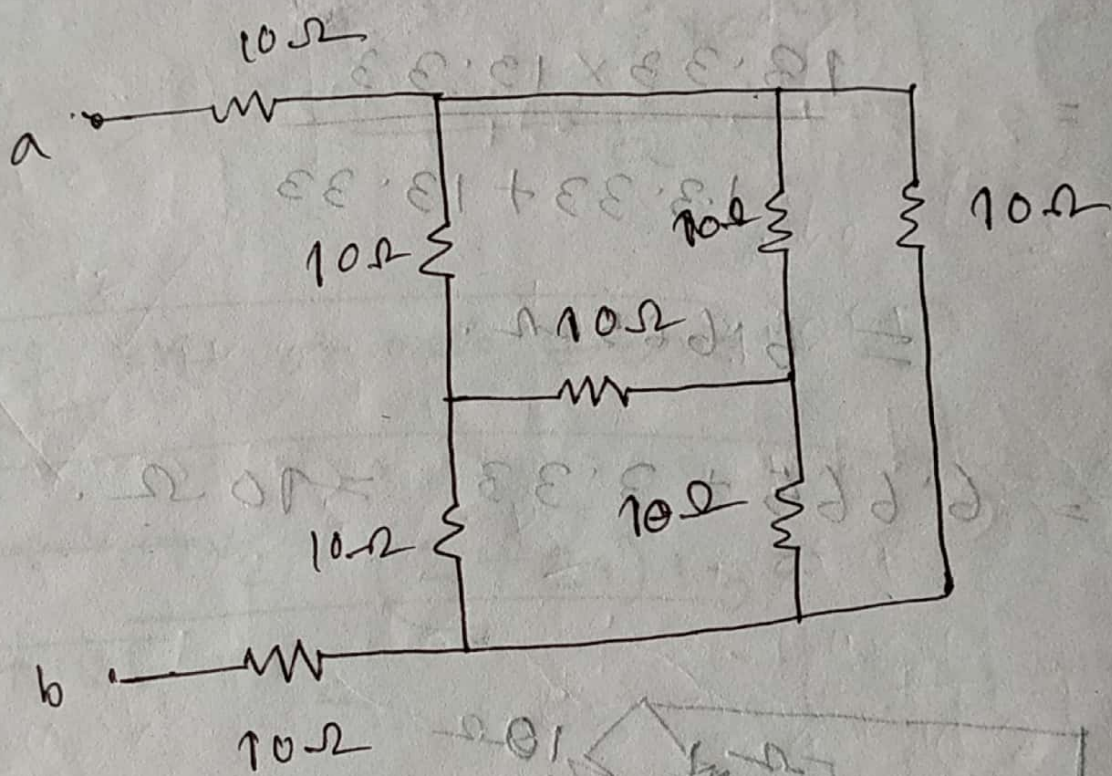


$$R_1 = \frac{10 \times 10}{30} = \frac{20}{30} = R_2 = R_3 = 3.33 \Omega$$

$$10 + R_1 = 13.33 \Omega$$


$$10 + R_2 = 13.33 \Omega$$

$$R = \frac{13.33 \times 13.33}{13.33 + 13.33} = 6.665 \Omega$$

$$R_T = 6.665 + 3.33 = 10 \Omega$$

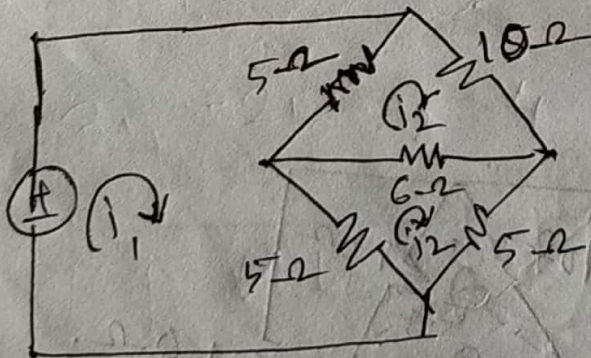

find i_1 , i_2 and i_3 .

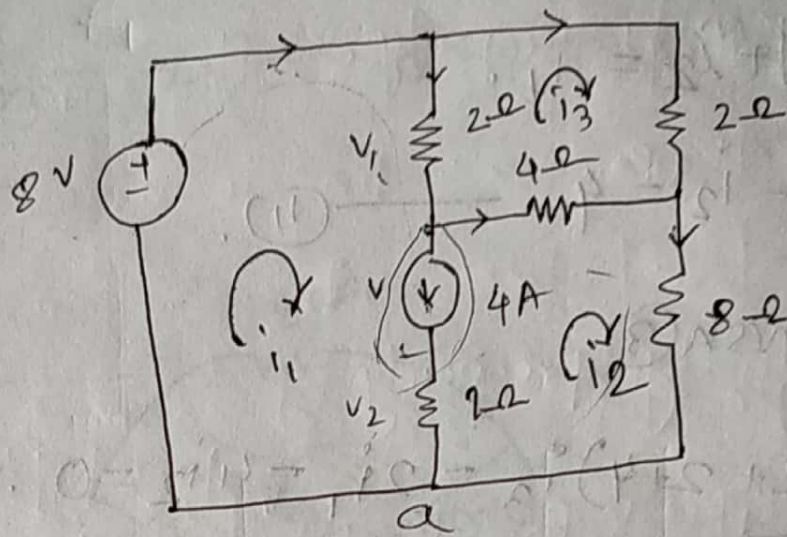

Use

applying KVL on mesh ① and ②

$$-8 + v_1 + v_2 + (2 + 2) i_3 = 8$$

$$-8 + 2v_1 + v_2 + 4i_3 = 8$$

applying KVL on meshes ① and ②

$$-8 + (2 + 4) i_3 + 8 i_2 = 0$$

$$\Rightarrow 6 i_3 + 8 i_2 = 8 \quad \text{--- ①}$$

$$-8 + 2 i_1 - 2 i_3 + (4 + 8) i_2 - 4 i_3 = 0$$

$$\Rightarrow 2 i_1 + 12 i_2 - 6 i_3 = 8 \quad \text{--- ②}$$

At node a, applying KCL,

$$4 + i_2 = i_1$$

$$\Rightarrow i_1 - i_2 = 4 \quad \text{--- (i)}$$

For mesh (iii),

$$(2 + 2 + 4)i_3 - 2i_1 - 4i_2 = 0$$

applying KVL on ~~node (a)~~ mesh (i),

$$-8 + 2i_1 + 4 + 0i_1 - 2i_3 - i_2 = 0$$

$$\Rightarrow 3i_1 - 2i_3 - i_2 = 4 \quad \text{--- (ii)}$$


applying KVL on mesh (ii),

$$-4 + 4i_2 + 8i_2 + i_2 - i_1 - 4i_3 = 0$$

$$\Rightarrow 13i_2 - i_1 - 4i_3 = 4 \quad \text{--- (iii)}$$

applying KVL on mesh (iii):

$$(2 + 2 + 4)i_3 - 2i_1 - 4i_2 = 0$$

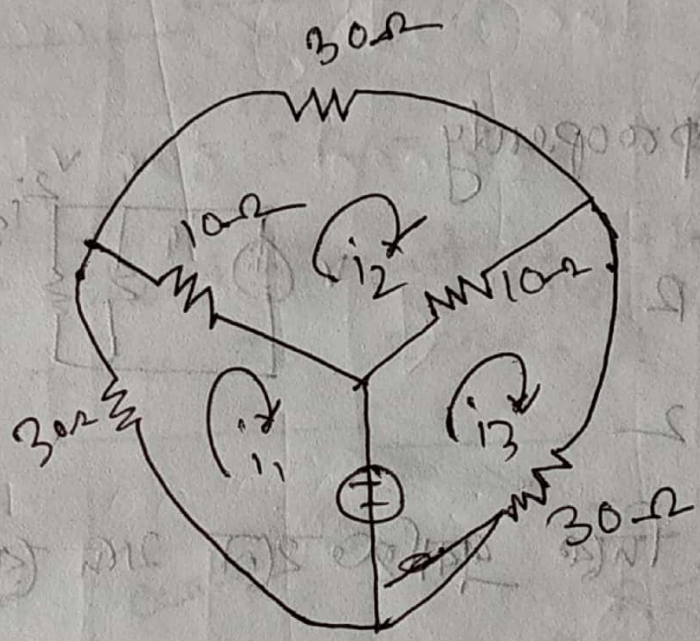

Linear circuit: (i) $KV = KI R$


(i) Homogeneity property: $i_1 + i_2$ (1 + 1 + 1)

$$KV = KI R$$

(ii) Additivity property


$$V = i_1 R + i_2 R$$

$$= V_1 + V_2$$

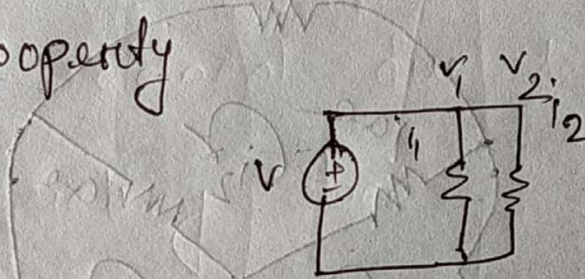


কারণে যেকোনো দিকে প্রবাহিত হলে মনে হোকিবে একই মতো
তাহলে নি Linear circuit.

Day 1

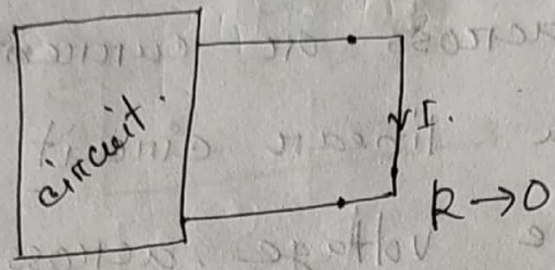

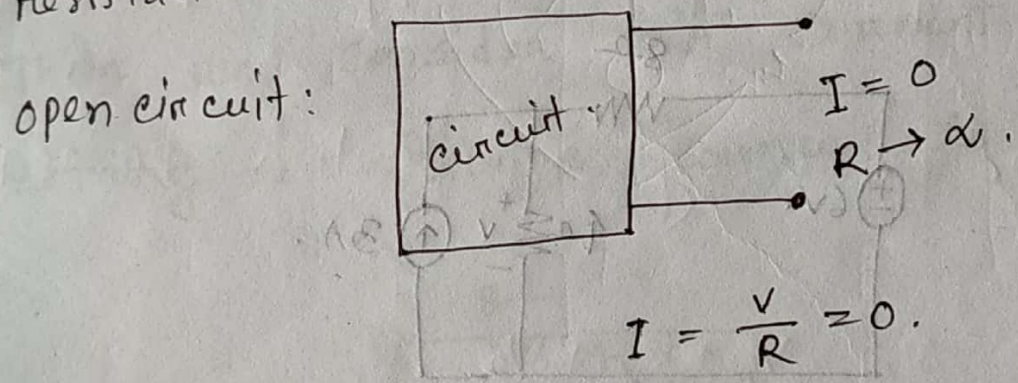Short circuit: short circuit is the circuit where resistance is tance to zero.




When we need to open current source or remove it we need to use open circuit. And when we need to remove voltage source we need to use short circuit.

VIN (P) / N
Date: / /
Page: /

Superposition theorem:

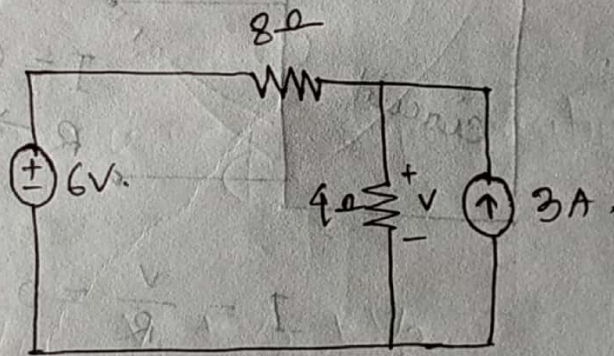The voltage across or current through an element in a linear circuit is the algebraic sum of the voltage across or current through that element due to each independent source acting alone.




V_1 for source 6V and V_2 for source 3A.

$$V = V_1 + V_2$$

At first, 3A current source is set to zero


We consider 6V voltage source.

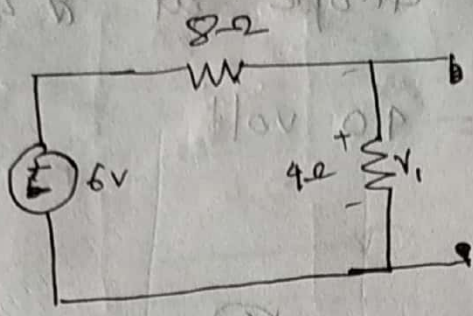

$$V_1 = \frac{4}{8+4} \times 6$$

$$= 2 \text{ volt}$$

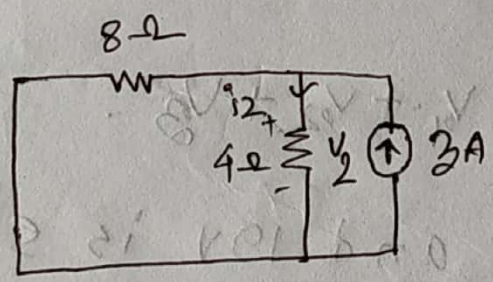
Then we consider 3A current source by setting 6v voltage source to zero.



$$i_2 = \frac{8}{8+4} \times 3$$

$$= 2 \text{ A}$$

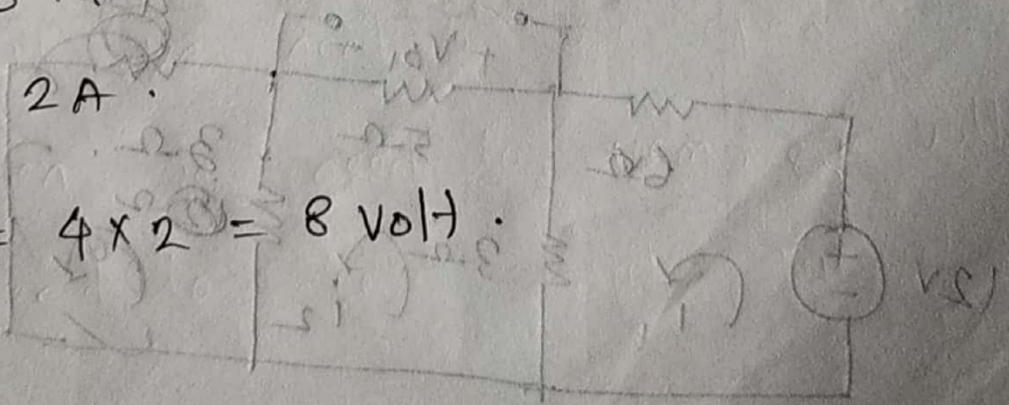
$$\therefore V_2 = 4 \times 2 = 8 \text{ volt}$$



∴ Total voltage drop at $4\ \Omega$,

$$V = 8 + 2 = 10 \text{ volt}$$

4.12

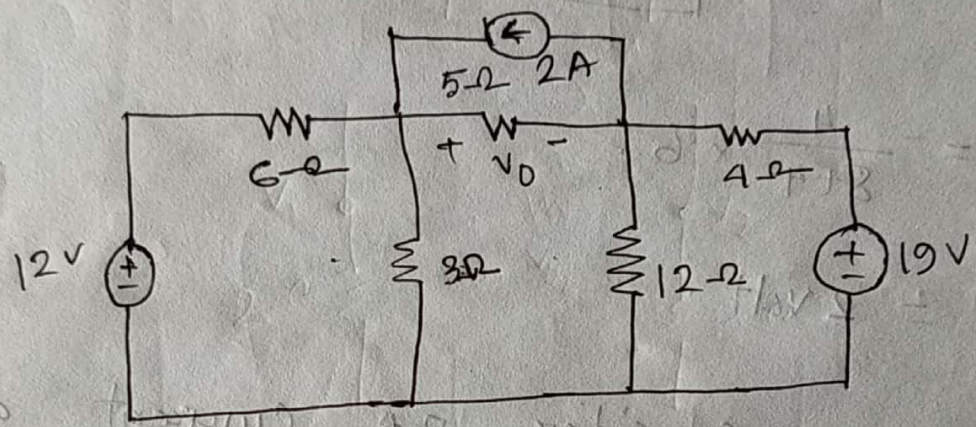


Determine V_0 using superposition principle.

Solⁿ


Here, $V_0 = V_{01} + V_{02} + V_{03}$.

At first, $2A$ and $19V$ is set zero.

We consider $12V$ source.

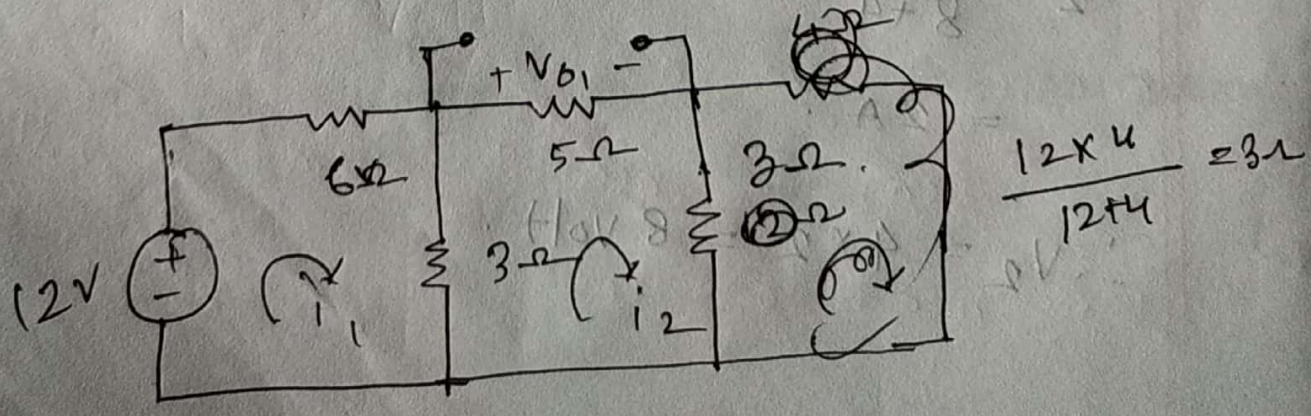


For loop 1, applying KVL,

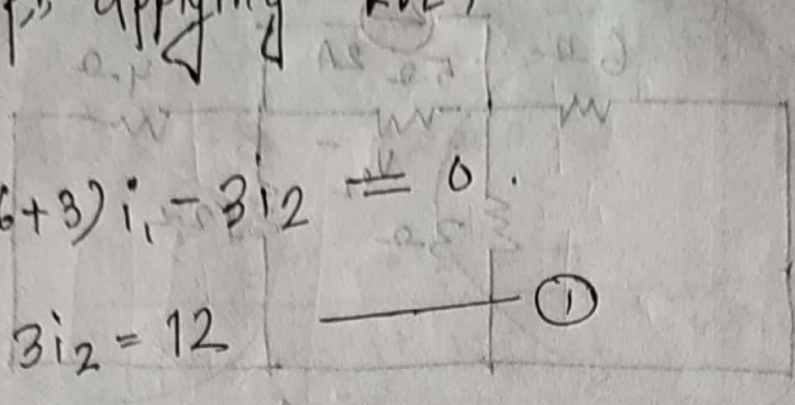

$$-12 + (6+3)i_1 - 3i_2 = 0$$

$$\Rightarrow 9i_1 - 3i_2 = 12$$

For loop 2, applying KVL,

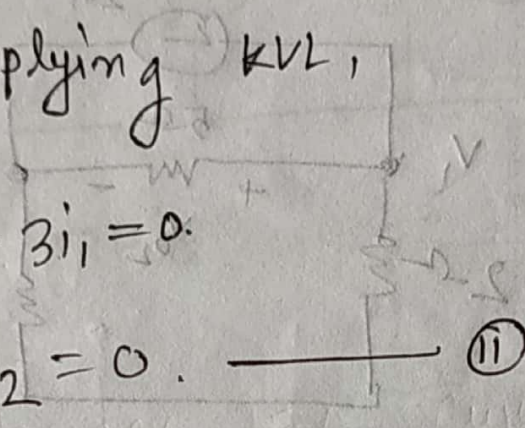

$$(3+5+3)i_2 - 3i_1 = 0$$

$$\Rightarrow -3i_1 + 11i_2 = 0$$

Solving the eqⁿ.




$$i_1 = 1.96$$

$$i_2 = 0.4A$$

$$V_{o1} = 5i_2 = 2V$$

We consider 2A source by setting 12V and

19V sources to zero.

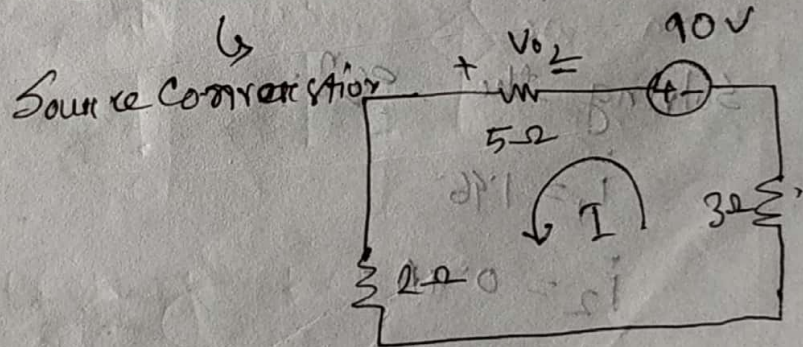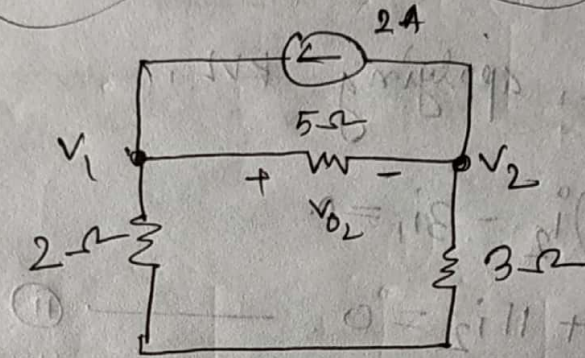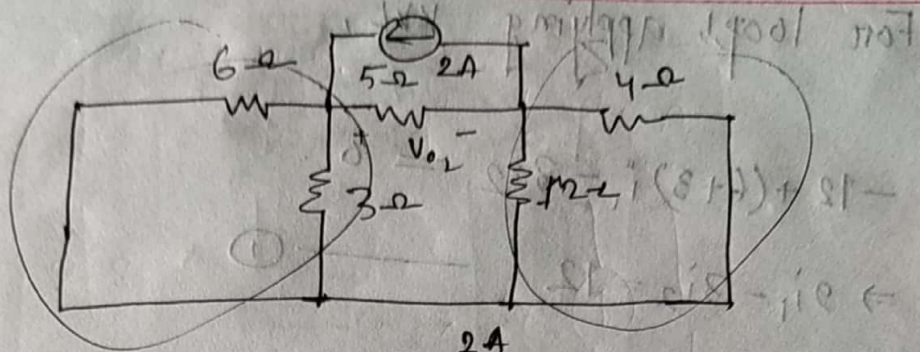


$$I = \frac{10}{2+5+3} = 1A$$


$$V = IR = 10V$$

$$V_{o2} = 5 \times 1 = 5 \text{ Volt}$$

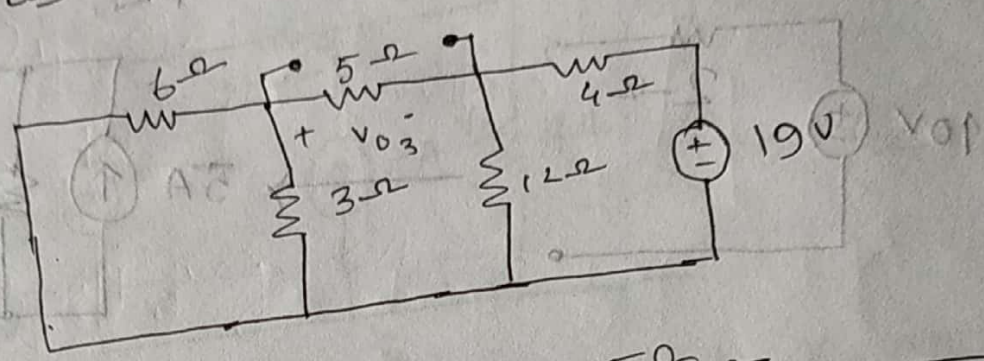We consider 19V source by setting 2A and 42V sources to zero.



For loop 1, we apply KVL,

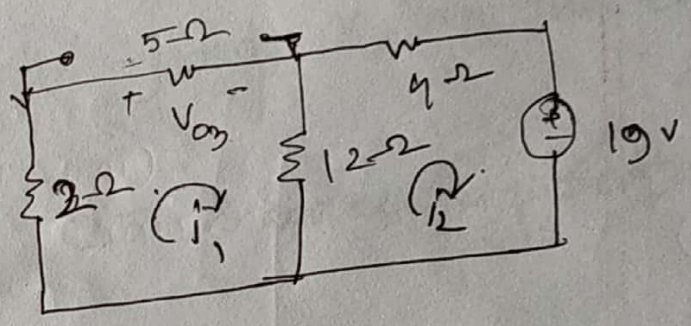

$$(2 + 5 + 12) i_1 - 12 i_2 = 0.$$

$$= 19 i_1 - 12 i_2 = 0. \quad \text{--- (1)}$$

For loop 2, we apply KVL,

$$(12 + 4) i_2 - 19 - 12 i_1 = 0.$$

$$\Rightarrow 16 i_2 + 19 - 12 i_1 = 0.$$

$$\therefore V_{03} = 7.125.$$


$$\Rightarrow -12 i_1 + 16 i_2 + 19 = 0.$$

$$\therefore i_1 = -1.425 \text{ A}$$

$$i_2 = -2.256 \text{ A}$$

Source conversion


$$I = \frac{V}{R} = 5A$$

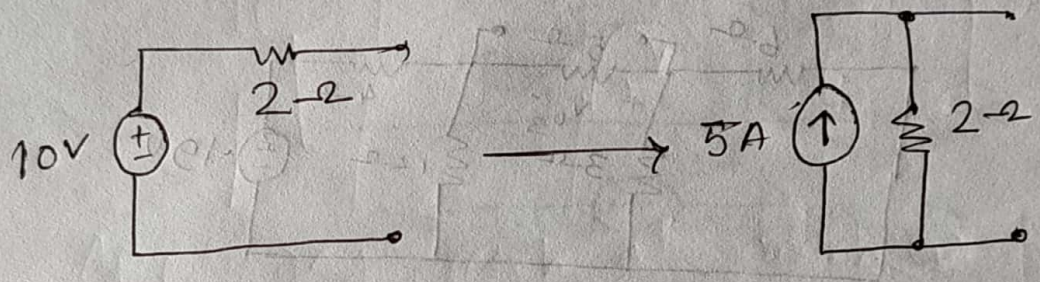

[Faint handwritten notes and diagrams, including circuit diagrams and mathematical expressions, are visible in this section.]

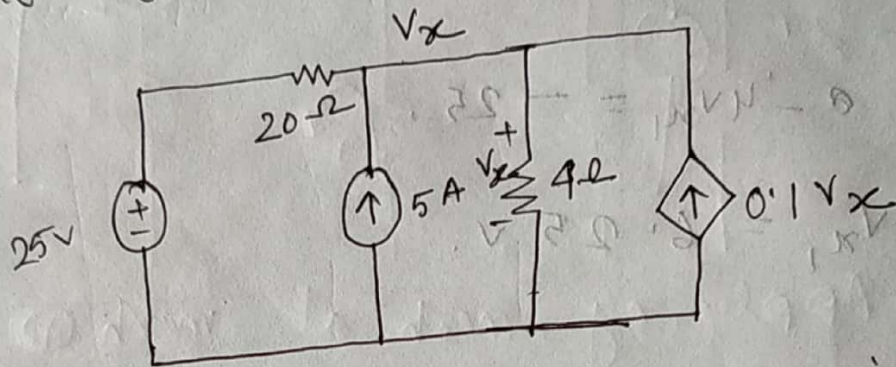
16.09.19
4th E

⊛ Dependent Source (अवलंबी) का प्रतिरोध (resistance) का मान ज्ञात करें।



Use superposition theorem to find V_x in the circuit

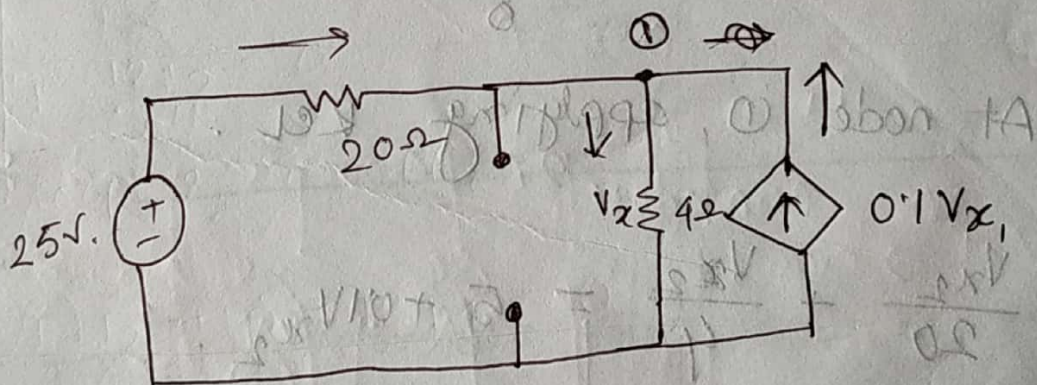Solⁿ: At first, we consider 25 source by setting 5A to zero.



At node 1, Applying KCL:



$$\frac{25 - V_{x1}}{20} + 0.1V_{x1} = \frac{V_{x1}}{4}$$

$$\Rightarrow \frac{25 - V_{x1}}{20} + 0.1V_{x1} - \frac{V_{x1}}{4} = 0$$

$$\Rightarrow \frac{25 - v_{x1} + 2v_{x1} - 5v_{x1}}{20} = 0$$

$$\Rightarrow -4v_{x1} = -25$$

$$v_{x1} = 6.25 \text{ V}$$

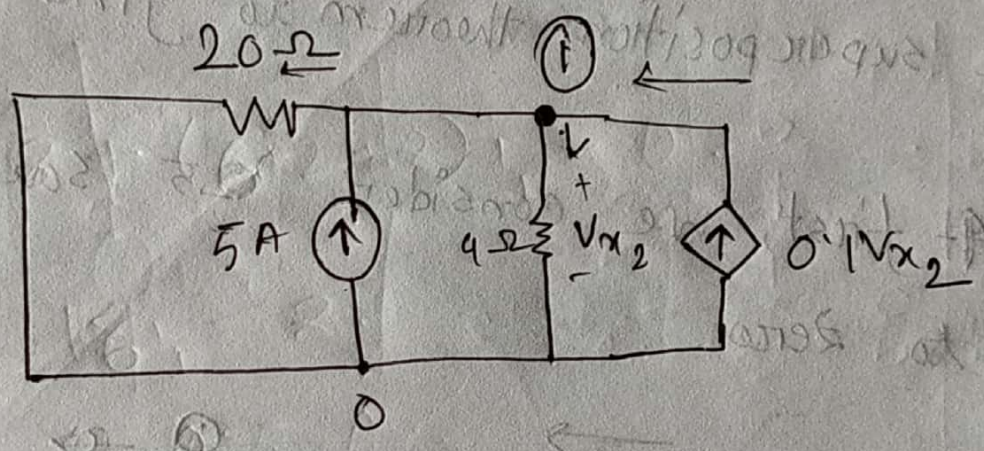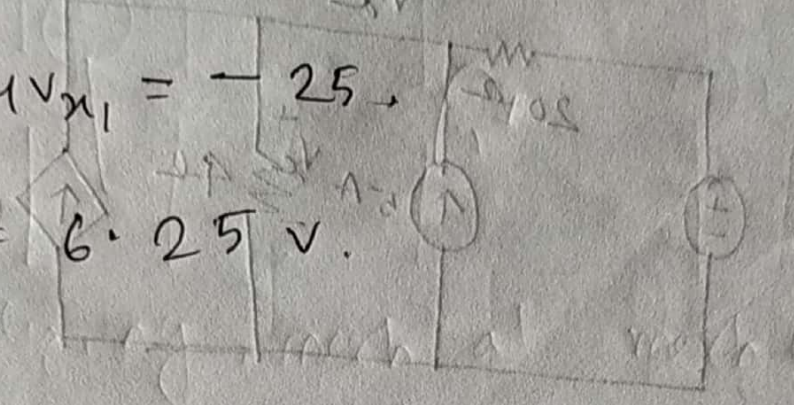

At node 1, applying KCL.

$$\frac{v_{x2}}{20} + \frac{v_{x2}}{4} = 5 + 0.1v_{x2}$$

$$\Rightarrow \frac{v_{x2}}{20} + \frac{v_{x2}}{4} - 5 - 0.1v_{x2} = 0$$

$$\Rightarrow \frac{v_{x2} + 5v_{x2} - 100 - 2v_{x2}}{20} = 0$$

$$\Rightarrow 4V_{x2} - 100 = 0$$


$$V_{x2} = 25 \text{ Volt}$$

$$\therefore V_x = V_{x1} + V_{x2}$$


$$= 6.25 + 25$$


$$= 31.25 \text{ Volt}$$

⊗

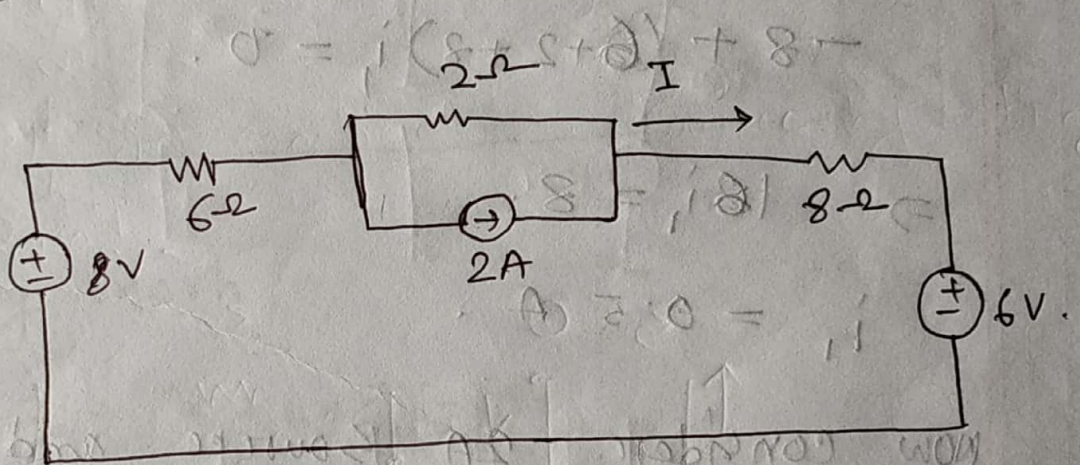

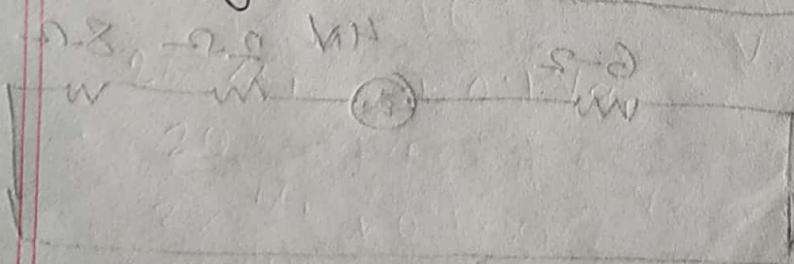
Soln: At first, we consider 8V source and setting 2A and 6V be zero.



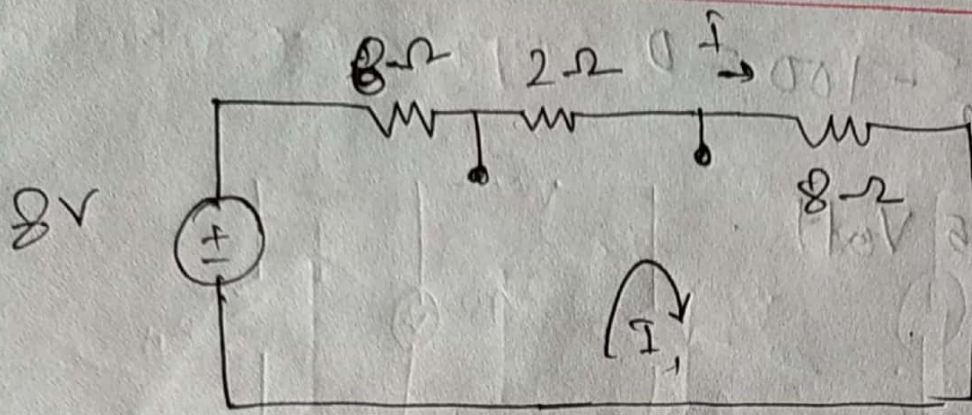



Applying mesh at mesh ①

$$-8 + (8 + 2 + 8)i_1 = 0$$

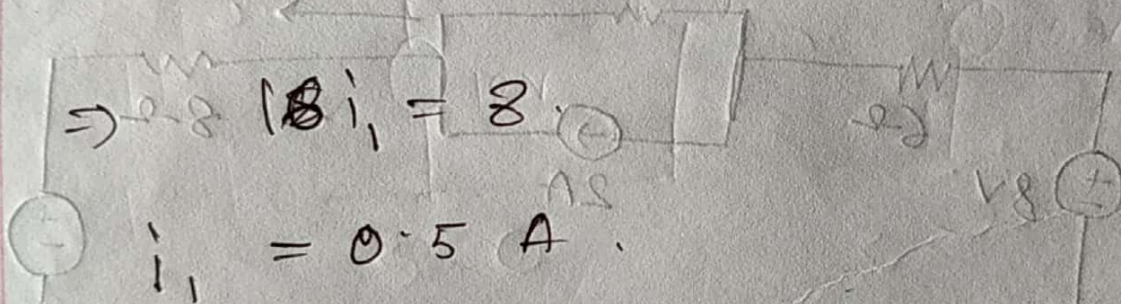

Now, consider 2A source and 8V and 6V

set zero,

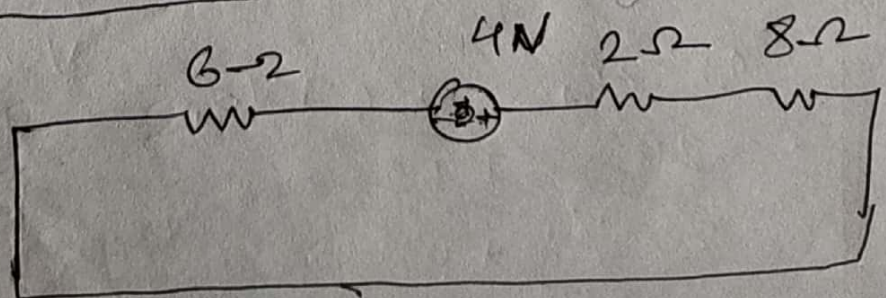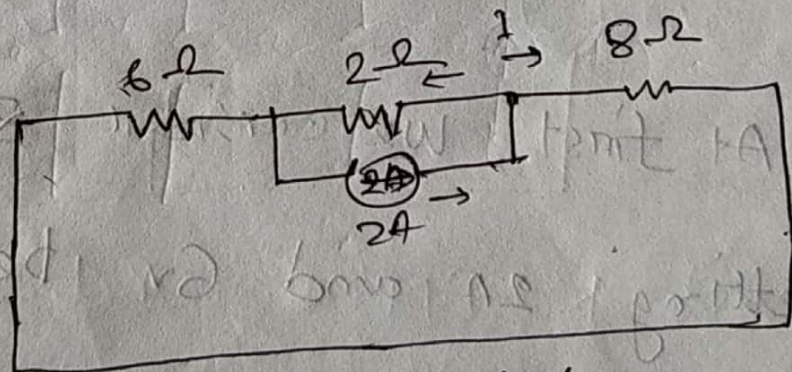


applying mesh,

$$-4 + (2 + 8 + 6)i_2 = 0$$

$$\Rightarrow 16i_2 = 4$$

$$\Rightarrow i_2 = 0.25$$

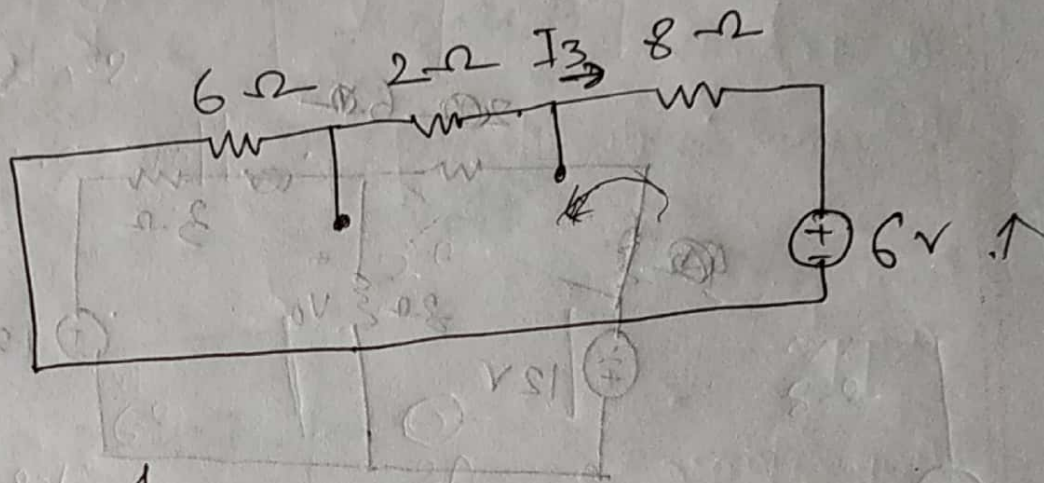

applying mesh,

$$-6 + (8 + 2 + 6)i_3 = 0$$




$$\Rightarrow 16i_3 = 6$$

$$\Rightarrow i_3 = -0.375$$


$$i = i_1 + i_2 + i_3$$

$$= -0.375 + 0.25 + 0.5$$
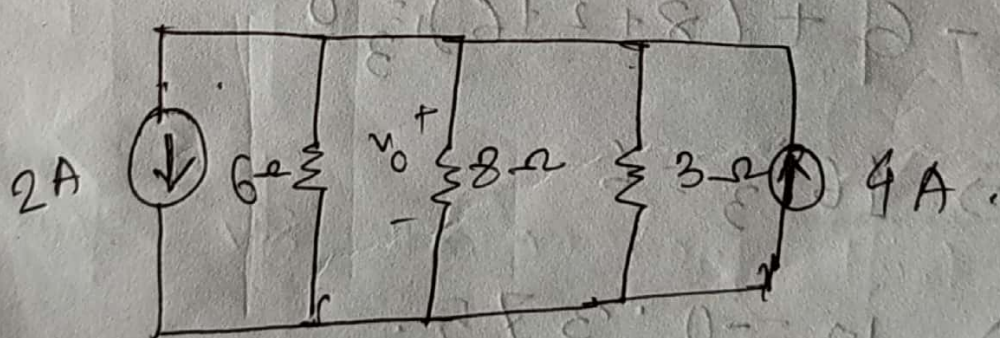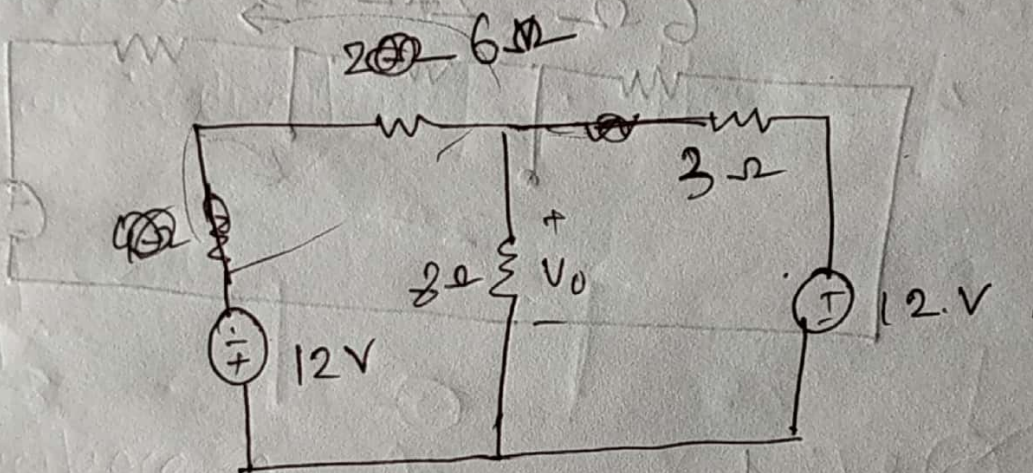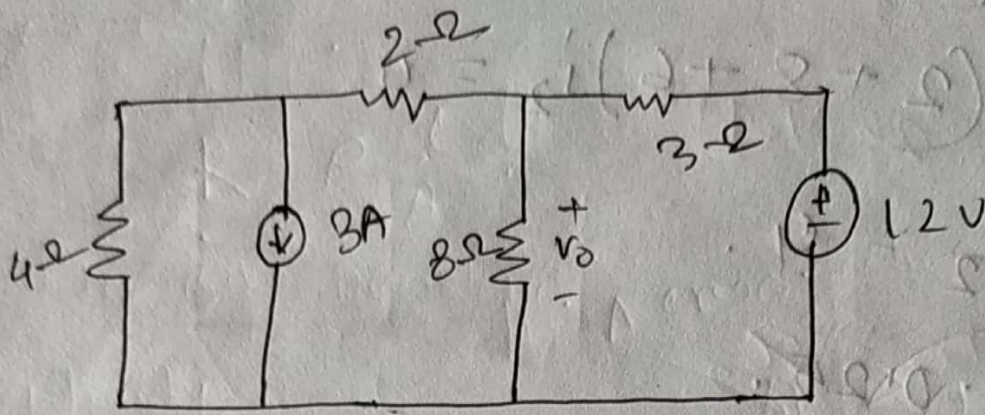
$$i = 1.125 \text{ A} - 0.375 \text{ A}$$



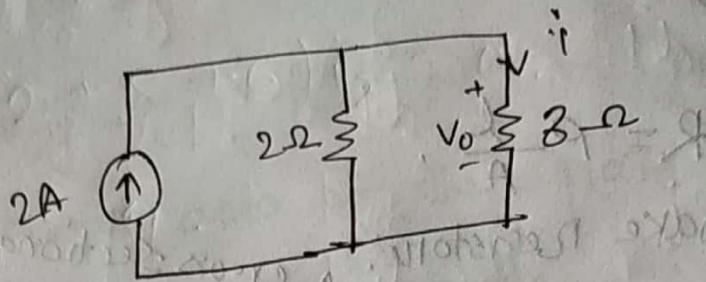
$4 - 2 = 2A$
 $6 \parallel 3 = \frac{6 \times 3}{6 + 3} = 2\Omega$



$$i = \frac{2}{2+8} \times 2 = 0.4 \text{ A}$$

$$V_0 = 0.4 \times 8 = 3.2 \text{ Volt}$$

$$E_x = 4.7, P.P = 4.7$$

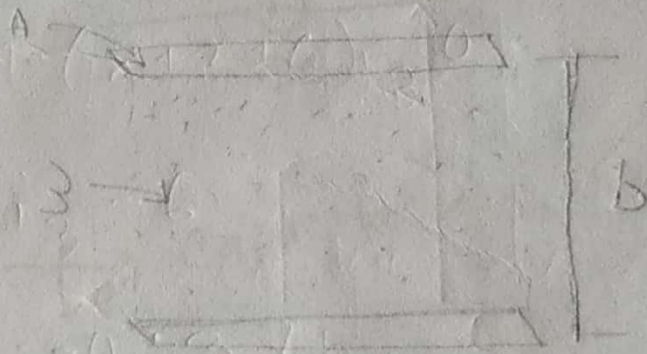

22.09.19
5th Day

Resistance


$$R = \rho \frac{l}{A}$$

consider to make Resistor: A cross sectional area.

(i) Resistivity


(ii) length

(iii) cross sectional area.

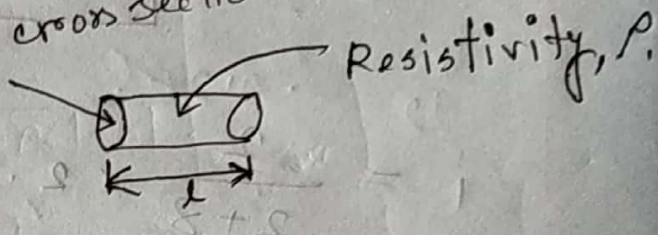

Cap

Capacitance

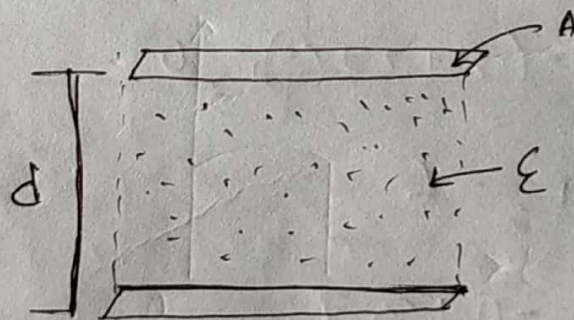

Permittivity
 ϵA → cross sectional area of each plate.

Electric field pass through medium, ϵ


$$\therefore C = \frac{\epsilon A}{d}$$

Permittivity is the property to pass electric flux through a medium.

Q.1) what factors we consider during make a capacitor

- (i) permittivity.
- (ii) cross sectional area of the plate.
- (iii) distance between two plate.

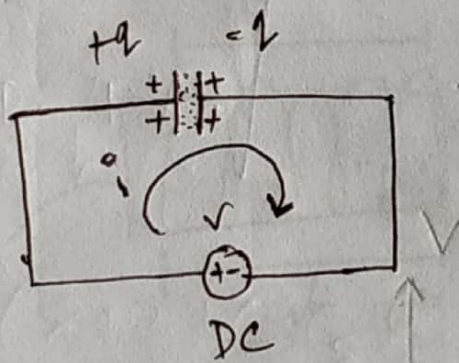Q.2) A capacitor consist of two parallel plate and separate from a dielectric medium.



$$Q \propto V$$

$$\therefore Q = CV$$

$$C = \frac{Q}{V}$$

Capacitance

$$C = \frac{Q}{V} = \frac{\epsilon \frac{Q}{d}}{\frac{Q}{d}} = \epsilon$$

What will be happen if $d \ll \epsilon$ is
 capacitance of any capacitor does not
 change.

$$i = \frac{dq}{dt} = \frac{d}{dt} cv$$


$$\therefore i = c \cdot \frac{dv}{dt}$$

For DC voltage, $v = \text{constant}$.

$$\therefore i = 0 \quad [\text{open circuit}]$$

⊕ Capacitor acts like an open circuit

in DC source.

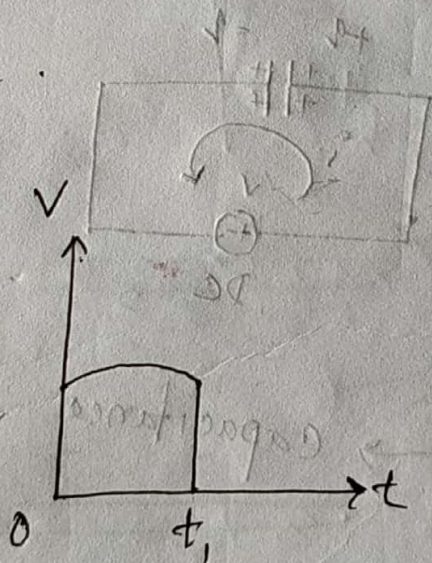

$$i = c \cdot \frac{dv}{dt}$$

$$dt = t_1 - t_0$$

$$dt \rightarrow 0$$

$$Z = \frac{1}{j\omega c} = 0$$

$$Z = \frac{1}{j2\pi f c}$$


in DC frequency 0, $f = 0$

$$\text{Reactance} \cdot Z = \frac{1}{0} = \infty$$


Why capacitor can not change its voltage abruptly / instantaneously?

Inductor store energy in magnetic field.

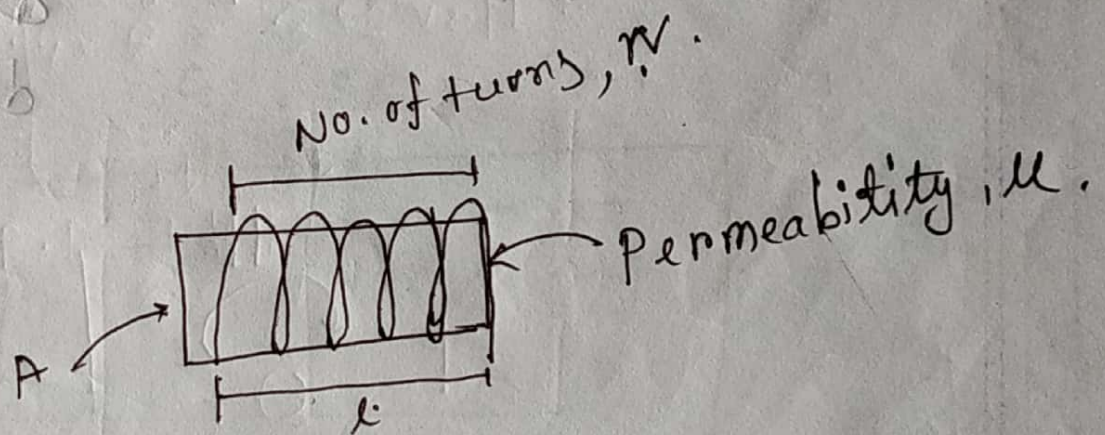Inductor: An inductor consists of a coil of conducting wire.



$$L = \frac{N^2 \mu A}{l}$$

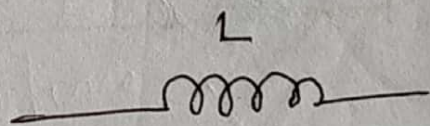

$$V = L \cdot \frac{di}{dt}$$

Inductor acts like a short circuit to DC.

$$V = L \cdot \frac{di}{dt} = L \cdot \frac{d}{dt} (\text{constant}) = 0$$

DC

Q. Why an inductor can not change its current abruptly / instantaneously?



$$V = L \cdot \frac{di}{dt}$$

$$V = L \cdot \frac{di}{0}$$

$$V \rightarrow \infty$$

$$dt = t_1 - t_0$$

$$dt \rightarrow 0$$

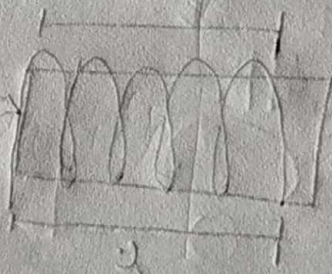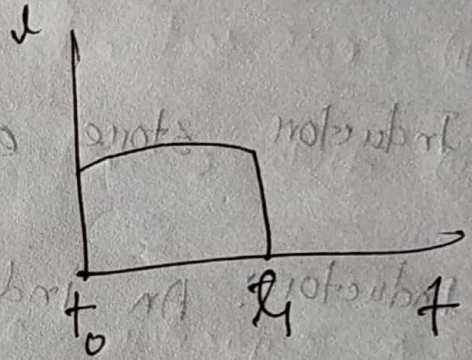

$$L = \frac{\mu_0 n^2 A l}{\mu_0}$$

$$V = L \cdot \frac{di}{dt}$$


E.

$$q = CV \quad q = CV.$$

$$i = \frac{dq}{dt}$$

$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int i dt$$

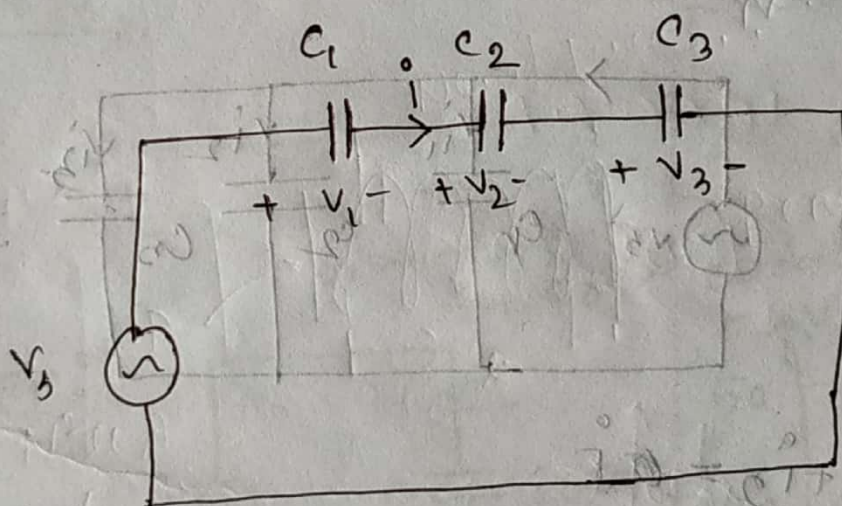

applying KVL.


$$V_3 = V_1 + V_2 + V_3$$
$$= \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt + \frac{1}{C_3} \int i dt$$

$$= \int i dt \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$
$$= \frac{1}{C_{eq}} \int i dt$$

⊕ Current:

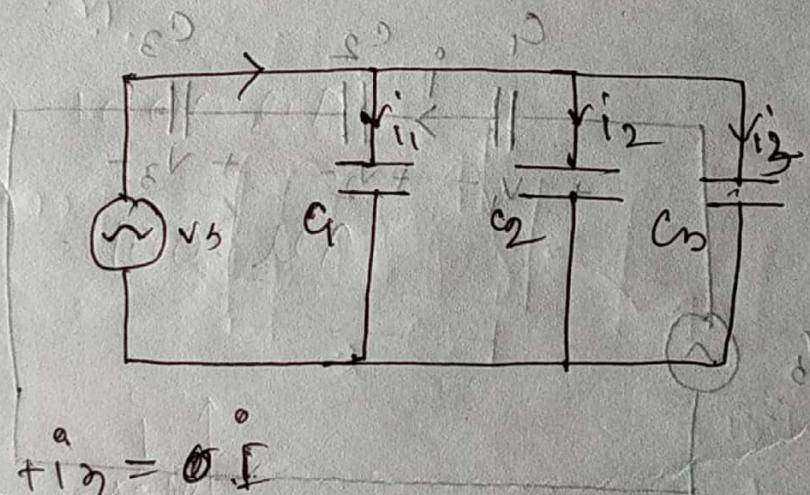- (i) conduction
- (ii) convection
- (iii) Displacement.

$$\otimes \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad ; \quad \dots = i$$



$$i_1 + i_2 + i_3 = i$$

$$= C_1 \frac{dv_s}{dt} + C_2 \frac{dv_s}{dt} + C_3 \frac{dv_s}{dt} = i$$



$$\Rightarrow \frac{dv_s}{dt} [C_1 + C_2 + C_3] = i$$

$$\therefore C_{eq} \frac{dv_s}{dt} = i \quad \left[C_{eq} = C_1 + C_2 + C_3 \right]$$

$$V = IR$$

$$R = \frac{V}{I}$$
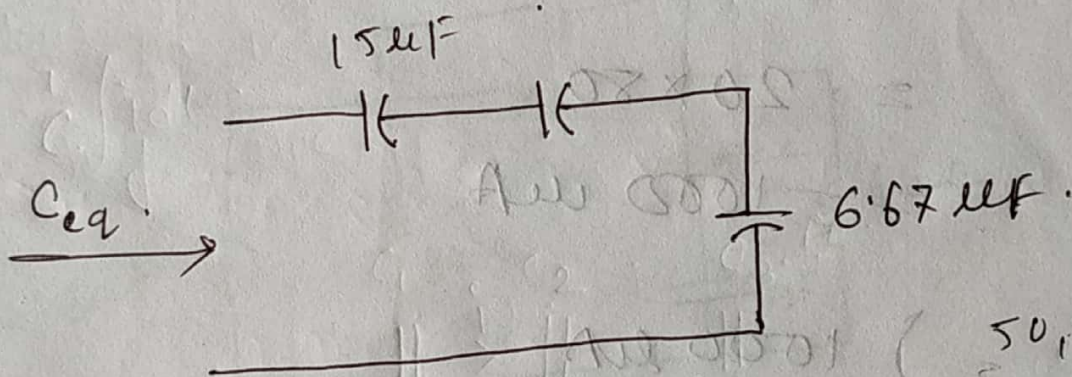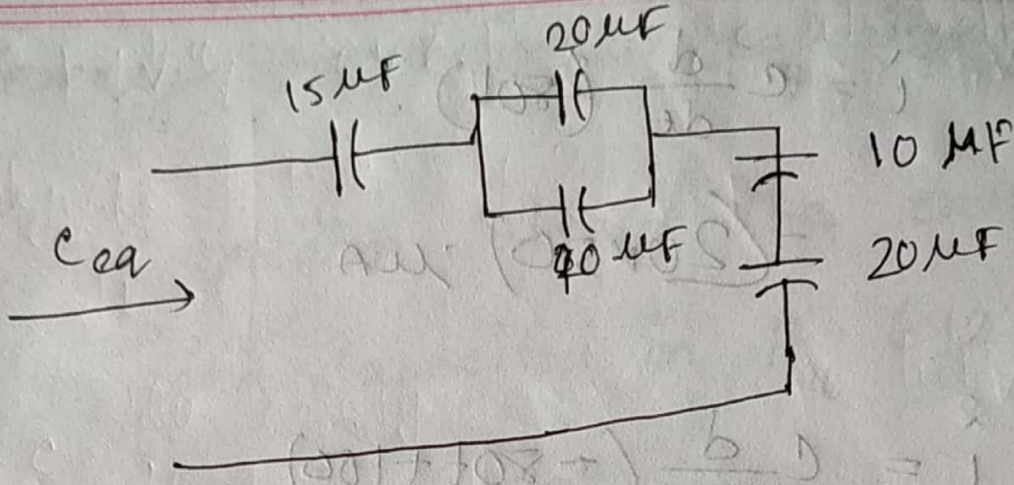
$$\frac{1}{R} = \frac{1}{10} + \frac{1}{20} = \frac{2+1}{20} = \frac{3}{20}$$



$$x + 50 = 50 - 50$$



$$\Rightarrow x + 50 = 0$$

$$\Rightarrow 50x = 100 = 50$$

$$\frac{x - 50}{50} = \frac{y - 10}{50 - 2}$$

$$\frac{x - 50}{50} = \frac{y - 1}{-1}$$

Inductor:

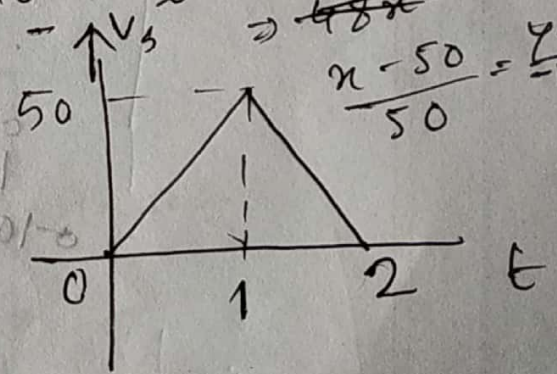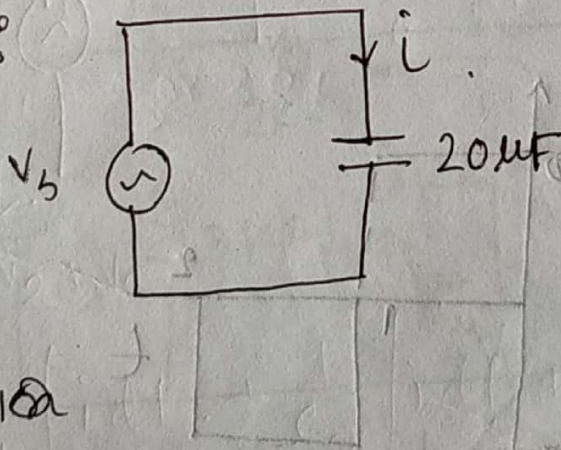

Find i and i_a

$$V_s = \begin{cases} 50t & 0 < t < 1 \\ -50t + 100 & 1 < t < 2 \end{cases}$$

$$i = c \frac{d}{dt} (180t)$$


$$= (20 \times 50) \mu A$$

$$i = c \frac{d}{dt} (-80t + 100)$$

$$= -20 \times 80$$

$$= -1000 \mu A$$

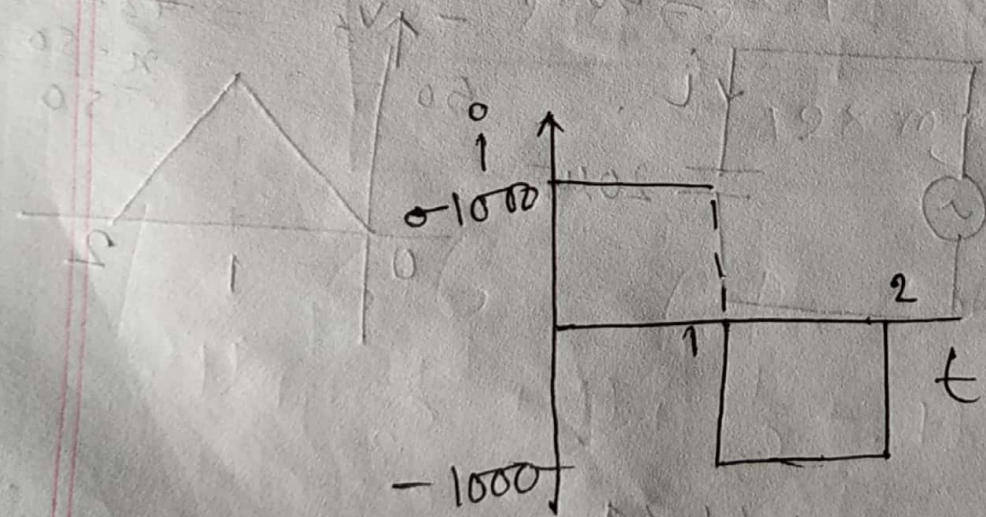
$i = \left. \begin{matrix} 1000 \mu A \\ -1000 \mu A \end{matrix} \right\}$



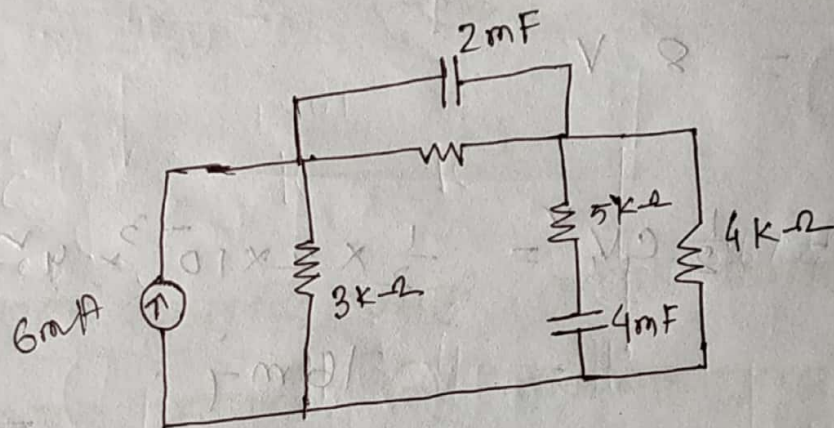
24.09.19
6th P

The energy stored in a capacitor $w = \frac{1}{2} CV^2$.

* Under DC condition, obtain the energy stored in each capacitor in Fig 6.12.



Soln.

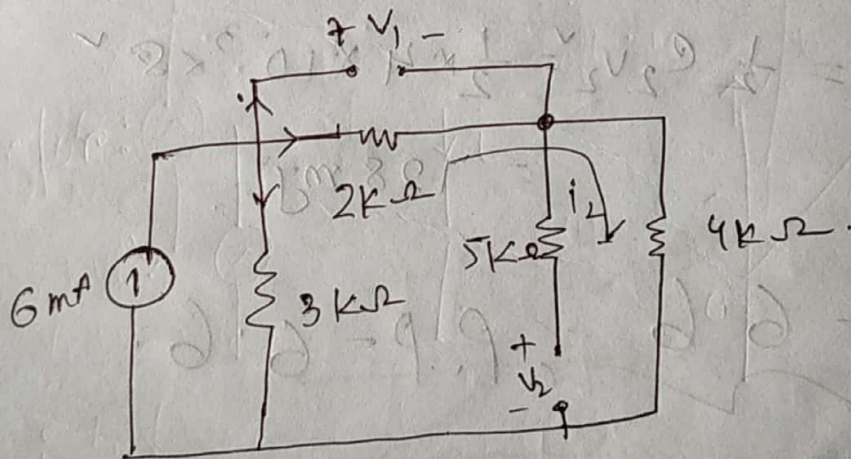

Applying current divider rule,

$$i_2 = \frac{3}{3+2+4} \times 6$$


$$= 1.8 \text{ mA} \cdot 2 \text{ mA}$$

$$V_1 = 2 \times 10^3 \times 2 \times 10^{-3}$$

$$V_1 = 4 \text{ V}$$

$$V_2 = 4 \times 10^3 \times 2 \times 10^{-3}$$

$$= 8 \text{ V}$$

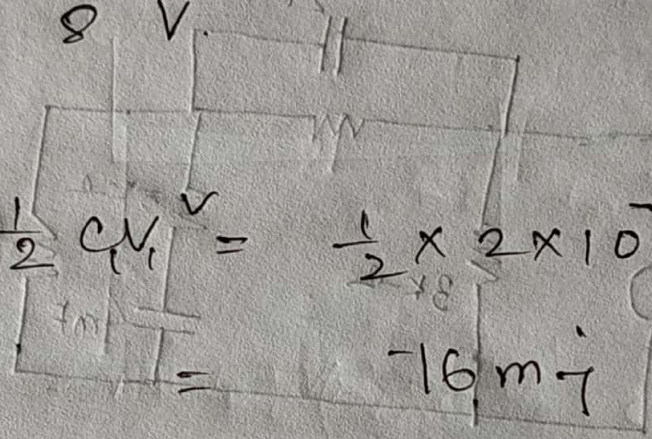


$$\therefore W_1 = \frac{1}{2} C_1 V_1^2 = \frac{1}{2} \times 2 \times 10^{-3} \times 4^2$$

$$W_2 = \frac{1}{2} C_2 V_2^2 = \frac{1}{2} \times 4 \times 10^{-3} \times 8^2$$

$$= 128 \text{ mJ}$$

Ex - 6.6

$$P.P = 6.6$$

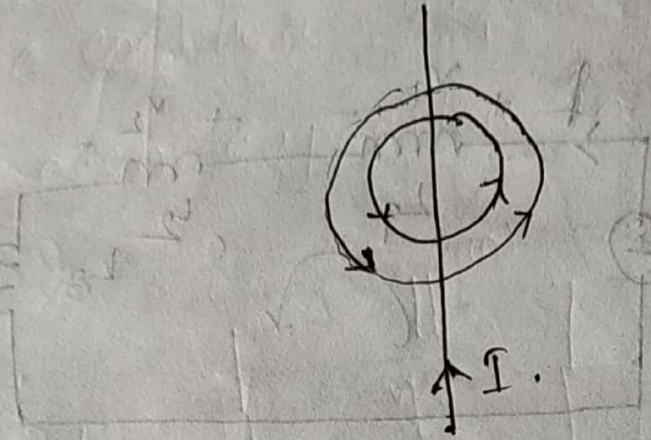


যদি কারেন্ট ক্রমাগতঃ তরক কোনো স্যামান্টিক ফিল্ড
 স্যামান করা হয় তাকে কিছু পরিমলন লক্ষ্য ব পাওয়া

যদি

$$C = N \frac{d\Phi}{dt}$$


$$L = \frac{N^2 \mu A}{l}$$

$$V = L \cdot \frac{dI}{dt}$$

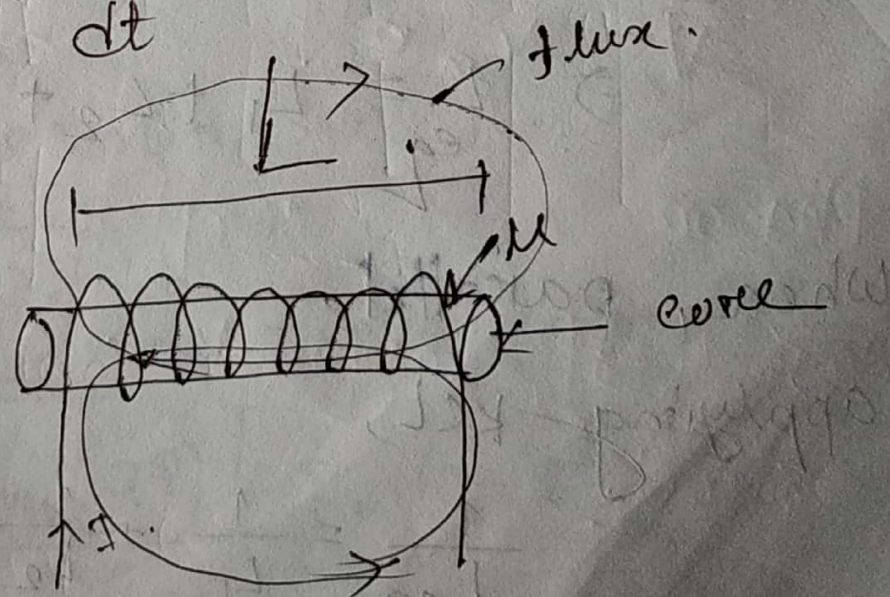

* Permiability ~~is~~ বেশি থলে কোরেট
 (যদি)

$$e = L \cdot \frac{dI}{dt}$$

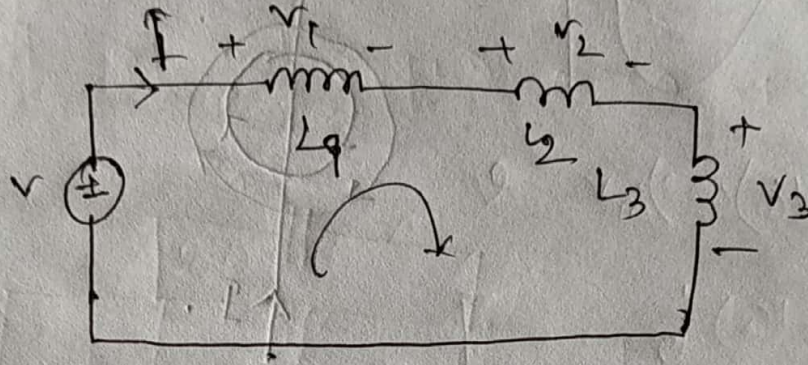

Applying KVL

$$-v + v_1 + v_2 + v_3 = 0$$

$$\Rightarrow v = v_1 + v_2 + v_3$$

$$= L \cdot \frac{dI}{dt} = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} + L_3 \frac{dI}{dt}$$

$$\Rightarrow L_{eq} = L_1 + L_2 + L_3$$

When parallel,

applying KCL,

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$


22/09/19
G+K D.1

$x + iy$

AC Circuit

Complex number, $z = x + jy$.



Rectangular

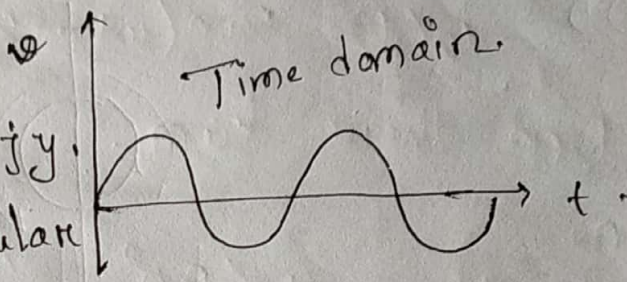

Time domain

$= r \angle \phi$, $r = \sqrt{x^2 + y^2}$.

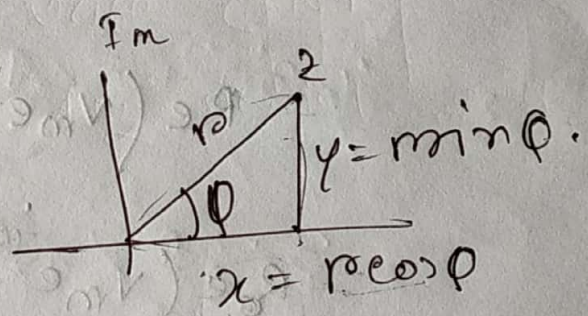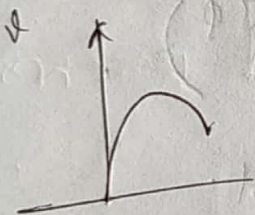Polar form, $\phi = \tan^{-1} \frac{y}{x}$.




$= r (\cos \phi + j \sin \phi)$.

~~$r (\cos \theta + j \sin \theta)$~~
 $= e^{j\theta}$

$= \boxed{r e^{j\phi}}$ Exponential form.

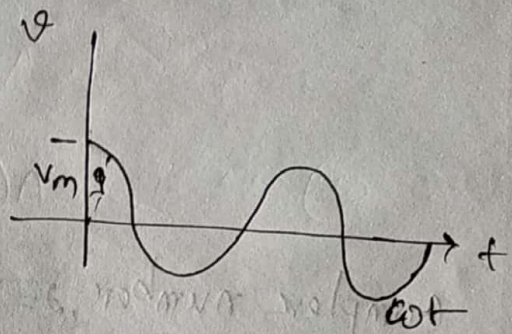$= \underline{\underline{Re(r e^{j\phi})}} + \underline{\underline{Im(r e^{j\phi})}}$



$$v = v_m \cos(\omega t + \phi).$$

$$= \text{Re} \left[v_m e^{j(\omega t + \phi)} \right].$$

$$= \text{Re} (v_m e^{j\omega t} \cdot e^{j\phi}).$$

$$= \text{Re} (v_m e^{j\phi} \cdot e^{j\omega t}).$$

$$\bar{V} = v_m e^{j\phi}$$

Phasor is a complex number which consists of magnitude and phase of a sinusoid.

$$v(t) = v_m \cos(\omega t + \phi)$$

$$\bar{V} = v_m \angle \phi$$

$$\text{Ex: } v(t) = 5 \cos(\omega t + 30^\circ)$$

$$\bar{V} = 5 \angle 30^\circ$$

$$\text{Ex } v = 7 \cos(2t + 40^\circ)$$

$$i = 4 \sin(10t + 10^\circ)$$

$$i = 2 \sin(5t + 50^\circ)$$

$$\Rightarrow \bar{V} = 7 \angle 40^\circ \text{ volt}$$

$$\bar{I}_1 = 4 \angle (90^\circ + 10^\circ + 10^\circ)$$

$$= 4 \angle 110^\circ$$

or

$$\bar{I}_1 = 4 \angle 100^\circ \text{ A}$$

$$i = 2 \cos(5t + 50^\circ - 90^\circ)$$

$$\bar{I} = 2 \angle -40^\circ \text{ A}$$

Ex 9.6 :

$$i_1(t) = 4 \cos(\omega t + 30^\circ) \cdot A$$

$$i_2(t) = 5 \sin(\omega t - 20^\circ) A = 5 \cos(\omega t - 20 - 90^\circ)$$

Find their sum.

solⁿ: $\bar{I}_1 = 4 \angle 30^\circ \cdot A$

$$\bar{I}_2 = 5 \angle -110^\circ \cdot A$$

$$\bar{I}_1 + \bar{I}_2 = 4 \angle 30^\circ + 5 \angle -110^\circ$$

$$= 3.22 \angle -56.97^\circ$$

$$v(t) = V_m \cos(\omega t + \phi)$$

Time-domain

$$\underline{V} = V_m \angle \phi$$

phasor domain

$$v = iR \rightarrow \text{Resistor}$$

$$i = C \frac{dv}{dt} \rightarrow \text{capacitor}$$

$$v = L \frac{di}{dt} \rightarrow \text{inductor}$$

$$\underline{I}(\omega) = \frac{i_b}{H_b}$$

$$\frac{\underline{V}}{\omega C} = i_b v$$

$$(\omega + \omega) \sin \frac{mV}{\omega} = i_b v$$

$$(\omega + \omega) \cos \frac{mV}{\omega} =$$

$$\frac{dv}{dt} = -V_m \sin(\omega t + \phi) \omega$$

$$= \omega V_m \cos(\omega t + \phi + 90^\circ)$$

$$= \omega V_m \cos e^{j(\phi + 90^\circ)} e^{j\omega t}$$

$$= \omega V_m \cdot e^{j\phi} \cdot e^{j90^\circ} \cdot e^{j\omega t}$$

$$= j\omega V_m e^{j\phi} e^{j\omega t}$$

$$= \text{Re}(j\omega V_m \angle \phi) e^{j\omega t}$$

$$\begin{aligned} e^{j90^\circ} &= \cos 90^\circ + j \sin 90^\circ \\ &= 0 + j \cdot 1 \\ &= j \end{aligned}$$

$$\frac{dV_m}{dt} = j\omega \bar{V}$$

$$\frac{di}{dt} = j\omega \bar{I}$$

$$\int v dt = \frac{\bar{V}}{j\omega}$$

$$\int v dt = \frac{V_m}{\omega} \sin(\omega t + \phi)$$

$$= \frac{V_m}{\omega} \cos(\omega t + \phi - 90^\circ)$$


$$= \frac{V_m}{\omega} \cdot e^{-j(\phi - 90^\circ)} e^{j\omega t}$$

$$= \text{Re} \left(-j \cdot \frac{V_m}{\omega} \angle \phi \right) e^{j\omega t}$$

$$= \text{Re} \left(-j \frac{j}{j\omega} \frac{V_m}{\omega} \angle \phi \right) e^{j\omega t}$$


$$= \text{Re} \left(\frac{V_m}{j\omega} \angle \phi \right) e^{j\omega t}$$
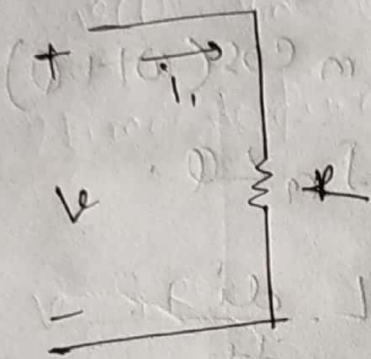
$$\frac{d}{dt} \int v dt = \frac{\bar{V}}{j\omega}$$



$$i = I_m \cos(\omega t + \phi)$$


$$\bar{I} = I_m \angle \phi$$

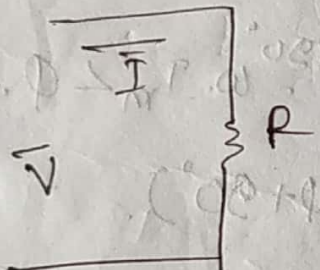

$$\bar{V} = \bar{I} R$$


$$V_m = R I_m \angle \phi$$

Phase diagram of a resistor

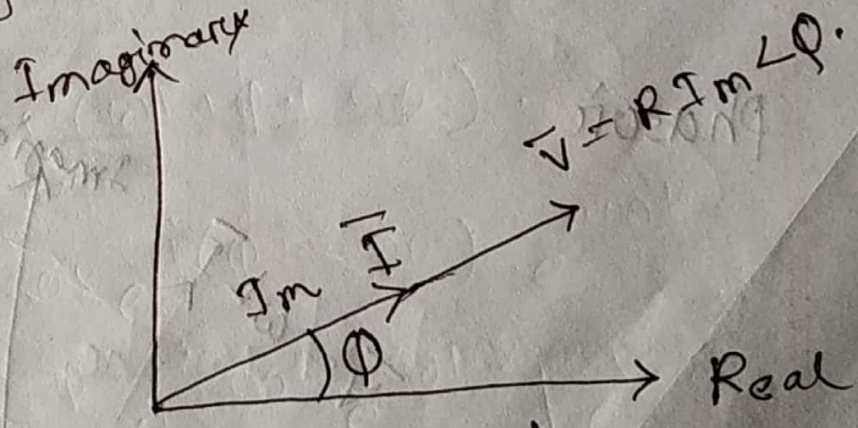

Resistor voltage

current is phase

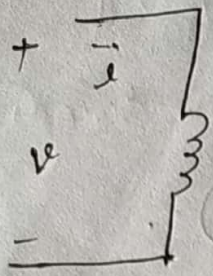

$$i = I_m \cos(\omega t + \phi)$$

$$I = I_m \angle \phi$$

$$V = L \frac{di}{dt}$$

$$= L \cdot j\omega \cdot I_m \angle \phi$$


$$= L \cdot e^{j90^\circ} \cdot \omega \cdot I_m \angle \phi$$

$$\bar{V} = \omega L \cdot I_m e^{j(\phi + 90^\circ)}$$

$$\bar{V} = \omega L \cdot I_m \angle \phi + 90^\circ$$

Phasor


Imaginary axis

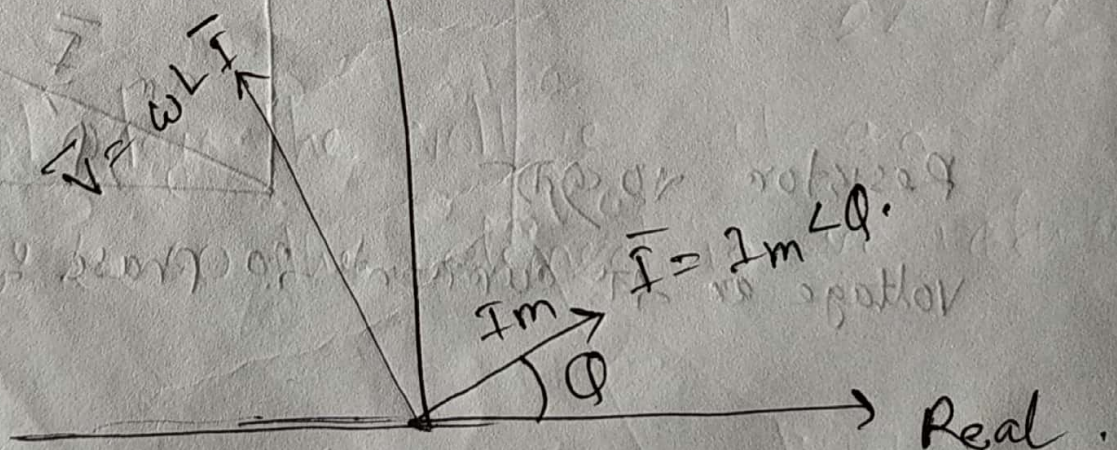


inductor a current and voltage out of phase a 90°

Phase 90° (for inductor) - 2A

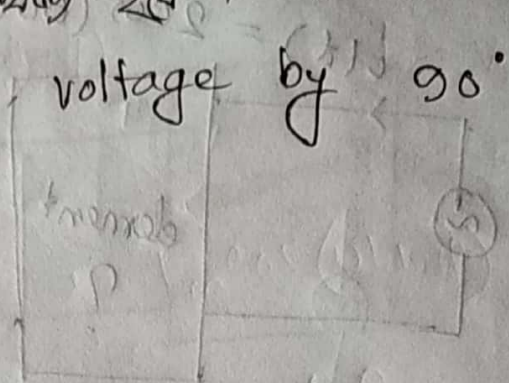Current lags the voltage by 90° angle for inductor.



□

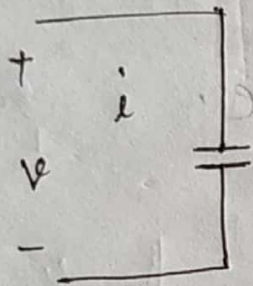

$$i = I_m \cos(\omega t + \phi)$$


$$\bar{I} = I_m \angle \phi$$

$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int i dt$$


$$\bar{V} = \frac{1}{C} \cdot \frac{1}{j\omega} \cdot \bar{I}$$
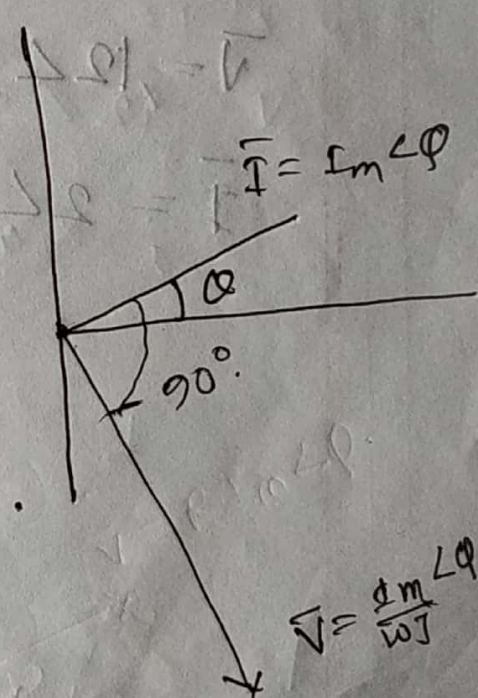
$$= \frac{1}{C} \cdot \frac{1}{j\omega} \cdot I_m \angle \phi$$



Current leads the voltage by angle 90° for capacitor.


14

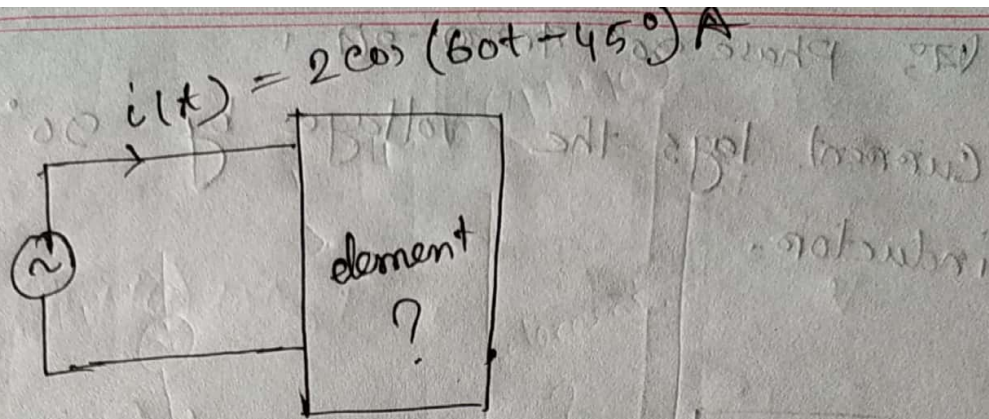

$v(t) = 12 \cos(60t + 45^\circ) \text{ voltage}$

$\bar{V} = 12 \angle 45^\circ \text{ V}$


$\bar{I} = 2 \angle -45^\circ \text{ A}$

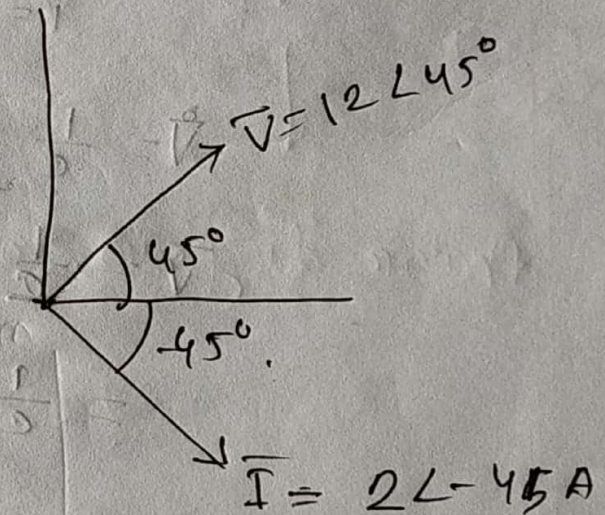

As current lags the voltage at an angle 90° so the element is an inductor.


$$i(t) = 50 \cos(100t + 120^\circ)$$

$$v(t) = 10 \cos(100t + 90^\circ)$$

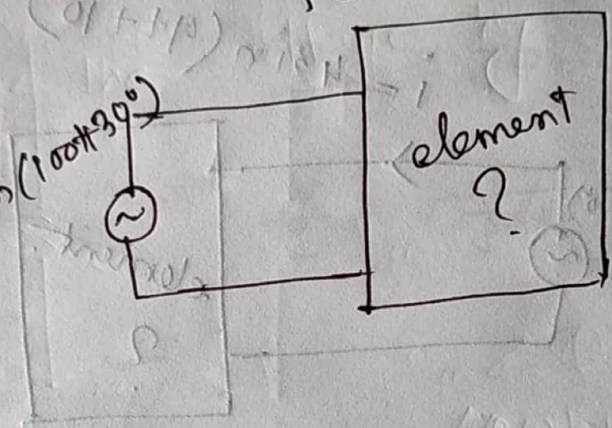

01/10/19
7th - A

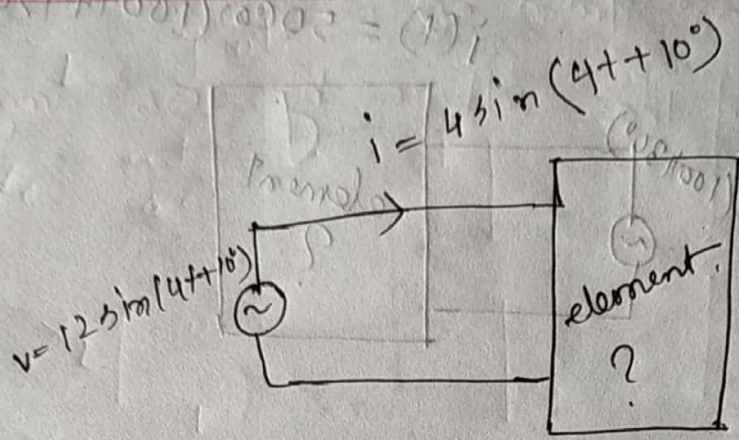$(\cos(10^\circ) + j\sin(10^\circ)) = (1 + j)$



$v = 12 \cos(4t + 10 - 90)$


$\bar{V} = 12 \angle -70^\circ$

$i = 4 \sin(4t + 10^\circ)$

$= 4 \cos(4t + 10 - 90^\circ)$

$\bar{I} = 4 \angle -80^\circ$

Ex - 9.8
P.P - 9.8.

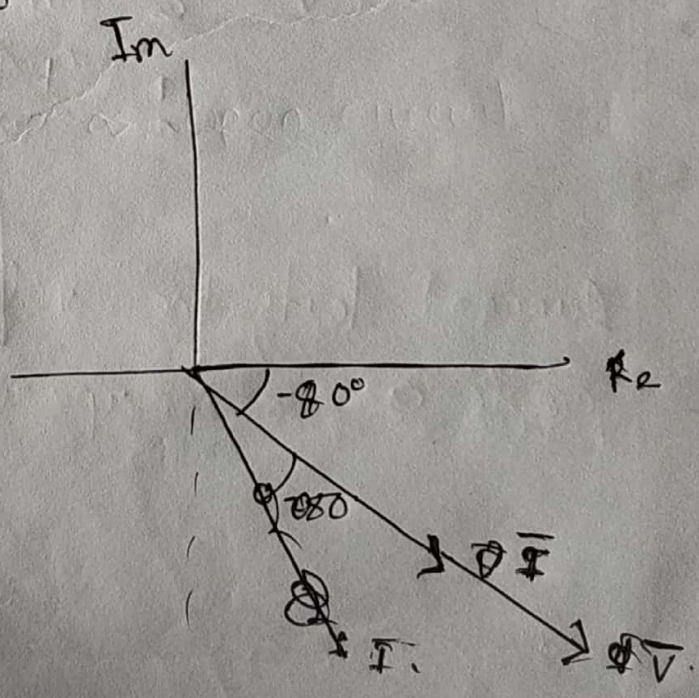

$$\bar{V} = \bar{I} R \quad \therefore \frac{\bar{V}}{\bar{I}} = R \quad (\text{resistor})$$

$$\bar{V} = j\omega L \bar{I} \quad \therefore \frac{\bar{V}}{\bar{I}} = j\omega L \quad (\text{inductor})$$

$$\bar{V} = \frac{\bar{I}}{j\omega C} \quad \therefore \frac{\bar{V}}{\bar{I}} = \frac{1}{j\omega C} \quad (\text{capacitor})$$

$$\text{impedance, } \bar{Z} = \frac{\bar{V}}{\bar{I}}$$

$$= R + jX$$

impedance is a complex number where a real part and an imaginary part is obtained.

$$\text{impedance } \bar{Z} = \frac{\bar{V}}{\bar{I}}$$

$$= R + jX$$

$X_L = \omega L$: inductive reactance

$X_C = \frac{1}{\omega C}$: capacitive reactance

DC supply \rightarrow reactance is zero.

$\bar{Z} = R + jX \rightarrow$ inductive reactance

$= R - jX \rightarrow$ capacitive reactance.

$$jX_L = j\omega L$$

$$-jX_C = \frac{-j}{\omega C}$$

$$\therefore X_L = \omega L$$

$$\therefore X_C = \frac{1}{\omega C}$$

⊗ at DC, $f = 0$, $\omega = 2\pi f = 0$.

inductor,

$$X_L = 0$$

$Z = j\omega L = 0$, short circuit.

capacitor,

$$Z = -jX_C = \frac{-j}{\omega C} = \infty, \text{ open circuit.}$$

Unit


ohm

$$\bar{Z} = R + jX \quad \text{ohm}$$

Admittance, $\bar{Y} = \frac{1}{\bar{Z}}$

conductance

S (siemens/mho)/Ω

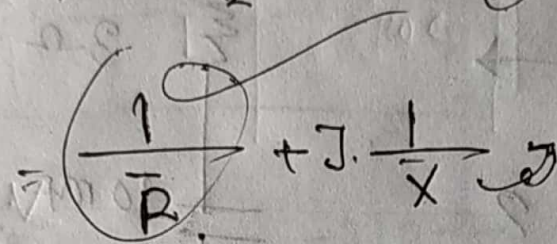


$$= G + jB \quad \leftarrow \text{susceptance}$$

siemens/mho/Ω

$$e = \frac{q}{\sigma}$$

$$0.01 = \frac{q}{\sigma}$$

13.10.12
 2th D.

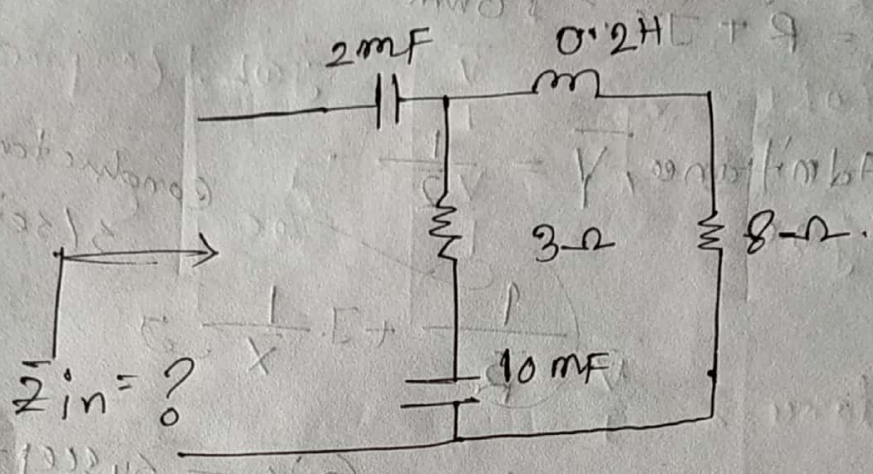

Assume, $\omega = 50 \text{ rad/s}$.



$$jX_L = j\omega L = j50 \times 0.2 = j10 \Omega.$$

2 mF, $jX_C = \frac{1}{j\omega C}$

$$\Rightarrow -jX_C = \frac{-j}{\omega C} = \frac{-j}{50 \times 2 \times 10^{-3}} = -j10 \Omega.$$

10 mF, $-jX_C = \frac{-j}{50 \times 10 \times 10^{-3}}$

$$\Rightarrow j2 \Omega.$$

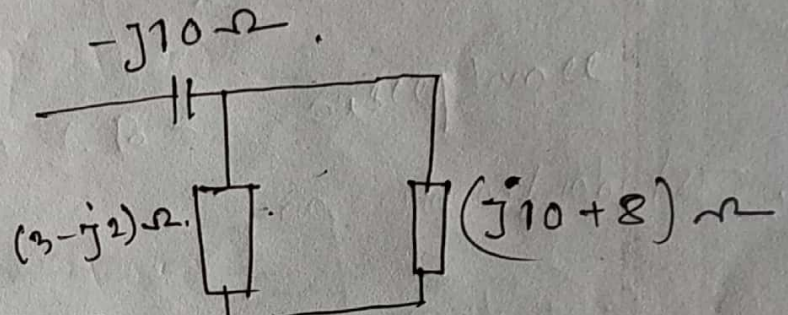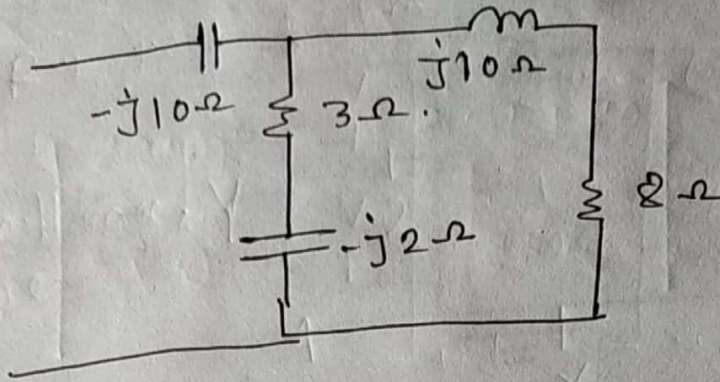

$$G_1 = \frac{1}{R} = \frac{1}{3 + j2} = 0.31 \angle -37^\circ$$

$$B = \frac{1}{X} =$$


$$= \frac{(3 - j2)(8 + j10)}{3 - j2 + 8 + j10} = \frac{24 + 30j - j16 - j^2 20}{11 + j8}$$

$$\bar{Z}_{in} = 3.22 - 1.07j = \frac{20 + 30j - 16j + 20}{11 + j8}$$

$$\bar{Y}_{in} = \frac{1}{\bar{Z}_{in}} = 0.024 + 0.08j$$

Problem - 9.68, 9.70.

Find I_x .

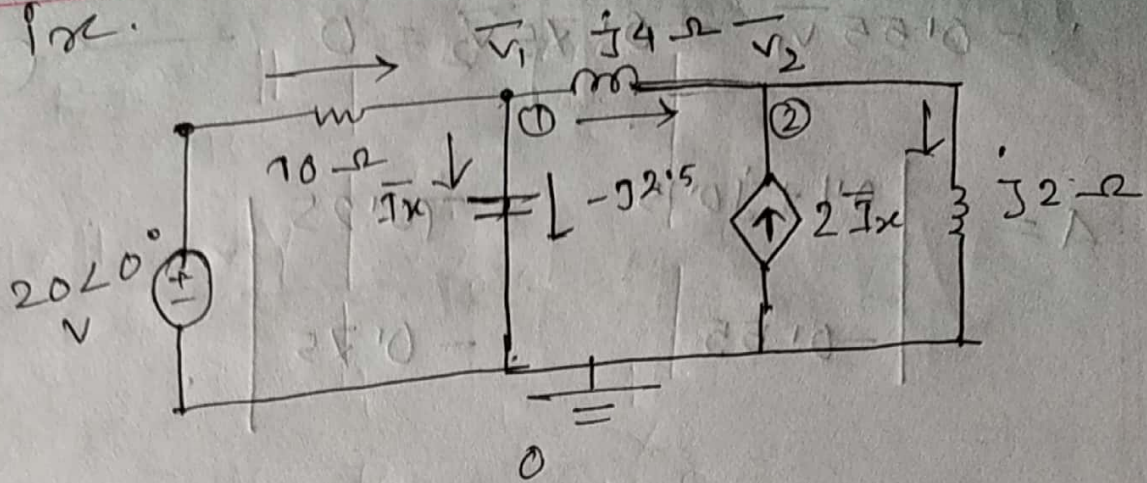

$$I_x = \frac{\bar{V}_1}{-j2.5}$$

At node ①, applying KCL,

$$\frac{20\angle 0^\circ - \bar{V}_1}{10} = \frac{\bar{V}_1 - \bar{V}_2}{j4} + \frac{\bar{V}_1}{-j2.5}$$

$$\Rightarrow 2\angle 0^\circ - 0.1\bar{V}_1 = -j0.25(\bar{V}_1 - \bar{V}_2) + j0.4\bar{V}_1$$

$$\Rightarrow 2\angle 0^\circ = (0.1 + j0.15)\bar{V}_1 + j0.25\bar{V}_2$$

$$\Rightarrow (0.1 + j0.15)\bar{V}_1 + j0.25\bar{V}_2 = 2\angle 0^\circ \quad \text{--- ①}$$

At node ② applying KCL,

$$\frac{\bar{V}_1 - \bar{V}_2}{4} + \frac{2\bar{V}_1}{-2.5} = 0 - \frac{\bar{V}_2}{2}$$

$$\Rightarrow 0.25\bar{V}_1 - 0.25\bar{V}_1 - 0.8\bar{V}_1 = 0.5\bar{V}_2$$

$$\therefore -0.55\bar{V}_1 - 0.75\bar{V}_2 = 0 \quad \text{--- (1)}$$

$$\Delta = \begin{vmatrix} 0.1 + j0.15 & -j0.25 \\ -0.55 & -0.75 \end{vmatrix}$$

$$= -0.075 + j0.1125 + j0.1375$$

$$= -0.075 + j0.25$$

$$\bar{V}_1 = \frac{\begin{vmatrix} 220^\circ & j0.25 \\ 0 & -0.75 \end{vmatrix}}{\Delta}$$

$$= \frac{(-1.5 \angle 0^\circ - 80)}{-0.075 + j0.25}$$

$$= \frac{-1.5}{-0.075 + j0.25}$$

$$= \frac{-1.5}{-0.075 + j0.25}$$

$$= \frac{-1.5}{-0.075 + j0.25}$$

ans will be
18.97 \angle 18.43°v

$$\bar{I}_x = \frac{V_1}{-j2.5 \text{ mV} + (mV) - 2.5 \angle -90^\circ \text{ mV}}$$


$$= \frac{18.97 \angle 18.43^\circ}{7.59 \angle 108.4^\circ} \text{ A}$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

Practice problem - 10.1

Example - 10.2.

~~AC~~ AC

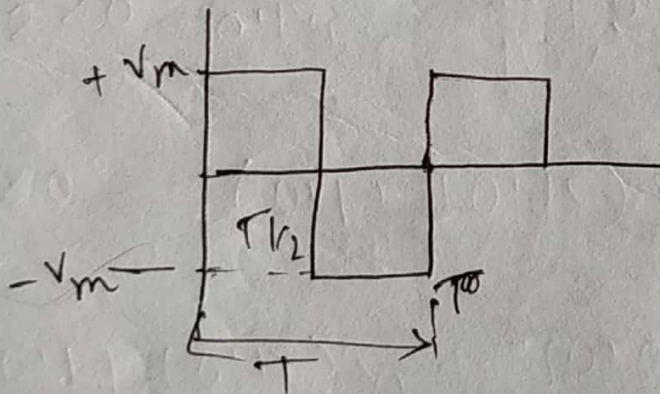


$$\text{Average value} = \frac{+V_m \times \frac{T}{2} + (-V_m) \times \frac{T}{2}}{T}$$

$$= 0.$$


$$\text{RMS value} = \sqrt{\frac{1}{T} \int_0^T (+V_m)^2 + (-V_m)^2 dt}$$

Practice problem of No. 1
Example - 10.2

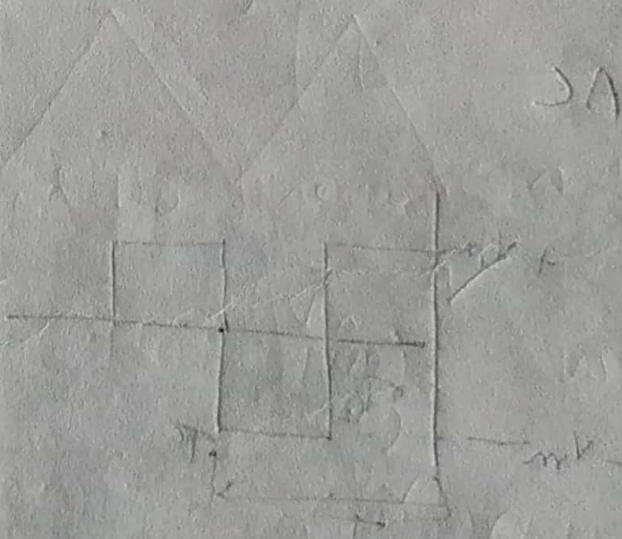

$$\frac{\frac{T}{2} \times (Vm)^2 + \frac{T}{2} \times (-Vm)^2}{T} = \text{Average value}$$

15.10.19
8th A

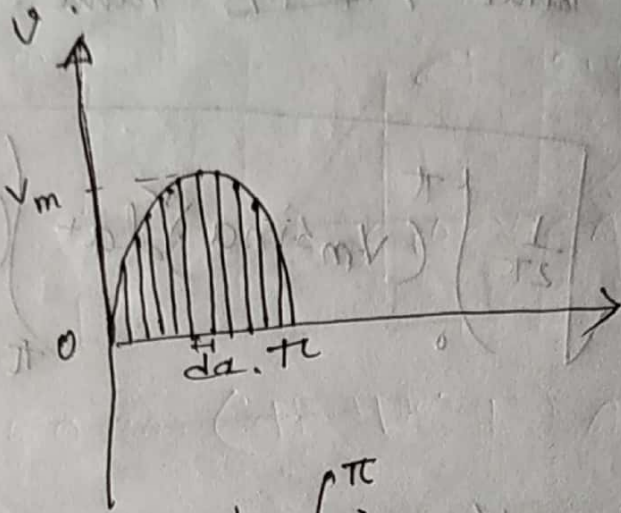

$$\text{Average value} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \alpha \cdot d\alpha$$

$$= \frac{1}{\pi} V_m [-\cos \alpha]_0^{\pi}$$

$$= \frac{V_m}{\pi} \cdot [2] = \frac{2V_m}{\pi}$$

$$= \frac{1}{2\pi} \left[\int_0^{\pi} V_m \sin \alpha \, d\alpha + \int_{\pi}^{2\pi} (-V_m + \sin \alpha) \, d\alpha \right]$$

$$= \frac{1}{2\pi} [2V_m - 2V_m]$$


$$= 0$$

12/10/21
A-119

Effective value / RMS value:

$$V_{\text{eff}} / V_{\text{RMS}} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \alpha)^2 d\alpha + \frac{1}{2\pi} \int_{\pi}^{2\pi} (-V_m \sin \alpha)^2 d\alpha}$$

$$= \frac{V_m}{\sqrt{2}}$$

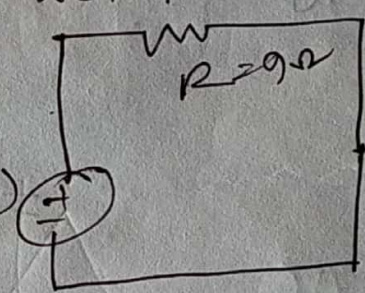


Power delivered to the resistor,

$$P = \frac{V_{\text{rms}}^2}{R} = \frac{\left(\frac{V_m}{\sqrt{2}}\right)^2}{9} \text{ Wat.}$$

$$I_{\text{rms}} R$$

*

Ex-11.7.

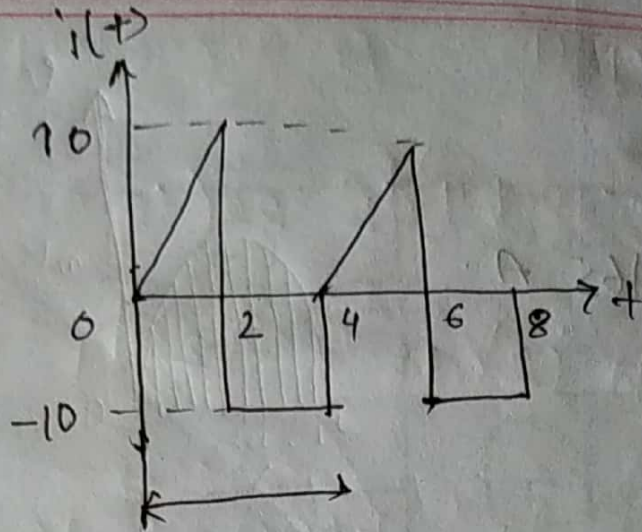

$$m = \frac{\Delta y}{\Delta x} = \frac{10}{2} = 5$$

Determine I_{rms} and average power absorbed by 2- Ω resistor.

$$i(t) = \begin{cases} 5t & , 0 < t < 2 \\ -10 & , 2 < t < 4 \end{cases}$$

$$I_{rms} = \sqrt{\frac{1}{4} \left[\int_0^2 (5t)^2 dt + \int_2^4 (-10)^2 dt \right]}$$

$$= \sqrt{\frac{1}{4} \left[25 \times \frac{t^3}{3} \Big|_0^2 + 100t \Big|_2^4 \right]}$$


$$= \frac{1}{4}$$

$$= 8.165 \text{ A}$$

Average

$$P_{\text{avg}} = I_{\text{rms}}^2 R$$


Ex-11.7

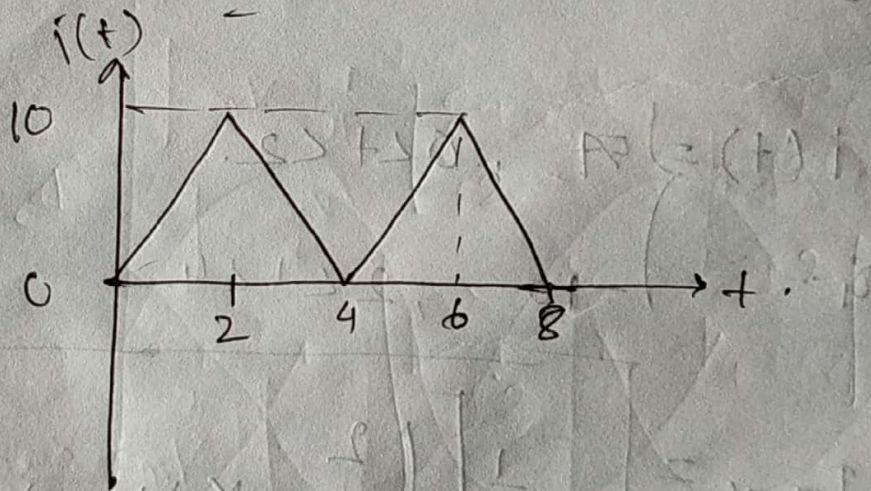

Determine V_{rms} and average power

absorbed by $2\text{-}\Omega$ resistor.

14

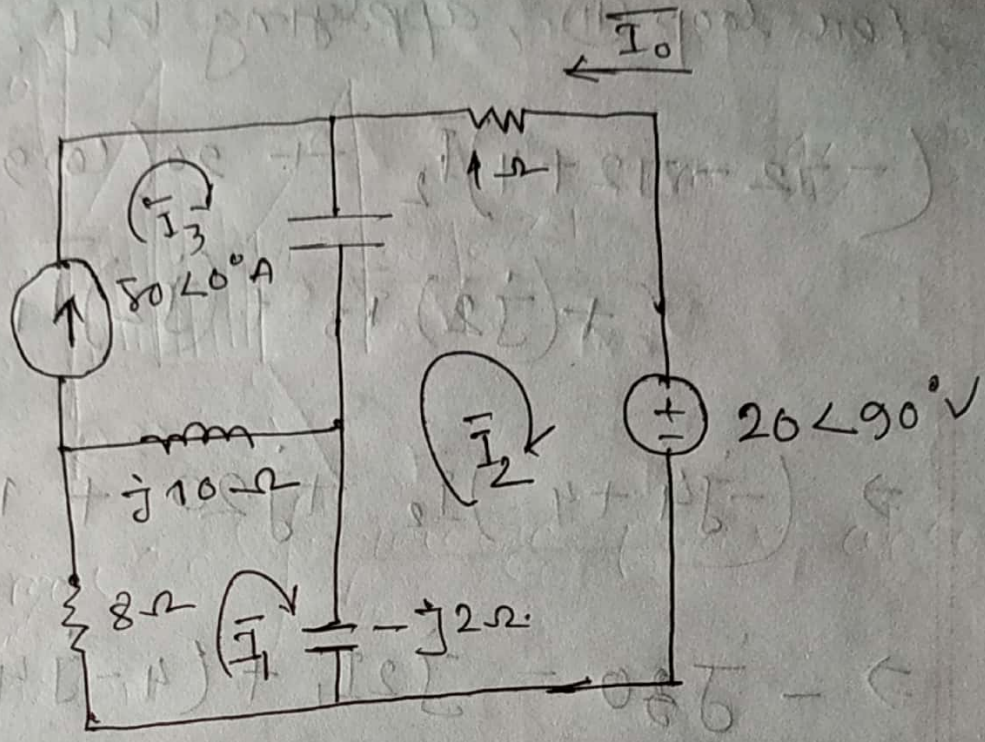

Find I_0 using mesh analysis.

Solⁿ

$$I_3 = 5 \angle 0^\circ \text{ A}$$

$$= 5(\cos 0^\circ + j \sin 0^\circ)$$

for ① applying KVL,

$$(8 + j10 - j2) i_1 - j10 i_3 + (j2) i_2 = 0$$

$$\Rightarrow (8 + j8) i_1 - j50 + j2 i_2 = 0$$

$$\Rightarrow j50 = (8 + j8) i_1 + j2 i_2 = 0$$

for loop ①, applying KVL.

$$(-j2 - j2 + 4)\bar{I}_2 + 20(\cos 90^\circ + j\sin 90^\circ) + (j2)\bar{I}_3 + (j2)\bar{I}_1 = 0.$$

$$\Rightarrow (-j4 + 4)\bar{I}_2 + j20 + 10j + j2\bar{I}_1 = 0.$$

$$\Rightarrow -j30 = j2\bar{I}_1 + (4 - j4)\bar{I}_2 \quad \text{--- (1)}$$

$$\bar{I}_2 = \frac{\begin{vmatrix} 8 + j8 & j50 \\ j2 & -j30 \end{vmatrix}}{\begin{vmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{vmatrix}}$$

$$= 6.12 \angle -35.22^\circ \text{ A}$$


$$\bar{I}_0 = -\bar{I}_2 = -6.12 \angle -35.22^\circ \text{ A}$$

$$P.P \Rightarrow 10 \cdot 3 \cdot \sqrt{2} \cdot 10 \cdot 2, 10 \cdot 4.$$

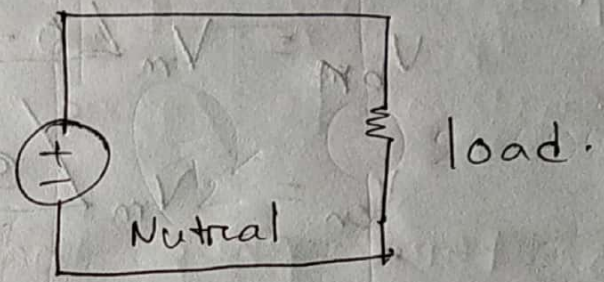
01.11.19
9th - E

Three - phase Circuit.

* Single Phase (1-φ): Single phase consists of a generator connected to a pair of wires to load.



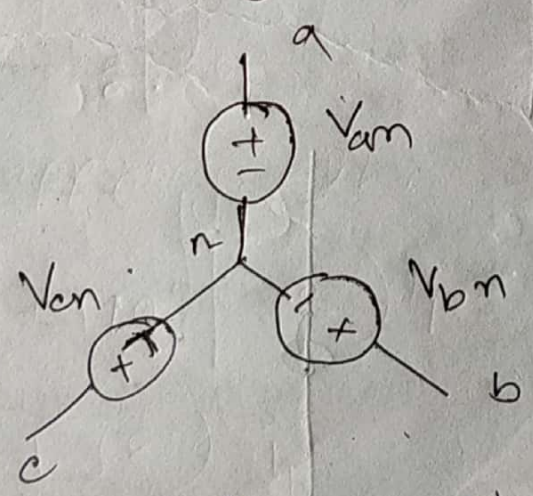* Three - phase System (3-φ): A three-phase system is produced by a generator consisting of three-voltage sources having equal in magnitude and frequency but out of phase by 120° from one each other.



$$V_{am} = V_m \sin(\omega t + \theta)$$

$$V_{bm} = V_m \sin(\omega t + \theta - 120^\circ)$$

$$V_{cm} = V_m \sin(\omega t + \theta + 120^\circ)$$



Y-connected Three-phase sources.


in phasor :

$$V_{an} = V_m \angle \theta$$

$$V_{bn} = V_m \angle \theta - 120^\circ$$
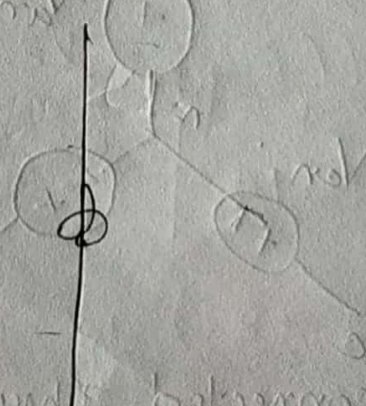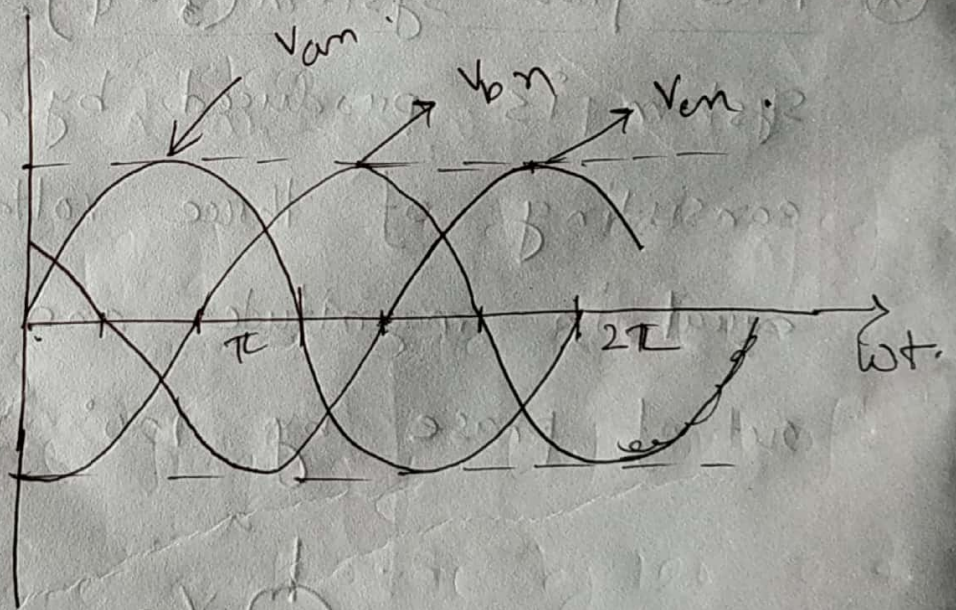
$$V_{cn} = V_m \angle \theta + 120^\circ$$



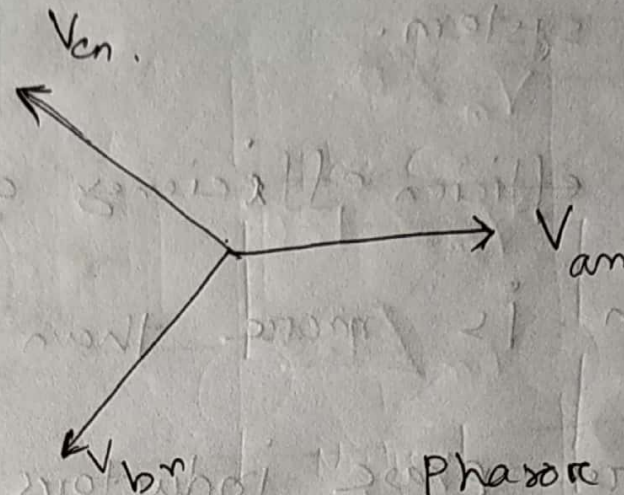

Phasor diagram.

Advantages of three phase system over single phase systems:

1. The instantaneous power of a three phase system is constant. For three phase instantaneous power, does not depend on time.
2. Three-phase system is economical than single phase system. To transmit same amount of power over same distance the required copper is less than single phase system.

3. All the generated power are in three phase system.

4. The efficiency of three-phase system is more than single phase.

5. Three-phase inductors are self starting but single-phase inductors are not.

Balance 3- ϕ System:

A 3- ϕ system is called balanced if the voltage sources are equal in magnitude and frequency but out of phase from one each other by 120° and the loads are equal.

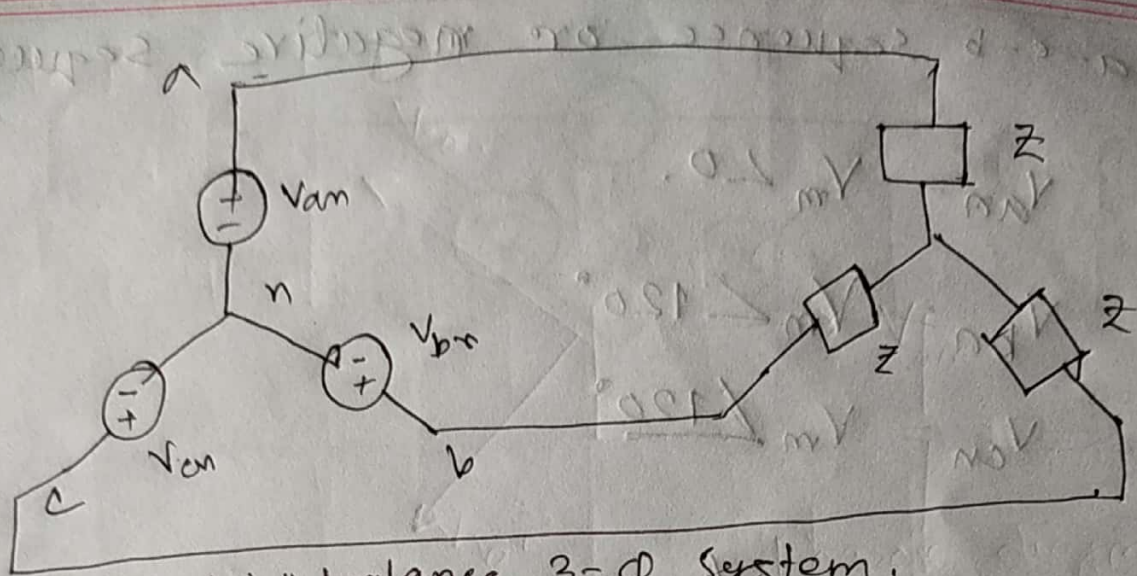


Fig: balance 3- ϕ system.

$$V_{an} = V_m \angle 0^\circ$$

$$V_{bn} = V_m \angle -120^\circ$$

$$V_{cn} = V_m \angle 120^\circ$$

⊗ Phase - Sequence: The phase sequence of a 3- ϕ system is the time order in which the voltage sources pass through their respective maximum.

a-b-c sequence


a leads b, b leads c, c leads a then it is called a-b-c sequence, or positive sequence.

a-e-b sequence or negative sequence.

$$V_{an} = V_m \angle 0^\circ$$

$$V_{bn} = V_m \angle 120^\circ$$

$$V_{cn} = V_m \angle -120^\circ$$

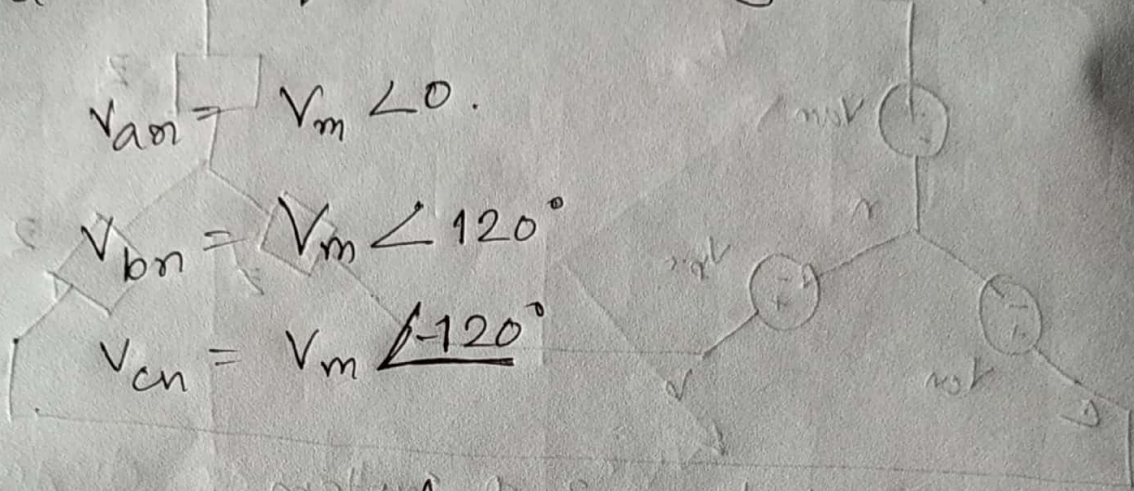

Two types of sources:

(i) Y-connected


(ii) Δ-connected

Two types of load:

(i) Y-connected


(ii) Δ-connected

20.10.19
8th-D

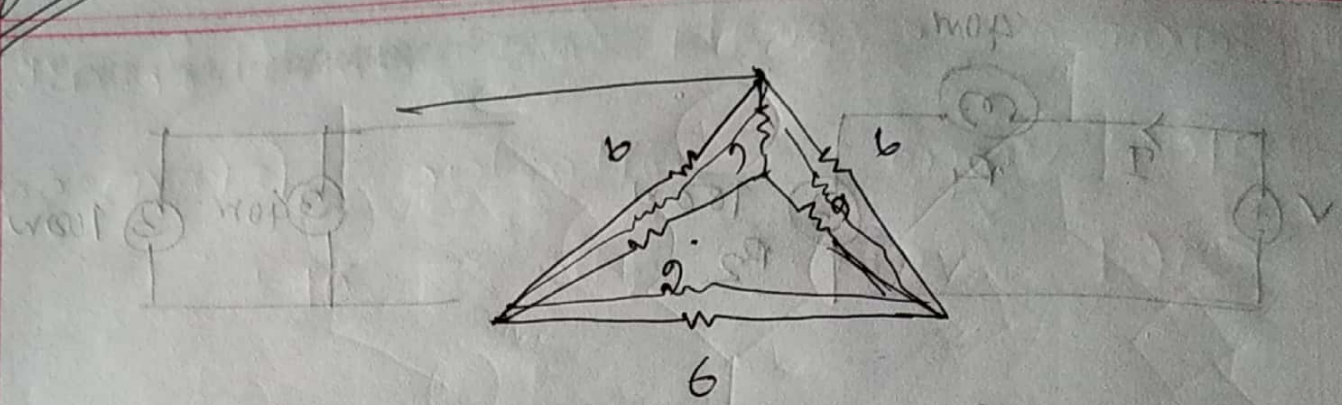

$$R_1 = \frac{6 \times 6 + 6 \times 2 + 6 \times 2}{2} = 27 \Omega = R_2 = R_3$$

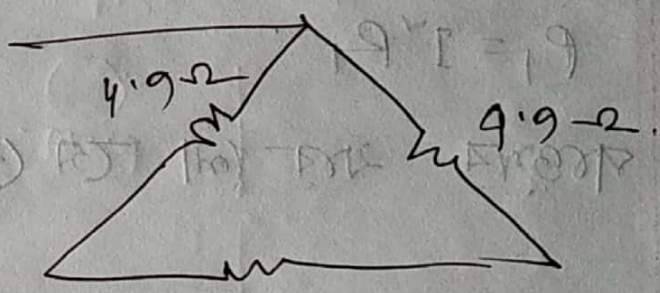
$$27 \parallel 6 = \frac{27 \times 6}{27 + 6} = 4.9 \Omega$$




$$4.9 + 4.9 = 9.8$$

$$9.8 \parallel 4.9 = \frac{9.8 \times 4.9}{9.8 + 4.9}$$

$$= 3.27 \Omega$$

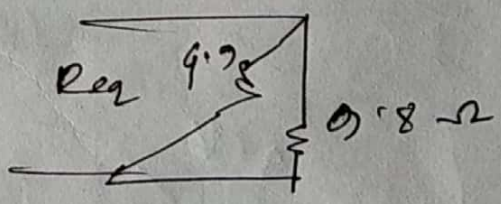

০১.০১.০১
D.N.D

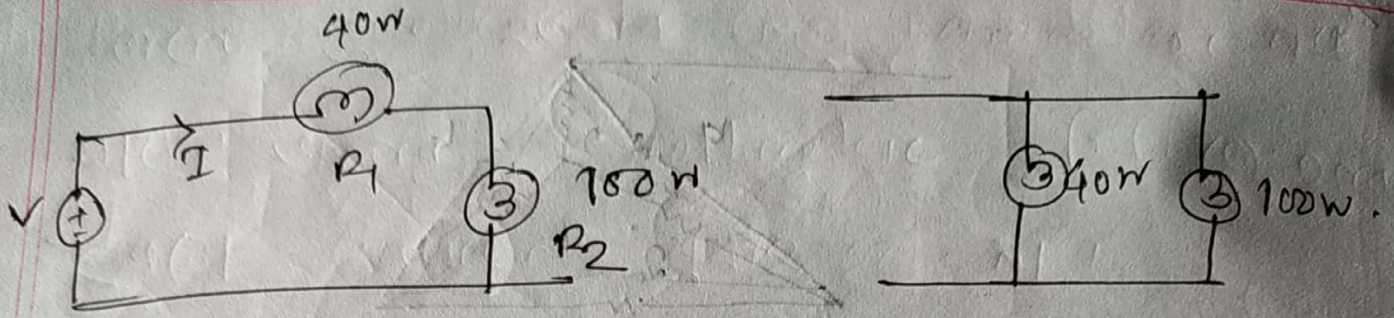

$$R_1 = \frac{P_1}{I^2}$$

$$R_2 = \frac{P_2}{I^2}$$


$$P_1 = I^2 R_1$$

সমস্ত অংশের মধ্য দিয়ে একই প্রবাহিত হবে অর্থাৎ

Parallel \Rightarrow 100W অংশের উপস্থিতি




(*) Current measurement :

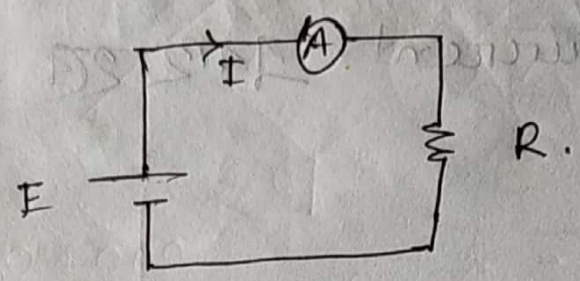

$$I = \frac{V}{R}$$

How to determine current in a circuit?

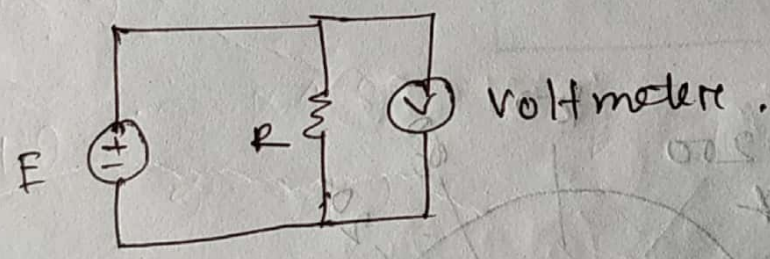
একটি ~~কিছু~~ Ammeter এর যৌথ প্রয়োগ।
 এবং Ammeter সরিষ্টে যুক্ত করতে হবে।





Voltmeter এর যৌথ প্রয়োগ দেখান।

(*) Ammeter এর যৌথ প্রয়োগ এবং parallel
 এ যুক্ত করলে কারেন্ট মাপার সঠিক দিবে যা হল
 Ammeter এর ভিতর দিয়ে যাবে এবং যেকোন পরিমাণ

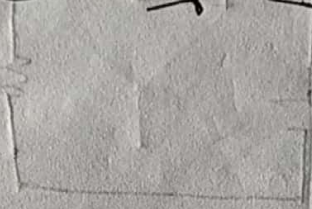যদিও এটি একটি স্কেল হিসাবে কাজ করে, Ammeter তেই স্থাপন
 করা যায়। আরও এ voltmeter পরিমিত স্থানে
 স্থাপন। Current প্রবাহ হবে না।



Resistance measurement:

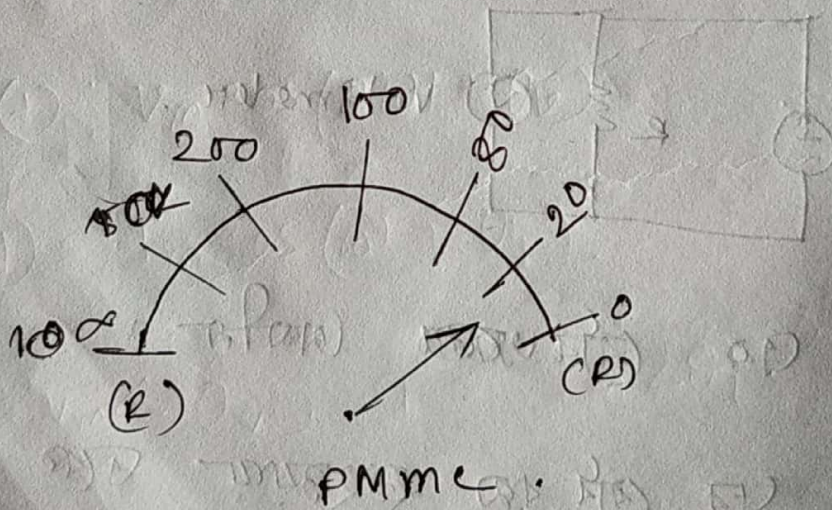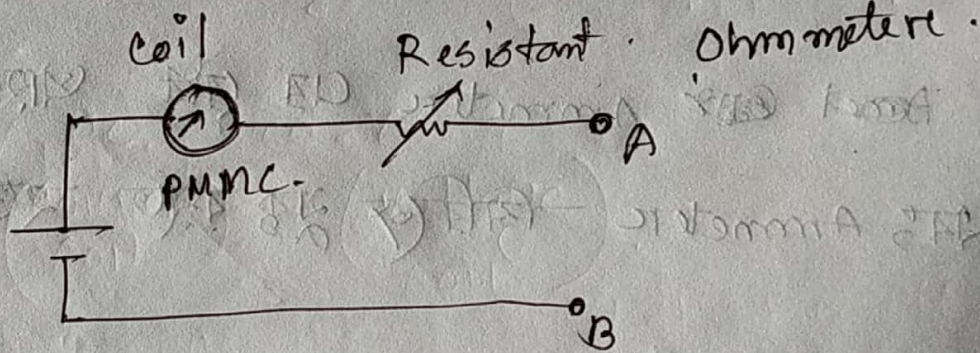


Permanent magnet moving coil

(i) A and B points are shorted.


Deflection current, $I_d = \frac{E}{R}$.

PMMC deflection = 0.

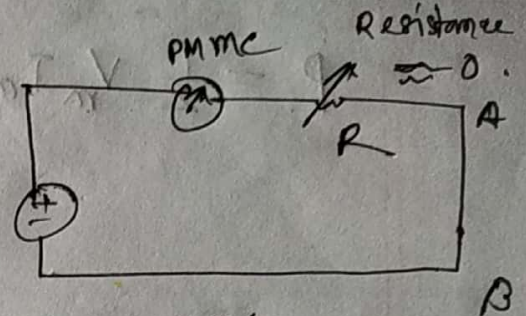


(ii) A and B points are open.

PMMC deflection = ∞.

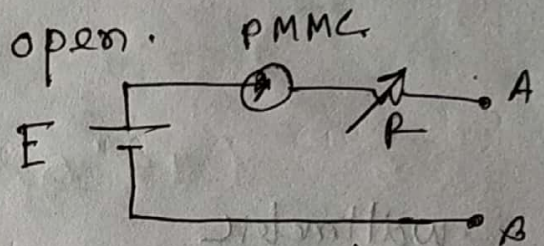


(iii) R_x is connected between A and B.

$$I_m = \frac{E}{R + R_x}$$

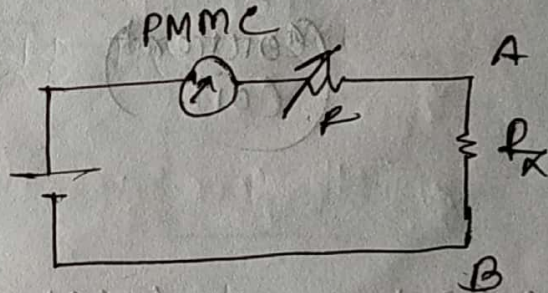

Power measurement: (using wattmeter) ①
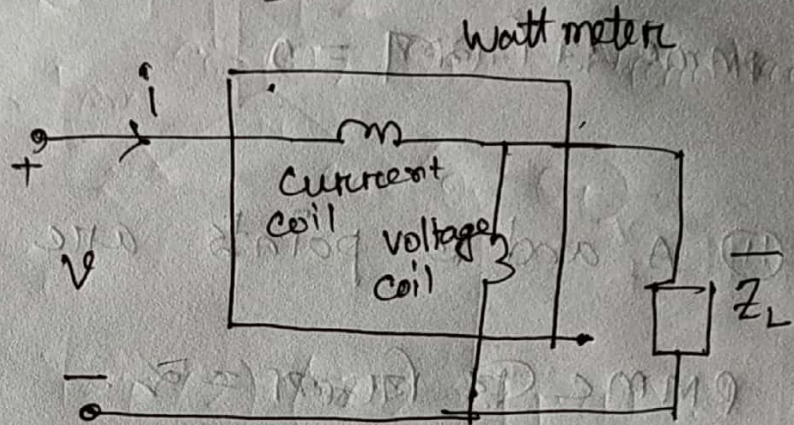
$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$



Wattmeter

contains cc and vc

(Current Coil) (Voltage coil)

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$I(t) = I_m \cos(\omega t + \theta_i)$$

$$V = V_m \angle \theta_v, \quad I = I_m \angle \theta_i$$

average power, $P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$\bar{Z}_1 = \text{Resistive,}$

$$P = \frac{1}{2} V_m I_m \cos \theta$$

$$[\because \theta_v = \theta_i = 0]$$


When, $\bar{Z}_1 = \text{inductive/capacitive.}$

$$P = 0.$$

$$[\because \theta_v - \theta_i = \pm 90^\circ]$$

$$\cos 90^\circ = 0.$$

Ex 11.16

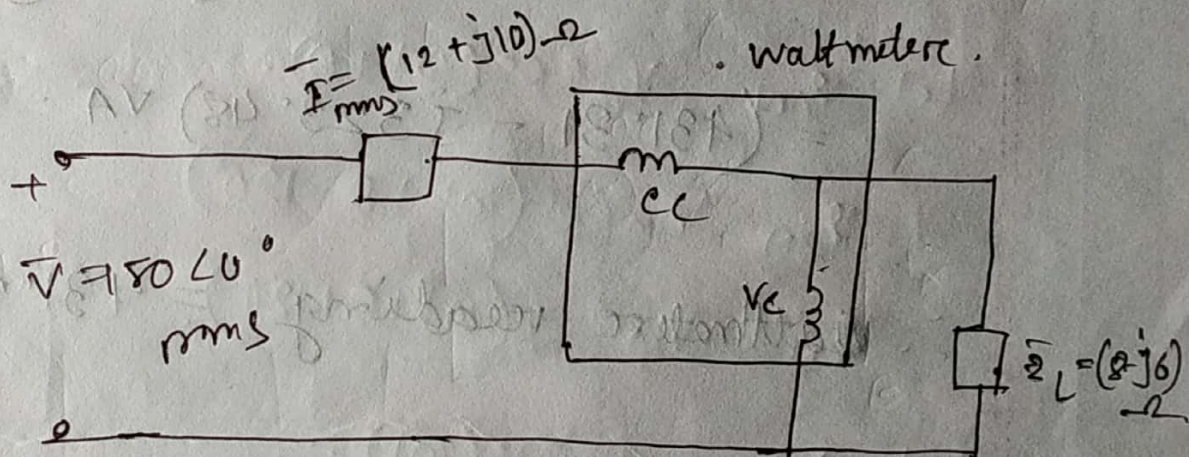

Find the wattmeter reading

$$\bar{I}_{rms} = \frac{9 \angle 0^\circ}{7.2 - j1.44} \text{ A}$$

$$\bar{V}_{rms} = \bar{I}_{rms} \bar{Z}_L = (7.2 - j1.44)(8 - j6)$$

$$= 48.96 - 54.72j$$

$$\begin{aligned} \therefore \text{complex power, } \bar{S} &= \overline{V_{\text{rms}}} \overline{I_{\text{rms}}} \\ &= V_{\text{rms}} I_{\text{rms}} \angle 0_v + \theta_i \\ &= V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) + j V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i) \\ &= V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) \end{aligned}$$

$$\bar{S} = (48 \angle 0_v - j 54.72) (7.2 + j 1.44)$$

$$= (431.31 - j 323.48) \text{ VA}$$


$$\therefore \text{wattmeter reading} = 431.31 \text{ watt}$$

VAR \rightarrow Volt ampere reactive power.

$$\text{var meter reading} = 323.48 \text{ VAR}$$

23.11.19
12th D. Day

S-PD
JA

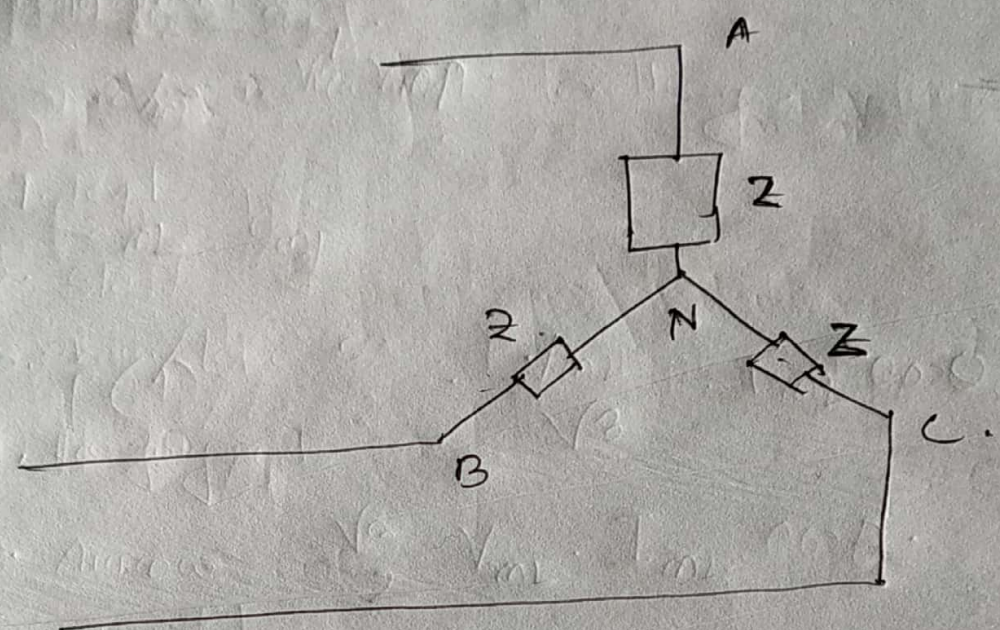

Let, $V_{AN} = V_m \cos(\omega t + \theta)$.

$V_{BN} = V_m \cos(\omega t + \theta - 120^\circ)$.

$V_{CN} = V_m \cos(\omega t + \theta + 120^\circ)$.

Let, $i_{AN} = I_m \cos(\omega t)$.

$i_{BN} = I_m \cos(\omega t - 120^\circ)$.

$i_{CN} = I_m \cos(\omega t + 120^\circ)$.

Advantage

(i) Total absorbed instantaneous power,

$$P(t) = V_{AN} i_{AN} + V_{BN} i_{BN} + V_{CN} i_{CN}$$
$$= V_m i_m \cos(\omega t + \theta) \cos(\omega t) + V_m i_m \cos(\omega t + \theta - 120^\circ) \cos(\omega t - 120^\circ) + V_m i_m \cos(\omega t + \theta + 120^\circ) \cos(\omega t + 120^\circ)$$

$$= \frac{1}{2} V_m i_m \left[\cos(\theta) + \cos(2\omega t + \theta) + \cos(\theta) + \cos(2\omega t + \theta - 240^\circ) + \cos(\theta) + \cos(2\omega t + \theta + 240^\circ) \right]$$

$$= \frac{3}{2} V_m i_m \left[3 \cos \theta + \cos(2\omega t + \theta) + 2 \cos(2\omega t + \theta) + \cos(240^\circ) \right]$$

$$P(t) = \frac{3}{2} V_m i_m \cos \theta = \frac{3}{2} V_{mp} I_{mp} \cos \theta$$

The instantaneous power of a three phase system is constant,

where, V_m is the peak value of phase voltage
 I_m is the peak value of phase current.

For a Y-connected system,

$$V_{ML} = \sqrt{3} V_{mp}$$

$$I_{ML} = I_{mp}$$

$$P(\pm) = \frac{3}{2} \cdot \frac{V_{mL}}{\sqrt{3}} \cdot I_{mL} \cos \theta$$

$$= \frac{\sqrt{3}}{2} V_{mL} \cdot I_{mL} \cdot \cos \theta$$

$$= \sqrt{3} \cdot \frac{V_{mL}}{\sqrt{2}} \cdot \frac{I_{mL}}{\sqrt{2}} \cdot \cos \theta$$



$$= \sqrt{3} V_L \cdot I_L \cdot \cos \theta \quad \left[\begin{array}{l} V_L = \text{R.M.S. value} \\ I_L = \text{R.M.S. value} \end{array} \right]$$

where, V_L is the R.M.S value of line voltage.

I_L is the R.M.S value of line current.

2

Copper loss = $I^2 R$

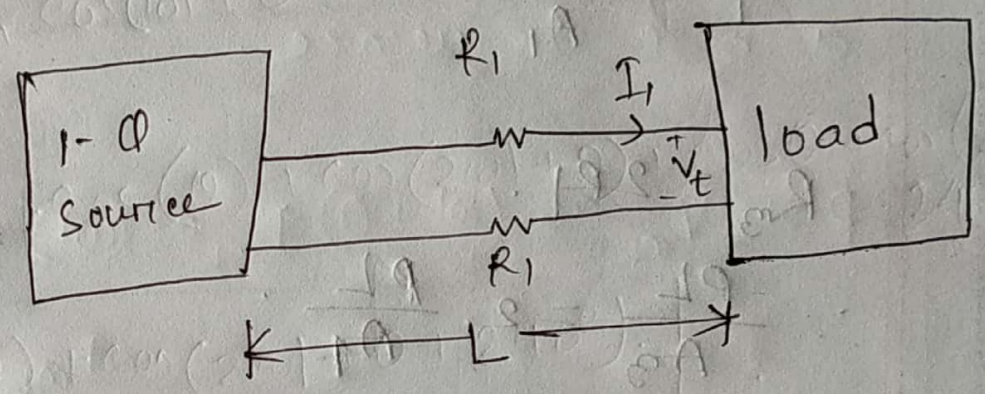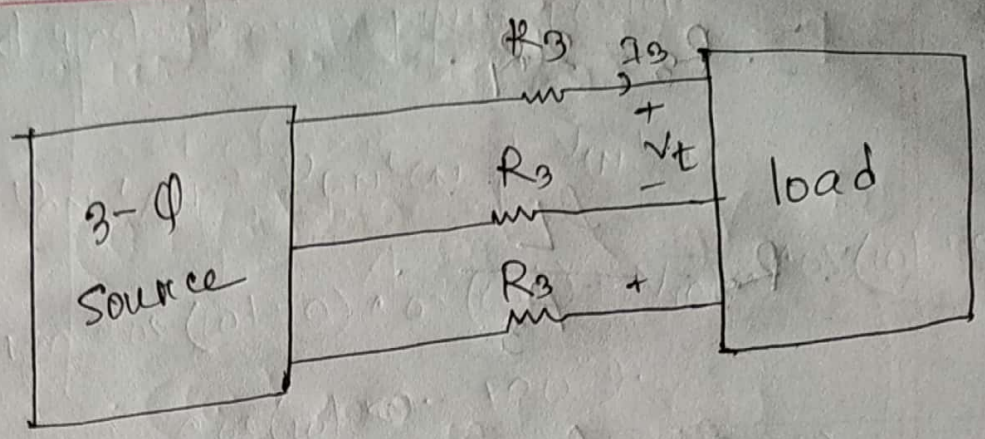

For three phase system,

$$P = \sqrt{3} V_t I_3 \cos \theta = V_t I_1 \cos \theta$$

$$\Rightarrow \sqrt{3} I_3 = I_1$$

Cu loss in 3-φ system = $3 I_3^2 R_3$

Cu loss in 1-φ system = $2 I_1^2 R_1$

$$3 I_3^2 R_3 = 2 I_1^2 R_1$$

$$\Rightarrow 3 I_3^2 R_3 = 2 \cdot 3 \cdot I_3^2 R_1$$

$$\therefore R_3 = 2R_1$$

$$\therefore R_3 = \frac{\rho L}{A_3}$$

$$R_1 = \frac{\rho L}{A_1}$$

$$R_3 = 2R_1$$

$$\therefore \frac{\rho L}{A_3} = 2 \frac{\rho L}{A_1}$$

$$\Rightarrow A_1 = 2A_3$$

$$\text{Volume of cu in 3-}\phi = 3 \times A_3 \times L$$

$$\text{Volume of cu in 1-}\phi = 2 \times A_1 \times L$$

$$\therefore \frac{\text{wt. of cu in 3-}\phi}{\text{wt. of cu in 1-}\phi} = \frac{3A_3L}{2A_1L}$$


$$= \frac{3}{2} \frac{1}{2}$$

$$= \frac{3}{4}$$

∴ wt. of cu in 3- ϕ = ~~50~~ 75% of wt. of cu
in 1- ϕ system.

Measurement of power in three phase system:

Method → Two wattmeter Method

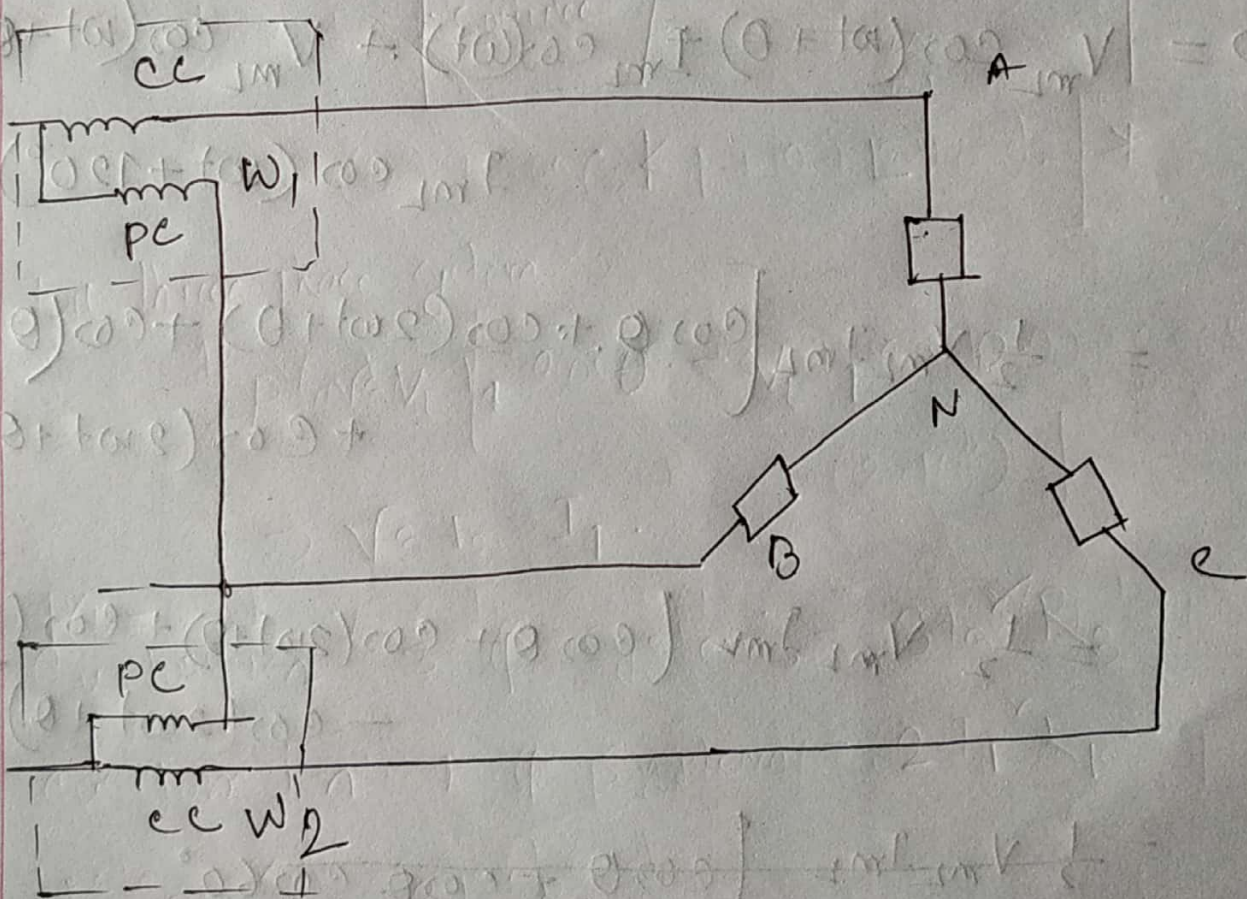

$$P = V_{AB} \hat{i}_{AN} + V_{CB} \hat{i}_{CN}$$

Let, $V_{AB} = V_{mL} \cos(\omega t + \theta)$.

$$\hat{i}_{AN} = I_{mL} \cos(\omega t)$$

a-b-c sequence.

$$P = V_{mL} \cos(\omega t + \theta) I_{mL} \cos(\omega t) + V_{mL} \cos(\omega t + \theta + 60^\circ) I_{mL} \cos(\omega t + 120^\circ)$$

$$= \frac{1}{2} V_{mL} I_{mL} [\cos \theta + \cos(2\omega t + \theta) + \cos(\theta - 60^\circ) + \cos(2\omega t + \theta + 120^\circ)]$$

$$= \frac{1}{2} V_{mL} I_{mL} [\cos \theta + \cos(2\omega t + \theta) + \cos(\theta - 60^\circ) - \cos(2\omega t + \theta)]$$

$$= \frac{1}{2} V_{mL} I_{mL} [\cos \theta + \cos \theta \cos 60^\circ]$$

$$= \frac{1}{2} V_{mL} I_{mL} [\cos(\theta - 30^\circ + 30^\circ) + \cos(\theta - 30^\circ - 30^\circ)]$$

$$= \frac{1}{2} V_{mL} I_{mL} \cdot [2 \cdot \cos(\theta - 30^\circ) \cdot \cos 30^\circ]$$

$$= \frac{1}{2} V_{mL} I_{mL} \cdot 2 \cdot \frac{\sqrt{3}}{2} \cdot \cos(\theta - 30^\circ)$$

Measurement of Power in three phase system
 method

